
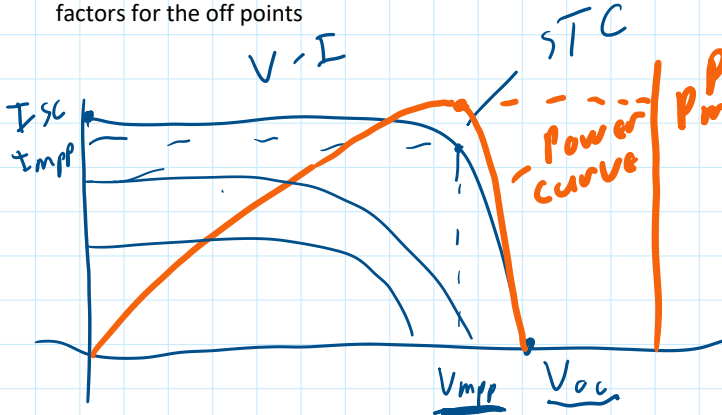


- Solar "array" discussion
- Standard test conditions (5.6)
- PV system shading effects (5.8.1)

The PV I-V Curve Under Standard Test Conditions

- PV I-V curve shifts around continually
- Insolation changes -> changes I_{sc}
 - Shading, clouds
- Temperature effects -> R_p, R_s, V_{oc} ...
- To compare cells in a uniform, "apples-to-apples" way, we use Standard Test Conditions (STC):
 - $I_{BC} = 1 \text{ kW/m}^2$ (1 sun)
 - Air mass ratio, $m = 1.5$ (AM 1.5) -> associated solar spectrum
 - $T_{cell} = 25 \text{ C}$ (298 k) -> cell temp, not ambient temp
- Manufacturers report cell/module specs at STC, with derating factors for the off points

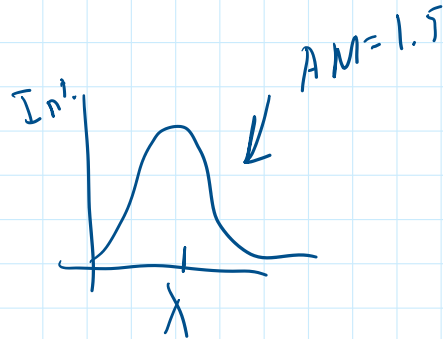

Power = VI
 $P = f(V)$
 $P(0) = 0 \times I_{sc} = 0$
 $P(V_{oc}) = V_{oc} \times 0 = 0$

* If this curve is shown for STC


$V_{mpp} = V_R$
 $I_{mpp} = I_R$
 $P_{mpp} = P_R$

R = rated value

Another value reported is Fill Factor


Fill Factor = $\frac{I_{mpp}}{V_{oc} \times I_{sc}} = \frac{V_{mpp} \times I_{mpp}}{V_{oc} \times I_{sc}}$

What does this look like

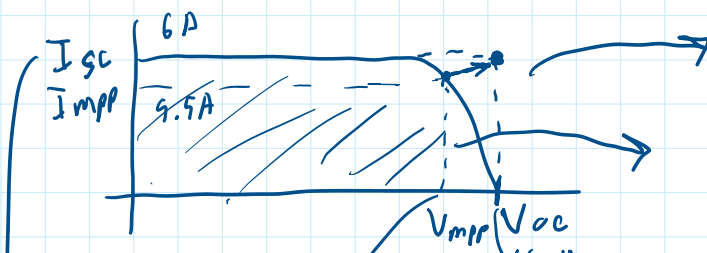

Area = $I_{sc} \times V_{oc} = 6 \times 48 = 288 \text{ W}$

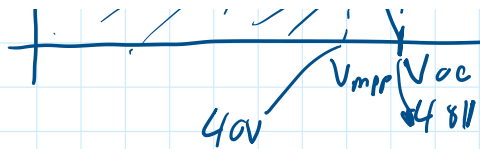
Area = $I_{mpp} \times V_{mpp} = 5.5 \times 40 = \underline{220 \text{ W}}$



$$F = \frac{220}{288} = \underline{0.76}$$

F.F. = Ratio of inner rectangle to outer

Power Elect

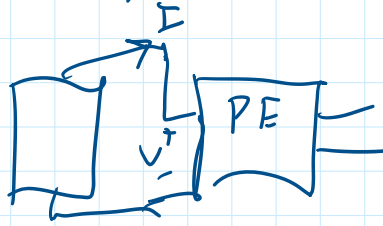



$$\begin{aligned} V_R &=? & V_{oc} &\approx V_{mpp} \\ I_R &=? & I_{sc} &\approx I_{mpp} \end{aligned}$$

- Best commercial FF. $\approx 70\%$ or higher
- Typically P_R are "Peak watts", $W_p - \underline{220W}$

Shading impacts on I-V curves



Monday, April 20, 2020 10:10 AM

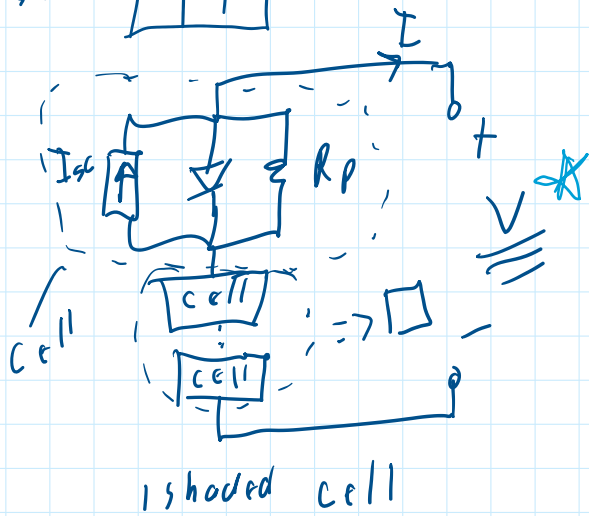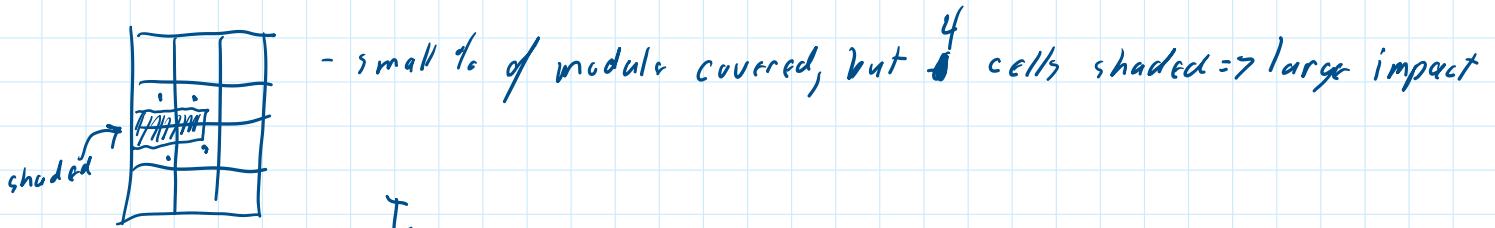- We've talked a bit about how shading can impact a P.V. cell.
 ↳ Why we introduced R_p
- When even a single cell is shaded, the output of the entire module/array can be reduced



$$V = n \cdot V_i = n \cdot V_d$$

$$V_{cell} = V/n$$

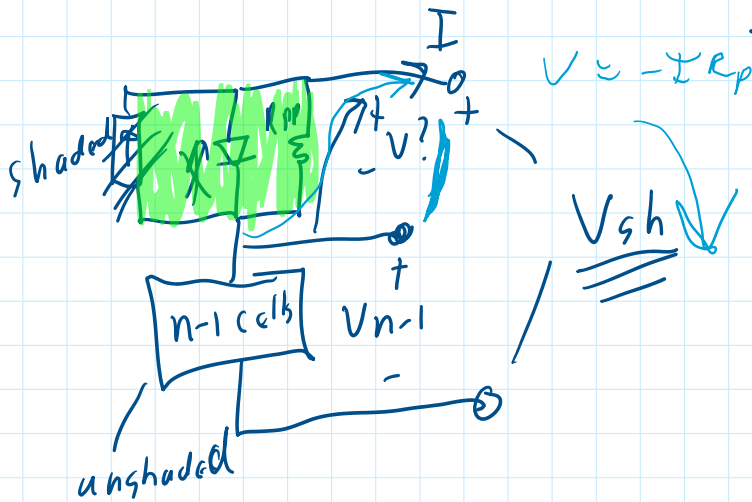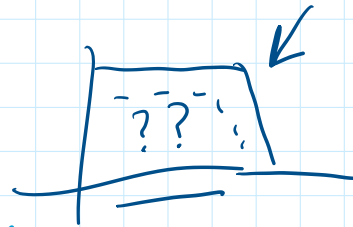

n -cell is shaded
 $I_{sc} = 0$

$V_d = -I R_p < 0 \Rightarrow$ diode is "off"
 All module current flows through R_p in shaded cell

$$V_{sh} = V_{n-1} - I R_p$$

\Rightarrow when unshaded, output voltage is V

\Rightarrow each cell add V/n volts


$$\Rightarrow V_{n-1} = (n-1) \cdot \frac{V}{n} = \left(\frac{n-1}{n}\right)V = V_{n-1}$$

$$V_{sh} = \left(\frac{n-1}{n}\right)V - I R_p$$


$$\Delta V = V - V_{sh} = V - \left(1 - \frac{1}{n}\right)V + I R_p = \frac{V}{n} + I R_p$$

$\Delta V = \frac{V}{n} + I R_p \Rightarrow$ this is how much voltage decreases

Full-sun curve

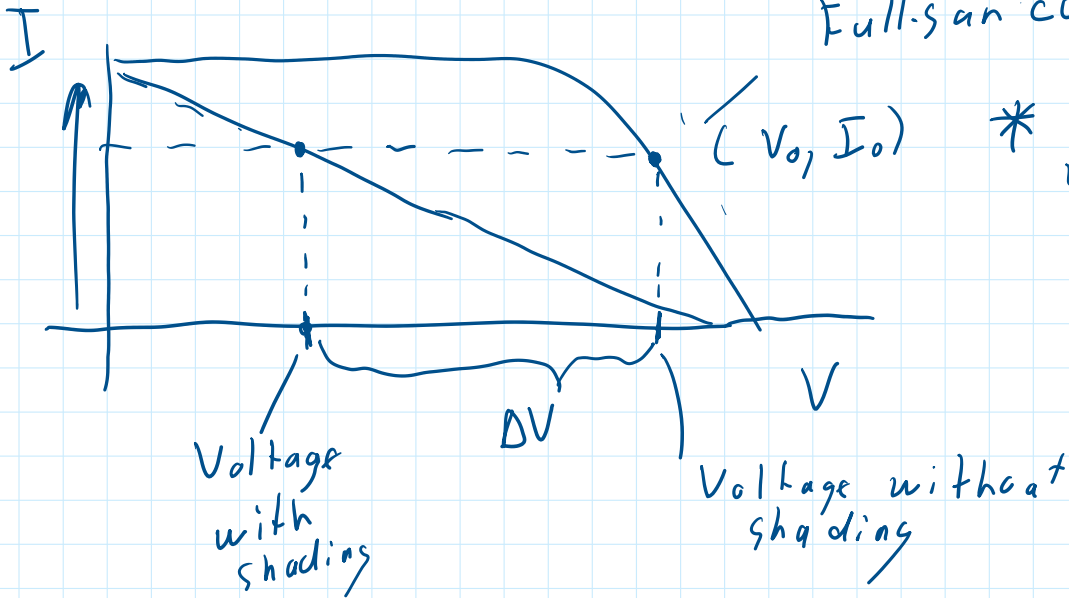

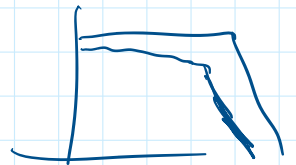* similar to what we saw with R_s , but $R_p \gg R_s$ so effect is larger




o For a given current, the module voltage is reduced

↳ by ΔV
↳ big deal

↳ lose shaded cell voltage output
↳ drop voltage across $R_p \rightarrow I R_p$

* this is power loss in form of heat

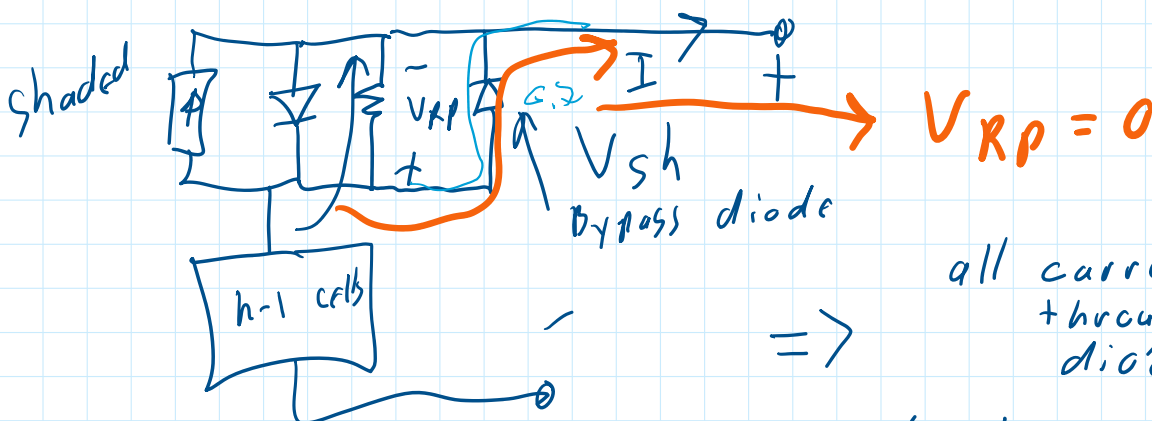How do we fix this? \Rightarrow Bypass diodes



\Rightarrow all current I flows through bypass diode ($V = 0$)

no shade $\Delta V = \frac{V}{n}$

