

Today


Monday, April 13, 2020 10:47 AM

- Exam 2 Review
- Solar Cell Circuit Models

Electric Circuit Equivalent Circuit

Monday, April 13, 2020 10:49 AM

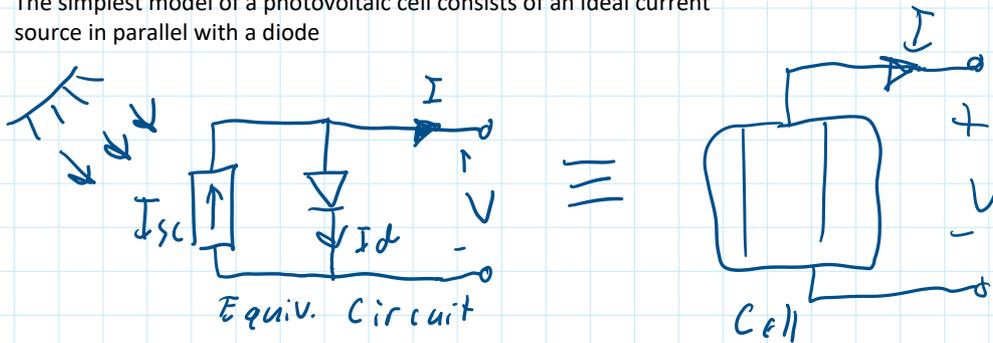The simplest model of a photovoltaic cell consists of an ideal current source in parallel with a diode



As with any other electric device, we want to obtain the V-I characteristics to compute currents, voltages and power once it is part of a larger circuit.

Recall: I_d = diode current from PN junction

$$I_d = I_0 \left(e^{\frac{qV_d}{kT}} - 1 \right)$$

- where: V_d = Voltage across diode terminals
- I_0 = reverse saturation current
- q = electron charge ($1.602 \cdot 10^{-19} \text{ C}$)
- k = Boltzmann's constant ($1.381 \cdot 10^{-23} \text{ J/K}$)
- T = Temp in Kelvin

Note, $V_d = V$

$$I_{sc} = I_d + I \quad \Rightarrow \quad I = I_{sc} - I_d = I_{sc} - I_0 \left(e^{qV/kT} - 1 \right)$$


$$I = f(I_{sc}, V)$$

For any given I_{sc} , we can find the relation between the cell current and voltage

$f(I_{sc}, V)$ = diode I-V characteristic turned upside-down and shifted by I_{sc}


Let's look at 2 key conditions:

1) short circuit

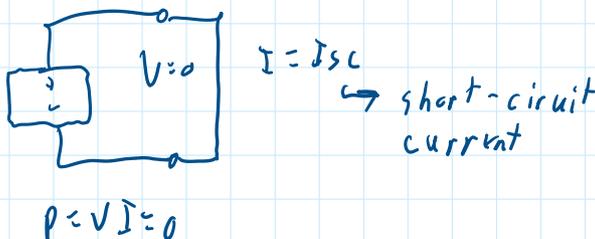


↳ gives magnitude of the ideal current source

2) Open circuit

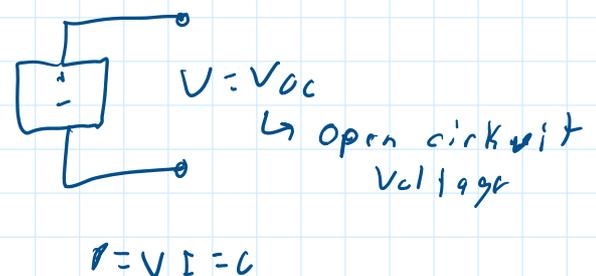

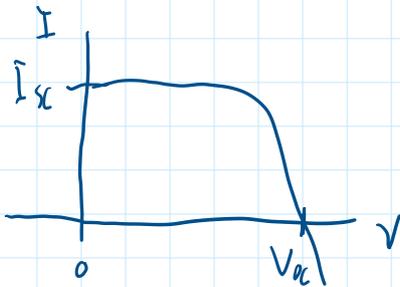↳ gives magnitude of the ideal current source



Let's make life easier:

$$\frac{q}{kT} \Big|_{T=298K} = 38.1 \left[\frac{1}{V} \right] = \frac{kT}{q} = \frac{1}{38.9} = 0.0257 [V]$$

$$I_d = I_0 (e^{38.9V} - 1)$$

$$I_{sc} = I_d + I = I_0 (e^{\frac{1}{0.0257}} - 1) + I = I \quad \text{measure this. It will vary with light, for example } I_{sc} = 4A$$

$$V_{oc}, I = 0$$

$$0 = I_{sc} - I_0 (e^{38.9V_{oc}} - 1)$$

$$V_{oc} = \left[\ln \left(\frac{I_{sc}}{I_0} + 1 \right) \right] \frac{1}{38.9} = \boxed{0.0257 \ln \left(\frac{I_{sc}}{I_0} + 1 \right)}$$


Example, $I_0 = 10^{-9} A$, $I_{sc} = 4A$

$$V_{oc} = 0.0257 \ln \left(\frac{4}{10^{-9}} + 1 \right) = 0.57 V$$

$$I_{sc} = 10$$

$$V_{oc} = 0.0257 \ln \left(\frac{10}{10^{-9}} + 1 \right) = 0.59 V$$


This doesn't change much

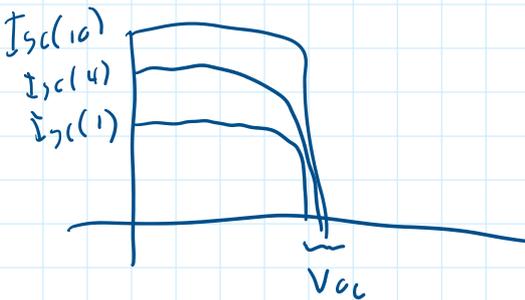

A more accurate model


Monday, April 13, 2020 4:06 PM

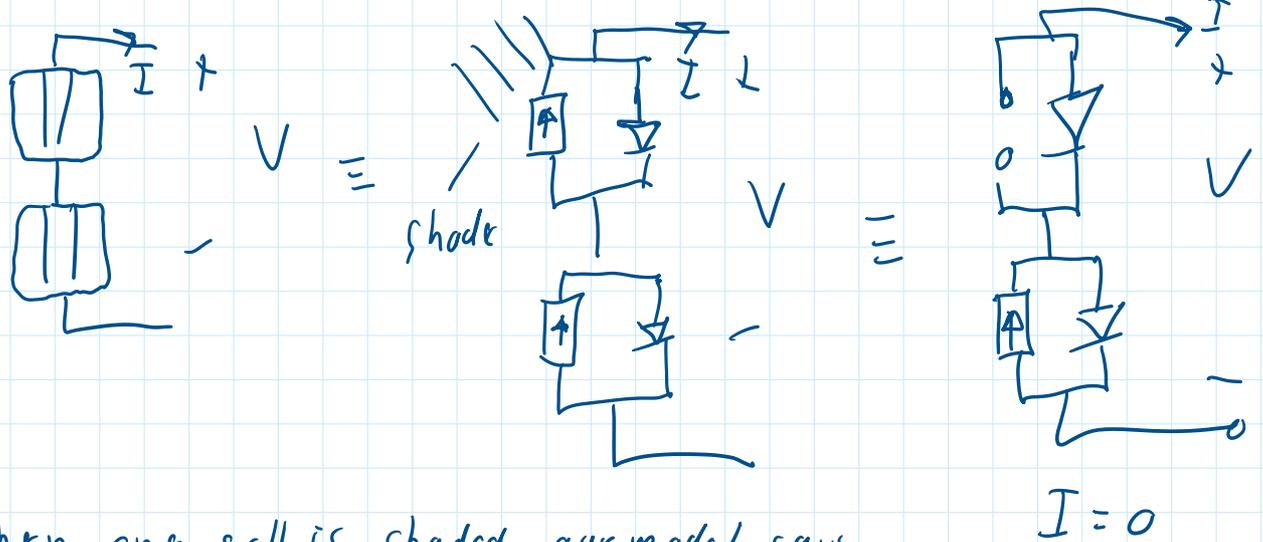- First model is not realistic when discussing shading effects
- assume we connect cells in series (more on this later)




When one cell is shaded, our model says that $I=0$, while shading effects have a big impact on power output, it is not as dramatic as this simplified model suggests

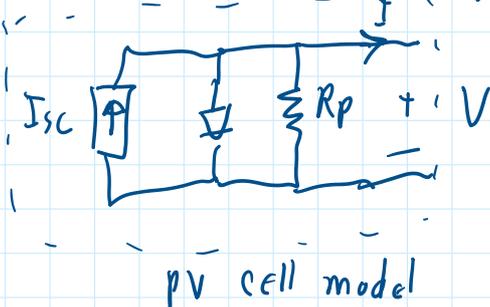Better model: Add parallel resistance \rightarrow due to leakage current paths through cell



$$I = I_{sc} - I_s - V/R_p$$

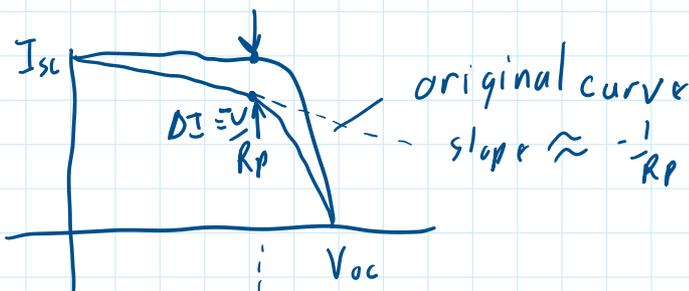For any output voltage, current is reduced from simplified model by V/R_p




for cell to have less than 1% loss in R_p ,

$$R_p > \frac{100V_{oc}}{I_{sc}}$$

Better model: add series resistance \rightarrow accounts for the fact that diode voltage \neq output voltage

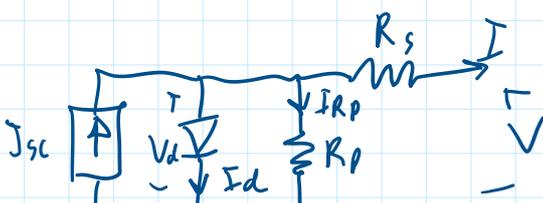- contact resistance between cell & wire leads
- Resistance of semiconductor





$$I = I_{sc} - I_d - I_{rp}$$

$$I = I_{sc} - I_0 (e^{38.9 V_d} - 1) - \frac{V_d}{R_p} \Rightarrow \text{wont in terms of } V$$

$$V_d = V + I R_s$$

$$I = I_{sc} - I_0 (e^{38.9 (V + I R_s)} - 1) - \frac{V + I R_s}{R_p}$$

- yuck! I is on both sides of Eqn. no good way to solve for I or V in terms of the other

↳ how do we use this?

↳ Matlab
or

- 1) write $I = I_{sc} - I_0 (e^{38.9 V_d} - 1) - V_d / R_p$ (parallel model)
- 2) Pick value for V_d ($0 \leq V_d \leq V_{oc}$)
- 3) Find I
- 4) $V_d = V + I R_s \rightarrow$ solve for V
- 5) sweep V_d , repeat (2-4) to generate VI curve

Result

