
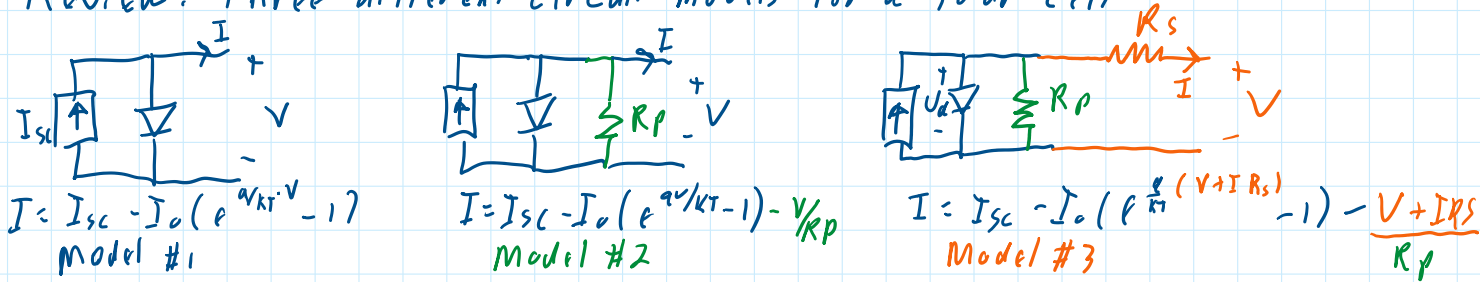


- Review
- From cells to modules
- From modules to arrays
- Maximum Power Point of a PV array
- Impacts of Temperature and Insolation on an V-I Curve

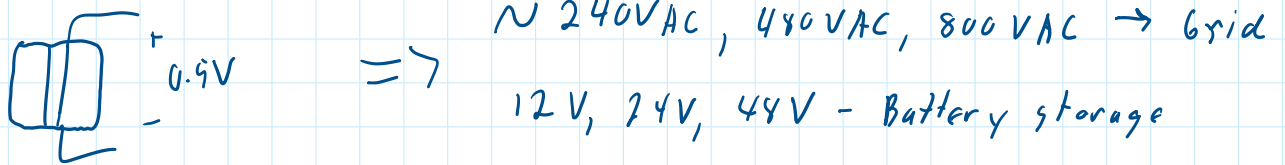Review: Three different circuit models for a solar cell



From the example at the end of last lecture, we saw that the open circuit voltage is around 0.6 V. When loaded, we can assume the terminal voltage is about 0.5 V.



Instead of single cells, use multiple in an ARRAY
 ↳ series/parallel combination of cells enclosed in a weather resistant package


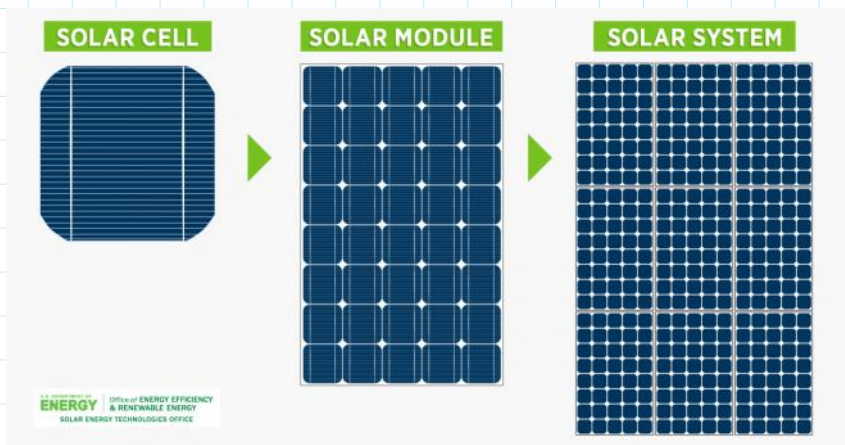



Photo credit: Energy.gov

From Cells to Modules

Wednesday, April 15, 2020 9:56 AM

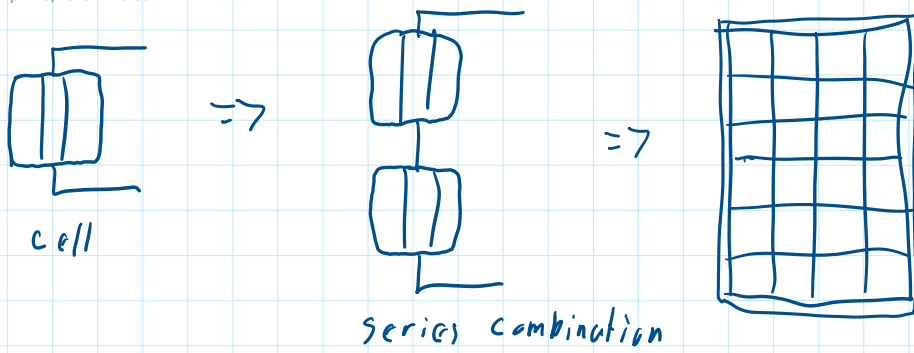


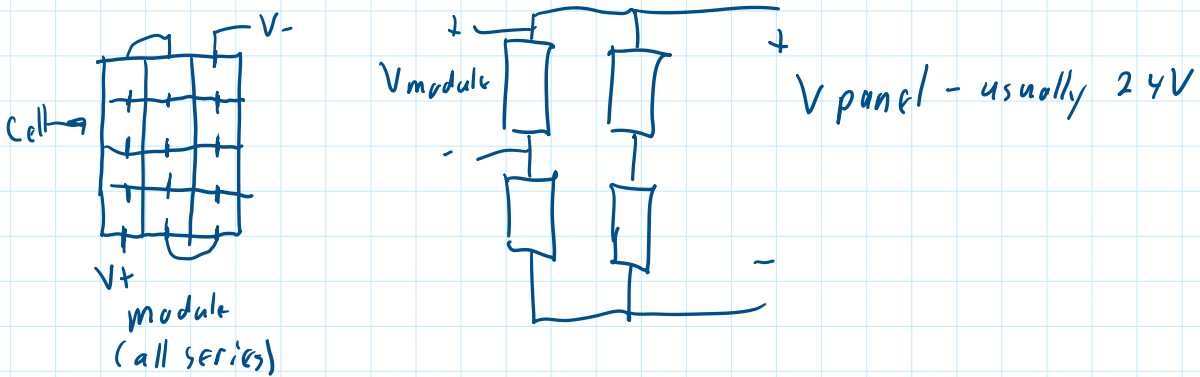- Definition: Module - a series string of PC cells pre-wired and packaged together
- Modules/panels are made of cells
- 72, 96, and 128 cell modules are common today
- A solar panel is made of 1 or more modules, wired in series and/or parallel



V-I curve of a Module

Recall: $q/kT/298 = 38.9 [1/v]$

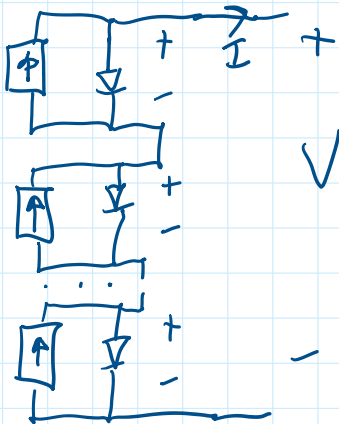

$$V = V_1 + V_2 + \dots + V_n$$

$$I = I_{sc} - I_d$$

For one cell:

$$I = I_{sc} - I_0 (e^{38.9V} - 1)$$

$$\Rightarrow I_{sc} - I = I_0 (e^{38.9V} - 1)$$

$$\Rightarrow e^{38.9V} = \frac{I_{sc} - I}{I_0} + 1$$


Assume no shading:

$$V_i = \frac{1}{38.9} \ln \left(\frac{I_{sc} - I + I_0}{I_0} \right)$$

assume $V_1 = V_2 = V_3 = \dots = V_n$

$$V = n V_i$$

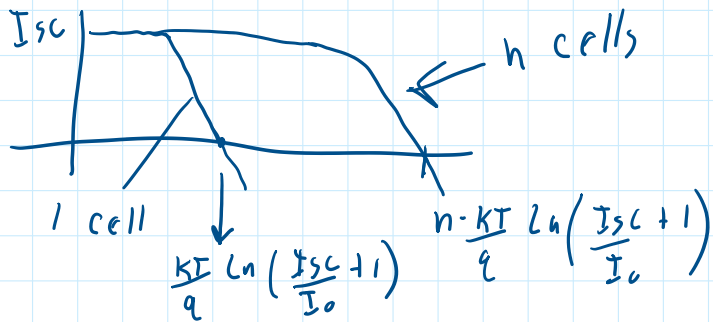
$$\Rightarrow V = n \frac{1}{38.9} \ln \left(\frac{I_{sc} - I + I_0}{I_0} \right) \Rightarrow I = I_{sc} - I_0 (e^{38.9V/n} - 1)$$



This makes sense - like stacking batteries to get higher voltage

note: $V_{oc} = n V_{i,oc}$

Now R_p ?

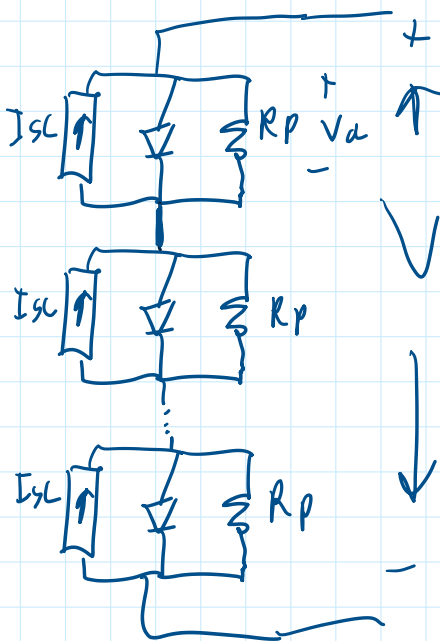



Assuming no shading:



- ① $V = n V_d$
- ② $V_d = \frac{kT}{q} \ln\left(\frac{I_d}{I_0} + 1\right)$
- ③ $I_d = I_{sc} - I - I_{RP}$
 $= I_{sc} - I - V_d/R_p$

combine ①, ② & ③

$$V = n \frac{kT}{q} \ln\left(\frac{I_{sc} - I - \frac{V}{nR_p} + 1}{I_0}\right)$$

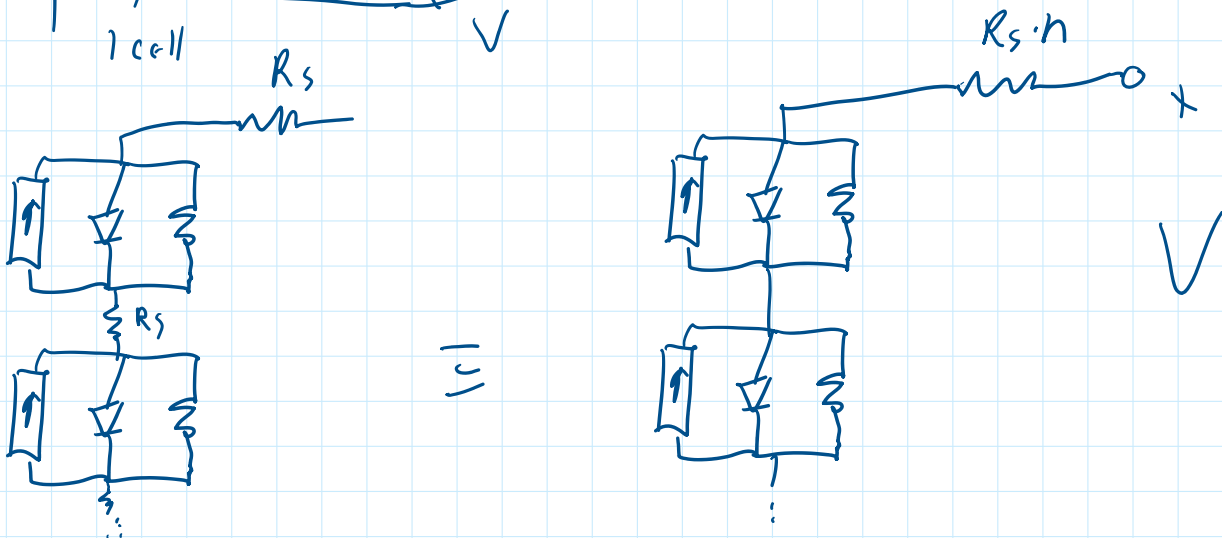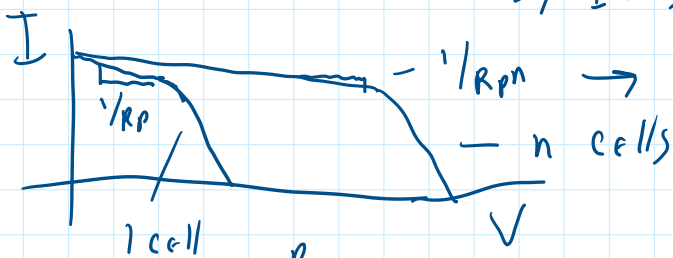
$$\Rightarrow I = I_{sc} - I_0 \left(e^{\frac{qV}{n kT}} - 1 \right) - \frac{V}{R_p \cdot n}$$



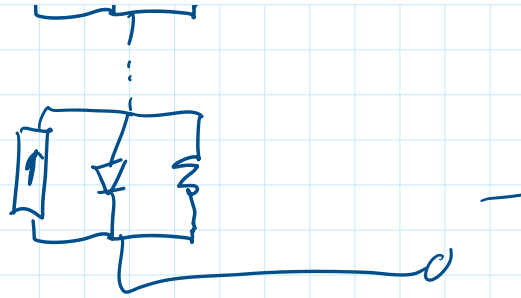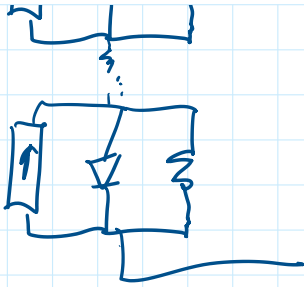

Again - Assuming no shading

Equivalent Model

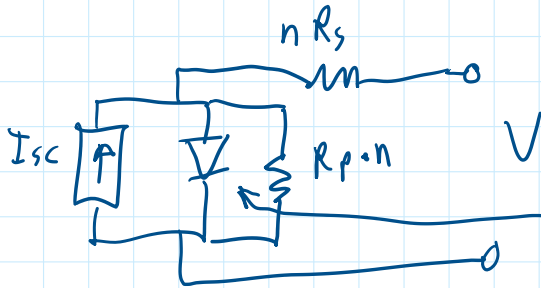


this is a diode with characteristic:
 $I_d = I_0 e^{(qV/nkT) - 1}$

$$I = I_{sc} - I_0 \left(e^{q/nkT (V + nR_s I)} - 1 \right) - \frac{V + nR_s I}{n \cdot R_p}$$


From Modules to Arrays

Wednesday, April 15, 2020 10:35 AM

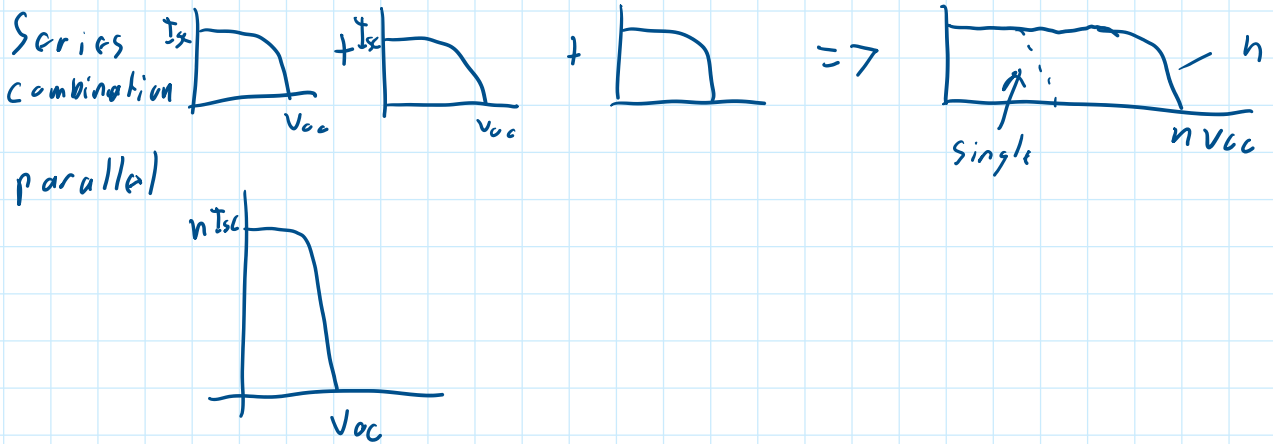- We can see that modules can be wired in series to increase voltage, and in parallel to increase current
- In practice, arrays are made up of a combination of series and parallel modules
- From the previous analysis, we can see how we can obtain V-I curves for any given parallel/series combination




what about combination?

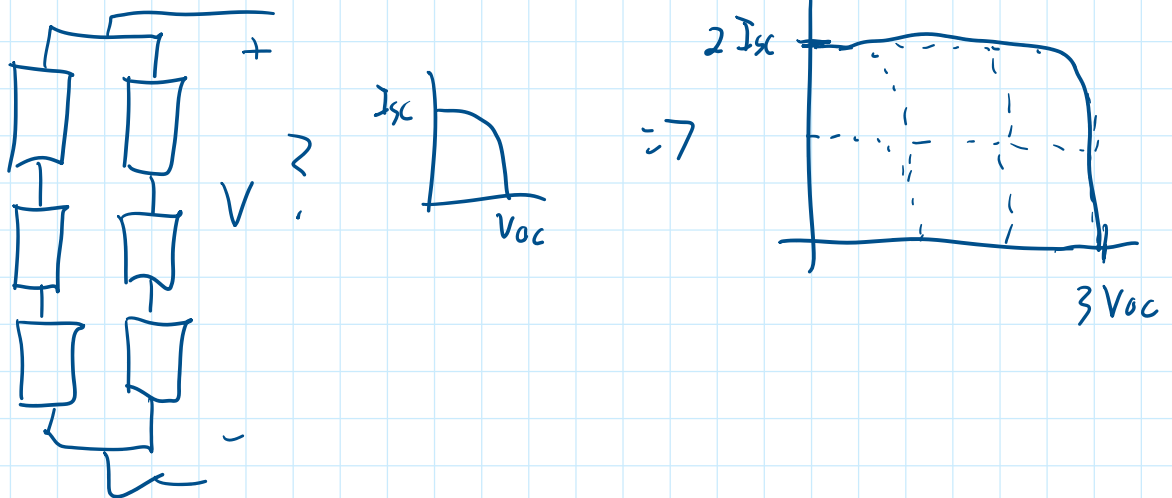

ways to wire

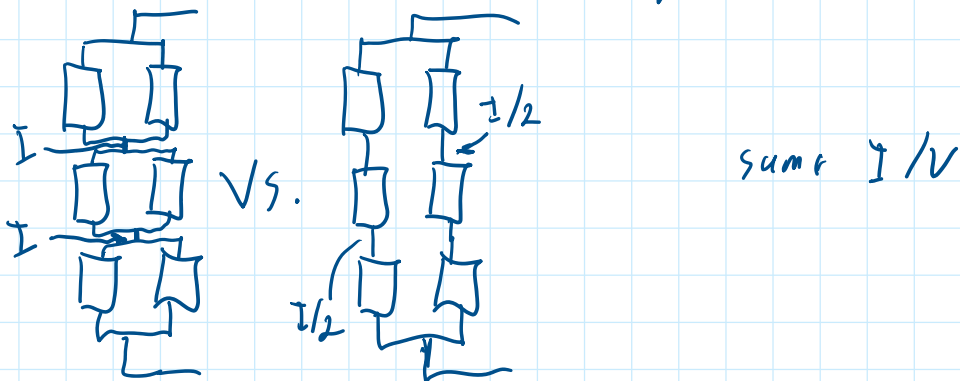- i) parallel first, then series (parallel/series)
- ii) series then parallel (series/parallel)




→ the series/parallel is preferred

↳ can remove single string and still deliver same voltage

↳ minimizes interconnecting wires & I^2R losses

Maximum Power Point of a PV Array

Wednesday, April 15, 2020 10:49 AM

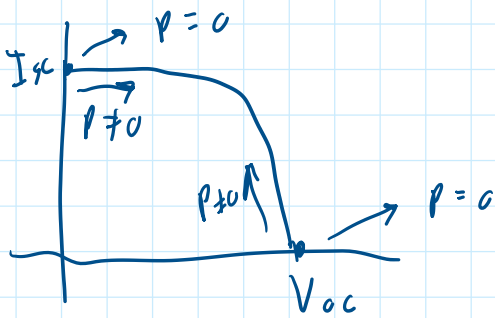

Question: what point on the curve extracts the most power from the cell/module/array?


The hard way:

$$P = VI = V \left[I_{sc} - I_0 e^{\frac{qV}{nkT}} - 1 \dots \right]$$

$$\frac{dP}{dV} = 0 \Rightarrow \dots \text{ Math}$$

OR

Notice that $V \cdot I = P$

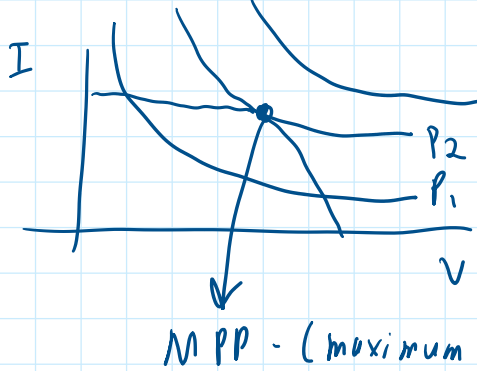


→ These curves are constant power


→ The maximum occurs for the curve that is tangent to the I-V curve
 ↳ this occurs at the knee of the solar I-V curve

MPP - (maximum power point)

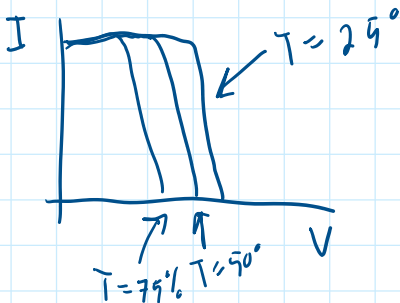Impacts of temp. and Insolation on I-V curves




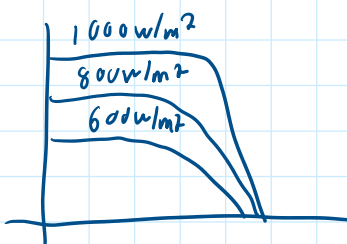V_{oc} decreases $\sim 0.33\%$ per $^{\circ}C$
 I_{sc} only decreases $\sim 0.05\%$



As insolation drops, short-circuit current drops in direct proportion. cutting insolation in half drops I_{sc} by half

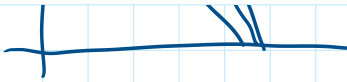Decreasing insolation also decreases V_{oc} , but only at a logarithmic rate. V_{oc}



Decreasing insolation also decreases V_{oc} ,
but only at a logarithmic rate. V_{oc}
is only affected slightly

\Rightarrow Solar cells work best on cold, clear days