

ECE 329 Tutorial 17

(2019/11/18)

Reflection Coefficient at Load:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Reflection Coefficient at Source:

$$\Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0}$$

Voltage Standing Wave Ratio (VSWR):

$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

Input Impedance (seen by the source):

$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tanh(\gamma L)}{Z_0 + Z_L \tanh(\gamma L)}$$

Where γ is the complex wave number:

$$\gamma = \alpha + j\beta$$

If we assume lossless Transmission Line, then $\alpha = 0$ and $\gamma = j\beta$, and the input impedance for the case of lossless Transmission Line becomes:

$$Z_{in(Lossless)} = Z_0 \frac{Z_L + jZ_0 \tan(\beta L)}{Z_0 + jZ_L \tan(\beta L)}$$

Where L is the length of Transmission Line, and β the propagation wave number along the line.

Problem 1 (Warm-Up Calculation):

A source with source impedance $Z_S = 50\Omega$ drives a transmission line with characteristic impedance $Z_0 = 50\Omega$ that is $\frac{1}{8}$ of a wavelength long, and is terminated by a load with load impedance $Z_L = 50 - 25j\Omega$.

- (a) Calculate the reflection coefficient at load Γ_L .
- (b) Calculate the Voltage Standing Wave Ratio (VSWR).
- (c) Calculate the input impedance seen by the source, assuming lossless transmission line.

Problem 2 (Calculation with Input Impedance):

The input impedance for a 30-cm length of lossless transmission line with characteristic impedance $Z_0 = 100\Omega$ operating at frequency $f = 2GHz$ is $Z_{in} = 92.3 - 67.5j\Omega$. The propagation phase velocity is $0.7 c$. Determine the load impedance.

ECE 329 Tutorial 17 Solution

(2019/11/18)

Problem 1:

$$(a) \quad I_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{-25j}{100 - 25j} = \frac{25e^{-j\frac{\pi}{2}}}{\sqrt{100^2 + 25^2} e^{-j\arctan(\frac{1}{4})}} = \frac{25}{\sqrt{100^2 + 25^2}} e^{j(\arctan(\frac{1}{4}) - \frac{\pi}{2})}$$

$$(b) |I_L| = \frac{25}{\sqrt{100^2 + 25^2}} \Rightarrow VSWR = \frac{1+|I_L|}{1-|I_L|}$$

$$(4) \quad \beta L = \frac{2\pi}{\lambda} \frac{\lambda}{8} = \frac{\pi}{4} \Rightarrow Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta L)}{Z_0 + jZ_L \tan(\beta L)}$$

$$= Z_0 \frac{Z_L + jZ_0}{Z_0 + jZ_L}, \text{ with } Z_L = 50 - 25j \Omega$$

$$Z_0 = 50 \Omega$$

Problem 2:

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi \cdot 5}{V_p} = \frac{2\pi \cdot 2 \times 10^9}{0.7 \cdot 3 \times 10^8} = \frac{40\pi}{2 \cdot 1} \Rightarrow \beta L = \frac{40\pi}{2 \cdot 1} \times 0.3 = \frac{40\pi}{7}$$

$$\text{We have: } Z_{in} = 92.3 - 67.5 j = Z_0 \frac{Z_L + j Z_0 \tan(\beta L)}{Z_0 + j Z_L \tan(\beta L)}$$

$$0.923 - 0.675j = \frac{Z_L + 100j \tan\left(\frac{40\pi}{7}\right)}{100 + Z_L j \tan\left(\frac{40\pi}{7}\right)}$$

Solve for Z_L , we have: $Z_L = 49.997 + 0.015j$ Ω

ECE 329 Tutorial 18

(2019/11/21)

Reflection Coefficient at Load:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Input Impedance (seen by the source):

$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tanh(\gamma L)}{Z_0 + Z_L \tanh(\gamma L)}$$

Where γ is the complex wave number:

$$\gamma = \alpha + j\beta$$

If we assume lossless Transmission Line, then $\alpha = 0$ and $\gamma = j\beta$, and the input impedance for the case of lossless Transmission Line becomes:

$$Z_{in(Lossless)} = Z_0 \frac{Z_L + jZ_0 \tan(\beta L)}{Z_0 + jZ_L \tan(\beta L)}$$

Where L is the length of Transmission Line, and β the propagation wave number along the line.

Input Voltage:

$$\tilde{V}_{in} = \tilde{V}_s \frac{Z_{in}}{Z_s + Z_{in}}$$

The voltage phasor at any point on the Transmission Line (starting at $z = -L$, terminating at $z = 0$ by the load) is:

$$\tilde{V}(z) = \tilde{V}_0^+ (e^{-\gamma z} + \Gamma_L e^{+\gamma z})$$

It is easy to see that:

$$\tilde{V}_{in} = \tilde{V}(z = -L) \quad \tilde{V}_{Load} = \tilde{V}(z = 0)$$

Problem 1 (Warm-Up):

The reflection coefficient at the load for a Transmission Line with $Z_0 = 50\Omega$ is measured as $\Gamma_L = 0.516e^{j8.2^\circ}$ at a certain operation frequency f . Find the load impedance Z_L .

Problem 2 (Find the Voltage Across the Load):

Consider the lossless Transmission Line shown in the figure below. The source voltage is $V_s(t) = 10\cos\left(\omega t + \frac{\pi}{6}\right) V$ with source impedance $Z_s = 25\Omega$. The Transmission Line has a characteristic impedance of $Z_0 = 50\Omega$ and length of $L = \frac{\lambda}{4}$, terminated by the load with load impedance of $Z_L = 100\Omega$. Find the voltage across the load as a function of time ($V_L(t)$).

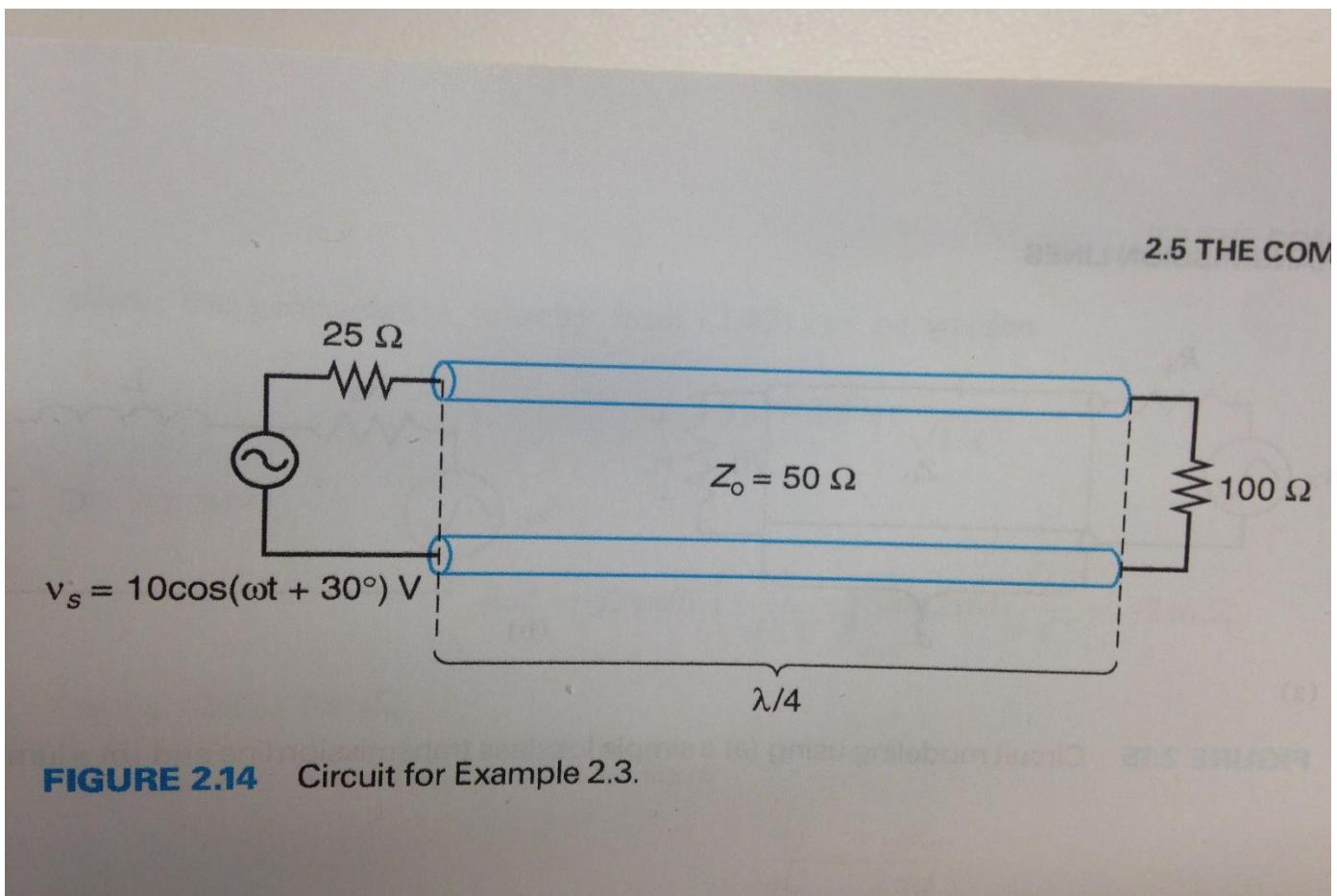


FIGURE 2.14 Circuit for Example 2.3.

ECE 329 Tutorial 18 Solution

(2019/11/21)

Problem 1:

$$V_s(t) = 10 \cos(\omega t + \frac{\pi}{6}) \Rightarrow \tilde{V}_s = 10 e^{j\frac{\pi}{6}}$$

$$I_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50}{150} = \frac{1}{3}$$

$$\beta L = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2} \Rightarrow \tan(\beta L) = \tan(\frac{\pi}{2}) = \infty$$

$$\begin{aligned} \text{We have: } Z_{in} &= Z_0 \frac{Z_L + jZ_0 \tan(\beta L)}{Z_0 + jZ_L \tan(\beta L)} \quad (\text{assuming lossless } \gamma \rightarrow j\beta) \\ &= Z_0 \frac{Z_0}{Z_L} \\ &= 25 \Omega \end{aligned}$$

$$\text{consequently, we have: } \tilde{V}_{in} = \tilde{V}_s \frac{Z_{in}}{Z_{in} + Z_s} = \frac{1}{2} \tilde{V}_s = 5 e^{j\frac{\pi}{6}}$$

$$\begin{aligned} \tilde{V}_{in} &= \tilde{V}_o (e^{-\gamma z} + I_L e^{\gamma z}) \Big|_{z=-L} \\ &= \tilde{V}_o (e^{\gamma L} + I_L e^{-\gamma L}) \\ &= \tilde{V}_o (e^{j\beta L} + I_L e^{-j\beta L}), \text{ since lossless } \gamma = j\beta \\ &= \tilde{V}_o (e^{j\frac{\pi}{2}} + I_L e^{-j\frac{\pi}{2}}) \\ &= \tilde{V}_o \left(\frac{2}{3} j \right) \end{aligned}$$

$$\tilde{V}_o = \frac{3 \tilde{V}_{in}}{2j} = \frac{3 \tilde{V}_{in}}{2 e^{j\frac{\pi}{2}}} = \frac{15}{2} e^{-j\frac{\pi}{3}}$$

$$\begin{aligned}
 \text{Therefore, } \tilde{V}_L &= \tilde{V}(z=0) = \tilde{V}_0^+ (e^{-j\frac{\pi}{3}} + I e^{j\frac{\pi}{3}}) \Big|_{z=0} \\
 &= \tilde{V}_0^+ (1 + I_L) \\
 &= \frac{4}{3} \tilde{V}_0^+ \\
 &= 10 e^{-j\frac{\pi}{3}} \Rightarrow V_L(t) = \operatorname{Re} \{ \tilde{V}_L e^{j\omega t} \} \\
 &= 10 \cos(\omega t - \frac{\pi}{3}) V
 \end{aligned}$$

Problem 2:

$$I_L = \frac{Z_L - Z_0}{Z_L + Z_0} \Rightarrow Z_L = \frac{Z_0(1+I_L)}{1-I_L}, \text{ with } Z_0 = 50 \Omega \text{ and } I_L = 0.516 e^{j8.2^\circ}$$

↓

$$Z_L = 108.93 + 66.58 j \Omega$$