

LOGIC GATES USING BJT :


We will now use the BJT to design logic gates.

For logic gate design the BJT has the following two states of operation:

① ..SATURATION OR ② OFF

i.e the voltages and resistors are picked so that the above conditions hold. The transistor now behaves as a SWITCH

Consider the following circuit :

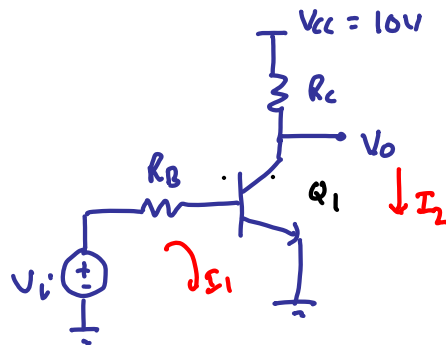

$$R_C = 1 \text{ k}\Omega$$

$$R_B = 1 \text{ k}\Omega$$

$$V_{BE(\text{on})} = 0.7 \text{ V}$$

Let :

Voltage	Logic Level
10 V →	1
0 V →	0

V_i	logic state i/p	Q_1 state	V_o	V_o State
0 V	0	OFF	10 V	1
10 V	1	SAT	0.2 V	0

∴ the circuit performs the NOT function

NOTE : $I_1 = \frac{10 - 0.7}{1 \text{ k}\Omega} = 9.3 \text{ mA}$


if we assume Q_1 is FA :

$$I_2 = \beta I_1 = 930 \text{ mA} \Rightarrow V_o = 10 - 930 \times 1 = -920 \text{ V}$$

∴ $Q_1 \rightarrow$ Saturated

$$I_2 = \frac{10 - 0.2}{1 \text{ k}\Omega} \Rightarrow \text{I}_2 = 9.8 \text{ mA}$$

②

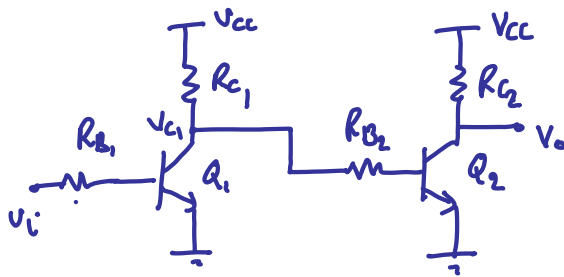


$V_{CC} = 10V$
 $R_{C1} = R_{C2} = R_{B1} = R_{B2} = 1k\Omega$
 $V_{BE(on)} = 0.7V$
 $V_{CE(sat)} = 0.2V$
 $\beta = 100$

V_i	Q_1	V_{C1}	Q_2	V_o
0V	OFF	10V	Sat	0.2V
10V	Sat	0.2V	OFF	10V


Assume : High : 5V - 10V
 Low : 0 - 1V

Input	Output
0	0
1	1

NOTE:

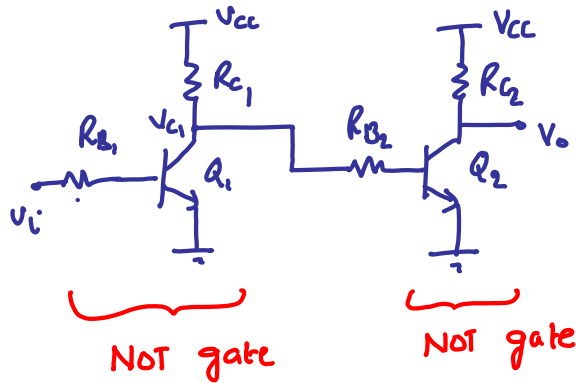

②

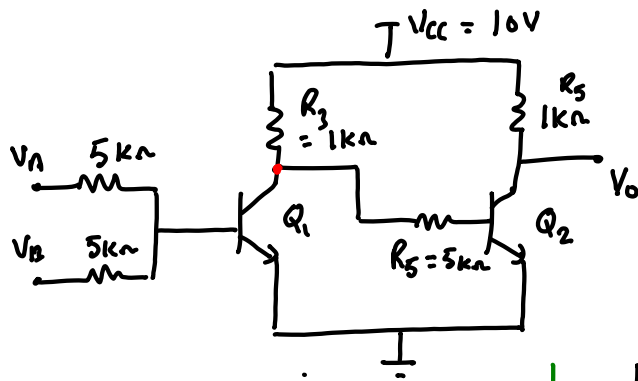

$V_{BE(ON)} =$
 $\beta = 100$


V_A	V_B	Q_1	Q_2	V_O
0V	0V	OFF	SAT	0.2
0V	10V	SAT	OFF	10V
10V	0V	SAT	OFF	10V
10V	10V	SAT	OFF	10

LOGIC FUNCTION :

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1


⇒ **OR GATE**

Transistor as a switch :

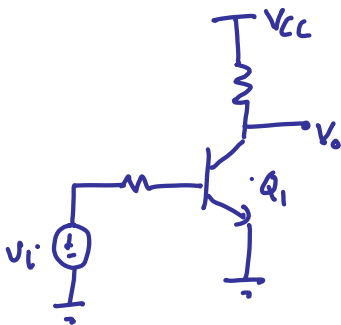


$V_i = 0 \Rightarrow Q_1 \text{ OFF}$


$V_{CC} = 10V$
 $V_{CE(sat)} = 0.2V$

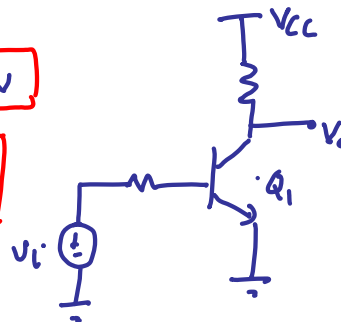

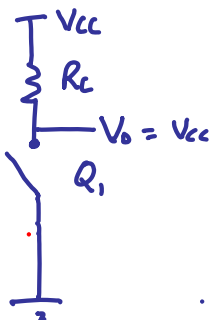$V_i = 10V \Rightarrow Q_1 \text{ SAT (ON)}$




$\therefore V_O = V_{CC}$

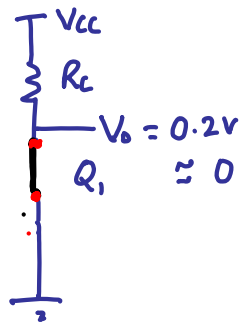

$V_O = 0.2V \approx 0V$


Consider two transistor in series

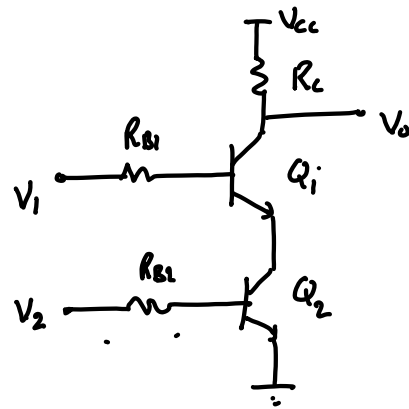


$$V_{CC} = 10V$$

$$V_{CE(sat)} = 0.2V$$

① $V_1 = V_2 = 0V$

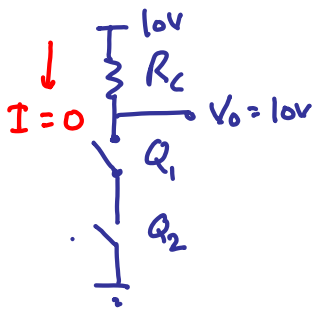

② $V_1 = 10V$ $V_2 = 0V$

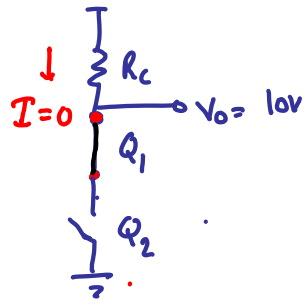

③ $V_1 = 0V$ $V_2 = 10V$

