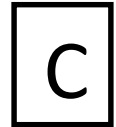


INSTRUCTIONS:



Begin the test when you are verbally instructed. You have **40 minutes** to complete the exam.

Write your name and netid on first page.

This is a closed book, closed notes quiz. **An equation sheet is provided at the end of the quiz.** A calculator is allowed.

No credit will be given for each problem if you do not show the complete work, even if the answer is correct. **Numerical answers must be followed by units wherever units exist.**


Re-grading policy: You must request a regrade within 5 days following the day in which the exams are returned to the class. You must clearly state the reason you are requesting a regrade.

By signing below, as the student named above, I agree that I will observe the Student Code of the University of Illinois.


Signature: _____

UIN: _____

Problem 1 (6 points)

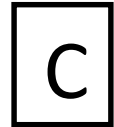

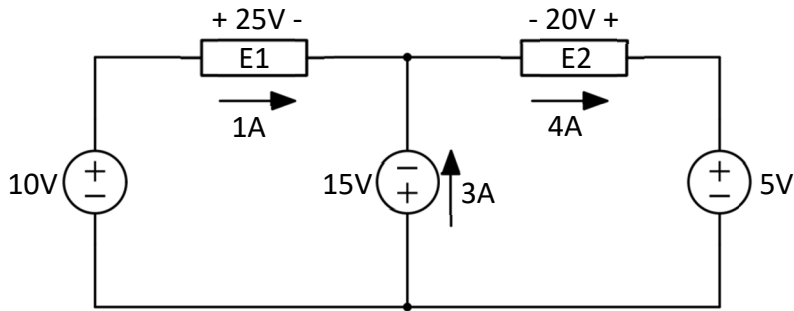
In the circuit shown below, find the power consumed or supplied by each element.




| Element | Power |
|---------|-------|
| E1 | |
| E2 | |
| 15V | |

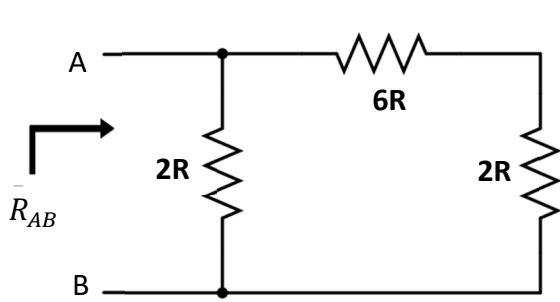Problem 2 (6 points)

Find equivalent resistance in the circuit shown below.



(a)

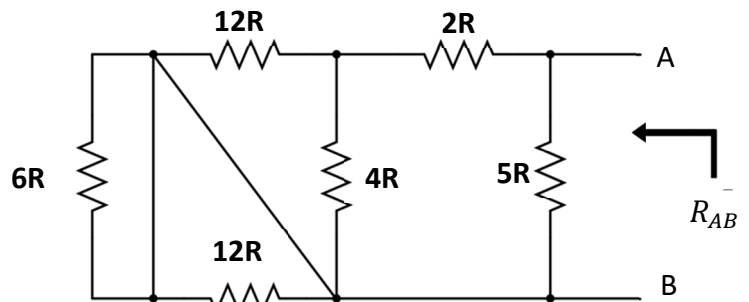


(b)


$R_{AB} =$

$R_{AB} =$


C**Problem 3 (6 points)**

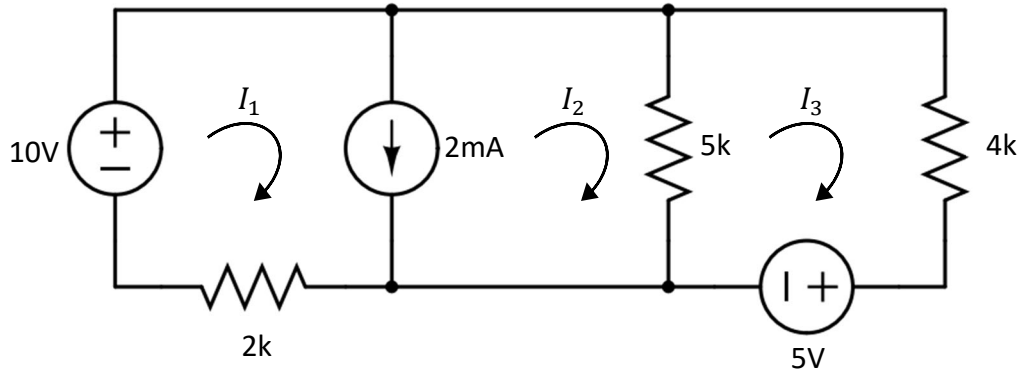Use **loop analysis** method to write a system of **at most three** equations you could use to find loop currents in the circuit below (DO NOT SOLVE).



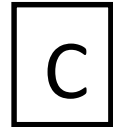Problem 4 (8 points)

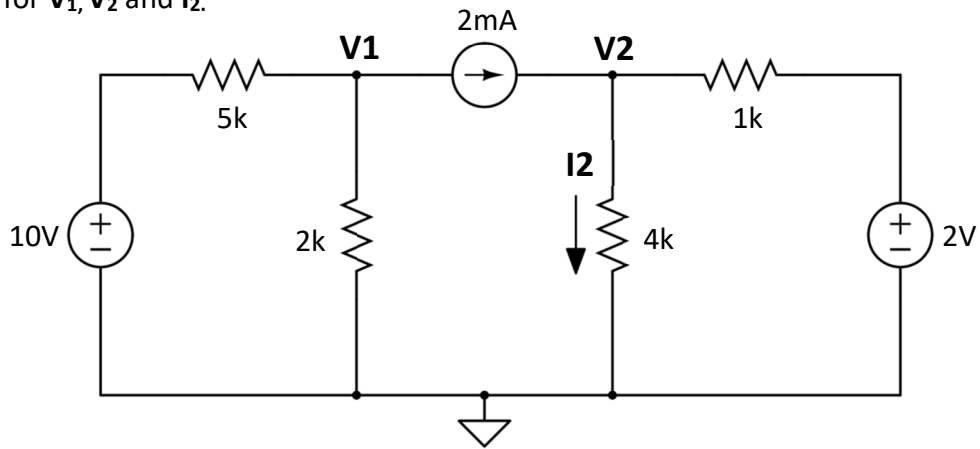- (a) Use node analysis and write **at most three** equations you would use to solve for V_1 , V_2 and I_2 .




- (b) Solve equations you obtained in part (a) to compute V_1 , V_2 and I_2 .

| | |
|-------|--|
| V_1 | |
| V_2 | |
| I_2 | |

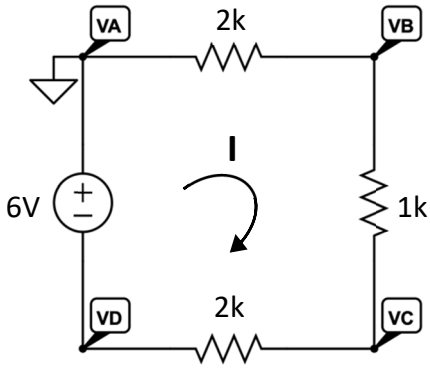Problem 5 (7 points)

C

In the circuit shown below, (a) Find the current I , voltage V_{AD} and V_A , (b) Find voltage V_B and V_C .




| | |
|----------|--|
| I | |
| V_{AD} | |
| V_A | |

| | |
|-------|--|
| V_B | |
| V_C | |

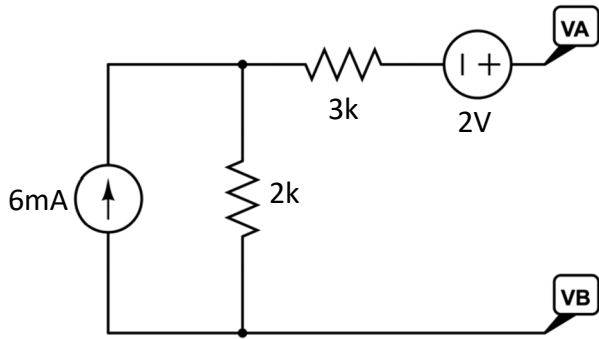Problem 6 (7 points)


C

Draw the **Thevenin equivalent circuit** between the terminals A-B in the circuit below.



Equivalent Circuit:


Ohm's Law:

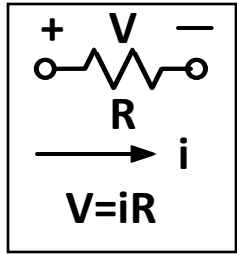

Resistor Combinations:

(a) Series:


$$R_{eq} = \sum_{k=1}^N R_N$$

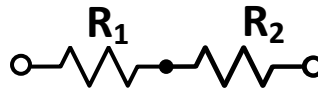

$$R_{eq} = R_1 + R_2$$

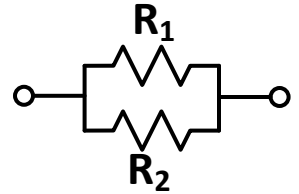
(b) Parallel:

$$\frac{1}{R_{eq}} = \sum_{k=1}^N \frac{1}{R_k}$$




$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Voltage and Current Dividers:

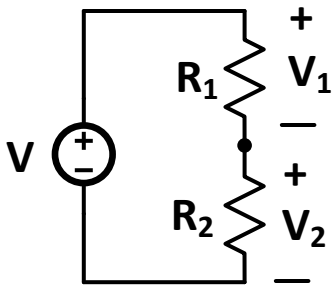

$$V_1 = \frac{VR_1}{R_1 + R_2}$$


$$V_2 = \frac{VR_2}{R_1 + R_2}$$

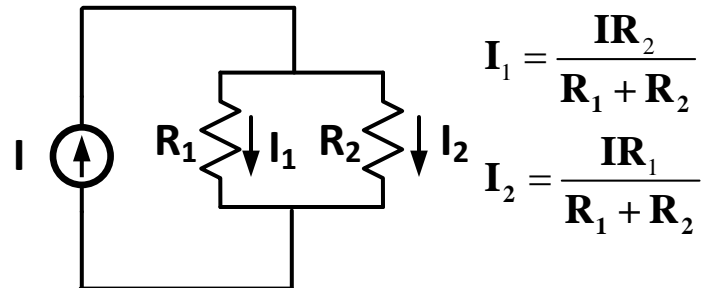

$$I_1 = \frac{IR_2}{R_1 + R_2}$$

$$I_2 = \frac{IR_1}{R_1 + R_2}$$

Source transformation

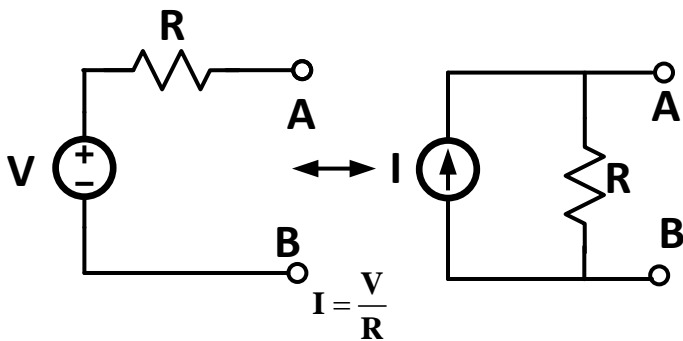

Thevenin Equivalent

