

Lecture 4 : Circuit Analysis, Resistors - Series/Parallel

Learning Objectives:

1. Combine basic elements to sketch a complete circuit
2. Identify series and parallel combination of resistors
3. Compute equivalent resistance between two terminals

1. Circuit

An electrical circuit can be seen as an interconnection of electrical elements in a closed path such that current can continuously flow. An example of a circuit is shown below.

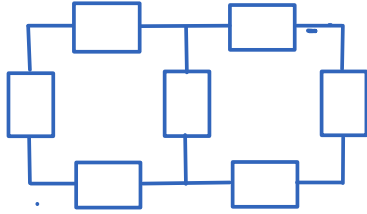


Fig 4.1 A simple electrical circuit.

2. Node

A point at which two or more elements are connected is called a node. This is illustrated below

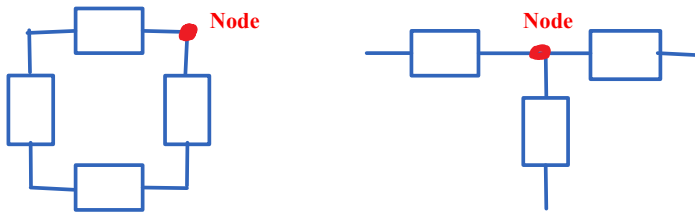


Fig 4.2 A simple electrical circuit.

3. Loop

Loop is a closed path in a circuit starting at a node, traversing through a series of nodes, and ending at the starting node without passing through the same node twice.

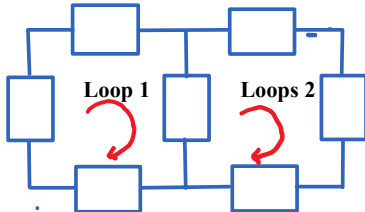


Fig 4.3 Loops in a circuit

4. Series-Connected Elements

Elements are said to be connected in series if:

1. They share **one** common node.
2. The elements carry the same current.

Figure below illustrates a series connection of elements. One can see that the same current flows in a serial fashion through the elements. It should also be noted that the order of elements does not matter for series connected elements.



Fig 4.4 Series connected elements. The order of elements can be changed.

5. Parallel-connected Elements

Two elements are connected in parallel if both ends of one element are connected to both ends of another elements by wires. Parallel connected elements have same voltage across them.

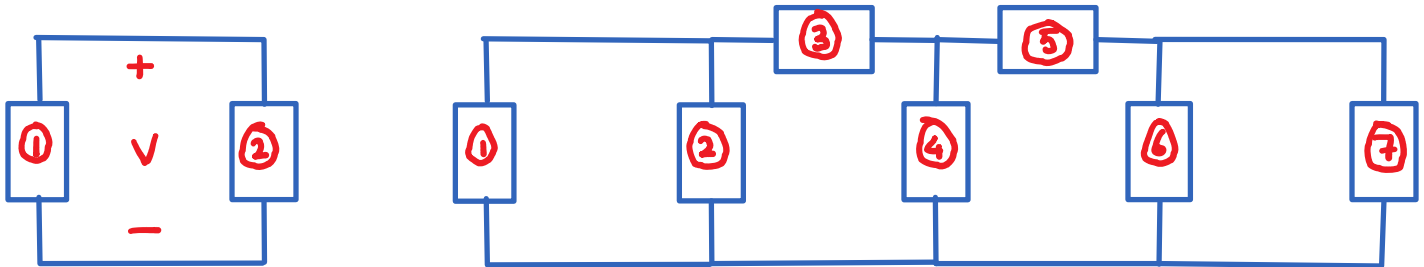


Fig 4.5 (a)

Fig 4.5 (b)

Fig. 4.5(a) and 4.5 (b) Examples of parallel connected elements.

Example:

Identify parallel connected elements in Fig. 4.5 (a) and Fig. 4.5 (b).

Solution:

Fig. 4.5 (a) - Elements 1 and 2.

Fig. 4.5 (b) - Elements 1,2 and Elements 6 and 7.

6. Series and Parallel connected resistors

We will now look at series and parallel connection of resistors. Often these resistors can be combined into an equivalent resistance and this can simplify circuit analysis considerably.

6.1 Series Connected resistors

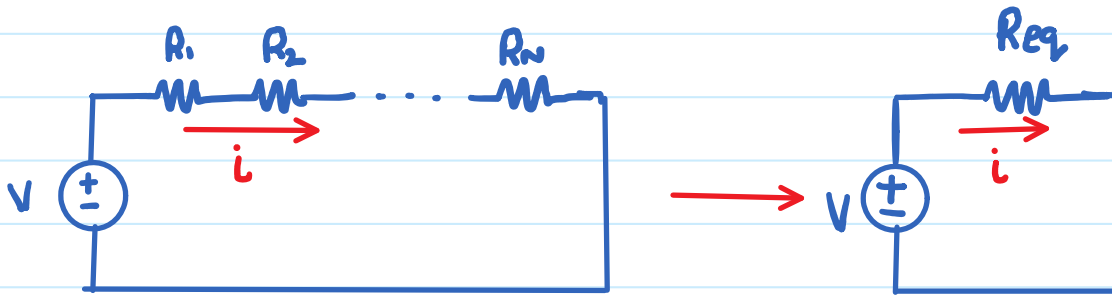


Fig. 4.6. Series connected resistors

Fig. 4.6 shows N resistors, R_1, R_2, \dots, R_N connected in series in a circuit. These N resistors can be replaced by an equivalent resistance R_{eq} given by,

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{k=1}^N R_k$$

i.e. series connected resistors can be replaced by an equivalent resistance of value equal to sum of the individual resistors. We will prove this in a later lecture when we discuss Kirchhoff's voltage law.

6.2 Parallel connected resistors

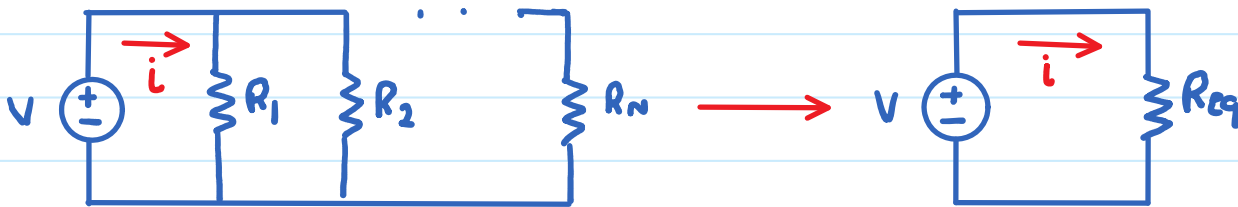


Fig 4.7. Parallel connected resistors

Fig. 4.7. shows N resistors, R_1, R_2, \dots, R_N , connected in parallel. The parallel resistors can be replaced by an equivalent resistance R_{eq} given by,


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = \sum_{k=1}^N \frac{1}{R_k}$$

We will prove this result when we discuss Kirchhoff's current law. For **two resistors**, R_1 and R_2 , in parallel the above expression takes a simpler form.


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Examples:

1. Compute equivalent resistance between terminals A-B in the circuits shown below

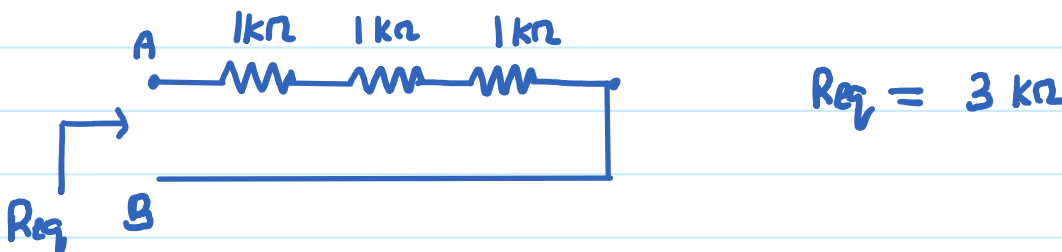

Ex 2.

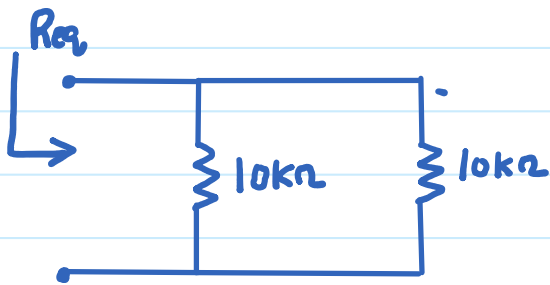


$$R_{eq} = \frac{10 \times 10}{10 + 10} = 5k\Omega$$

Note: N identical resistors have a parallel equivalent of

$$R_{eq} = \frac{R}{N}$$


Ex 3.

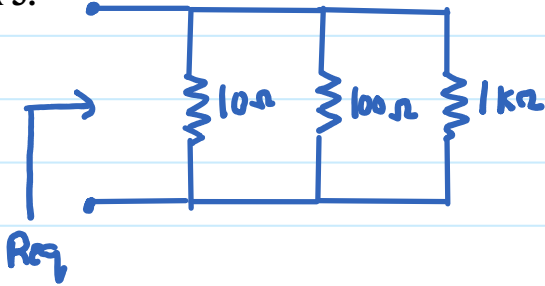

$$R_{eq} = 10 // 100 // 1000 = 9.01\Omega$$


Note: Parallel combination of resistors is dominated by the smallest value.

Ex 4.

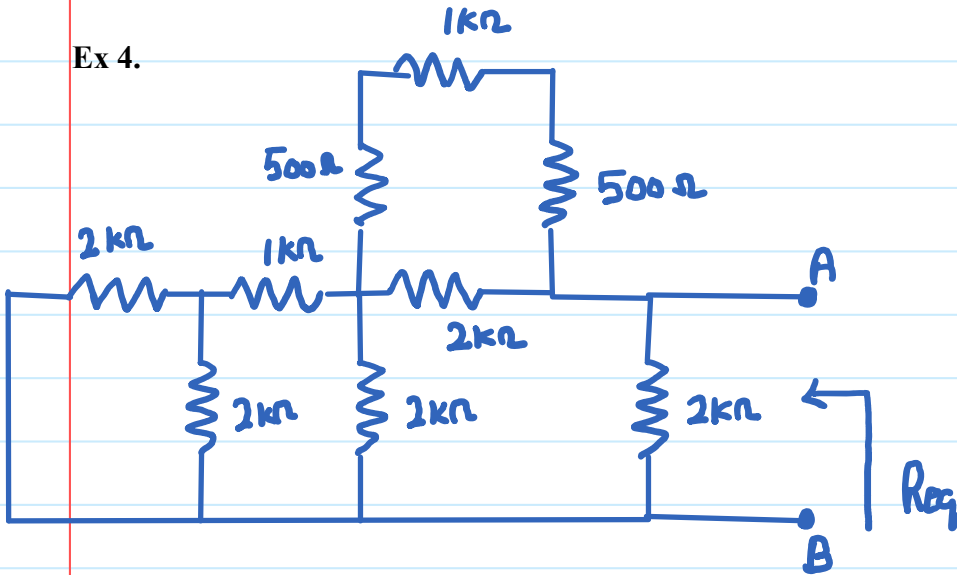


$$R_{eq} = (1+1) // 2$$


$$R_{eq} = 1k\Omega$$

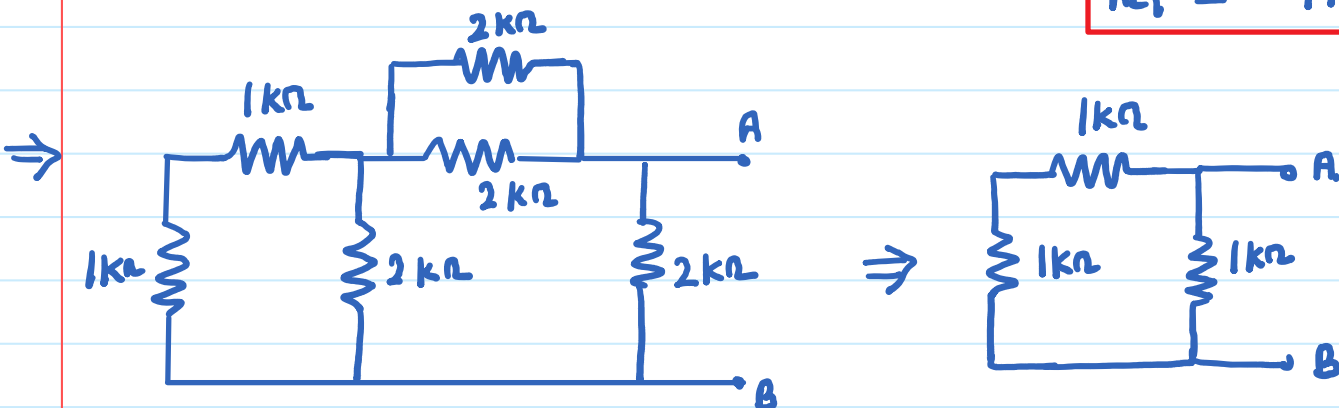



Ex 5. Solved in class!

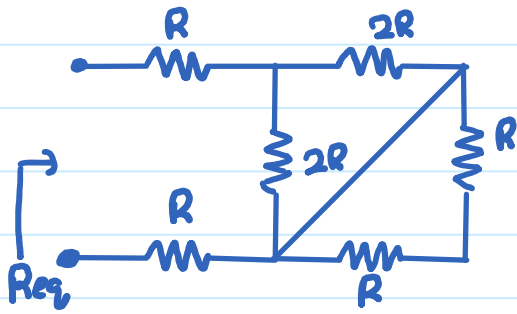


Ex 6. Solved in class!

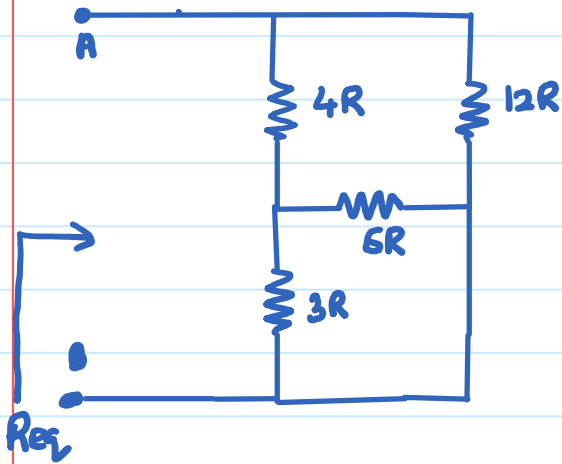

Ex 7. Find R_{eq} current I in the circuits shown below.

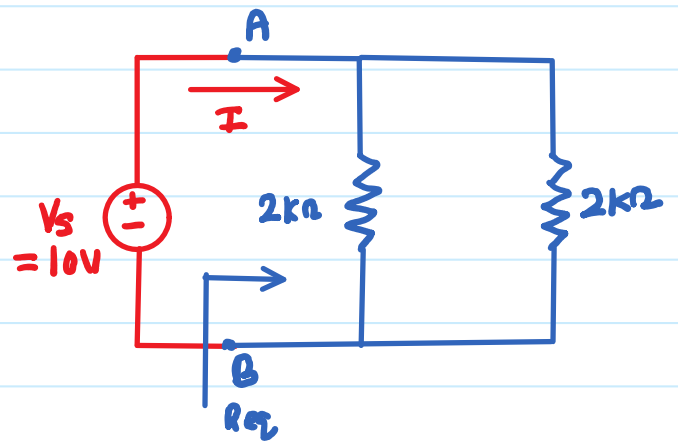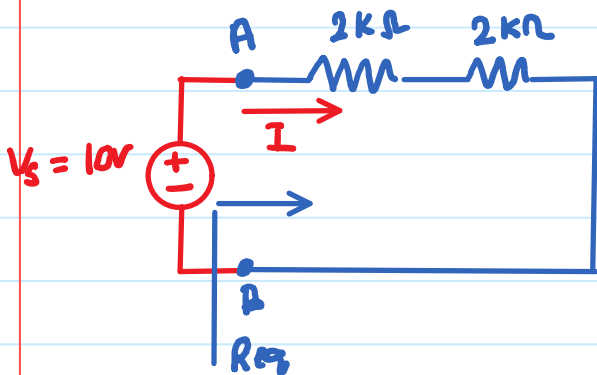

Ex 8. Find R_{eq} and current I in the circuit shown below.

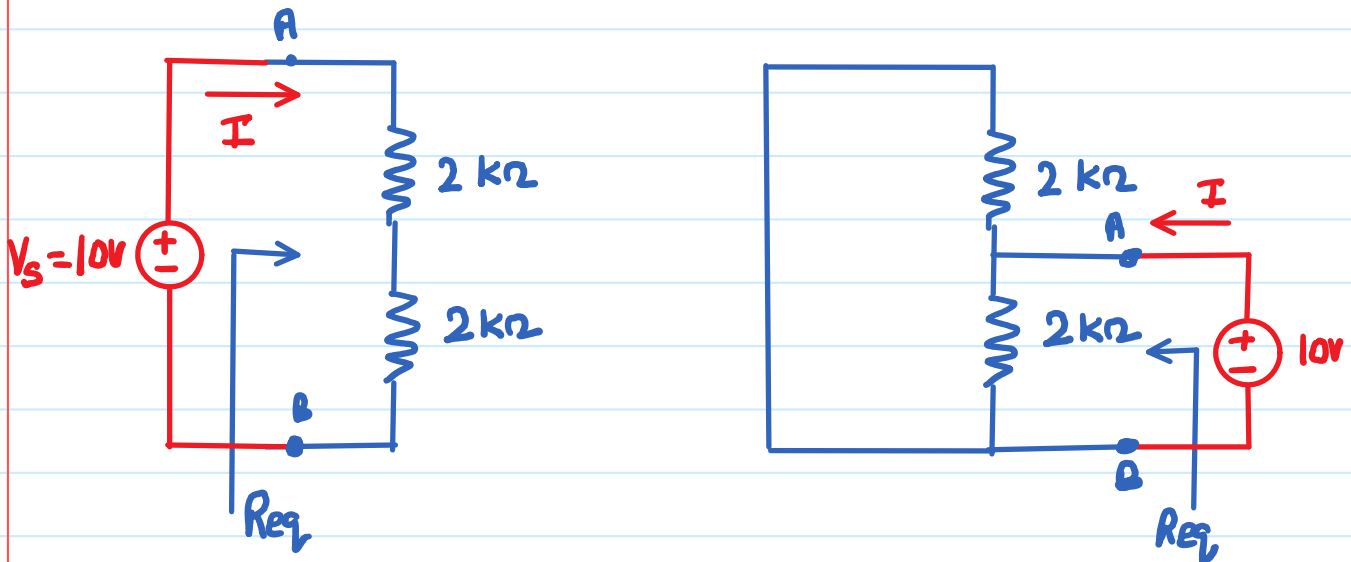

Ex 9. Find R_{eq} and current I in the circuit shown below.

