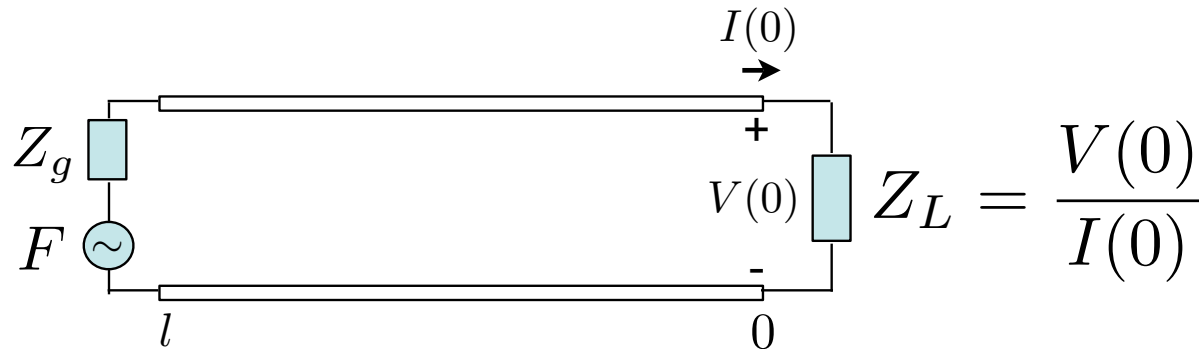


TL terminated by arbitrary load




normalized load
impedance:

$$z_L \equiv \frac{Z_L}{Z_0} = r_L + jx_L$$

load reflection
coefficient:

$$\Gamma_L \equiv \Gamma(d=0) = \frac{V^-(0)}{V^+(0)} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$

TL terminated by arbitrary load

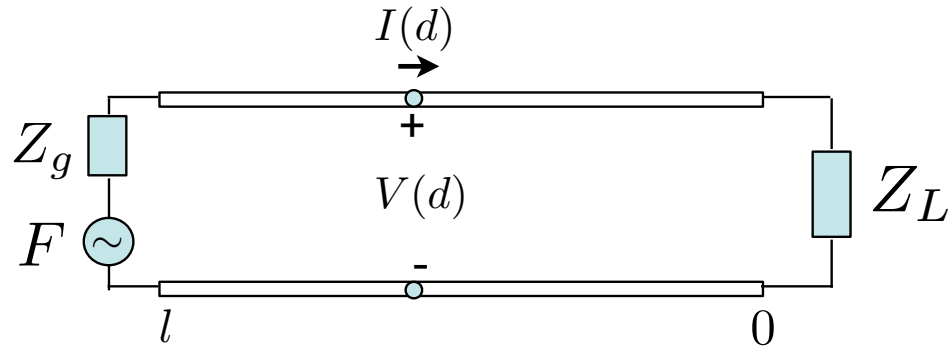

normalized line
impedance:

$$z(d) \equiv \frac{Z(d)}{Z_0} = \frac{V(d)}{Z_0 I(d)} = \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

generalized
reflection
coefficient:

$$\Gamma(d) \equiv \frac{V^-(d)}{V^+(d)} = \Gamma_L e^{-j2\beta d} = \frac{z(d) - 1}{z(d) + 1}$$

Graphical representation of $\Gamma(d)$ transformations:

$$\Gamma(d) = \Gamma_L e^{-j2\beta d} \quad \text{where} \quad |\Gamma(d)| = |\Gamma_L| \leq 1$$

$$\angle\Gamma(d) = \angle\Gamma_L - 2\beta d$$


As d changes, we trace out a **circle of constant radius** on the complex Γ plane:

A **full circle** is traced out when

$$2\pi = 2\beta d = 2(2\pi/\lambda)d$$

$$d = \lambda/2$$

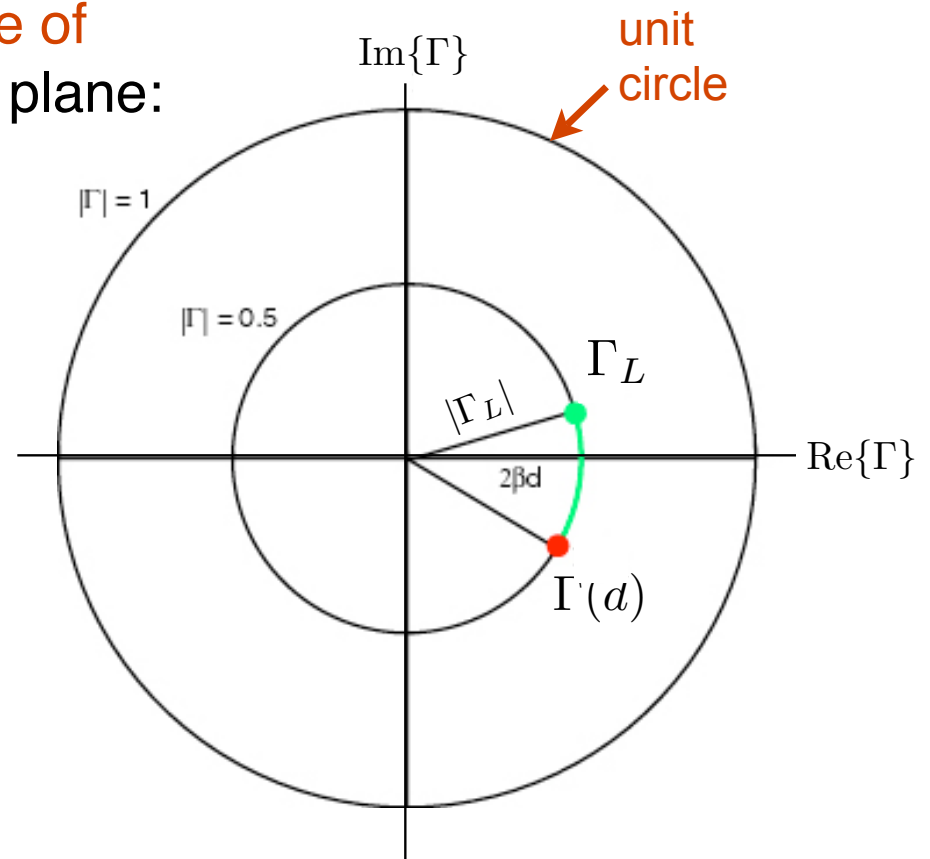Increasing d (towards generator) corresponds to **CLOCKWISE** rotation around the circle




Visualize standing wave patterns in voltage and current:

$$V(d) \propto |1 + \Gamma(d)|$$

$$I(d) \propto |1 - \Gamma(d)|$$

standing waves characterized by:

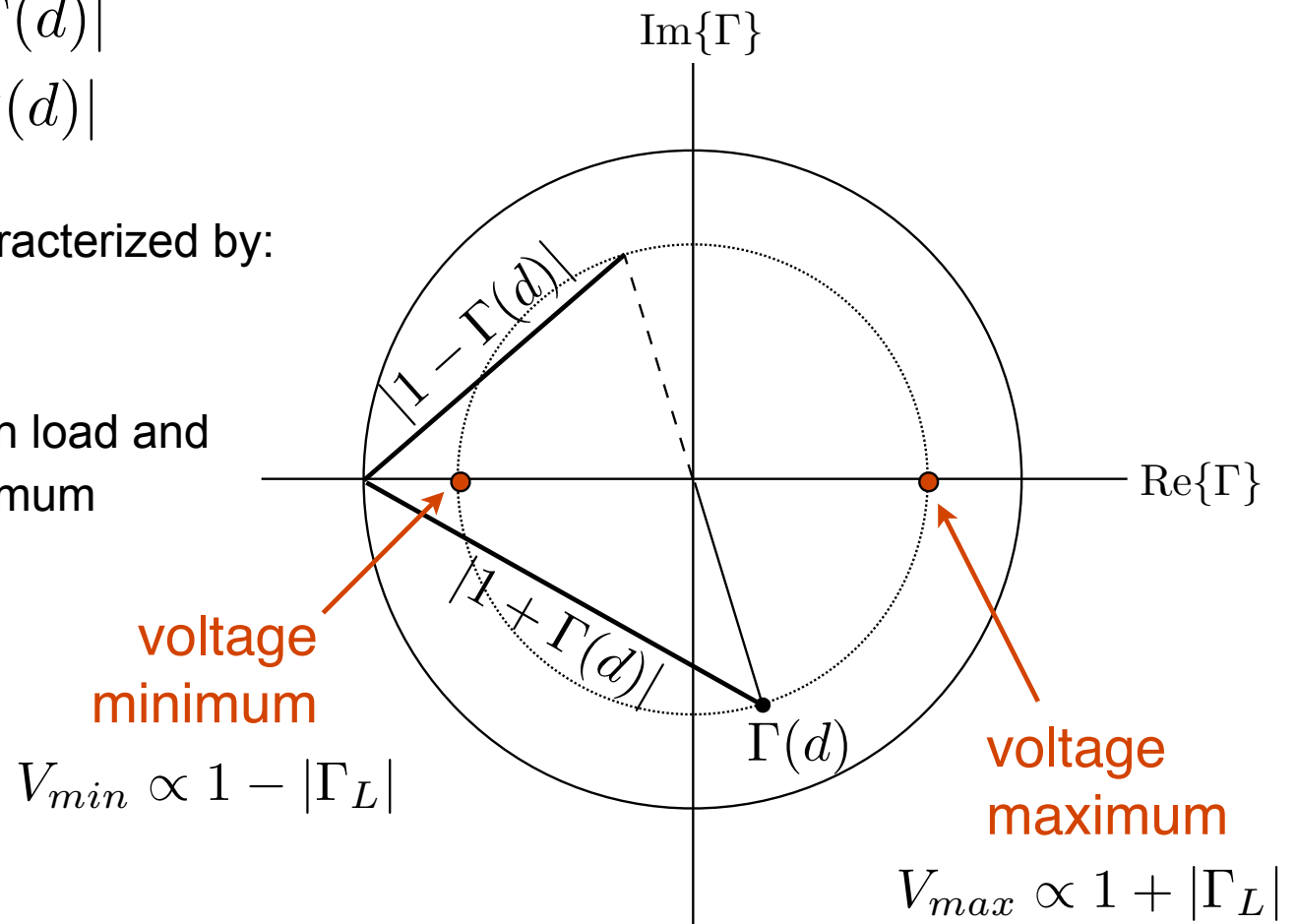- (1) $SWR = V_{max}/V_{min}$
- (2) wavelength
- (3) distance between load and first voltage minimum




Separate real and imaginary parts of Γ to find special cases:

$$\begin{aligned}\Gamma(d) = \Gamma_r + j\Gamma_i &= \frac{(r + jx) - 1}{(r + jx) + 1} \\ &= \frac{r^2 - 1 + x^2}{(r + 1)^2 + x^2} + j \frac{2x}{(r + 1)^2 + x^2}\end{aligned}$$

CASE: $z(d)$ purely real (so $x = 0$)

$$\Gamma(d) = \frac{r - 1}{r + 1} + j0$$

r	Γ
0	-1
1/3	-1/2
1	0
3	1/2
∞	1

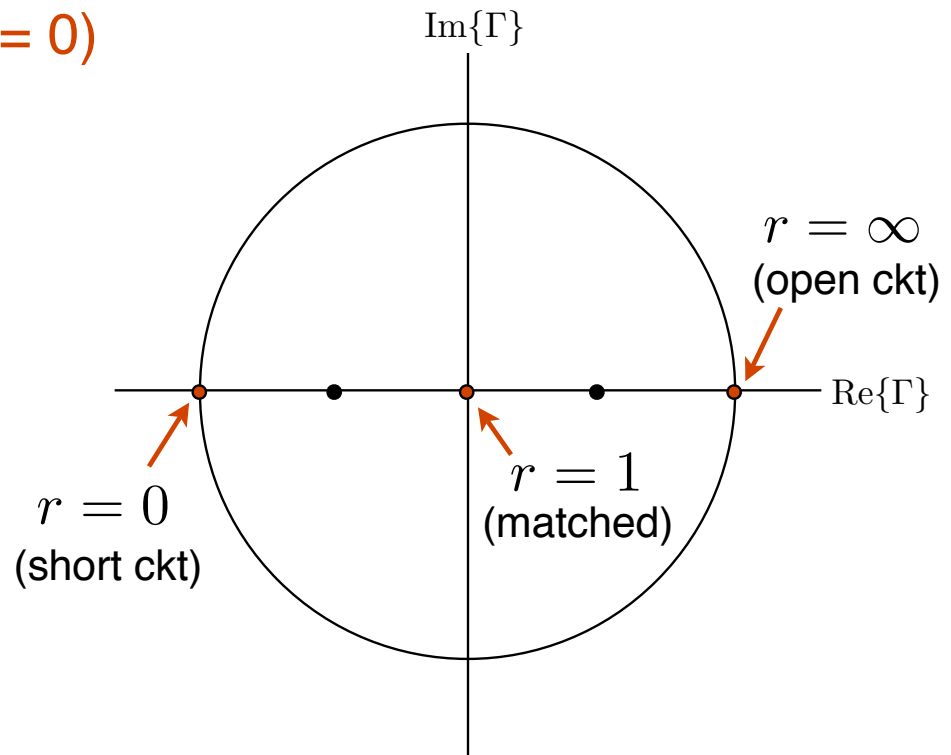


Separate real and imaginary parts of Γ to find special cases:

$$\begin{aligned}\Gamma(d) = \Gamma_r + j\Gamma_i &= \frac{(r + jx) - 1}{(r + jx) + 1} \\ &= \frac{r^2 - 1 + x^2}{(r + 1)^2 + x^2} + j \frac{2x}{(r + 1)^2 + x^2}\end{aligned}$$

CASE: $z(d)$ purely imaginary (so $r = 0$)

$$|\Gamma(d)| = \left| \frac{x^2 - 1}{x^2 + 1} + j \frac{2x}{x^2 + 1} \right| = 1$$

x	$\angle \Gamma$
0	π
1	$\pi/2$
∞	0
-1	$-\pi/2$
$-\infty$	$-\pi$

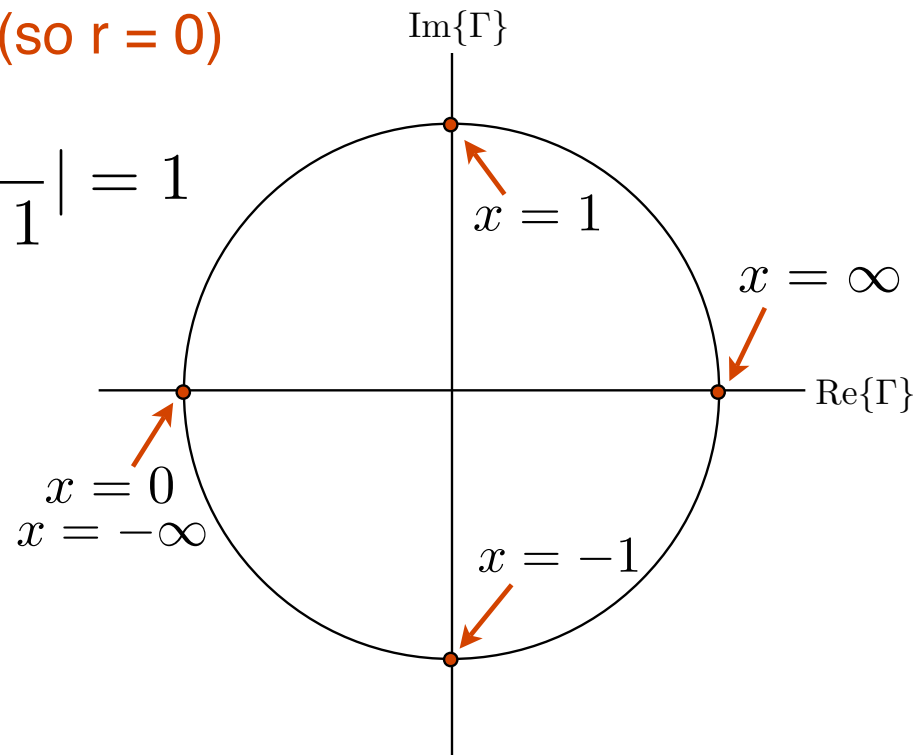

Separate real and imaginary parts of z to find general contours:

$$z = r + jx = \frac{1 + (\Gamma_r + j\Gamma_i)}{1 - (\Gamma_r + j\Gamma_i)} = \frac{1 - \Gamma_r^2 - \Gamma_i^2 + j2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$


contours of constant r? equate real parts of above expression

$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2$$

yields the equation of a circle with

center at: $(\Gamma_r, \Gamma_i) = \left(\frac{r}{1+r}, 0\right)$

radius of: $\frac{1}{1+r}$

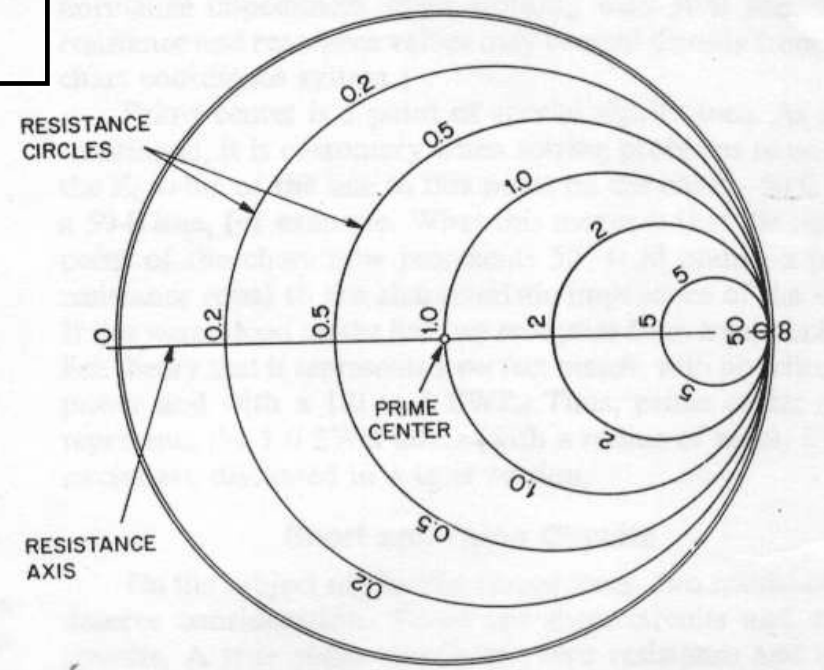

Separate real and imaginary parts of z to find general contours:

$$z = r + jx = \frac{1 + (\Gamma_r + j\Gamma_i)}{1 - (\Gamma_r + j\Gamma_i)} = \frac{1 - \Gamma_r^2 - \Gamma_i^2 + j2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$


contours of constant x ? equate imag. parts of above expression

$$\left(\Gamma_r - 1\right)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

yields the equation of a circle with


center at: $(\Gamma_r, \Gamma_i) = \left(1, \frac{1}{x}\right)$


radius of: $\frac{1}{x}$

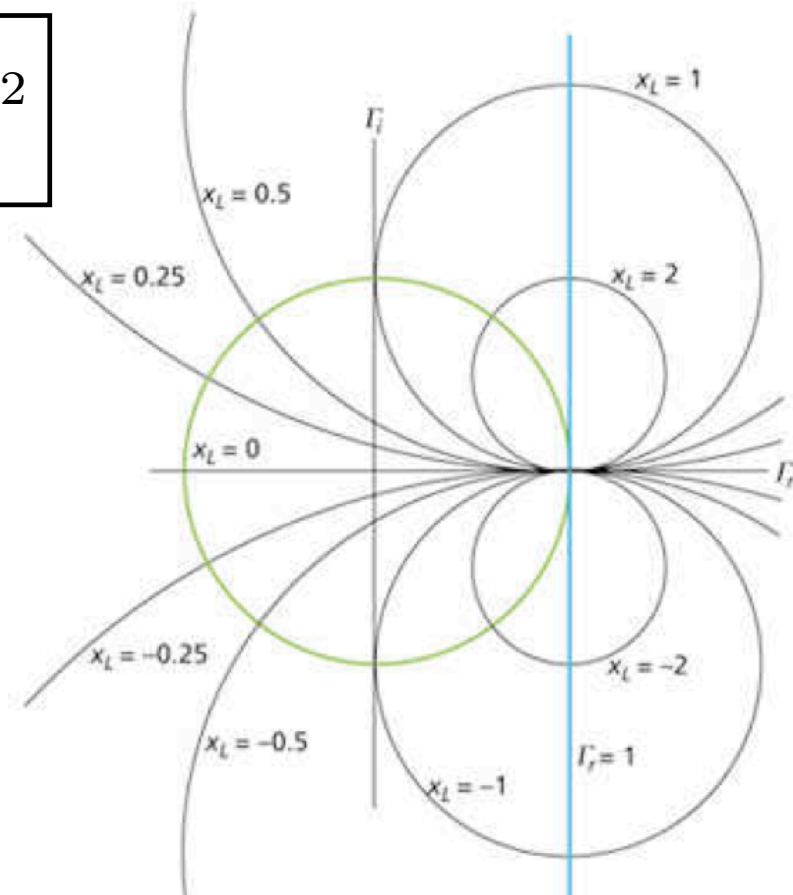


THE SMITH CHART

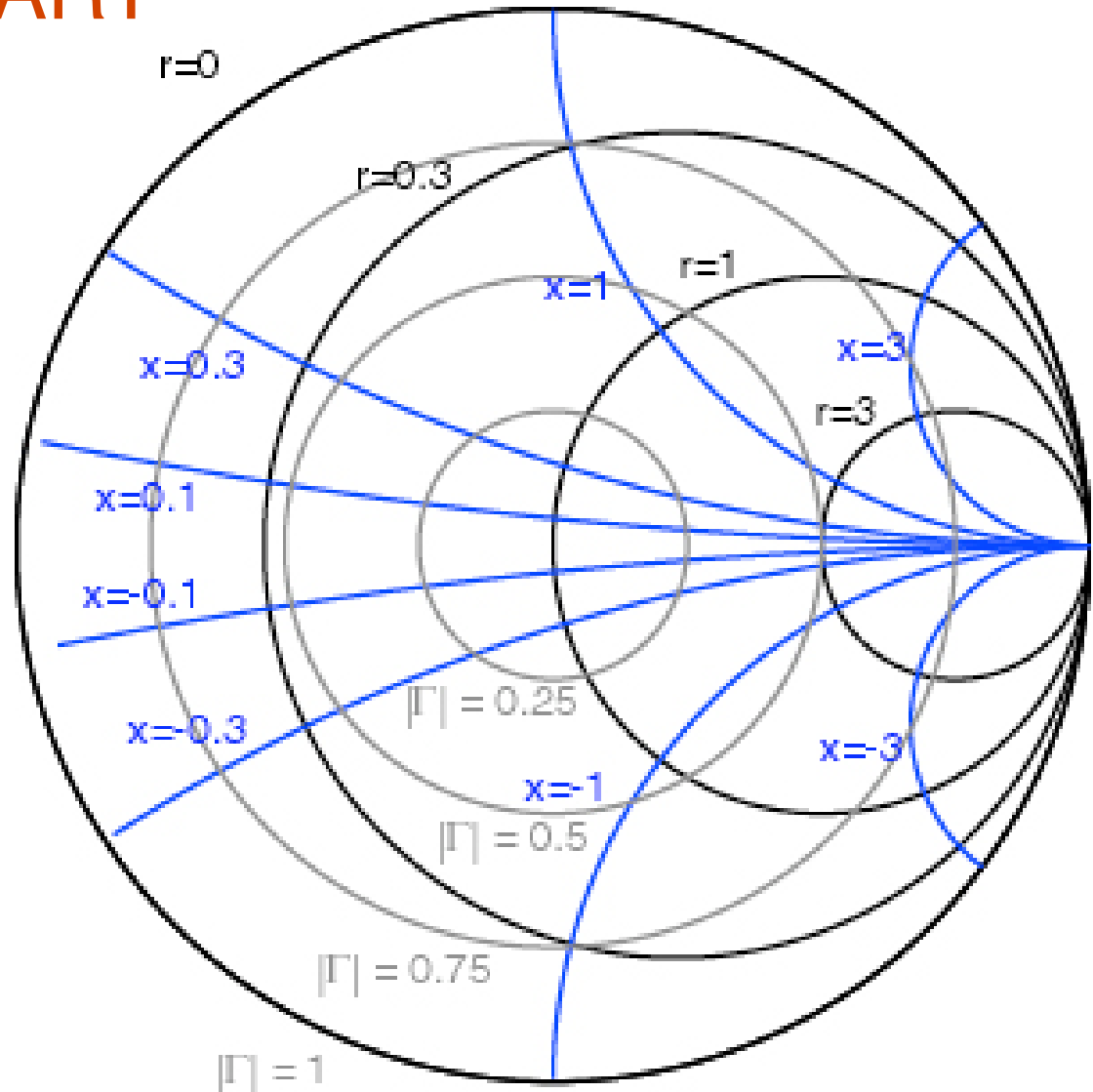- Superimposes constant r and x circles inside unit circle on the complex Γ plane
- By drawing the SWR circle on the chart, we can quickly relate $\Gamma(d)$ with the unique line impedance $z(d) = r + jx$ at that point



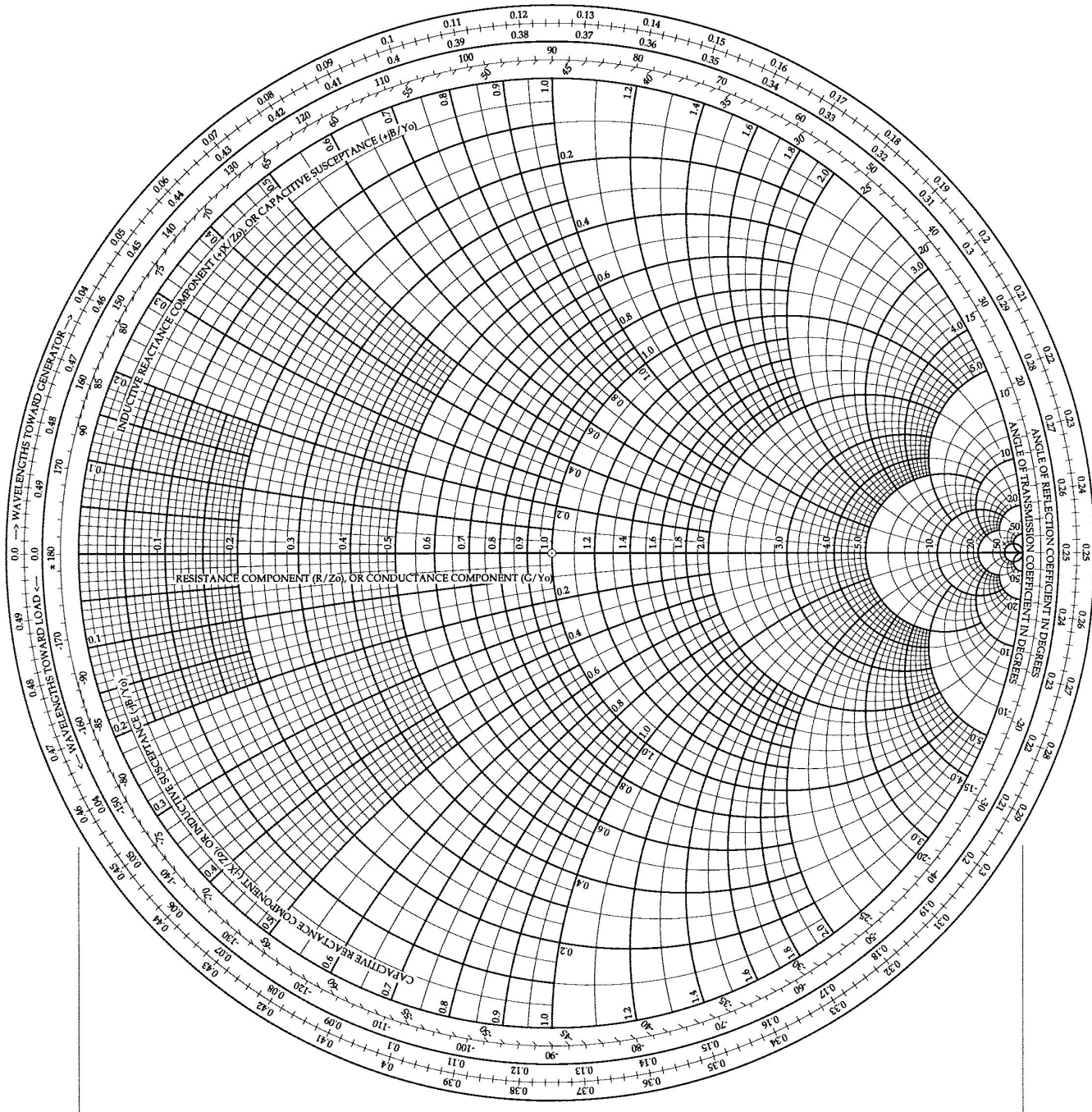

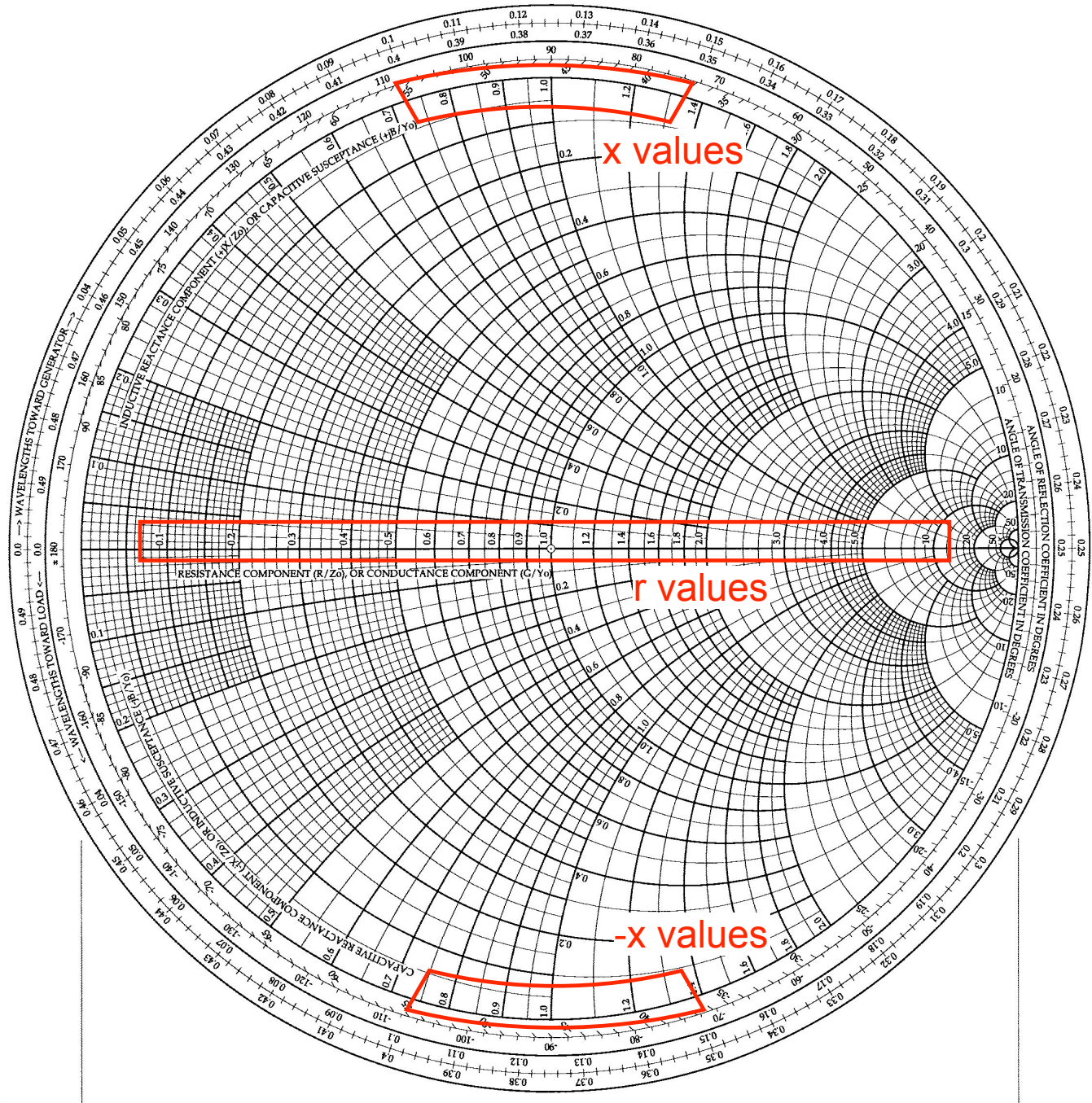


x values

r values

-x values


Distance (λ)
towards
generator

Distance (λ)
towards
load

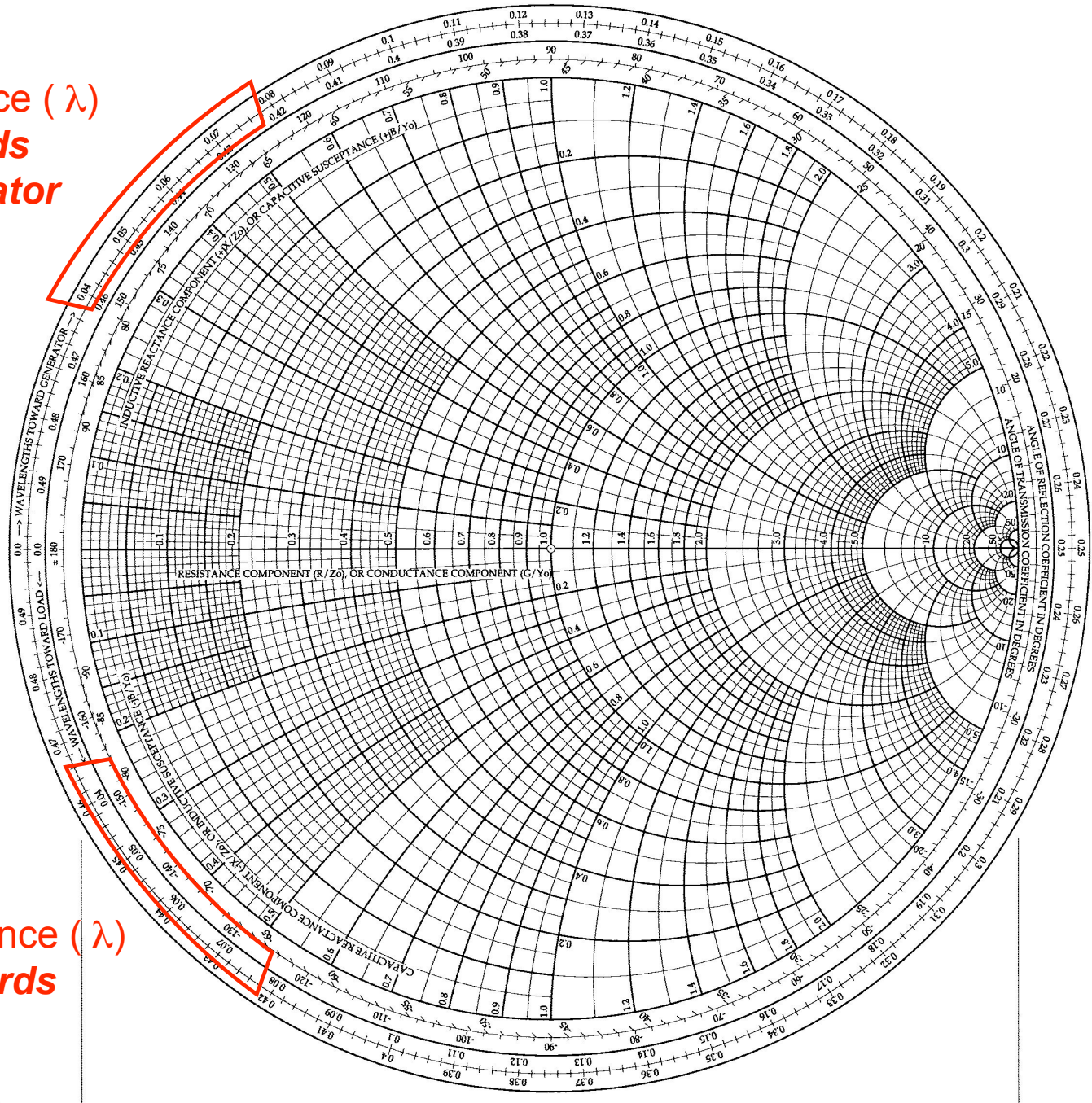

The standing wave ratio is read off of the chart by noting the r value where a constant Γ circle intersects the Γ_r axis

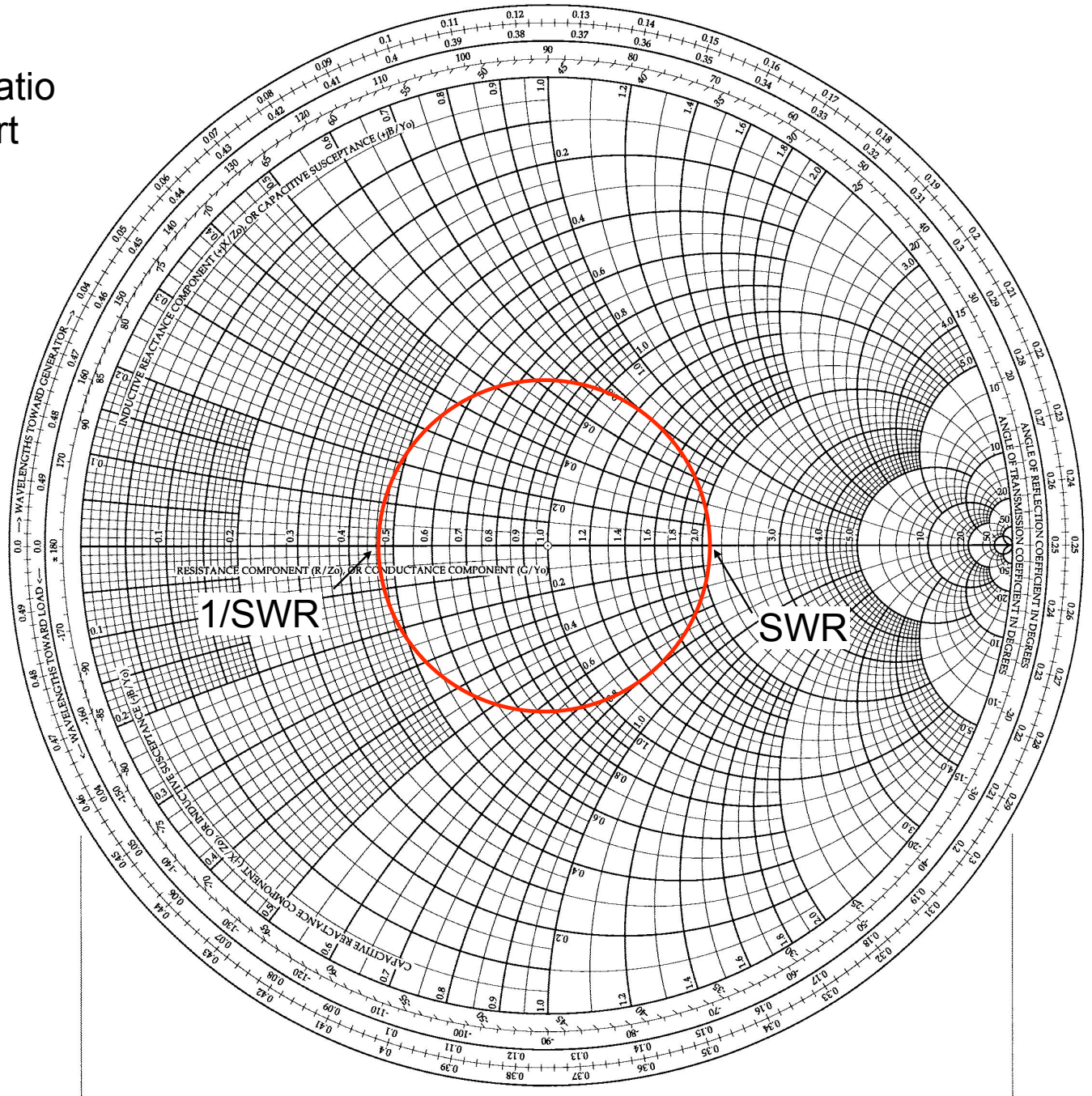
- 1) $SWR = Z_{max}/Z_0$
 $= z_{max}$
 $= r_{max}$
- 2) $SWR = Z_0/Z_{min}$
 $= 1/z_{min}$
 $= 1/r_{min}$



EXAMPLE:

If the effective reflection coefficient on a piece of 50Ω line is $\Gamma = 0.4 + j0.2$, what is the corresponding line impedance at that point ?

- 1) Find Γ on the Smith Chart

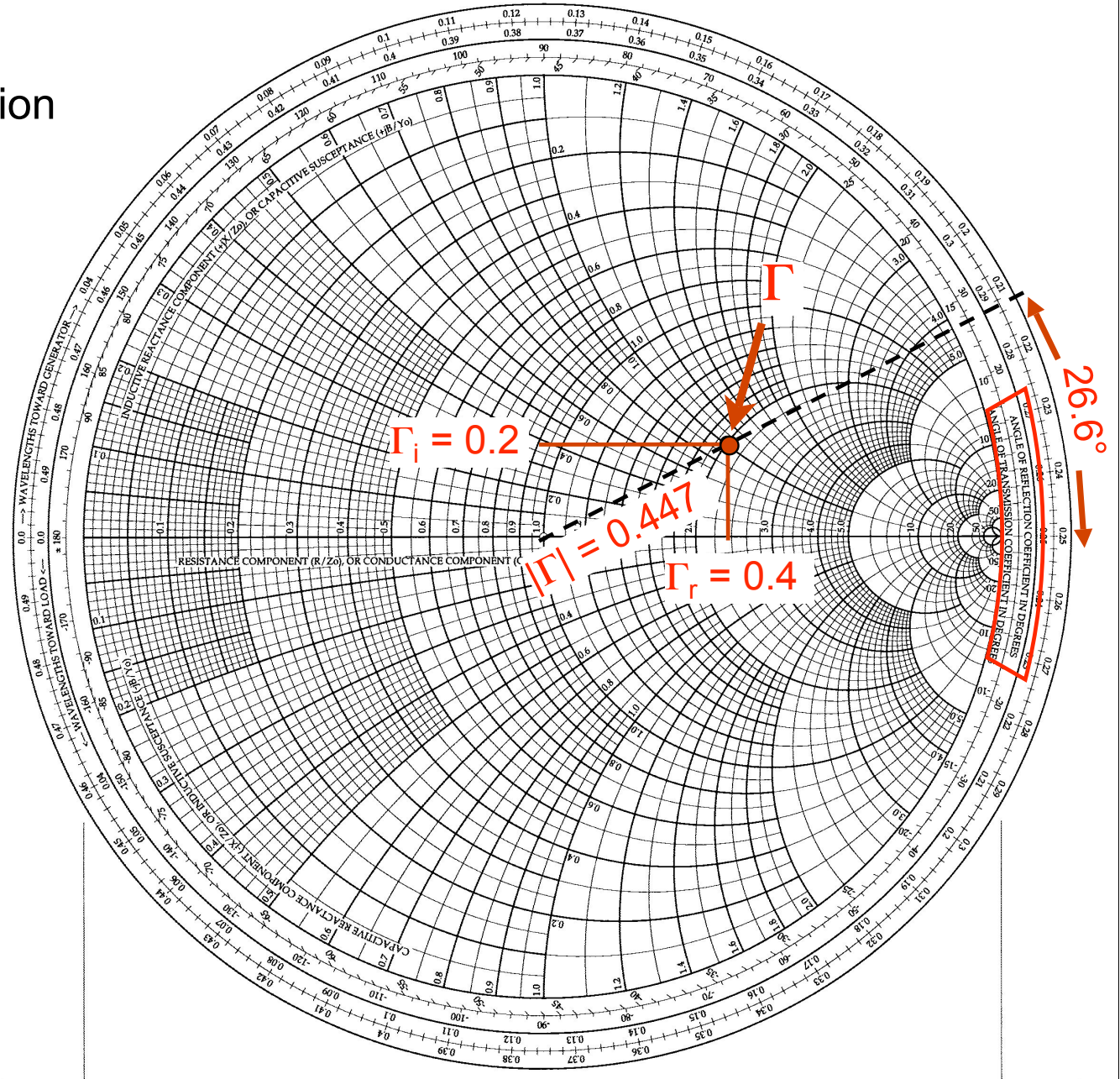


EXAMPLE:

If the effective reflection coefficient on a piece of $50\ \Omega$ line is $\Gamma = 0.4 + j0.2$, what is the corresponding line impedance at that point?

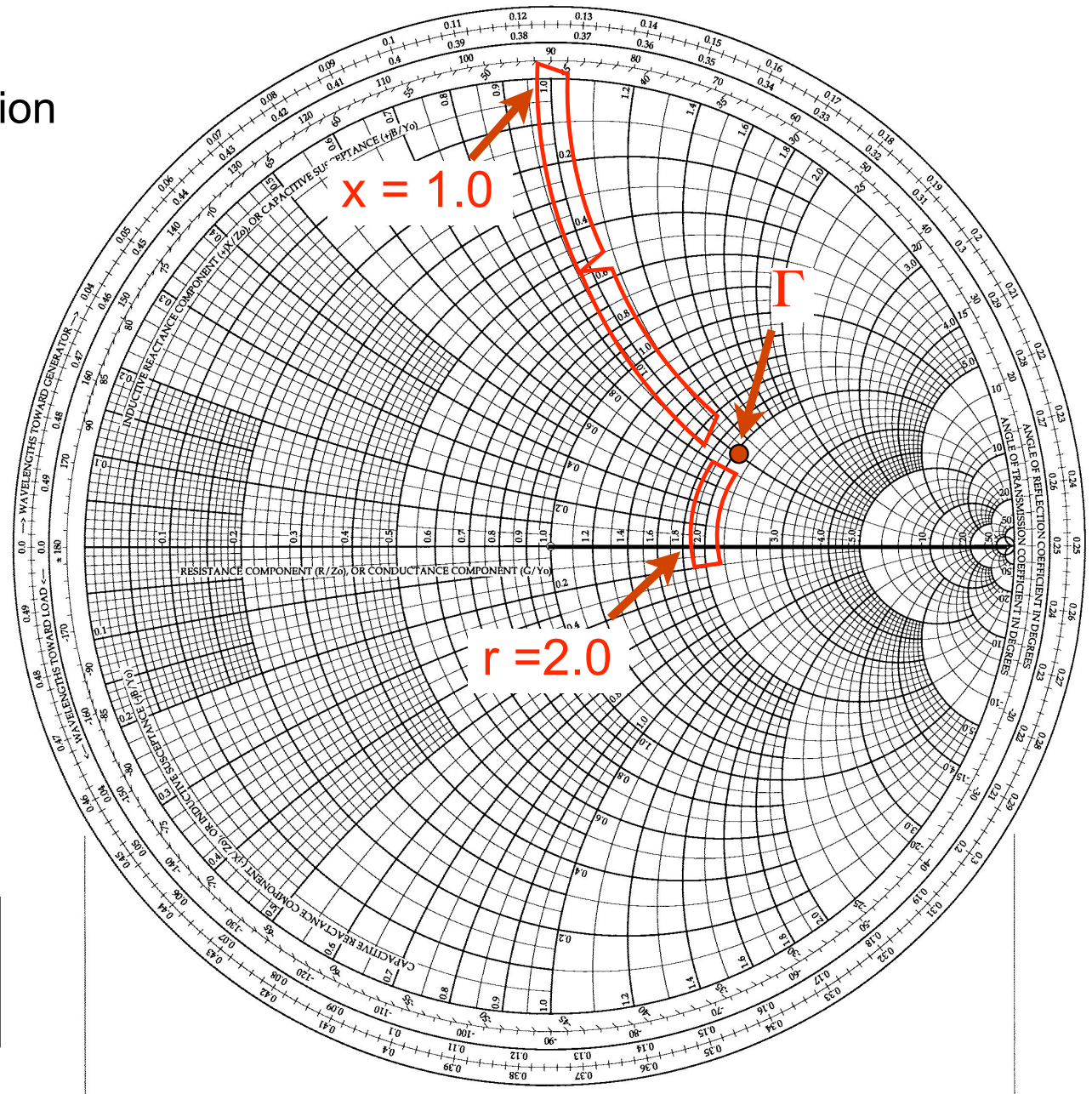- 1) Find Γ on the Smith Chart
- 2) Read r and x off of chart
- 3) Use Z_0 to re-normalize


$$Z = 50 (2.0 + j1.0) = 100.0 + j 50.0\ \Omega$$



EXAMPLE:

A load with $Z_L = 50 - j25$ is attached to a lossless, 100Ω T-L. Find $Z(d)$ at $d = 0.4\lambda$

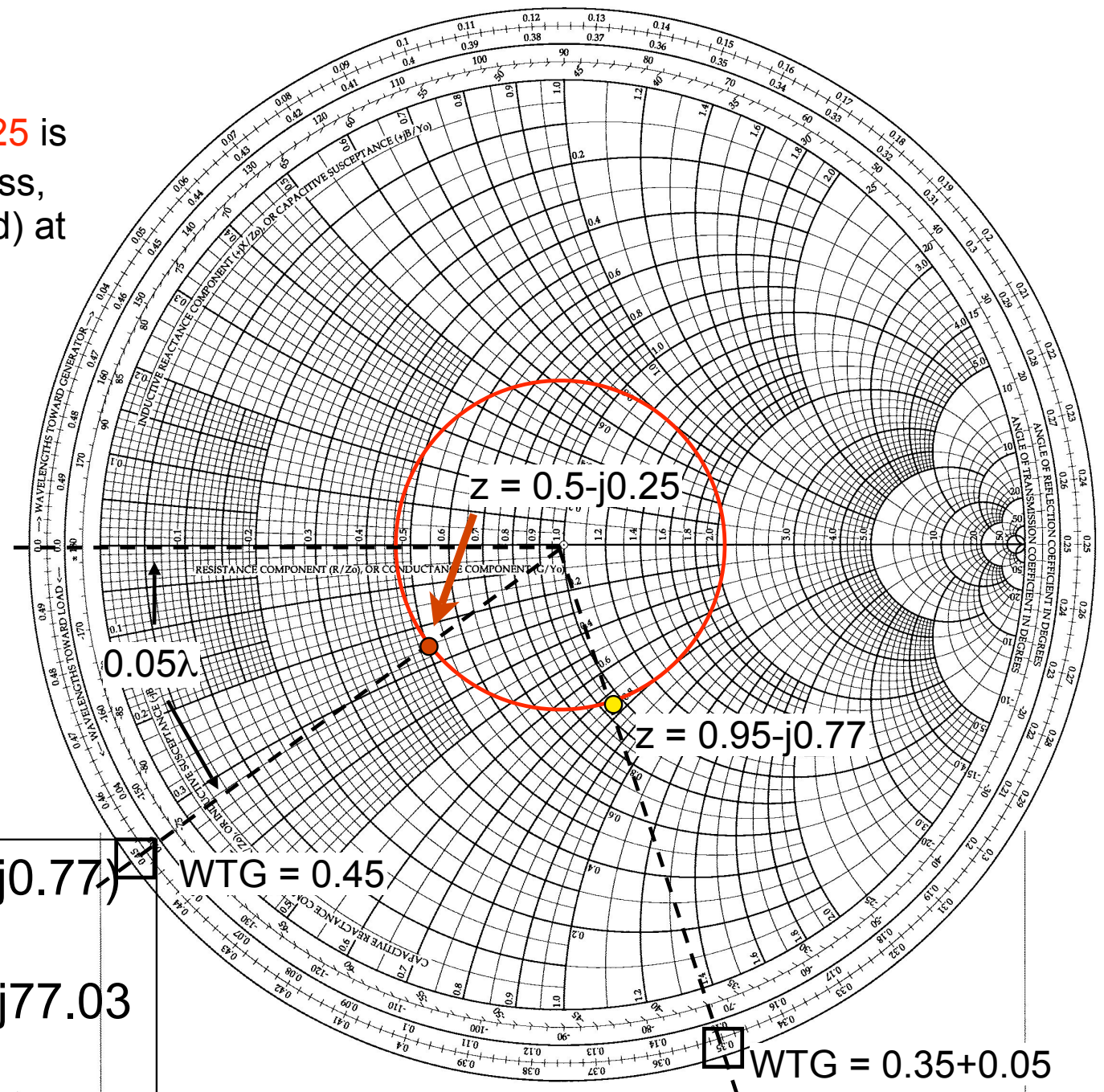- 1) Normalize Z_L
 $z_L = 0.5 - j0.25$
- 2) Find z_L on the Smith Chart
- 3) Rotate along constant Γ by 0.4λ
- 4) Read off new values of z
- 4) Use Z_0 to re-normalize



$$Z(d) = 100 (.95 - j0.77) \quad \Gamma = 0.45$$

$$= 95 - j77 \Omega$$

$$Z(d)_{\text{calc}} = 95.29 - j77.03$$

$$\% \text{error} \sim 0.2\%$$


Mapping between impedance and admittance:

$$y(d) = \frac{1}{z(d)} = \frac{1 - \Gamma(d)}{1 + \Gamma(d)} = \frac{1 - \Gamma_L e^{-j2\beta d}}{1 + \Gamma_L e^{-j2\beta d}}$$

$$= z\left(d \pm \frac{\lambda}{4}\right) \quad \text{since: } e^{-j2\beta(d \pm \frac{\lambda}{4})} = e^{-j2\beta d} e^{\mp j2\beta(\frac{\lambda}{4})}$$

$$= e^{-j2\beta d} e^{\mp \pi}$$

$$= -e^{-j2\beta d}$$

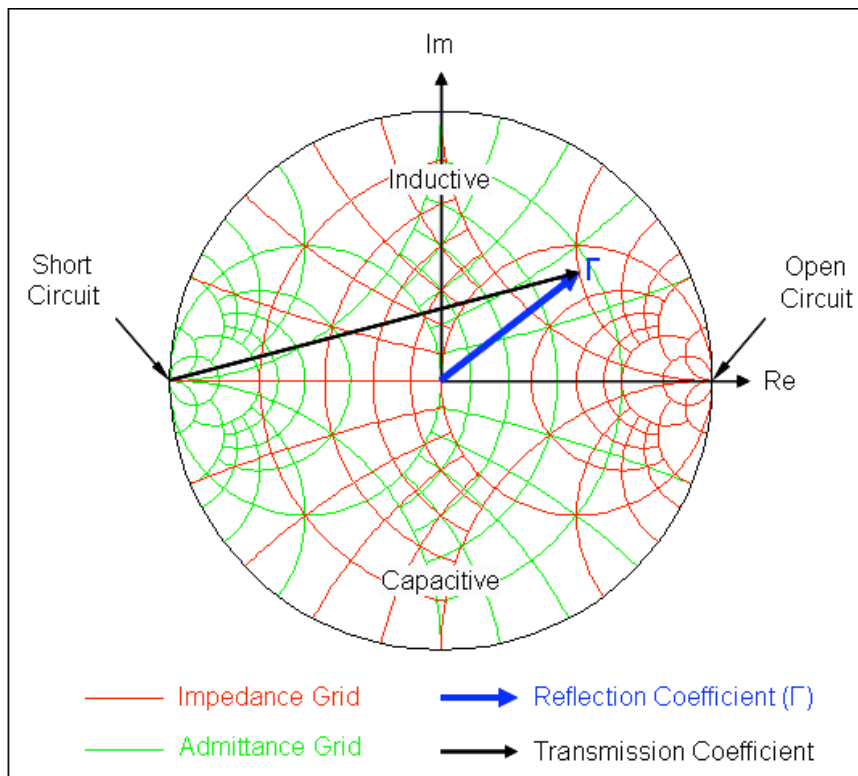

admittance grid is just the impedance grid reflected around the $\Gamma_r = 0$ axis

-or- can just read off values for $y(d) = g(d) + j b(d)$ as

$$g(d) = r\left(d \pm \frac{\lambda}{4}\right)$$

$$b(d) = x\left(d \pm \frac{\lambda}{4}\right)$$

We can transform z into y by rotating z half way around a constant Γ circle

Given $Z = 95 + j20$ on a 50Ω line, find Y

- 1) Find z
 $z = 1.9 + j0.4$
- 2) Draw Γ circle
- 3) Draw line through origin
- 4) Find intersection with Γ circle
- 5) Read off y
 $y = 0.5 - j0.1$
- 6) Renormalize y
 $Y = y/Z_0$
 $= 10 - j2 \text{ mS}$
 $Y_{\text{calc}} = 10.1 - j2.12 \text{ mS}$

