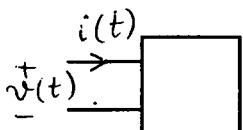


**Problem 1 (50 pts.)**

- a) If  $v(t) = 200\cos(377t - 10^\circ)$  and  $I(t) = -10\sin(377t - 130^\circ)$ , find the complex power  $P+jQ$ , PF (specify lead or lag)

$$P+jQ = \underline{866 + j500}, \quad PF = \underline{0.866}, \quad \text{Lead or Lag (Circle one)}$$



$$\bar{V} = \frac{200}{\sqrt{2}} \angle -10^\circ$$

$$\dot{i}(t) = -10\sin(377t - 130^\circ) = 10\cos(377t - 40^\circ)$$

$$\bar{I} = \frac{10}{\sqrt{2}} \angle -40^\circ$$

$$\bar{S} = \bar{V} \bar{I}^* = \left(\frac{200}{\sqrt{2}} \angle -10^\circ\right) \left(\frac{10}{\sqrt{2}} \angle 40^\circ\right) = 1000 \angle 30^\circ = 866 + j500$$

$$PF = \cos 30^\circ = 0.866 \text{ lag}$$

- b) Two loads in parallel, 30 kVA at 0.8 PF lag and 16 kW at 0.8 PF lead, are supplied by a source  $\bar{V} = 100\angle 0^\circ$  V. Find the total current (magnitude) supplied by the source and the combined PF (specify lead or lag)


$$I = \underline{404.5} \text{ A}, \quad PF = \underline{0.9889}, \quad \text{Lead or Lag (Circle one)}$$

$$\begin{aligned} \bar{S}_T &= \bar{S}_1 + \bar{S}_2 = 30(0.8 + j0.6) + \frac{16}{0.8} (0.8 - j0.6) \\ &= 24 + j18 + 16 - j12 = 40 + j6 \text{ kVA} \\ &= 40.45 \angle 8.53^\circ \text{ kVA} \end{aligned}$$

$$I = \frac{\bar{S}_T}{\bar{V}} = \frac{40450}{100} = 404.5 \text{ A}$$

$$PF = \cos 8.53^\circ = 0.9889 \text{ lag}$$

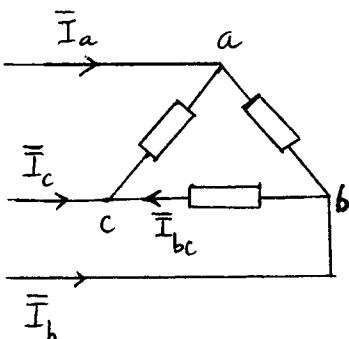- c) For the sequence a-b-c if  $\bar{I}_a = 30\angle -10^\circ$ , the phasor  $\bar{I}_{bc}$  is  $17.3 \angle -100^\circ$



$$\bar{I}_{ab} = \bar{I}_a \times \frac{1}{\sqrt{3}} \angle 30^\circ = \frac{30}{\sqrt{3}} \angle 20^\circ$$

$$\bar{I}_{bc} = \frac{30}{\sqrt{3}} \angle -100^\circ = 17.3 \angle -100^\circ$$

d) Two loads of  $100+j100$  kVA and  $60-j20$  kVA are connected in parallel. What is the kVar of capacitor required to improve the PF to 0.9 lagging


$$\bar{S}_T = 100+j100 + 60-j20 = 160+j80 \text{ kVA}$$

$$P = 160 \text{ kW}, Q_{\text{old}} = 80 \text{ kVAR}$$


$$Q_{\text{new}} = P \tan(\cos^{-1} 0.9) = 77.5 \text{ kVAR}$$

$$Q_{\text{cap}} = Q_{\text{new}} - Q_{\text{old}} = 77.5 - 80 = \boxed{-2.5 \text{ kVAR}}$$

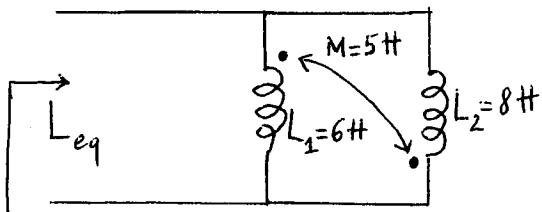e) Find the equivalent inductance of the circuit below,  $L_{\text{eq}} = \frac{23}{24} = 0.9583 \text{ H}$



Apply a test voltage at terminals

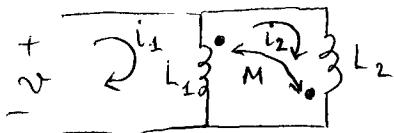

$$\text{Left loop: } v = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$\text{Right loop: } 0 = L_1 \frac{di_2}{dt} + L_2 \frac{di_2}{dt} + M \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$\Rightarrow 0 = (L_1 + L_2 + 2M) \frac{di_2}{dt} - (L_1 + M) \frac{di_1}{dt}$$

$$\Rightarrow \frac{di_2}{dt} = \frac{L_1 + M}{L_1 + L_2 + 2M} \frac{di_1}{dt}$$

Substitute into the first equation:

$$v = L_1 \frac{di_1}{dt} - (L_1 + M) \frac{di_2}{dt} = \left[ L_1 - \frac{(L_1 + M)^2}{L_1 + L_2 + 2M} \right] \frac{di_1}{dt}$$


$$v = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} \frac{di_1}{dt} \Rightarrow L_{\text{eq}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{23}{24}$$

f) Two coils which are coupled have  $L_1 = 81 \text{ mH}$ ,  $L_2 = 36 \text{ mH}$ , and the coupling coefficient  $k = 0.9$ . Find the mutual inductance.


$$M = \underline{48.6} \text{ mH}$$

$$M = k \sqrt{L_1 L_2} = 0.9 \sqrt{81 \times 36} = 48.6$$

g) Put dot markings on the coils

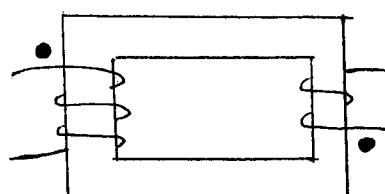

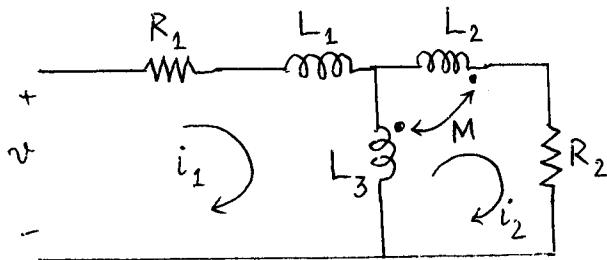h) Write the loop equations. Note that L<sub>1</sub> is not coupled to other coils




$$v = R_1 i_1 + L_1 \frac{di_1}{dt} + L_3 \frac{d}{dt}(i_2 - i_1) - M \frac{di_2}{dt}$$

$$0 = L_2 \frac{di_2}{dt} + R_2 i_2 + L_3 \frac{d}{dt}(i_2 - i_1) + M \frac{d}{dt}(i_2 - i_1) + M \frac{di_1}{dt}$$

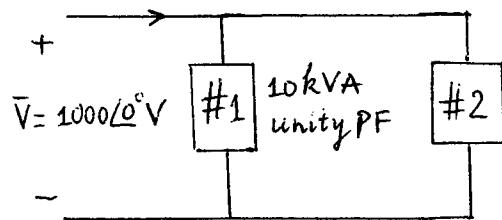i) Specify the load #2 in term of real power, PF (lead or lag)

$$P = 76.6 \text{ kW}, \quad PF = 0.8374, \quad \text{Lead or Lag (Circle one)}$$

$$\bar{I} = 100 \angle -30^\circ \text{A}$$





$$\begin{aligned} \bar{S}_2 &= \bar{V} \bar{I}^* - \bar{S}_1 \\ &= (1000 \angle 0^\circ)(100 \angle 30^\circ) - 10 \times 10^3 \\ &= 76.6 + j50 \text{ kVA} \\ &= 91.48 \angle 33.13^\circ \text{ kVA} \end{aligned}$$

$$PF = \cos 33.13^\circ = 0.8374 \text{ lag}$$

j) Find the fluxes flowed across the air gaps,  $\Phi_1 = 0.0375 \text{ Wb}$ ,  $\Phi_2 = 0.04 \text{ Wb}$
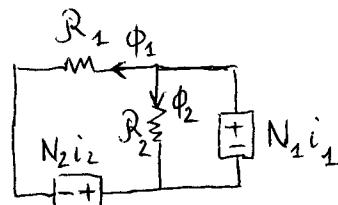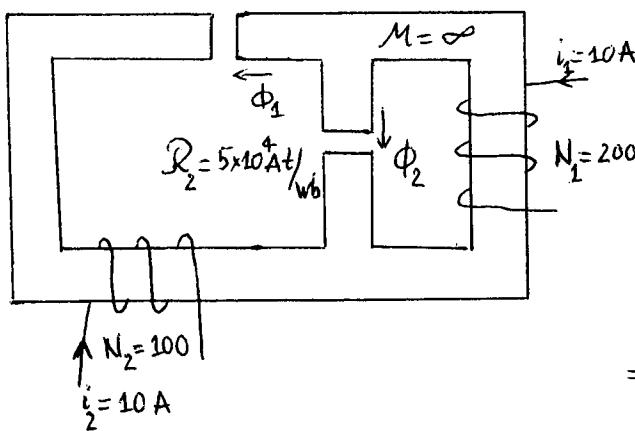
$$\mathcal{R}_1 = 8 \times 10^4 \text{ At/Wb}$$



$$\Phi_2 = \frac{N_1 i_1}{R_2} = \frac{200 \times 10}{5 \times 10^4} = 0.04 \text{ Wb}$$

$$N_1 i_1 - \mathcal{R}_1 \phi_1 + N_2 i_2 = 0$$

$$\Rightarrow \Phi_1 = \frac{N_1 i_1 + N_2 i_2}{\mathcal{R}_1} = \frac{2000 + 1000}{8 \times 10^4} = 0.0375 \text{ Wb}$$

**Problem 2 (25 pts.)**

The following balanced three phase loads are supplied from a wye-connected source whose line-line voltage is 2400 V. Load #1: 120 kVA at 0.96 PF lag; Load #2: 180 kVA at 0.8 PF lag; and Load #3: 100 + j100 kVA.

- (1) Find the total line current (magnitude) and PF of the total load
- (2) What is the total capacitive kVAr needed to improve the PF to 0.9 PF lag
- (3) What is the phase angle between  $\bar{I}_{ab}$  and  $\bar{V}_{ab}$ . Take  $\bar{V}_{an}$  as reference.

$$(1) \quad \bar{S}_T = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = 120 / \cos^{-1} 0.96 + 180 / \cos^{-1} 0.8 + 100 + j100 \\ = 359.2 + j241.6 \text{ kVA} = 432.89 / 33.93^\circ \text{ kVA}$$

$$I_L = \frac{S_T}{\sqrt{3} V_{LL}} = \frac{432.890}{\sqrt{3} \cdot 2400} = \boxed{104.14 \text{ A}}$$

$$\text{PF} = \cos 33.93^\circ = \boxed{0.8297 \text{ lag}}$$

$$(2) \quad P = 359.2 \text{ kW}, Q_{old} = 241.6 \text{ kVAR}$$

$$Q_{new} = P \tan(\cos^{-1} 0.9) = 173.97 \text{ kVAR}$$


$$Q_{cap} = Q_{new} - Q_{old} = \boxed{-67.63 \text{ kVAR}}$$

$$(3) \quad \bar{V}_{an} = V_{an} \angle 0^\circ, \quad \bar{V}_{ab} = V_{ab} \angle 30^\circ$$


$$\bar{I}_a = I_L \angle -33.93^\circ$$

$$\angle \bar{V}_{ab} - \angle \bar{I}_a = 30 + 33.93 = \boxed{63.93^\circ}$$


**Problem 3 (25 pts.)**

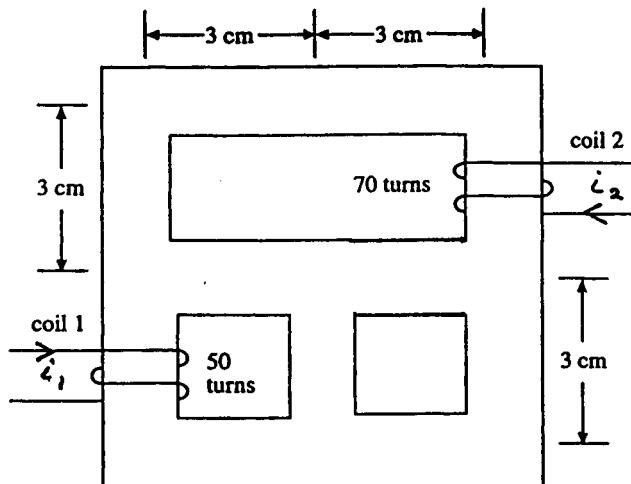

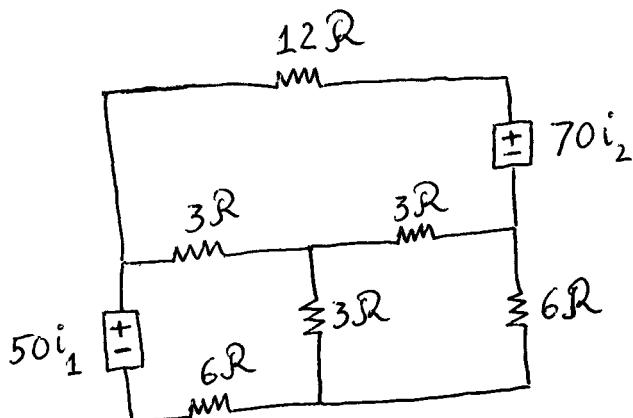- (1) Draw the equivalent circuit for the magnetic device shown above. The magnetic material of the core has reluctance  $\mathfrak{R}$  per cm.



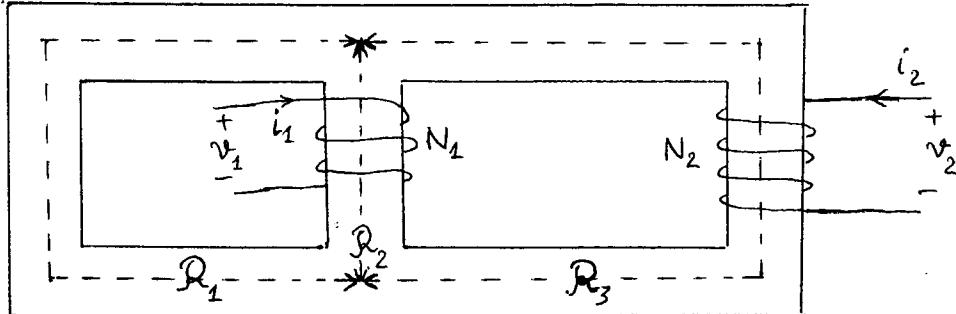(2) Determine the self inductances  $L_1$ ,  $L_2$ , and the mutual inductance  $M$  in terms of  $K$ ,  $N_1$ , and  $N_2$ .




$$R_1 = 2K$$

$$R_2 = K$$

$$R_3 = 3K$$

$$\phi_1 + \phi_2 + \phi_3 = 0$$
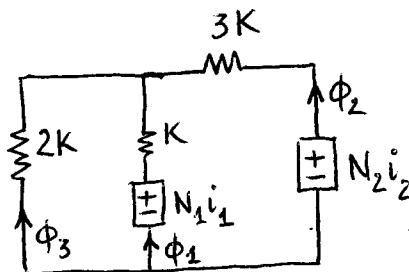
$$\Rightarrow \phi_3 = -\phi_1 - \phi_2$$



$$-N_1 i_1 + K\phi_1 - 2K\phi_3 = 0 \Rightarrow -N_1 i_1 + K\phi_1 - 2K(-\phi_1 - \phi_2) = 0$$

$$-N_1 i_1 + 3K\phi_1 + 2K\phi_2 = 0$$

$$\Rightarrow \phi_2 = \frac{1}{2K} (N_1 i_1 - 3K\phi_1)$$

$$-N_1 i_1 + K\phi_1 - 3K\phi_2 + N_2 i_2 = 0 \Rightarrow -N_1 i_1 + K\phi_1 - 3K \frac{1}{2K} (N_1 i_1 - 3K\phi_1) + N_2 i_2 = 0$$

$$-\frac{5}{2} N_1 i_1 + \frac{11K}{2} \phi_1 + N_2 i_2 = 0$$

$$\Rightarrow \phi_1 = \frac{5 N_1}{11K} i_1 - \frac{2 N_2}{11K} i_2$$

$$\lambda_1 = N_1 \phi_1 = \frac{5 N_1^2}{11K} i_1 - \frac{2 N_1 N_2}{11K} i_2 = L_1 i_1 + M i_2$$

$$\Rightarrow L_1 = \frac{5 N_1^2}{11K}, \quad M = -\frac{2 N_1 N_2}{11K}$$

$$\phi_2 = \frac{1}{2K} \left( N_1 i_1 - 3K \left( \frac{5 N_1}{11K} i_1 - \frac{2 N_2}{11K} i_2 \right) \right), \quad \lambda_2 = N_2 \phi_2 = -\frac{2 N_1 N_2}{11K} i_1 + \frac{3 N_2^2}{11K} i_2$$

$$= -\frac{2 N_1}{11K} i_1 + \frac{3 N_2}{11K} i_2$$

$$\Rightarrow L_2 = \frac{3 N_2^2}{11K} = M i_1 + L_2 i_2$$