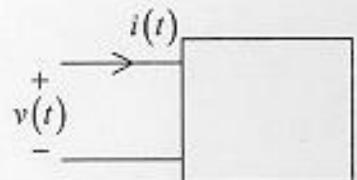


**Problem 1 (30 pts.)**

- a) If  $v(t) = 200 \cos(377t - 10^\circ)$  and  $i(t) = 10 \sin(377t + 125^\circ)$ , find the complex power  $P + jQ$ , PF (specify lead or lag)

$$P + jQ = \frac{500\sqrt{2} - 500\sqrt{2}j}{P.F. = \frac{1}{\sqrt{2}}} \quad \text{Lead or Lag (circle one)}$$

$$= 707.1 - 707.1j$$




$$V(t) = 200 \cos(377t - 10^\circ) \Rightarrow \bar{V} = \frac{200}{\sqrt{2}} \angle -10^\circ$$

$$i(t) = 10 \sin(377t + 125^\circ) = 10 \cos(377t + 35^\circ) \Rightarrow \bar{I} = \frac{10}{\sqrt{2}} \angle 35^\circ$$

$$\bar{I} (P + jQ) = \bar{V} I^* = \left(\frac{200}{\sqrt{2}} \angle -10^\circ\right) \left(\frac{10}{\sqrt{2}} \angle 35^\circ\right) = 1000 \angle -45^\circ$$

$$= 500\sqrt{2} - 500\sqrt{2}j \text{ kVA} \quad \text{PF} = \frac{1}{\sqrt{2}} \text{ lead}$$

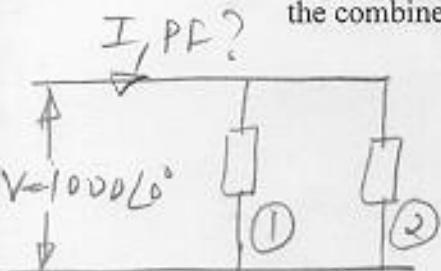- b) Two loads in parallel, 10 kVA at 0.8 PF lag and 16 kW at 0.8 lead are supplied by a source  $\bar{V} = 1000 \angle 0^\circ$ . Find the total current (magnitude) supplied by the source and the combined PF (specify lead/lag).



$$I = \frac{24.74 \text{ A}}{P.F. = \frac{0.97}{\text{Lead or Lag (circle one)}}}$$

$$\text{Load 1: } S_1 = 10 \text{ k} (0.8 + j0.6) = 8 + 6j \text{ kVA}$$


$$\text{Load 2: } S_2 = \frac{16 \text{ k}}{0.8} (0.8 - j0.6) = 16 - 12j \text{ kVA}$$

$$S = S_1 + S_2 = 24 - 6j \text{ kVA}$$

$$I = \frac{(S)^*}{V} = \frac{(24 + 6j) 10^3}{1000 \angle 0^\circ} = 24 + 6j = 24.74 \angle 14^\circ \text{ A}$$

- c) For the phase sequence a-b-c if  $\bar{I}_{ab} = 15 \angle 38^\circ$  and  $\bar{V}_{bc} = 10 \angle -112^\circ$  the total power  $S_T$  is  $450 \angle -30^\circ \text{ VA}$  lead

for a-b-c phase sequence

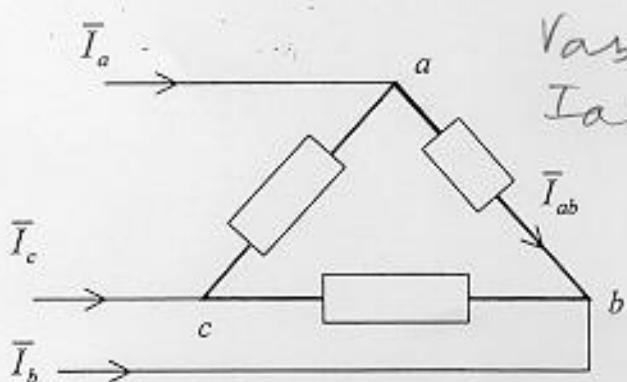

$$V_{ab} = 10 \angle (-112^\circ + 120^\circ) = 10 \angle 8^\circ$$

$$I_{ab} = 15 \angle 38^\circ$$



$$S_T = 3 S_\phi = 3 V_{ab} I_{ab}^*$$

$$= 3 (10 \angle 8^\circ) (15 \angle -38^\circ)$$

$$= (30)(15) \angle -30^\circ$$

$$= 389.7 - 225j \text{ VA}$$

d)

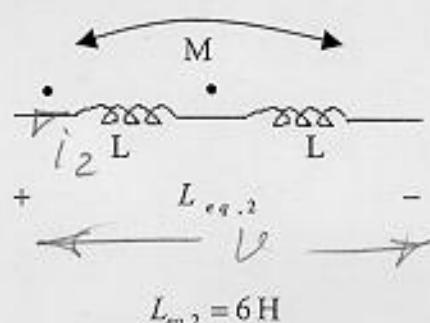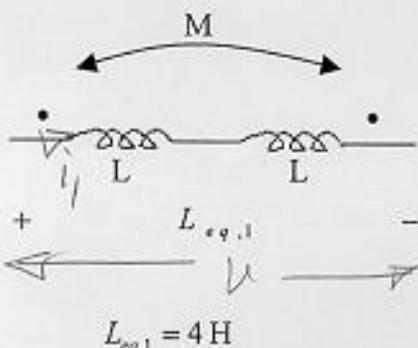

$$L = \frac{\sqrt{2}}{2} \text{ H}$$

$$L = \frac{1}{2} \text{ H}$$


$$V = \underbrace{2(L-M)}_4 \frac{di}{dt}$$

$$V = \underbrace{2(L+M)}_6 \frac{di_2}{dt}$$

- e) Two coils which are coupled have  $L_1 = 10 \text{ mH}$ ,  $L_2 = 20 \text{ mH}$ , and  $M = 14 \text{ mH}$ . Find the coupling coefficient  $k$ .

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{14 \text{ mH}}{\sqrt{10 \text{ mH} \cdot 20 \text{ mH}}} = \frac{14}{\sqrt{200}} = 0.9899$$

- f) Put dot markings on the coils.

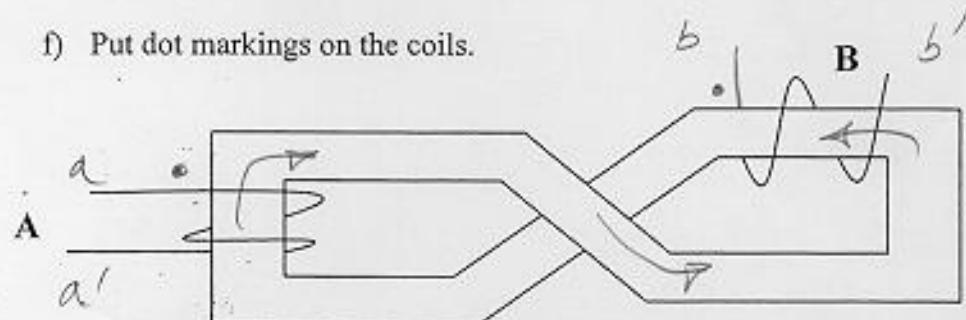


Dots are placed at ab or a'b'.

**Problem 2 (35)**

A three phase wye-connected load of 12 kW at 0.8 PF lagging is connected in parallel with another three phase wye-connected load of 24 kVA at 0.6 leading. The line to line voltage is 440 V.

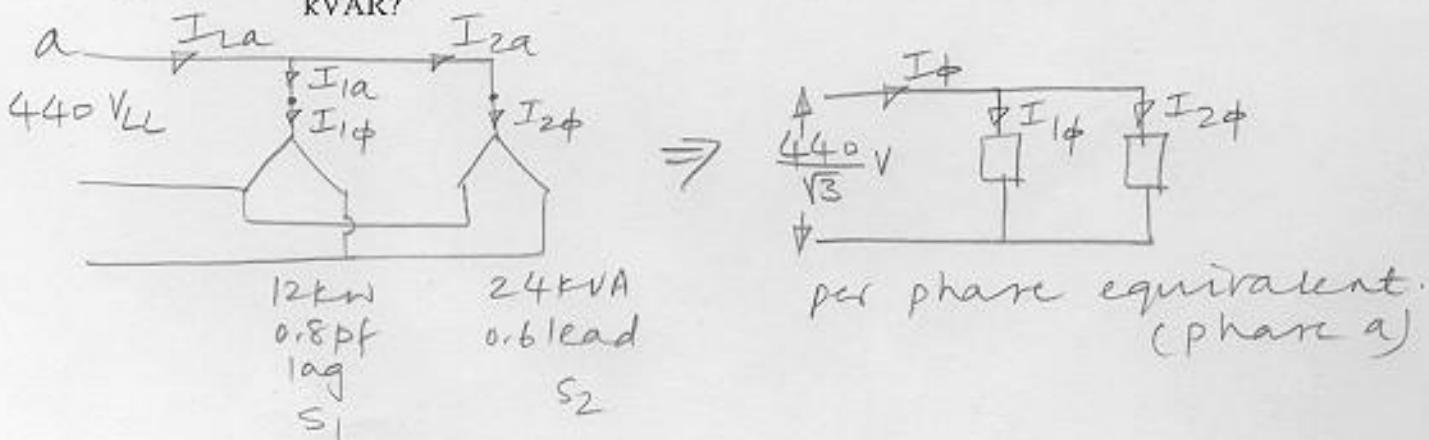- (15) (a) Find (i) total complex power, (ii) PF (state lead or lag) and (iii) the line current.  
 (15) (b) Assuming  $\bar{V}_{an}$  is reference phasor, compute the line currents in each load and the total line current in phasor form. Draw a phasor diagram.  
 (5) (c) Find kVAR needed to make the PF unity. Is it inductive or capacitive kVAR?



$$a) S_1 = \frac{12}{0.8} (0.8 + j0.6) = 12 + j9 \text{ kVA}$$

$$S_2 = 24 (0.6 - j0.8) = 14.4 - j19.2 \text{ kVA}$$

$$S_T = S_1 + S_2 = [26.4 - j10.2 \text{ kVA}] = 28.3 \times 10^3 \angle -21.13^\circ \text{ VA}$$

$\boxed{\text{PF} = 0.933 \text{ lead}}$

$$|S_T| = \sqrt{3} \cdot 440 \cdot I_L \Rightarrow I_L = \frac{28.3 \times 10^3}{\sqrt{3} \cdot 440} = \boxed{37.14 \text{ A}}$$

b) See the phasor diagram for phase 'a' on the next page.

Subscript 'a': phase a quantities

Ans:

$$I_{L1} = 19.68 \angle -36.87^\circ \text{ A}$$

$$I_{L2} = 31.49 \angle 53.13^\circ \text{ A}$$


$$I_L = 37.14 \angle 21.13^\circ$$

'1': Load 1

'2': Load 2

' $\phi$ ': phase quantities

'L': Line quantities

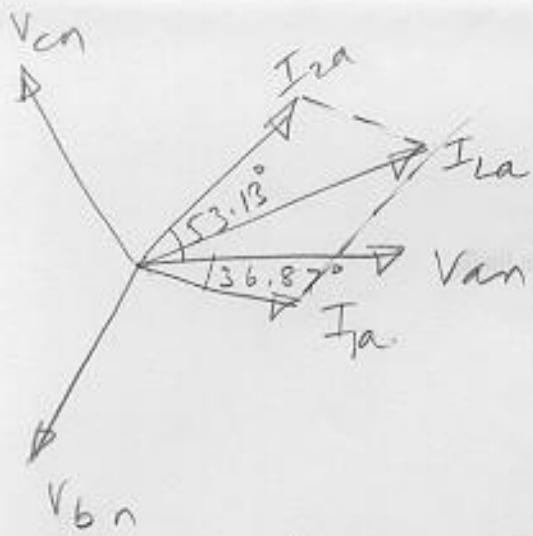

Phasor Diagram for phase 'a'

Load 1:

$$\frac{12+j9}{3} = \frac{440 \angle 0^\circ}{\sqrt{3}} I_{14}^*$$

$$I_{14} = \left( \frac{(12+j9)\sqrt{3}}{3 \times 440 \angle 0^\circ} \right)^*$$

$$= \frac{(12-j9) k}{\sqrt{3} \times 440}$$

$$= 15.75 - 11.8j$$

$$I_{1a} = 19.68 \angle -36.87^\circ$$

Load 2:

$$\frac{14.4-19.2j}{3} = \frac{440 \angle 0^\circ}{\sqrt{3}} I_{24}^*$$

$$\Rightarrow I_{24} = \frac{(14.4+19.2j) k}{\sqrt{3} \times 440 \angle 0^\circ}$$

$$I_{2a} = 18.9 + 25.19j = 31.49 \angle 53.13^\circ$$

$$I_{La} = I_{1a} + I_{2a} = 34.65 + 13.39j = 37.14 \angle 21.13^\circ$$

in Y connection, phase & line currents are identical

$$\text{Hence, } I_{1a} = 19.68 \angle -36.87^\circ$$

$$I_{1b} = 19.68 \angle -36.87^\circ - 120^\circ$$

$$I_{1c} = 19.68 \angle -36.87^\circ + 120^\circ$$

Similarly for  $I_{2a}, I_{2b}, I_{2c}$  &  $I_{La}, I_{Lb}, I_{Lc}$ .

c) kVAR needed to make the PF unity  
is 10.2. It is inductive kVAR.

ans! 10.2 kVAR.

### Problem 3

A 480/240 V, 4.8 kVA, 60-Hz, single-phase transformer is used to supply a 4.8 kVA load with a power factor of 0.8 lagging at rated voltage of 240 V.


- If you assume the transformer is ideal, what would be the magnitude of the expected primary side (480 Volt side) current?
- Again, if you assume the transformer is ideal, what is the apparent impedance of the load viewed from the primary side of the transformer?

Next, the transformer is tested to determine its parameters. The parameters, all referred to the high side, are found to be  $R_{eq} = 3\Omega$ ,  $X_{eq} = 4\Omega$ ,  $R_c = 6K\Omega$ , and  $X_m = 3K\Omega$ . Assuming the same load as mentioned above and using approximate equivalent circuit

- What is the primary (high) side terminal voltage magnitude needed to supply the load at a voltage of 240 V?
- What is the transformer's efficiency ( $\eta$ ) for this load?
- Finally, the load is accidentally shorted, resulting in a new load of 0 kVA (but with lots of current). Assuming the primary high side voltage during the short is 480 V, what are the transformer's total power losses during the short (before the circuit breakers trip).

$$a) \frac{4800 \text{ kVA}}{480} = 10 \text{ A}$$
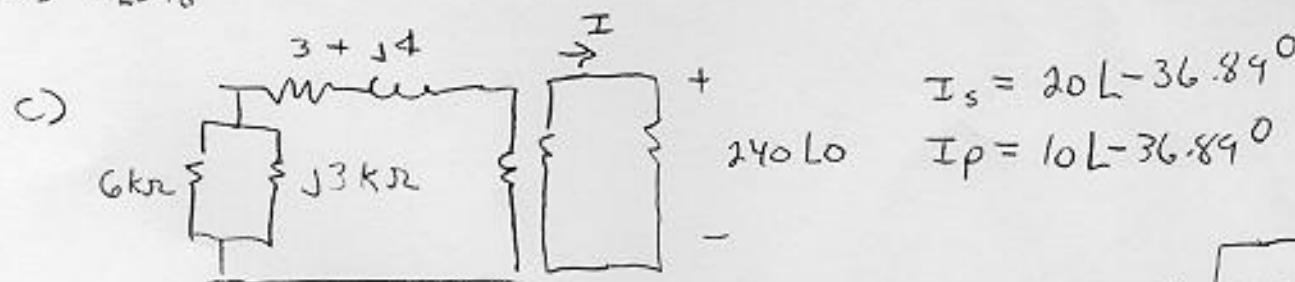
$$b) S_{load} = 4.8 [36.89^\circ] \text{ kVA} = V_o \left( \frac{V^*}{Z} \right) \Rightarrow Z = 48 [36.89^\circ] \Omega$$



$$V_{source} = 480 L o + (3 + j4) 10 L - 36.89 = 5.28 + j14 = 528.18 L 1.51^\circ$$

$$d) \eta = \frac{P_{out}}{P_{out} + P_{losses}} \quad P_{out} = 3840 \text{ W} \quad P_{loss} = \frac{528^2}{6000} + 10^2 \cdot 3 = 346.5 \text{ W}$$

$$\eta = 0.9172$$

e) During short model is

$$P = 96^2 \cdot 3 + 480^2 / 6000 = 27,686 \text{ W} = 27.6 \text{ kW}$$