

ECE430
Spring 2006
FINAL
May 10, 2006

Name Solutions
Section (C for Kimball MWF, F for Tate TR)

1:	_____
2:	_____
3:	_____
4:	_____
5:	_____
6:	_____
Total:	_____

Equations:

$$\bar{S}_{1\phi} = \bar{V}\bar{I}^* = \frac{|\bar{V}|^2}{\bar{Z}^*} = |\bar{I}|^2 \bar{Z}$$

$$\bar{S}_{3\phi} = 3\bar{V}_\phi \bar{I}_\phi^* = \sqrt{3} V_L I_L \angle \theta$$

$$P_{3\phi} = \sqrt{3} V_L I_L \cos \theta$$

$$Q_{3\phi} = \sqrt{3} V_L I_L \sin \theta$$

$$pf = \cos(\angle \bar{V} - \angle \bar{I})$$

$\theta > 0 \rightarrow lagging, \theta < 0 \rightarrow leading$

$$P^2 + Q^2 = S^2$$

$$X_c = -\frac{1}{\omega C}$$


$$X_L = \omega L$$

wye, abc sequence: $\bar{V}_L = \bar{V}_\phi (\sqrt{3} \angle 30^\circ), \bar{I}_L = \bar{I}_\phi$

delta, abc sequence: $\bar{V}_\phi = \bar{V}_L, \bar{I}_L = \bar{I}_\phi (\sqrt{3} \angle -30^\circ)$

$$\bar{Z}_\Delta = 3\bar{Z}_Y$$
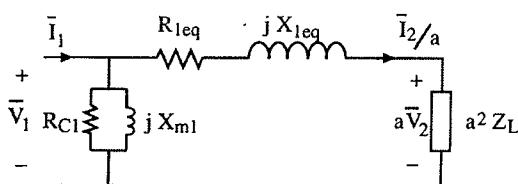
$$\bar{Z}_1 \parallel \bar{Z}_2 = (\bar{Z}_1^{-1} + \bar{Z}_2^{-1})^{-1}$$



Transformer Approximate Equivalent Circuit

$$\mathcal{R} = \frac{l}{\mu A}$$

$$\mu_0 = 4\pi \times 10^{-7} H/m$$

$$\lambda = N\Phi = Li$$

$$L = N^2 \mathcal{R} = \frac{N^2}{\mathcal{R}}$$

$$mmf (source) = Ni$$

$$mmf (drop) = \Phi \mathcal{R}$$

$\sum mmf = 0$ around loop


$$\oint \bar{H} \cdot d\bar{l} = \int \bar{J} \cdot \hat{n} da$$

$$\oint \bar{E} \cdot d\bar{l} = -\frac{\partial}{\partial t} \int \bar{B} \cdot \hat{n} da$$

$$\oint \bar{B} \cdot \hat{n} da = 0$$

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

$$v = \frac{d\lambda}{dt}$$

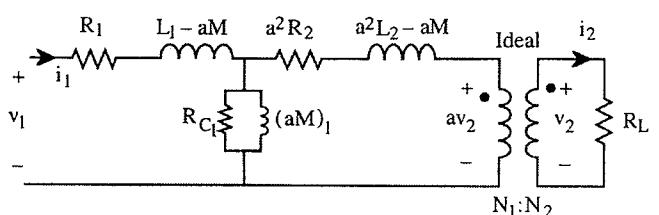

Transformer Equivalent Circuit

$$W_m = \int_0^\lambda id\hat{\lambda}$$

$$W_m' = \int_0^i \lambda di$$

$$T^e = \frac{\partial W_m'}{\partial \theta} = -\frac{\partial W_m}{\partial \theta}$$

$$f^e = \frac{\partial W_m'}{\partial x} = -\frac{\partial W_m}{\partial x}$$

$$EFE = \int_a^b id\lambda$$

$$EFM = - \int_a^b f^e dx$$

For $\dot{x}_1 = f_1(x_1, x_2)$ and $\dot{x}_2 = f_2(x_1, x_2)$,


$$\begin{bmatrix} \Delta \dot{x}_1 \\ \Delta \dot{x}_2 \end{bmatrix} \approx \begin{bmatrix} \left. \frac{\partial f_1}{\partial x_1} \right|_{x=x^e} & \left. \frac{\partial f_1}{\partial x_2} \right|_{x=x^e} \\ \left. \frac{\partial f_2}{\partial x_1} \right|_{x=x^e} & \left. \frac{\partial f_2}{\partial x_2} \right|_{x=x^e} \end{bmatrix} \begin{bmatrix} \Delta x_1 \\ \Delta x_2 \end{bmatrix}$$

$$x(t_0 + \Delta t) \approx x(t_0) + \Delta t \cdot \left. \frac{dx}{dt} \right|_{t=t_0}$$

For $\dot{x} = Ax$, the eigenvalues λ of the system are given by $|\lambda I - A| = 0$

$$\frac{d}{dx}(\ln x) = \frac{1}{x}$$

Synchronous machines

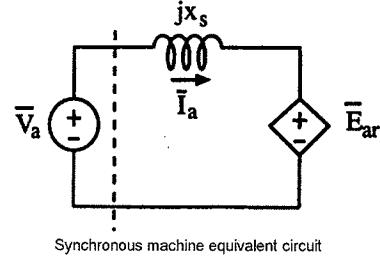

$$P_T = P_m = \frac{-3E_{ar}V_a \sin(\delta)}{x_s}$$

$$\omega_m = \frac{2}{p}\omega_s$$

$$E_{ar} = \frac{\omega_s M I_r}{\sqrt{2}}$$

$$T^e \omega_m = P_m$$

Induction machines

$$T^e = \frac{P_m}{\omega_m}$$

$$P_{ag} = 3 |\bar{I}'_r|^2 \frac{R'}{s}$$

$$P_m = 3 |\bar{I}'_r|^2 R'_r \left(\frac{1-s}{s} \right)$$


$$\omega_s = \omega_m \left(\frac{p}{2} \right) + \omega_r$$

$$s = \frac{\omega_r}{\omega_s} = \frac{N_s - N}{N_s}$$

$$s_{\max T} = \pm \frac{R'_r}{\sqrt{R_s^2 + (X_{ls} + X'_{lr})^2}}$$

$$N_s = f_s \frac{120}{p}$$

Problem 1 (25 points)

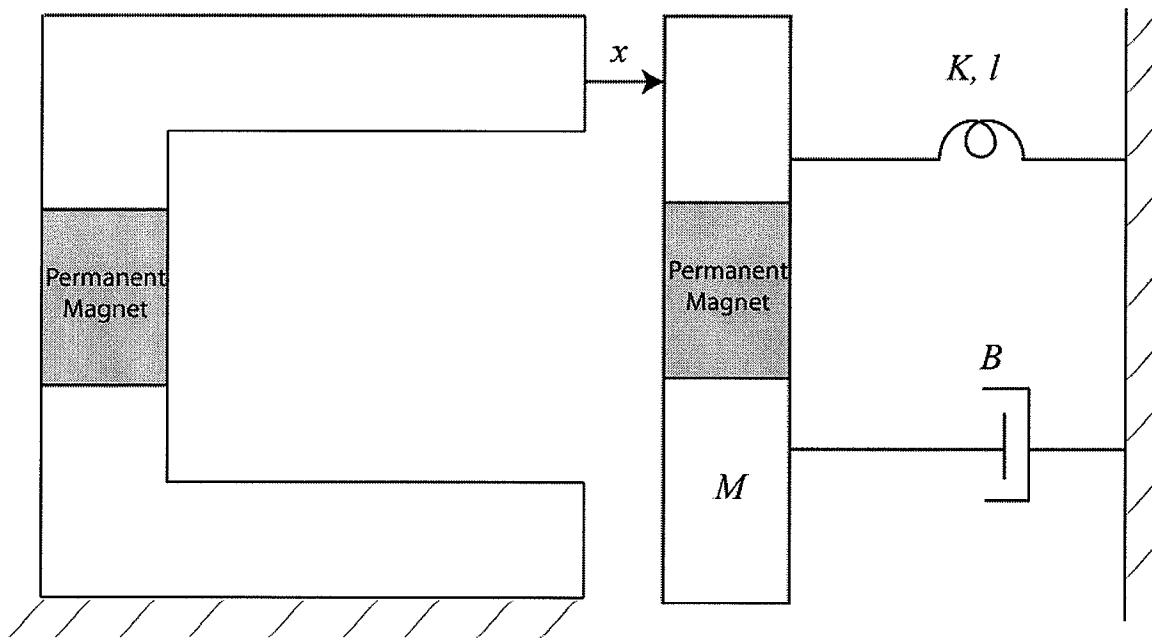

The permanent magnet / mechanical system shown above has the following co-energy expression:

$$W_m' = \ln(x)$$

The spring constant $K = 1 \text{ N/m}$, and the zero-force length l of the spring is 2 m (i.e., for $x = 2 \text{ m}$, the spring exerts no force on the mass). The dashpot damping coefficient $B = 2 \text{ N/(m/s)}$. The mass of the movable member (M) is 1 kg .

- a) Determine the force exerted by the permanent magnet on the movable member
- b) Write down the differential equations for this system in state space form
- c) Find all equilibrium points for the system
- d) Write the differential equations for the system after linearization at each equilibrium point
- e) Determine whether or not each equilibrium point is stable

Problem 1

2 pts. a) $f^e = \frac{\partial}{\partial x} W_m = \frac{\partial}{\partial x} \ln(x) = \boxed{\frac{1}{x}}$

10 pts. b) $M \ddot{x} = \frac{1}{x} - K(x-l) - B \dot{x}$

$$\ddot{x} = \frac{1}{x} - (x-2) - 2 \dot{x}$$

Let $y_1 = x$, $y_2 = \dot{x}$

$$\begin{cases} \dot{y}_1 = y_2 \\ \dot{y}_2 = \frac{1}{y_1} - (y_1 - 2) - 2y_2 \end{cases}$$

4 pts. c) $0 = y_2^e$
 $0 = \frac{1}{y_1^e} - (y_1^e - 2) - 2y_2^e \Rightarrow 0 = 1 - y_1^{e^2} + 2y_1^e \Rightarrow 0 = -y_1^{e^2} + 2y_1^e + 1$
 $y_1^e = \frac{-2 \pm \sqrt{4 + 4}}{-2} = \frac{-2 \pm 2\sqrt{2}}{-2} = 1 \mp \sqrt{2}$

But x must be > 0 , so only equil. is

$$\boxed{1 + \sqrt{2}} = 2.414$$

5 pts. d) $A = \begin{bmatrix} 0 & 1 \\ -\frac{1}{y_1^{e^2}} - 1 & -2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{(1+\sqrt{2})^2} - 1 & -2 \end{bmatrix} \approx \begin{bmatrix} 0 & 1 \\ -1.1716 & -2 \end{bmatrix}$


$$\Delta y = A \Delta y$$

4 pts. e) eigenvalues: $-1 \pm j0.4142$

Yes, $(\operatorname{Re}\{\lambda\}) < 0$ for all λ

stable

Problem 2 (25 points)

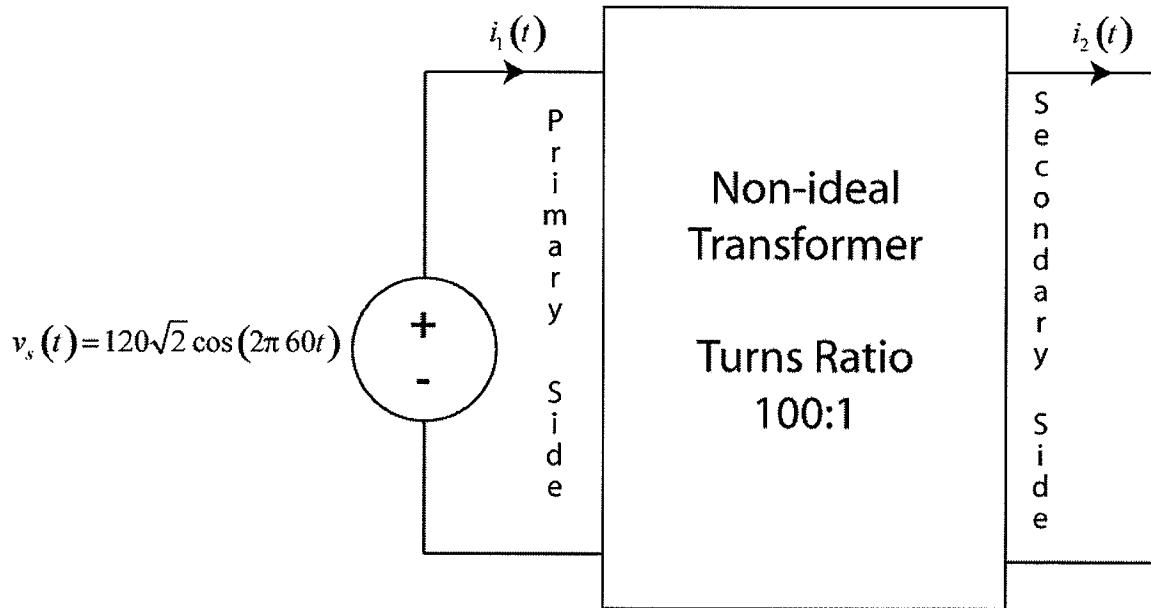


The figure above shows a single-phase voltage source hooked up through a non-ideal transformer to a short. The non-ideal transformer is to be modeled using the approximate transformer model, with $R_{1\text{eq}} = 1.42 \Omega$, $X_{1\text{eq}} = 1.82 \Omega$, $R_{C1} = 10 \Omega$, and $X_{m1} = 12 \Omega$.

Find:

- The time-domain expression for the current through the short ($i_2(t)$)
- The time-domain expression for the current leaving the source ($i_1(t)$)
- Average (real) power losses in the transformer

Problem 2

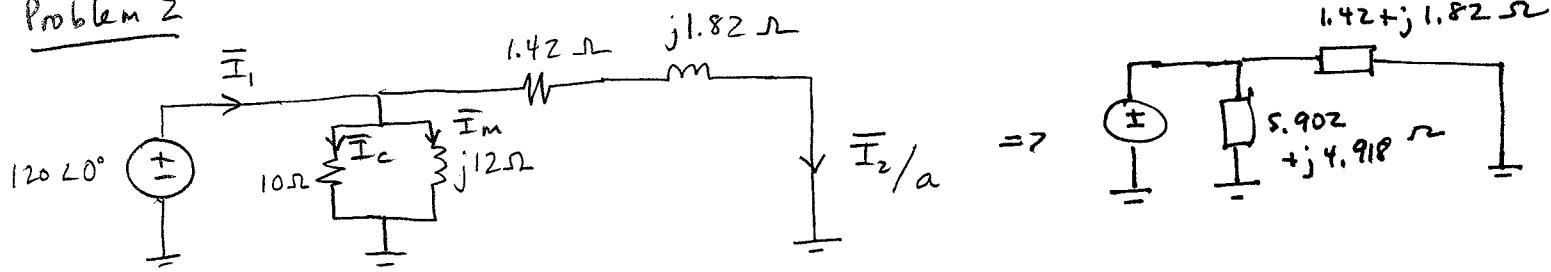

8 pts. a)

$$\bar{I}_2/a = \frac{120\angle 0^\circ}{1.42 + j1.82} = 31.977 - j40.985 = 51.984 \angle -52.078^\circ$$

$$\begin{aligned}\bar{I}_2 &= (100)(31.977 - j40.985) = 3197.7 - j4098.5 \\ &= 5198.36 \angle -52.04^\circ\end{aligned}$$

$$\begin{aligned}i_2(t) &= 5198.36 \sqrt{2} \cos(2\pi 60t - 52.04^\circ) \\ &= 7351.59 \cos(2\pi 60t - 52.04^\circ)\end{aligned}$$

b) $\bar{I}_c = \frac{120\angle 0^\circ}{10\angle 0^\circ} = 12\angle 0^\circ \text{ A}$ $\bar{I}_m = \frac{120\angle 0^\circ}{12\angle 90^\circ} = 10\angle -90^\circ = -j10 \text{ A}$

12 pts.

$$\begin{aligned}\bar{I}_1 &= \bar{I}_c + \bar{I}_m + \bar{I}_{2/a} = 12 - j10 + 31.977 - j40.985 \\ &= 43.9772 - j50.985 \\ &= 67.331 \angle -49.22^\circ\end{aligned}$$

$$\begin{aligned}i_1(t) &= 67.331 \sqrt{2} \cos(2\pi 60t - 49.22^\circ) \\ &= 95.220 \cos(2\pi 60t - 49.22^\circ)\end{aligned}$$

c) $P_C = \operatorname{Re}\{(120\angle 0^\circ)(12\angle 0^\circ)\} = 1440 \text{ W}$

$$P_R = |\bar{I}_{2/a}|^2 (1.42) = 3837.26 \text{ W}$$

$$P_C + P_R = 5277.26 \text{ W} = P_{\text{loss}}$$

Also,

$$\bar{S}_{in} = \bar{V}_{in} \bar{I}_{in}^* = (120\angle 0^\circ)(67.331 \angle 49.22') = 5277 + j6118 \text{ VA}$$

$$P_{\text{loss}} = 5277.26 \text{ W}$$

✓


Problem 3 (25 points)

A 60-Hz, three-phase, 4-pole synchronous motor is observed to have a terminal voltage of 460 V (line-line) and a terminal current of 120 A at a power factor of 0.95 lagging. The field current under this operating condition is 47 A. The machine synchronous reactance is equal to 1.68Ω . Assume the armature resistance to be negligible.

Calculate:

- a) The torque angle δ
- b) The magnitude of the field-to-armature mutual inductance
- c) The electrical power input to the motor and the torque on the shaft

Problem 3

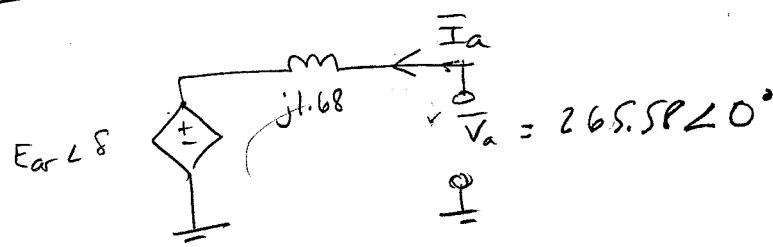

a) $\bar{I}_a = 120 \angle -\cos^{-1}(0.95)$

$\bar{I}_a = 120 \angle -18.195^\circ$

(10 pts.) $-E_{ar} \angle \delta - (\bar{I}_a)(1.68 \angle 90^\circ) + \left(\frac{460}{\sqrt{3}} \angle 0^\circ \right) = 0$

$$E_{ar} \angle \delta = \left(\frac{460}{\sqrt{3}} \angle 0^\circ \right) - (120 \angle -18.195^\circ)(1.68 \angle 90^\circ)$$

$E_{ar} \angle \delta = 278.82 \angle -43.39^\circ$

$\delta = -43.39^\circ$

b) $278.82 = \frac{\omega_s M I_r}{r^2} \rightarrow M = \frac{\sum \cdot 278.82}{(2\pi 60)(47)} = 0.022254 \text{ H}$

(5 pts.)

c) $P_T = \frac{3 \operatorname{Re}\{\bar{V}_a \bar{I}_a^*\}}{j\sqrt{3}} = \frac{3 \operatorname{Re}\left\{\left(\frac{460}{\sqrt{3}} \angle 0^\circ\right) (120 \angle 18.195^\circ)\right\}}{j\sqrt{3}} = 3 \cdot \operatorname{Re}\{30276 + j 9951.32\}$

$= 3 \cdot 30276 = 90828.7 \text{ W}$

(10 pts.)

$$P_T = -3 \cdot 278.82 \cdot \left(\frac{460}{\sqrt{3}} \right) \cdot \sin(-43.39^\circ)$$


$= 90828.7 \text{ W}$

$$\omega_M = \frac{z}{p} \cdot 2\pi 60 = \frac{z}{4} \cdot 2\pi 60 = 188.495 \text{ rad/s}$$

$$T^e w_m = P_m \rightarrow T^e = \frac{90828.74 \text{ W}}{(188.495 \text{ rad/s})} = 481.86 \text{ Nm}$$

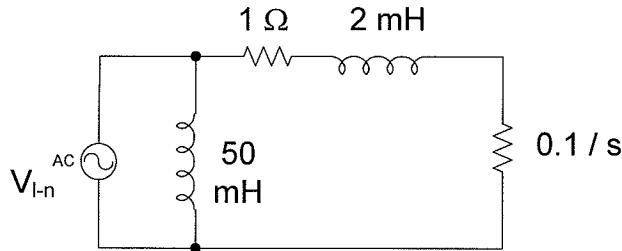Problem 4 (25 points)

A four-pole induction motor with the approximate equivalent circuit shown below is operated from 240 V (line-to-line), 60 Hz, three-phase power. Rated speed is 1760 RPM.




- (a) Find mechanical power at rated slip, in horsepower (1 hp = 746 W) (5 pts).
- (b) Find the slip for maximum torque (5 pts).
- (c) Find the maximum torque (5 pts).

Next, the machine is shipped to Europe, where it is operated from 220 V (line-to-line), 50 Hz three-phase power.

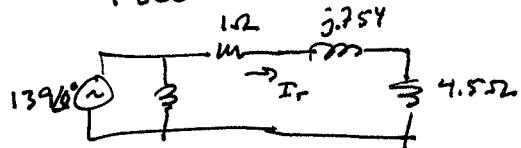- (d) Find the slip for maximum torque (5 pts).
- (e) Find the maximum torque (5 pts).

$$a) \quad s = \frac{1800 - 1760}{1800} = 0.02222 \quad ①$$



$$I_r = \frac{139\angle 0^\circ}{1 + 4.5 + j7.54} = 24.96 \angle -7.806^\circ \quad ②$$

$$P_m = 3(24.96)^2 (0.1) \left(\frac{1 - 0.02222}{0.02222} \right)$$

$$P_m = 8224 \text{ W} = 11.02 \text{ hp} \quad ③$$

$$b) \quad s_{maxT} = \pm \frac{R_r'}{\sqrt{R_s'^2 + (X_{rs}' + X_{rr}')^2}} = \pm \frac{0.1}{\sqrt{1^2 + 0.754^2}} = 0.07985 \quad ④$$


$$c) \quad P_{maxT} = 3 |I_r'|^2 R_r' \left(\frac{1 - s_{maxT}}{s_{maxT}} \right) \quad \frac{R_r'}{s_{maxT}} = \frac{0.1}{0.07985} = 1.252$$

$$I_r' = \frac{139\angle 0^\circ}{2.252 + j7.54} = 58.53 \angle -18.51^\circ \quad ⑤$$

$$P_{maxT} = 3(58.53)^2 (0.1) \left(\frac{1 - 0.07985}{0.07985} \right) = 11.84 \text{ kW} \quad ⑥$$

$$\omega_{m_{maxT}} = (1 - s_{maxT}) \left(\frac{2}{P} \right) (377) = 173.4 \text{ rad/s} \quad ⑦$$
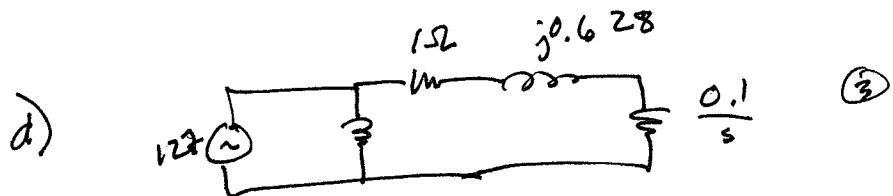
$$T_{max} = \frac{P}{\omega_m} = 68.26 \text{ N·m} \quad ⑧$$



$$S_{\text{maxT}} = \frac{0.1}{\sqrt{1^2 + 0.628^2}} = 0.08469 \quad (2)$$

e)

$$\bar{I}'_r = \frac{127 \angle 0^\circ}{1 + \frac{0.1}{0.08469} + j0.628} = 55.96 \angle -16.06^\circ \quad (2)$$


$$P = 3 (55.96)^2 (0.1) \left(\frac{1 - 0.08469}{0.08469} \right) = 10.15 \text{ kW} \quad (1)$$

$$\omega_m = (1 - S_{\text{maxT}}) \left(\frac{2}{P} \right) \omega_s = 143.8 \text{ rad/s} \quad (1)$$

$$T_{\text{max}} = \frac{10.15 \text{ kW}}{143.8 \text{ rad/s}} = 70.60 \text{ N·m} \quad (1)$$


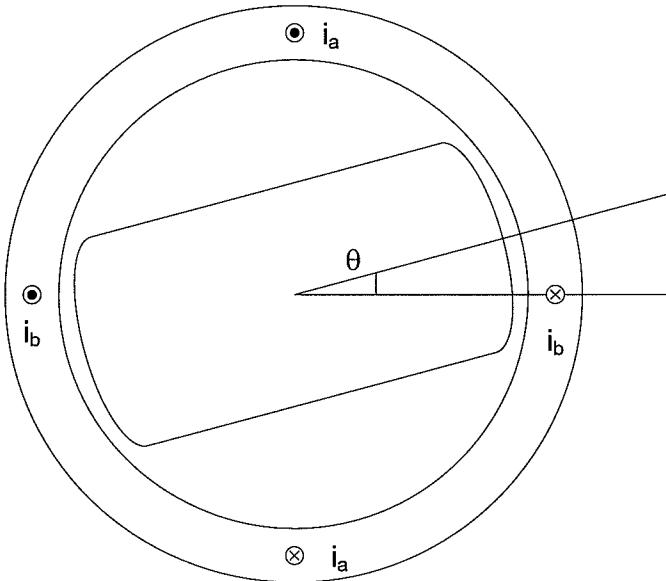
Problem 5 (25 points)

The motor shown below is a synchronous reluctance machine—essentially, a synchronous machine with no field winding. Assume that all inductances are zero, constant, or vary as $L_0 + L_1 \cos\phi$, where ϕ is some function of θ . For example, adding or subtracting 90° or 180° could convert the cosine to a sine or change the plus to a minus. Express all answers in terms of θ .




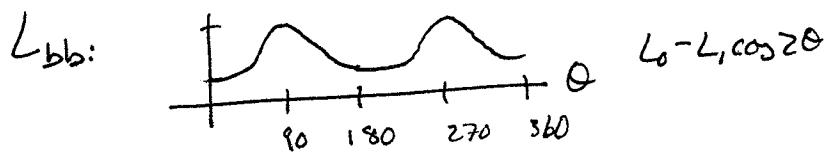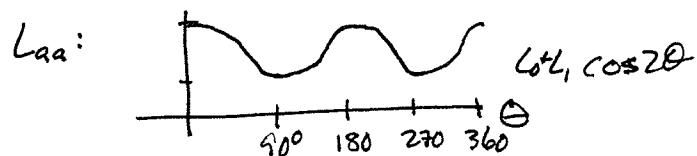- (a) Determine the flux linkage matrix relating $\begin{bmatrix} \lambda_a \\ \lambda_b \end{bmatrix}$ to $\begin{bmatrix} i_a \\ i_b \end{bmatrix}$ (10 pts).
- (b) Determine the co-energy W_m' (8 pts).
- (c) Determine the torque of electric origin $T^e(i_a, i_b, \theta)$ (7 pts).


$$a) \begin{bmatrix} \lambda_a \\ \lambda_b \end{bmatrix} = \begin{bmatrix} L_{aa} & L_{ab} \\ L_{ba} & L_{bb} \end{bmatrix} \begin{bmatrix} i_a \\ i_b \end{bmatrix} \quad L_{ab} = L_{ba}$$




L_{ab} :

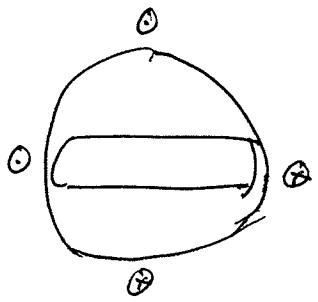

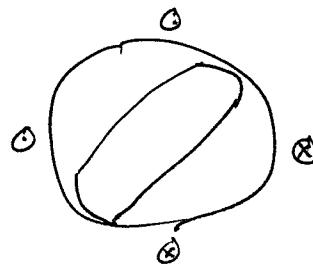
$$\begin{array}{l} \text{---} \\ L_{ab}=0 \\ 0, 180^\circ \end{array}$$


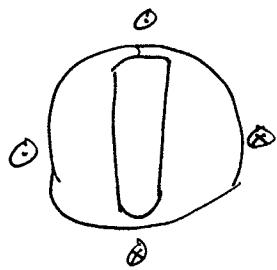
$$\begin{array}{l} L_{ab}=+ \max \\ 45^\circ, 225^\circ \end{array}$$


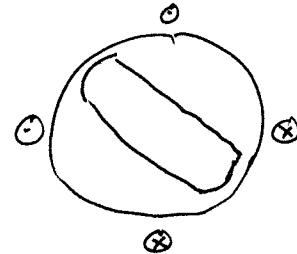
$$\begin{array}{l} L_{ab}=0 \\ 90^\circ, 270^\circ \end{array}$$



$$\begin{array}{l} L_{ab}=-\max \\ 135^\circ, 315^\circ \end{array}$$

$$M \sin 2\theta$$


$$\begin{bmatrix} d_a \\ d_b \end{bmatrix} = \begin{bmatrix} L_0 + L_1 \cos 2\theta & M \sin 2\theta \\ M \sin 2\theta & L_0 - L_1 \cos 2\theta \end{bmatrix} \begin{bmatrix} i_a \\ i_b \end{bmatrix}$$

b) $w_m' = \frac{1}{2} (L_0 + L_1 \cos 2\theta) i_a^2 + M \sin 2\theta i_a i_b + \frac{1}{2} (L_0 - L_1 \cos 2\theta) i_b^2$


c) $T^e = \frac{\partial w_m'}{\partial \theta} = -L_1 \sin 2\theta i_a^2 + 2M \cos 2\theta i_a i_b + L_1 \sin 2\theta i_b^2$

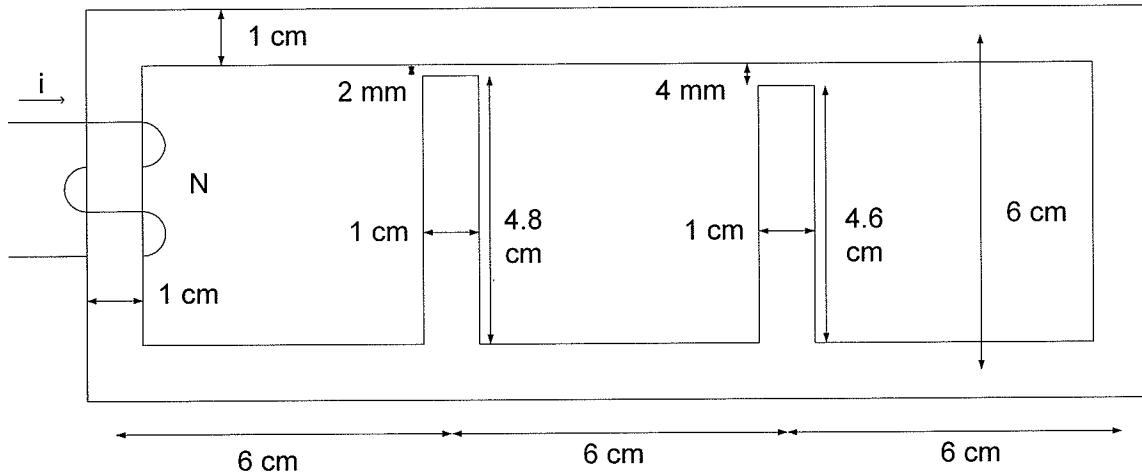Problem 6 (25 points)

Consider the magnetic structure below. $N = 100$. Depth into the page is 2 cm. Include the effects of fringing. Use the lengths provided for reluctance paths. Relative permeability of the iron is $\mu_r = 1000$.



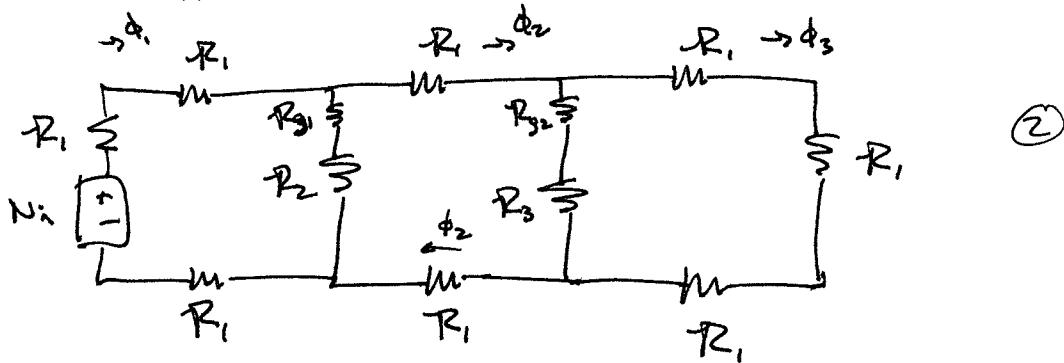- (a) Draw the magnetic equivalent circuit (12 pts).
 (b) Find $\lambda(i)$ (flux linkage in the coil as a function of current) (13 pts).



$$R_1 = \frac{l_1}{\mu A_1} = \frac{0.06}{1000(4\pi \times 10^{-7})(0.01)(0.02)} = 238.7 \text{e}3 \quad ②$$

$$R_2 = \frac{0.048}{1000\mu_0 (0.01)(0.02)} = 191 \text{e}3 \quad ②$$

$$R_3 = \frac{0.046}{1000\mu_0 (0.01)(0.02)} = 183 \text{e}3 \quad ②$$

$$R_{g1} = \frac{0.002}{\mu_0 (0.012)(0.022)} = 6.027 \text{e}6 \quad ②$$

$$R_{g2} = \frac{0.004}{\mu_0 (0.014)(0.024)} = 9.471 \text{e}6 \quad ②$$

$$\left. \begin{aligned}
 b) \quad N_i - 3\phi_1 R_1 - (\phi_1 - \phi_2)(R_{S1} + R_2) &= 0 \\
 (\phi_2 - \phi_1)(R_{S1} + R_2) + 2R_1 \phi_2 + (\phi_2 - \phi_3)(R_{S2} + R_3) &= 0 \\
 (\phi_3 - \phi_2)(R_{S2} + R_3) + 3R_2 \phi_3 &= 0
 \end{aligned} \right\} \quad (8)$$

$$(3R_1 + R_{S1} + R_2)\phi_1 + (-R_{S1} - R_2)\phi_2 + 0\phi_3 = N_i$$

$$(-R_{S1} - R_2)\phi_1 + (2R_1 + R_{S1} + R_2 + R_{S2} + R_3)\phi_2 + (-R_{S2} - R_3)\phi_3 = 0$$

$$0\phi_1 + (-R_{S2} - R_3)\phi_2 + (3R_2 + R_{S2} + R_3)\phi_3 = 0$$

$$\phi_3 = \frac{R_{S2} + R_3}{3R_1 + R_{S2} + R_3} \phi_2 = 0.9309 \phi_2$$

~~$$\phi_2 = \frac{(-R_{S2} - R_3)\phi_3 + (-R_{S1})}{(R_{S2} + R_3) + (R_{S1})}$$~~

$$(-R_{S1} - R_2)\phi_1 + (2R_1 + R_{S1} + R_2 + R_{S2} + R_3 + (-R_{S2} - R_3)(0.9309))\phi_2 = 0$$

$$\phi_2 = \frac{R_{S1} + R_2}{()} \phi_1 = 0.8446 \phi_1$$

$$N_i = \phi_1 (3R_1 + R_{S1} + R_2 - 0.8446(R_{S1} + R_2))$$

$$N_i = \phi_1 (1.682e6)$$

$$\phi_1 = (59.44e-6)i \quad (3)$$

$$\lambda = N\phi_1 = (5.944mH)i \quad (2)$$