

Section (Check one) MWF 10am _____ MWF 12pm _____ MWF 2pm _____

1. _____/25 2. _____/25
 3. _____/25 4. _____/25 TOTAL _____/100

USEFUL INFORMATION


$\sin(x) = \cos(x - 90^\circ)$ $\bar{V} = \bar{Z}\bar{I}\bar{S} = \bar{V}\bar{I}^* = P + jQ$ $\bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$
 $0 < \theta < 180^\circ$ (lag) $I_L = \sqrt{3}I_\phi$ (delta) $\bar{Z}_Y = \bar{Z}_\Delta / 3$
 $-180^\circ < \theta < 0$ (lead) $V_L = \sqrt{3}V_\phi$ (wye) $\mu_0 = 4\pi \times 10^{-7} \text{H/m}$

ABC phase sequence has A at 0, B at -120°, and C at +120°


$\int \underline{H} \cdot \underline{dl} = \int \underline{J}_f \cdot \hat{n} dA$ $\int \underline{E} \cdot \underline{dl} = -\frac{d}{dt} (\int \underline{B} \cdot \hat{n} dA)$ $\mathcal{R} = \frac{l}{\mu A}$ $Ni = \mathcal{R}\phi$

$\phi = BA$ $\lambda = N\phi = Li$ (if linear) $v = \frac{d\lambda}{dt} k = \frac{M}{\sqrt{L_1 L_2}}$

1hp=746 W

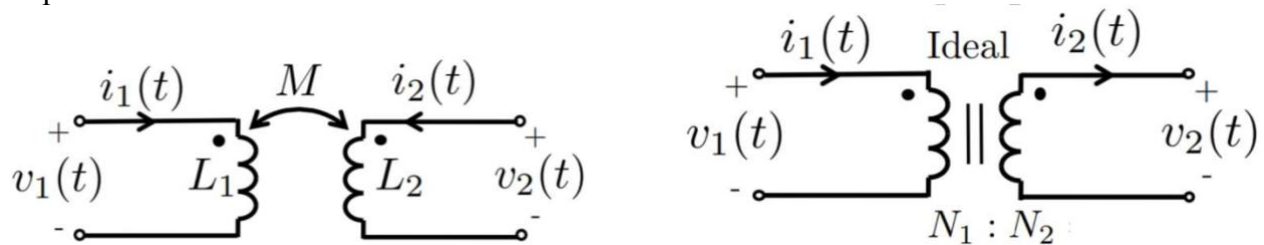

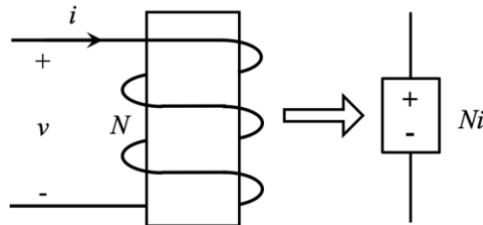$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$ $a = \frac{N_1}{N_2} N_1 i_1 = N_2 i_2$
 $v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$ $\frac{v_1}{v_2} = \frac{N_1}{N_2}$



Problem 1 (25 points)

A feeder with an impedance of $0.1 + j0.2 \Omega$ supplies a single-phase 10 kW 0.8 lagging power factor load. The voltage across the load is $v_L(t) = \sqrt{2} \sin(377t + 40^\circ) \text{ V}$. Calculate:


a) The source current phasor \bar{I}_s

$$\bar{Z}_f = 0.22 \angle 63.4^\circ \Omega$$

$$S = \frac{P}{PF} = \frac{10 \text{ kW}}{0.8} = 12.5 \text{ kVA}$$

$$\theta = \cos^{-1}(0.8) = 36.9^\circ$$
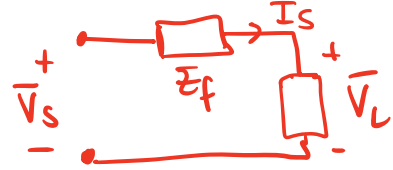
$$= \sqrt{2} \cos(377t - 90^\circ + 40^\circ) \Rightarrow \bar{V}_L = \frac{\sqrt{2}}{\sqrt{2}} \angle -50^\circ = 1 \angle -50^\circ \text{ V}$$



$$\bar{S}_L = \bar{V}_L \cdot \bar{I}_s^* \Rightarrow \bar{I}_s = \left(\frac{\bar{S}_L}{\bar{V}_L} \right)^* = \left(\frac{12.5 \text{ kVA} \angle 36.9^\circ}{1 \angle -50^\circ} \right)^* = 12.5 \text{ kA} \angle -86.9^\circ \text{ A}$$

$\bar{I}_s = 12.5 \angle -86.9^\circ \text{ kA}$

b) The source (sending end) voltage phasor \bar{V}_s

$$\bar{V}_s = \bar{V}_f + \bar{V}_L = \bar{I}_s \cdot \bar{Z}_f + \bar{V}_L = 2521.64 - j1096.76 = 2750 \angle -23.26^\circ \text{ V}$$

\downarrow
 $0.64 - j0.76 \text{ V}$

$$12.5 \text{ kA} \angle -86.9^\circ \cdot 0.22 \angle 63.4^\circ =$$

$$= 2750 \angle -23.5^\circ \text{ V} =$$

$$= 2521 - j1096 \text{ V}$$

$\bar{V}_s = 2750 \angle -23.26^\circ \text{ V}$

c) The total complex power supplied by the source, \bar{S}_t

$$\bar{S}_t = \bar{V}_s \cdot \bar{I}_s^* = 2750 \angle -23.26^\circ \cdot 12.5 \angle 86.9^\circ = 34 \angle 63.64^\circ \text{ MVA}$$

$$\bar{S}_t = \underline{34 \angle 63.64^\circ \text{ MVA}}$$

d) The power factor at the source (sending end). Specify whether it is lagging or leading.

$$\text{PF} = \cos(63.4^\circ) = 0.44$$

$$\text{PF} = \underline{0.44}$$

Circle one: Lagging / Leading

Problem 2 (25 points)

Two 3-phase loads are connected in parallel to a wye-connected source of 208V line to line. The loads are given as:

Load 1: wye-connected, 10 A (line current), 3200 W (3-phase) lagging power factor

Load 2: delta-connected, 8 A (phase current), 0.9 power factor lagging.

a) What is the total line current \bar{I}_L being supplied by the source?

Per-phase eq. circuit:

$\bar{V}_{an} = \frac{208}{\sqrt{3}} \angle 0^\circ \text{ V}$
 $P = \frac{3200}{3} = 1066 \text{ W}$
 $\bar{I}_{L1}: I_{L1} = 10 \text{ A}; P = V \cdot I \cdot \cos \theta \Rightarrow \text{PF} = \frac{P}{V \cdot I} = \frac{1066}{120 \cdot 10} = 0.88$
 $\theta = \cos^{-1}(0.88) = 28.4^\circ$
 $\bar{I}_{L1} = 10 \angle -28.4^\circ \text{ A} = 8.8 - j4.8 \text{ A}$

$I_{L2} = \sqrt{3} I_\phi = 8\sqrt{3} \text{ A}; \bar{I}_{L2} = 8\sqrt{3} \angle -25.8^\circ \text{ A}$
 $\text{PF} = 0.9 \text{ lag} \Rightarrow \theta = \cos^{-1}(0.9) = 25.8^\circ \Rightarrow \theta_c = -25.8^\circ$

$\nearrow 12.5 - j6 \text{ A}$

$\bar{I}_L = \bar{I}_{L1} + \bar{I}_{L2} = 21.3 - j10.8 = 23.8 \angle -26.5^\circ \text{ A}$

b) How many capacitive VARs PER-PHASE needed to bring overall power factor to unity? Justify your answer. Answers without justification will receive no credit.


$\bar{S}_{t,1\phi} = \bar{V}_{an} \cdot \bar{I}_L^* = \frac{208}{\sqrt{3}} \angle 0^\circ \cdot 23.8 \angle 26.5^\circ = 2856 \angle 26.5^\circ =$
 $= \underbrace{2556}_P + j \underbrace{1274}_Q \text{ VA}$

$\text{PF} = 1 \rightarrow \theta_v = \theta_i \rightarrow Q = 0 \rightarrow$
 add 1274 VARs of capacitance per-phase

$Q_c = 1274 \text{ VARs of capacitance per-phase}$

Reason:

Problem 3 (25 points)

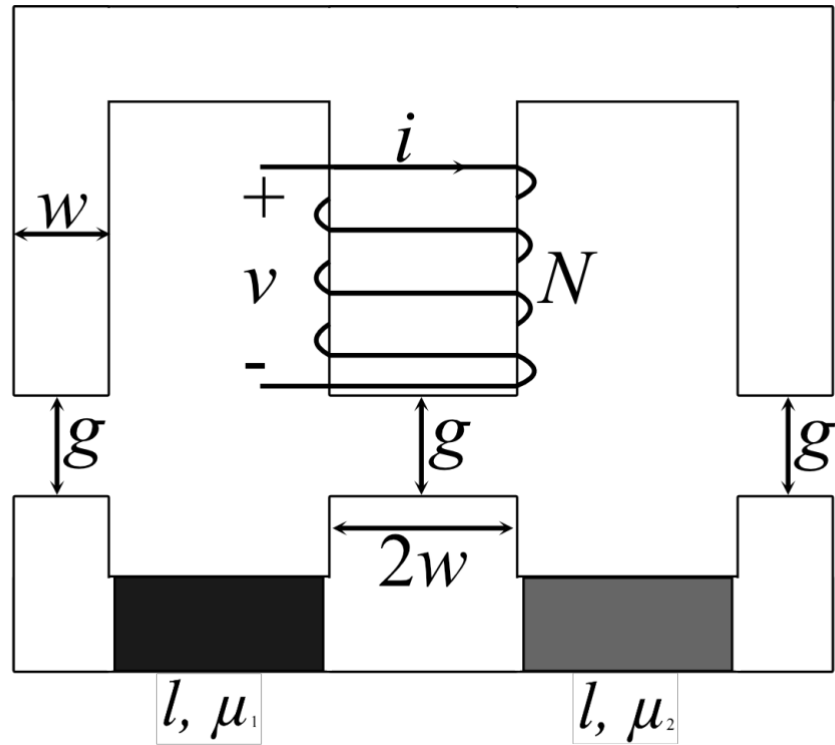

An iron core with infinite permeability, width $w=2$ cm, air gap length $g=3$ mm, and depth into the page $d=3$ cm has a coil wrapped around it as given above with $N=250$. The iron core also has two inserts in it with length $l=10$ cm and permeabilities $\mu_1 = 2500\mu_0$ and $\mu_2 = 1250\mu_0$. Fringing effects can be neglected.

a) Draw the magnetic equivalent circuit for this system. (8 points)


b) What is the flux through the coil? (12 points)

$\phi =$ _____

c) What is the voltage drop across the coil in terms of the unknown current i ? (5 points)

$v =$ _____

3)

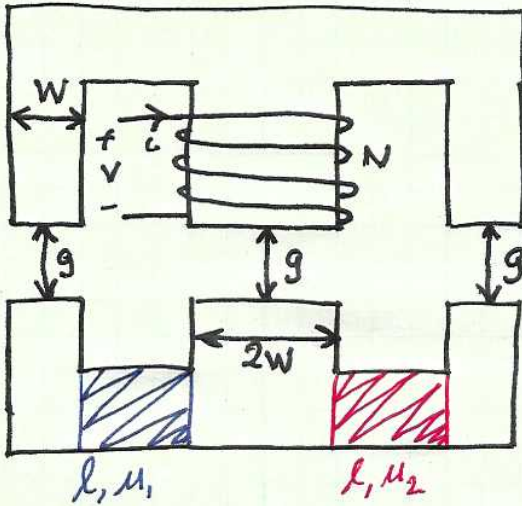

$$d = 3 \text{ cm}$$

$$W = 2 \text{ cm}$$

$$L = 10 \text{ cm}$$


$$g = 3 \text{ mm}$$

$$\mu_1 = 2500 \mu_0$$

$$\mu_2 = 1250 \mu_0$$

$$N = 250$$

a)

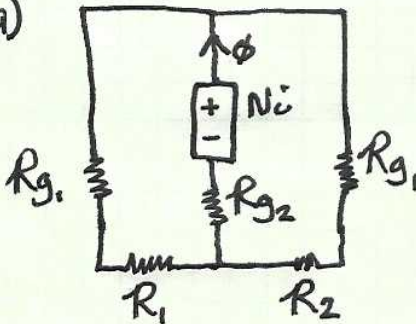


$$R_{g1} = \frac{3 \text{ mm}}{\mu_0 (6 \text{ cm}^2)} = 3.979 \times 10^6 \text{ At/Wb}$$

$$R_{g2} = \frac{3 \text{ mm}}{\mu_0 (12 \text{ cm}^2)} = 1.989 \times 10^6 \text{ At/Wb}$$

$$R_1 = \frac{10 \text{ cm}}{2500 \mu_0 (6 \text{ cm}^2)} = 5.305 \times 10^4 \text{ At/Wb}$$

$$R_2 = \frac{10 \text{ cm}}{1250 \mu_0 (6 \text{ cm}^2)} = 1.061 \times 10^5 \text{ At/Wb}$$

b) Redrawing circuit

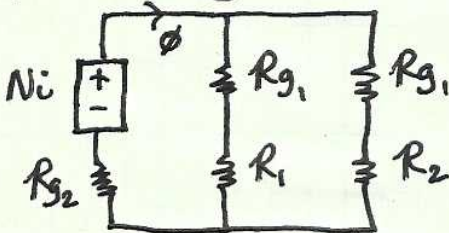

$$R_{eq} = R_{g2} + \left(\frac{1}{R_{g1} + R_1} + \frac{1}{R_{g1} + R_2} \right)^{-1}$$

$$R_{eq} = 4.019 \times 10^6 \text{ At/Wb}$$

$$\phi = \frac{Ni}{R_{eq}} \Rightarrow \phi = 6.221 \times 10^{-5} i \text{ Wb}$$


$$c) v = \frac{d\lambda}{dt}$$

$$\lambda = N\phi \Rightarrow \lambda = 0.0156 i$$

$$v = 0.0156 \frac{di}{dt} \text{ V}$$

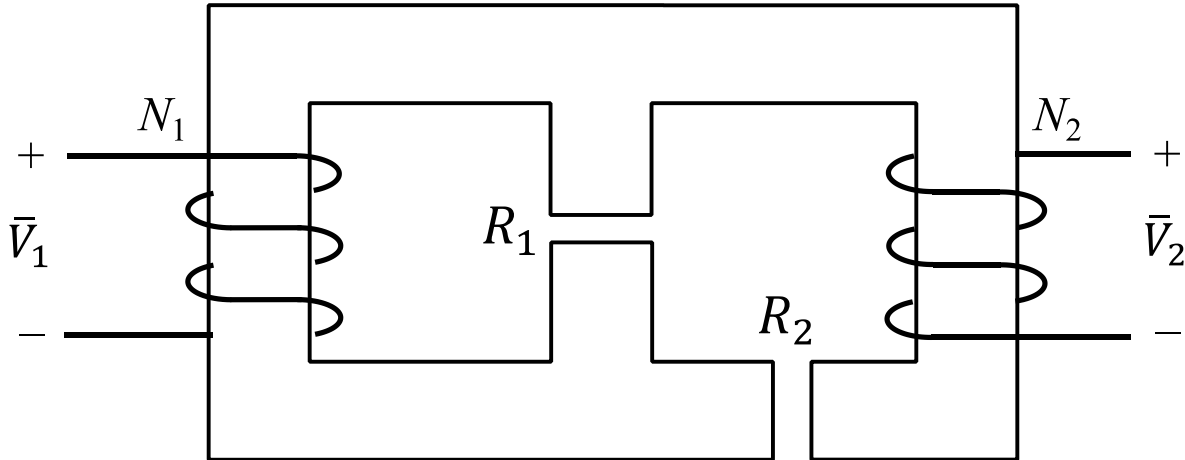Problem 4 (25 Points)

You are consulting for a wind farm company who is looking to install a high voltage transformer to minimize their transmission loss. A schematic of the transformer is shown below.



The first coil has $N_1 = 10$ turns while the second coil has $N_2 = 500$ turns. The transformer contains two air gaps, with reluctances $R_1 = 50$ At/Wb and $R_2 = 1000$ At/Wb as labeled. You may treat the permeability of the magnetic core as infinite.

a) Assuming for now that the transformer is ideal, what would the output voltage \bar{V}_2 be (at open circuit) with an input voltage $\bar{V}_1 = 1\angle 0^\circ$ kV (rms) at 60 Hz? (Please specify both the phase and the magnitude of the output voltage \bar{V}_2 , and briefly justify your answer.)



$$\bar{V}_2 = -\frac{N_2}{N_1} \bar{V}_1 = -\frac{500}{10} 1\angle 0^\circ \text{ kV} = 50\angle 180^\circ \text{ kV} \quad (-50\angle 0^\circ \text{ kV})$$

Reason: If ideal transformer, $V_1:V_2$ determined purely by $N_1:N_2$. But because way coils are wound, expect 180° phase shift.



Have to label current yourself.

Doesn't matter, so pick easier choice.

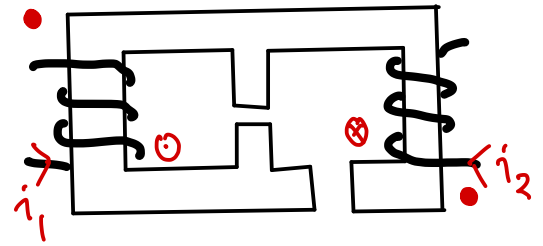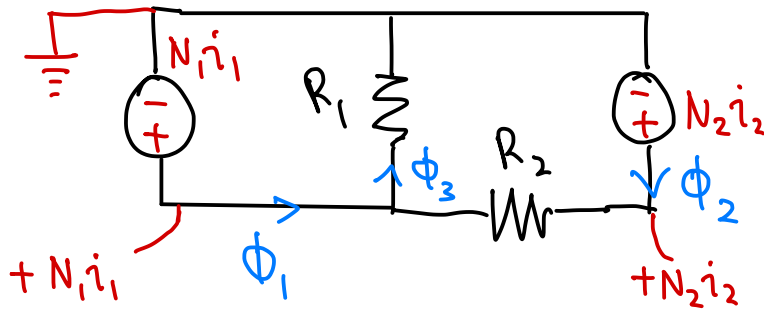b) Compute the self inductances L_1 , L_2 , and the mutual inductance M of the two coils.



close-ups:

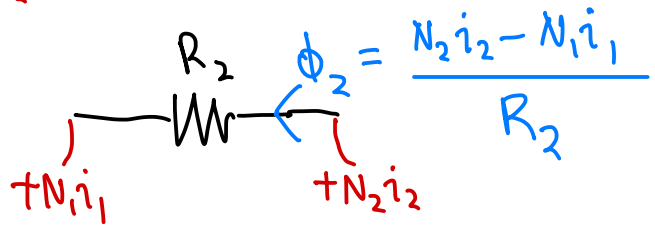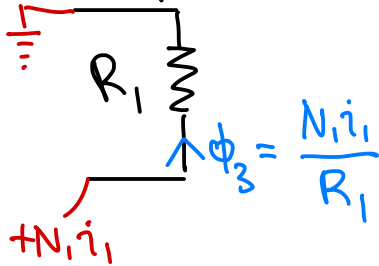

$$\phi_2 = \frac{N_2 i_2 - N_1 i_1}{R_2}$$

$$\phi_1 + \phi_2 = \phi_3$$

$$\phi_1 + \frac{N_2 i_2 - N_1 i_1}{R_2} = \frac{N_1 i_1}{R_1}$$

$$\lambda_2 = \frac{N_2^2}{R_2} i_2 - \frac{N_1 N_2}{R_2} i_1$$

$$\lambda_1 = N_1^2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) i_1 - \frac{N_1 N_2}{R_2} i_2$$

$L_1 \geq 0$

$L_2 \geq 0$


$M \geq 0$

$$L_1 = N_1^2 (R_1^{-1} + R_2^{-1}) = 2.1 \text{ H}$$

$$L_2 = N_2^2 / R_2 = 250 \text{ H}$$

$$M = N_1 N_2 / R_2 = 5 \text{ H}$$

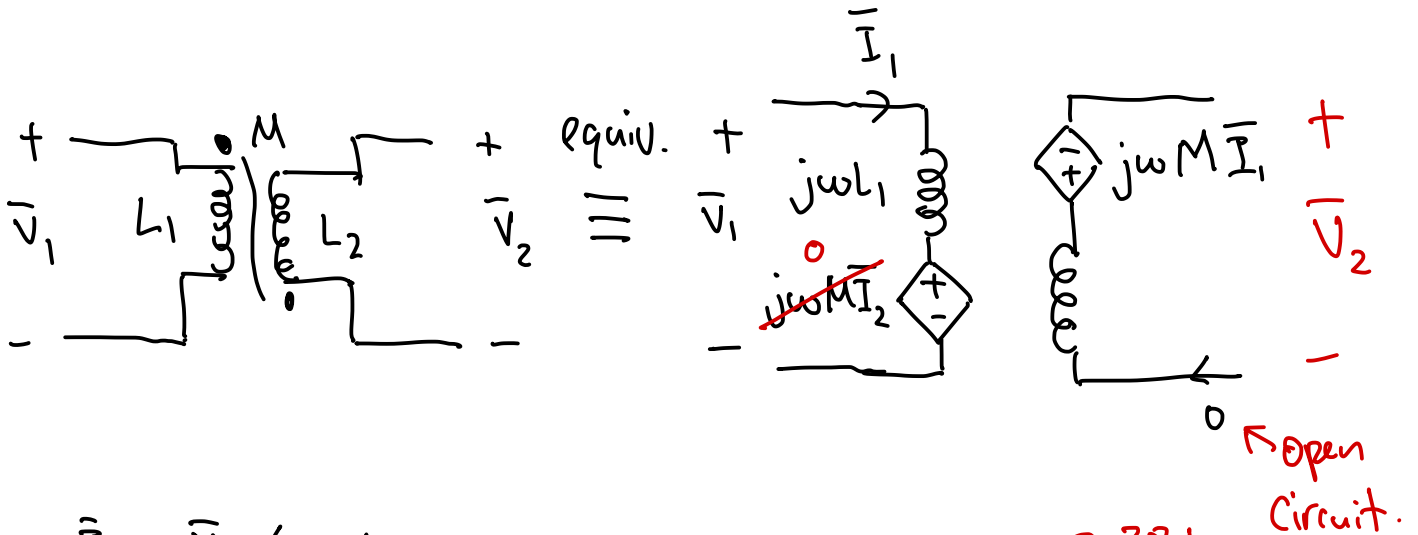c) Use the self and mutual inductance values you have just computed above as a more realistic model of the transformer. What would the output voltage \bar{V}_2 be (at open circuit) with an input voltage $\bar{V}_1 = 1 \angle 0^\circ$ kV (rms) at 60 Hz? (Please specify both the phase and the magnitude of the output voltage \bar{V}_2 , and briefly justify your answer.)



$$\bar{I}_1 = \bar{V}_1 / j\omega L_1$$

$$\bar{V}_2 = -j\omega M \bar{I}_1 = -\frac{j\omega M}{j\omega L_1} \bar{V}_1 = \frac{5}{2.1} \angle 180^\circ \text{ kV}$$

2.381

$$\bar{V}_2 = 2.381 \angle 180^\circ \text{ kV}$$

Reason: $i_2 = 0$ because of open circuit, so $M \frac{di_2}{dt} = 0$, and i_1

is entirely determined by L_1 . Once known, $v_2 = M \frac{di_1}{dt}$.

Finally, adjust for phasing: 180° due to polarity dots.

