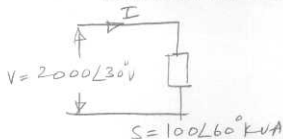


Problem 1 (30 pts.) (No partial credit)

- a) A single-phase load takes a complex power of $100 \angle 60^\circ$ kVA and the voltage across the load is $2000 \angle 30^\circ$ V. The current in phasor form is $\underline{50 \angle -30^\circ}$ A.




$$\bar{S} = \bar{V} \bar{I}^* \Rightarrow I = \left(\frac{\bar{S}}{\bar{V}} \right)^* = 50 \angle -30^\circ \text{ A}$$

- b) Two loads in parallel have the complex powers as $100 + j100$ kVA and $50 + jQ$ kVA. The total complex power is $150 - j50$ kVA. The value of Q is $\underline{-150 \text{ kVA}}$. Is it **capacitive** or inductive (circle one)?

$$100 + j100 + 50 + jQ = 150 - j50 \Rightarrow Q = -150 \text{ kVA}$$

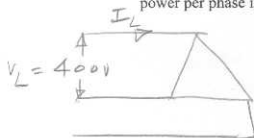- c) A 3 phase, delta connected load has a line to line voltage of 400 V. The complex power per phase is $1000 + j500$ VA. The magnitude of the line current is $\underline{4.84}$ A.



$$1000 + j500 = V_{ph} I_{ph}^* \Rightarrow I_{ph} = (2.5 - j1.25) \text{ A}$$

$$= 400 I_{ph}^* \Rightarrow I_{ph} = 2.795 \angle 26.56^\circ \text{ A}$$


$$|I_L| = \sqrt{3} |I_{ph}| = 4.84 \text{ A}$$

- d) A coil of 500 turns is wound on an iron core whose reluctance $\mathfrak{R} = 4.6 \times 10^6$ At/Wb. The inductance of the coil is $\underline{53.35 \text{ mH}}$.

$$L = \frac{N^2}{\mathfrak{R}} = \frac{500^2}{4.6 \times 10^6} = 53.35 \text{ mH}$$

$$\left(\lambda = N\phi = N \frac{Ni}{\mathfrak{R}} = \frac{N^2 i}{\mathfrak{R}} = Li \Rightarrow L = \frac{N^2}{\mathfrak{R}} \right)$$

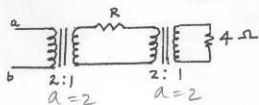- e) Input resistance at "ab" is 100Ω ($R > 0$). The value of R is 9Ω .




Ideal transformers

$$100 = a^2(R + a^2 4)$$

$$\therefore 100 = 4(R + 16) \Rightarrow R = 9$$

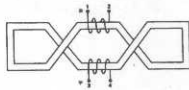- e) Put the dot markings on the two coils.



Dots at 1 and 3
OR 2 and 4.


Problem 2 (35)

The following two three phase loads are connected in parallel across a three phase wye connected source of 2400 V (line to line)

Load #1 120 kVA at 0.8 PF lead

Load #2 180 kW at 0.6 PF lag

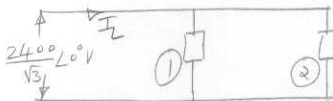- Find total complex power
- Find the total line current (magnitude) from the source.
- What kVAR of capacitor is needed to make the overall PF=0.8 lead



per phase equivalent circuit

a) Load #1 : $S_1 = 120 (0.8 - j0.6) = 96 - j72 \text{ kVA}$
#2 : $S_2 = \frac{180}{0.6} (0.6 + j0.8) = 180 + j240 \text{ kVA}$

Total Power = $S_1 + S_2 = \underline{\underline{276 + j168 \text{ kVA}}}$

b) $\text{PF} = \cos(\tan^{-1} \frac{168}{276}) = 0.854 \text{ lag}$

Now $276 = \sqrt{3} (2400) I_L (0.854)$

$\Rightarrow \underline{\underline{I_L = 77.75 \text{ A}}}$


c) $Q_{\text{new}} = 276 \tan(\cos^{-1} 0.8) = -207 \text{ kVAR.}$ (-ve for capacitive)

$Q_{\text{old}} + Q_{\text{cap}} = Q_{\text{new}}$

$\therefore 168 + Q_{\text{cap}} = -207 \text{ kVAR}$

$\Rightarrow \underline{\underline{Q_{\text{cap}} = -376 \text{ kVAR.}}}$

Problem 3 (35)

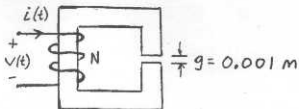

$$v(t) = 120\sqrt{2} \cos(2\pi 60t)$$

$$\sigma_{\text{wire}} = \infty$$

$$\text{Cross section area } A = 0.0016 \text{ m}^2$$

Neglect fringing and leakage

- a) Find the value of N so that the peak value of the flux density in the iron is 1.0 Tesla
 b) Using this N , find the current $i(t)$ (if you cannot find N in a), just use the symbol N)

$$a) \quad 120\sqrt{2} \cos 2\pi 60t = N \frac{d\phi}{dt}$$

$$\phi = \frac{120\sqrt{2} \sin 2\pi 60t}{2\pi 60N} \quad \text{Want } \frac{120\sqrt{2}}{2\pi 60N} = (1.0)(0.0016)$$

$$\Rightarrow \boxed{N = 281 \text{ Turns}}$$

$$b) \quad H_{\text{gap}} g = Ni \Rightarrow i = \frac{H_{\text{gap}} \times 0.001}{281}$$

$$= \frac{0.001 B_{\text{gap}}}{281 \times 4\pi \times 10^7}$$

$$\therefore i = \frac{0.001}{281 \times 4\pi \times 10^7} \frac{\phi}{A} = \frac{0.001 \times 120\sqrt{2} \sin 2\pi 60t}{281 \times 4\pi \times 10^7 \times 2\pi 60 \times 281 \times 0.0016}$$

$$\therefore \boxed{i = 2.8 \sin 2\pi 60t \text{ A}}$$