

ECE 330 Exam 1: Spring 2019
90 minutes

NAME Solution

Section (Check one) MWF 2pm _____ MWF 3pm _____

1. _____/25 2. _____/25
3. _____/25 4. _____/25 TOTAL _____/100

USEFUL INFORMATION


$\sin(x) = \cos(x - 90^\circ)$ $\bar{V} = \bar{Z}\bar{I}$ $\bar{S} = \bar{V}\bar{I}^* = P + jQ$ $\bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$
 $0 < \theta < 180^\circ$ (lag) $I_L = \sqrt{3}I_\phi$ (delta) $\bar{Z}_Y = \bar{Z}_\Delta / 3$
 $-180^\circ < \theta < 0$ (lead) $V_L = \sqrt{3}V_\phi$ (wye) $\mu_0 = 4\pi \times 10^{-7} \text{H/m}$

ABC phase sequence has A at 0°, B at -120°, and C at +120°


$\int \underline{H} \cdot \underline{dl} = \int \underline{J}_f \cdot \hat{n} dA$ $\int \underline{E} \cdot \underline{dl} = -\frac{d}{dt} \left(\int \underline{B} \cdot \hat{n} dA \right)$ $\mathcal{R} = \frac{l}{\mu A}$ $Ni = \mathcal{R}\phi$

$\phi = BA$ $\lambda = N\phi = Li$ (if linear) $v = \frac{d\lambda}{dt}$ $k = \frac{M}{\sqrt{L_1 L_2}}$


1hp = 746 W

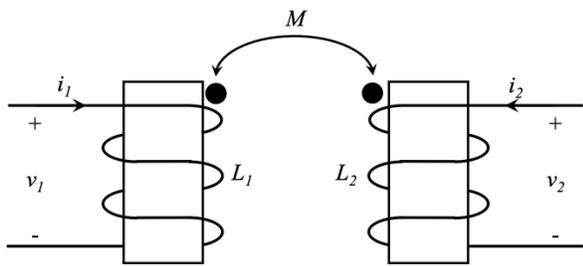

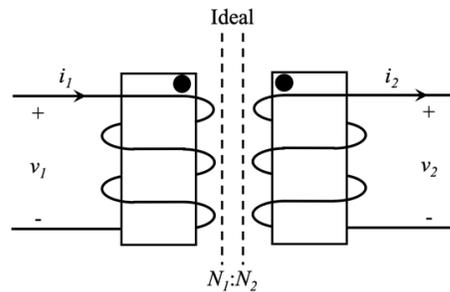$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$
 $v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$



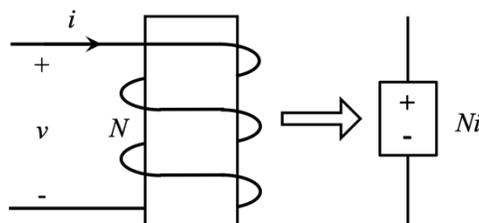$a = \frac{N_1}{N_2}$ $N_1 i_1 = N_2 i_2$
 $\frac{V_1}{V_2} = \frac{N_1}{N_2}$



Problem 1 (25 Points)

3 single-phase loads are connected in parallel to a generator that supplies 240 V. The loads are given as:

- 1) A purely resistive load that consumes 100 kW
- 2) A load that consumes 300 kVA at a power factor of 0.8 lagging
- 3) A load with impedance $Z=30+j40 \Omega$

a) What is the total power supplied by the source? (12 points)

$$\begin{aligned} \bar{S}_1 &= 100 \angle 0^\circ \text{ kVA} \\ \theta_2 &= \cos^{-1}(0.8) \Rightarrow \theta_2 = 36.87^\circ \\ \bar{S}_2 &= 300 \angle 36.87^\circ \text{ kVA} \\ \bar{Z}_3 &= 30 + j40 \Omega \\ &= 50 \angle 53.13^\circ \Omega \\ V &= \bar{Z}_3 \bar{I}_3 \Rightarrow \bar{I}_3 = \frac{V}{\bar{Z}_3} \\ \bar{S}_3 &= V \bar{I}_3^* = \frac{V^2}{\bar{Z}_3^*} \Rightarrow \bar{S}_3 = \frac{240^2}{50 \angle -53.13^\circ} \Rightarrow \bar{S}_3 = 1.152 \angle 53.13^\circ \text{ kVA} \end{aligned}$$


$$\begin{aligned} \bar{S}_{TOT} &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 \\ &= (100 + j0) + (240 + j180) \\ &\quad + (0.691 + j0.922) \end{aligned}$$

$$\begin{aligned} \bar{S}_{TOT} &= 340.691 + j180.922 \text{ kVA} \\ &= 385.75 \angle 27.97^\circ \text{ kVA} \end{aligned}$$

b) What is the source current? (5 points)

$$\begin{aligned} \bar{S}_{TOT} &= V \bar{I}_s^* \\ \bar{I}_s^* &= \frac{\bar{S}_{TOT}}{V} \Rightarrow \bar{I}_s^* = 1607.3 \angle 27.97^\circ \text{ A} \\ \bar{I}_s &= 1607.3 \angle -27.97^\circ \text{ A} \end{aligned}$$

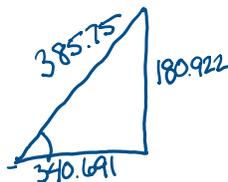c) A capacitor is connected in parallel with the loads. How much power should it supply to achieve an overall power factor of 0.975 lagging? (8 points)



$$\begin{aligned} \theta_n &= \cos^{-1}(0.975) \\ \theta_n &= 12.84^\circ \\ Q_n &= P \tan(\theta_n) \\ Q_n &= 77.65 \text{ kVAR} \end{aligned}$$

$$\begin{aligned} Q_n &= Q_{old} + Q_c \\ Q_c &= Q_n - Q_{old} \Rightarrow Q_c = -103.272 \text{ kVAR} \\ &= 103.272 \text{ kVAR of capacitance} \end{aligned}$$

Problem 2 (25 points)


Three 3-phase loads are connected in parallel to a wye-connected source with 480 V line to line. The loads are given as:

- 1) A wye connected load consuming 250 kVA at a 0.707 lagging power factor
- 2) A wye connected load consuming 75 kW at a 0.9 lagging power factor
- 3) A delta connected load with impedance $Z=100+j100 \Omega$

a) What is the total line current supplied by the source? (13 points)


$$\begin{aligned} \bar{S}_1 &= 250 \angle 45^\circ \text{ kVA} \\ P_2 &= S_2 (\text{PF}) \Rightarrow S_2 = \frac{P_2}{\text{PF}_2} \Rightarrow S_2 = 83.33 \text{ kVA} \quad \theta_2 = \cos^{-1}(0.9) \Rightarrow \theta_2 = 25.84^\circ \\ \bar{S}_2 &= 83.33 \angle 25.84^\circ \text{ kVA} \\ \bar{I}_{\phi_3} &= \frac{V_{\phi}}{Z_{\phi}} \Rightarrow \bar{I}_{\phi_3} = 3.39 \angle 45^\circ \text{ A} \\ \bar{S}_3 &= 3(480)(3.39) \angle 45^\circ \Rightarrow \bar{S}_3 = 4.882 \angle 45^\circ \text{ kVA} \\ \bar{S}_{\text{TOT}} &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 \\ &= (176.78 + j176.78) + (75 + j36.32) + (3.45 + j3.45) \text{ kVA} \\ &= 255.23 + j216.55 \text{ kVA} \\ \bar{S}_{\text{TOT}} &= 334.72 \angle 40.31^\circ \text{ kVA} = \sqrt{3} V_L I_L \angle \theta \\ \bar{I}_L &= 402.61 \angle -40.31^\circ \end{aligned}$$

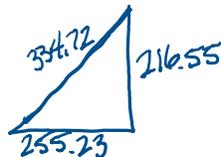b) A delta connected capacitor bank is added in parallel to the three loads to make the overall power factor 0.99 lagging. What is the new line current? (12 points)



$$\begin{aligned} \theta_n &= \cos^{-1}(0.99) \\ \theta_n &= 8.11^\circ \\ Q_n &= 255.23 \tan(8.11^\circ) \\ &= 36.37 \text{ kVAR} \\ \bar{S}_n &= 255.23 + j36.37 \text{ kVA} \\ &= 257.81 \angle 8.11^\circ = \sqrt{3} V_L I_L \angle \theta \\ \bar{I}_L &= 310.1 \angle -8.11^\circ \end{aligned}$$

Problem 3 (25 Points)

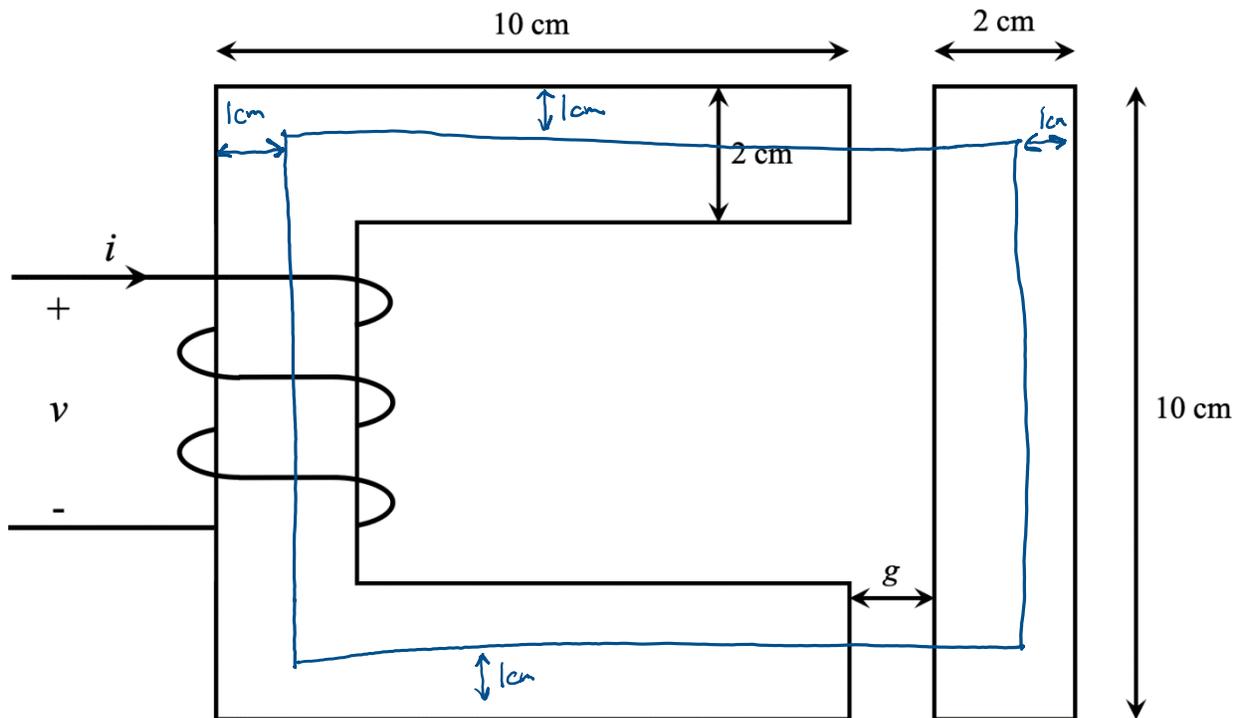

A coil is wound 150 times around an iron core (dimensions given above) with relative permeability 2500 that has an air gap g of 20 mm and depth into the page of 3 cm. With the voltage polarity and current direction as defined above:


- a) What is the reluctance path length inside the iron core? (7 points)

$$9 + 9 + 8 = 26 \text{ cm}$$

$$1 + 1 + 8 = 10 \text{ cm}$$

$$l_c = 36 \text{ cm}$$

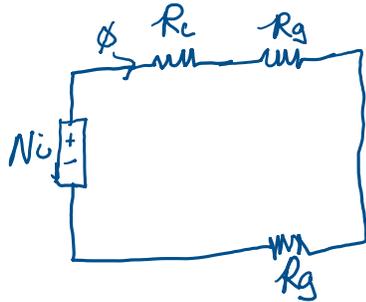- b) Draw the magnetic equivalent circuit and determine the reluctance values for the iron and air gap (neglect fringing). (8 points)



$$R_c = \frac{l_c}{\mu_0 \mu_r A} \Rightarrow R_c = 1.910 \times 10^5 \text{ At/Wb}$$

$$A = 6 \text{ cm}^2$$

$$R_g = \frac{g}{\mu_0 A} \Rightarrow R_g = 2.65 \times 10^7 \text{ At/Wb}$$

- c) What is the inductance of the coil? (10 points)

$$\phi = \frac{Ni}{2R_g + R_c}$$


$$\phi = 2.82 \times 10^{-6} i$$

$$\lambda = N\phi$$

$$\lambda = 0.423 \times 10^{-3} i = Li$$


$$L = 0.423 \text{ mH}$$

Problem 4 (25 Points)

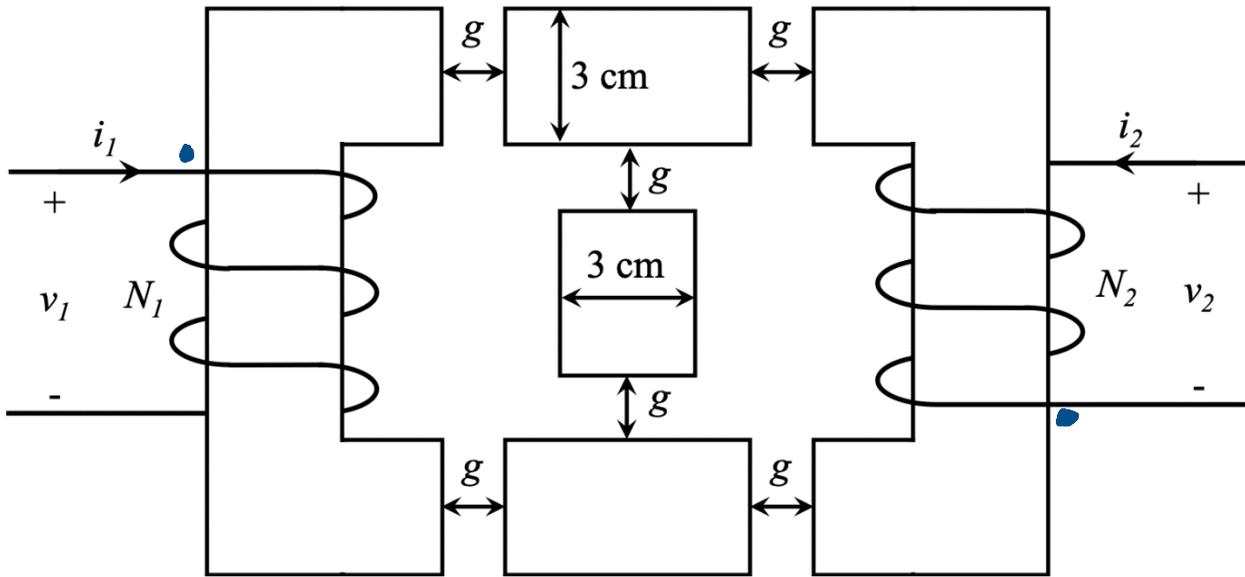

Two coils are wrapped around an iron core with infinite permeability as shown. Coil 1 has 200 turns while coil 2 has 100 turns. The air gap g is 10 mm and the depth into the page is 3 cm. Neglect fringing.

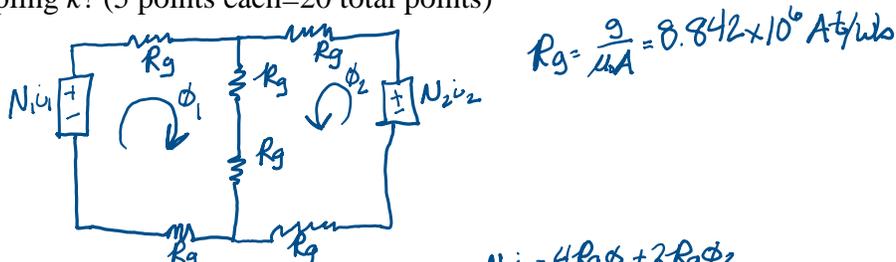- Put the dot markings on the two coils. (5 points)
- What is the self-inductance of the two coils, the mutual inductance, and the coefficient of coupling k ? (5 points each=20 total points)



$$R_g = \frac{g}{\mu_0 \mu_r} = 8.842 \times 10^6 \text{ At/Wb}$$

$$N_1 i_1 = R_g \phi_1 + 2R_g(\phi_1 + \phi_2) + R_g \phi_1 \Rightarrow N_1 i_1 = 4R_g \phi_1 + 2R_g \phi_2$$

$$N_2 i_2 = R_g \phi_2 + R_g(\phi_1 + \phi_2) + R_g \phi_2 \Rightarrow N_2 i_2 = 2R_g \phi_1 + 4R_g \phi_2$$

$$\phi_2 = \frac{N_2 i_2 - 2R_g \phi_1}{4R_g}$$

$$N_1 i_1 = 4R_g \phi_1 + \frac{1}{2}(N_2 i_2 - 2R_g \phi_1)$$

$$N_1 i_1 = 3R_g \phi_1 + \frac{1}{2} N_2 i_2$$

$$\frac{N_1 i_1 - \frac{1}{2} N_2 i_2}{3R_g} = \phi_1 \Rightarrow \phi_1 = 2.54 \times 10^{-6} i_1 - 1.89 \times 10^{-6} i_2$$

$$\phi_2 = \frac{N_2 i_2 - \frac{2}{3}(N_1 i_1 - \frac{1}{2} N_2 i_2)}{4R_g} \Rightarrow \phi_2 = -\frac{2}{3} N_1 i_1 + \frac{4}{3} N_2 i_2 \Rightarrow \phi_2 = -3.77 \times 10^{-6} i_1 + 3.77 \times 10^{-6} i_2$$

$$\lambda_1 = N_1 \phi_1 = 1.508 \times 10^{-3} i_1 - 0.377 \times 10^{-3} i_2$$

$$\lambda_2 = N_2 \phi_2 = -0.377 \times 10^{-3} i_1 + 0.377 \times 10^{-3} i_2$$

$$L_1 = 1.508 \text{ mH}$$

$$L_2 = 0.377 \text{ mH}$$

$$M = 0.377 \text{ mH}$$

$$k = \frac{M}{\sqrt{L_1 L_2}} = 0.5$$