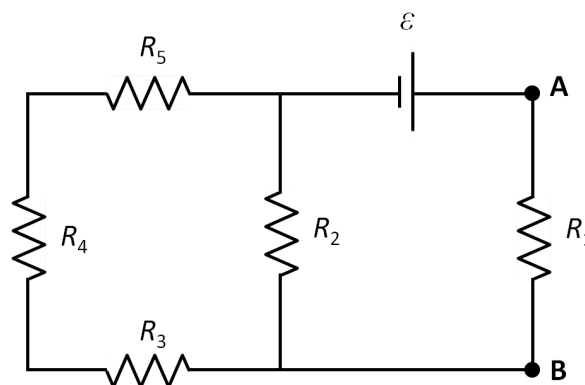


The next three questions pertain to the situation described below.


Consider an electrical circuit shown. It consists of an ideal battery and five resistors, whose values are:  $\varepsilon = 12 \text{ V}$ ,  $R_1 = 4 \text{ } \Omega$ ,  $R_2 = R_3 = R_4 = R_5 = 3 \text{ } \Omega$ .



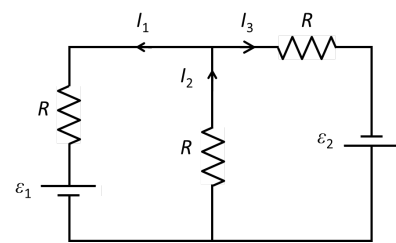- 1) What is the ratio  $I_2/I_3$  of the currents flowing through  $R_2$  and  $R_3$ ?
  - a.  $I_2/I_3 = 0.333$
  - b.  $I_2/I_3 = 1$
  - c.  $I_2/I_3 = 3$
  
- 2) What is the electric potential difference between the points **A** and **B**?
  - a.  $V_A - V_B = 12 \text{ V}$
  - b.  $V_A - V_B = 7.68 \text{ V}$
  - c.  $V_A - V_B = -7.68 \text{ V}$
  - d.  $V_A - V_B = -3 \text{ V}$
  - e.  $V_A - V_B = 3 \text{ V}$
  
- 3) If the ideal battery is now replaced with a non-ideal battery of the same voltage, how would the current  $I_1$  through  $R_1$  change?
  - a. stay the same
  - b. increase
  - c. decrease

The next two questions pertain to the situation described below.

Consider an electrical circuit shown. It consists of two ideal batteries and three identical resistors, whose values are:  $\epsilon_1 = 12 \text{ V}$ ,  $\epsilon_2 = 15 \text{ V}$ ,  $R = 5 \Omega$ . The positive directions for the currents  $I_1$ ,  $I_2$  and  $I_3$  are indicated by the directions of the arrows.




4) Which of the following equations is not valid?

- a.  $I_1 R_1 + I_2 R_2 - \epsilon_1 = 0$
- b.  $I_2 = I_1 + I_3$
- c.  $I_2 R_2 + I_3 R_3 - \epsilon_2 = 0$

5) What is the current  $I_1$ ?

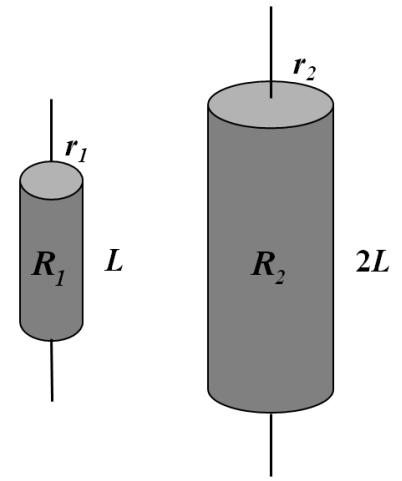- a.  $I_1 = 0.6 \text{ A}$
- b.  $I_1 = -0.6 \text{ A}$
- c.  $I_1 = 2.6 \text{ A}$
- d.  $I_1 = -7.8 \text{ A}$
- e.  $I_1 = -2.6 \text{ A}$

Two cylindrical resistors are made of the same material with known resistivity. Their lengths are  $L$  and  $2L$ , respectively, as shown. If the ratio of their resistance values is  $R_2/R_1 = 4$ , what is the ratio of their radii  $r_2/r_1$ ?




6)

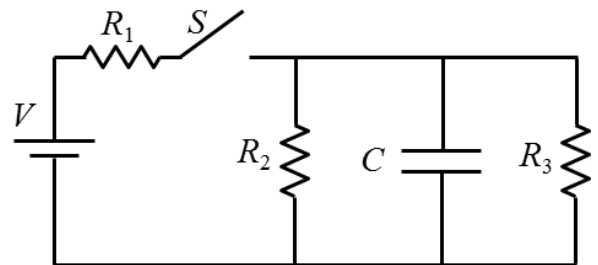- a.  $r_2/r_1 = 1.41$
- b.  $r_2/r_1 = 0.5$
- c.  $r_2/r_1 = 0.707$

The next two questions pertain to the situation described below.

A circuit is constructed with three resistors and one capacitor as shown. The values for the resistors are:  $R_1 = R_2 = R_3 = 6 \Omega$ . The capacitance is  $C = 50 \mu\text{F}$  and the battery voltage is  $V = 10 \text{ V}$ . The switch  $S$  is initially open.



7) What is the magnitude of the current through  $R_2$  immediately after the switch is closed?


- a. 0 A
- b. 1.67 A
- c. 3.33 A

8) After being closed for a long time the switch is opened again. What is the charge on the capacitor at a time  $200 \mu\text{s}$  after the switch is opened?

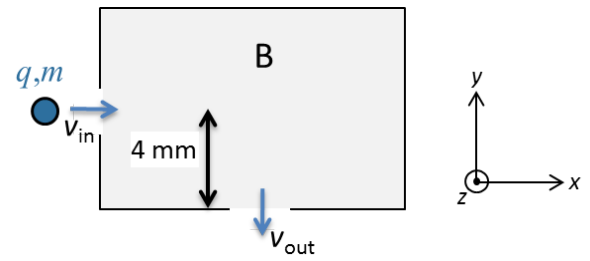- a.  $358 \mu\text{C}$
- b.  $132 \mu\text{C}$
- c.  $85.6 \mu\text{C}$
- d.  $119 \mu\text{C}$
- e.  $43.9 \mu\text{C}$

The next two questions pertain to the situation described below.

A particle of charge  $q = 20 \mu\text{C}$  moving with constant velocity  $v = 50 \text{ m/s } \hat{x}$  enters a region containing a constant magnetic field of magnitude 12 T. The particle leaves the field region with a velocity in the  $-y$  direction, having moved a vertical distance of 4 mm, as shown below.



9) In what direction could the magnetic field point in order to make the particle have the trajectory shown above?


- a. +y direction
- b. -z direction
- c. +z direction

10) Assume that the particle's initial velocity is perpendicular to the direction of the magnetic field, and that it moves only in the x-y plane. Find the mass of the particle.

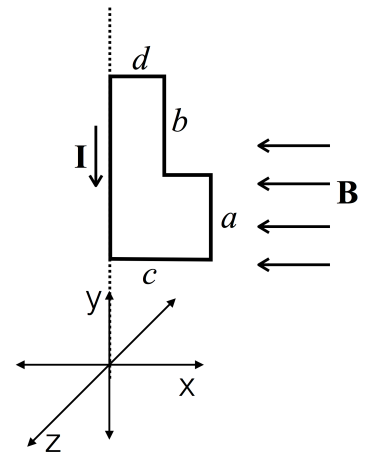- a.  $0.96 \times 10^{-8} \text{ kg}$
- b.  $3.84 \times 10^{-8} \text{ kg}$
- c.  $1.92 \times 10^{-8} \text{ kg}$
- d.  $9.11 \times 10^{-31} \text{ kg}$
- e.  $1.66 \times 10^{-27} \text{ kg}$

The next three questions pertain to the situation described below.

A wire loop is attached to an axis (dotted line in Figure) about which it can freely rotate. There is a constant magnetic field and a current flowing counter-clockwise in the wire as shown in the image. The length of the line segments are  $a$ ,  $b$ ,  $c$ , and  $d$  as indicated.




11) What is the net torque about the axis on the wire loop?

- a. 0
- b.  $IB(a + b + c + d)\hat{y}$
- c.  $-IB(ac + bd)\hat{y}$
- d.  $IB(ac + bd)\hat{y}$
- e.  $-IB(a + b + c + d)\hat{y}$

12) The loop is allowed to relax to its lowest energy position. What is the work done on the loop by the magnetic field?

- a.  $-IB(ac + bd)$
- b.  $IB(a + b + c + d)$
- c.  $-IB(a + b + c + d)$
- d.  $2IB(a + b + c + d)$
- e.  $IB(ac + bd)$

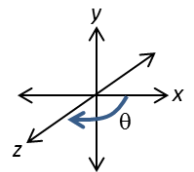
13) Which of these sketches best represents the potential energy as a function of the rotation of the wire loop? (The angle  $\theta = 0$  initially when the loop is in the x-y plane, and increases with clockwise rotation around the y-axis, as depicted at right).



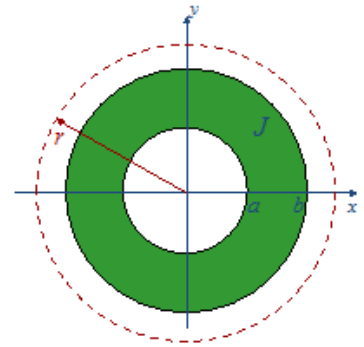- a.
- b.
- c.

The next two questions pertain to the situation described below.


A conducting cylinder is oriented along the z-axis as shown in the picture. The inner radius is  $a = 4$  cm, the outer radius is  $b = 8$  cm, and the current density through the cylinder is  $J = 30$  A/m<sup>2</sup>.



14) What is the magnitude of the magnetic field at a distance  $r = 12$  cm from the center of the cylinder?


- a.  $10.1 \times 10^{-5}$  T
- b.  $2.51 \times 10^{-7}$  T
- c.  $7.54 \times 10^{-5}$  T
- d.  $10.1 \times 10^{-7}$  T
- e.  $7.54 \times 10^{-7}$  T

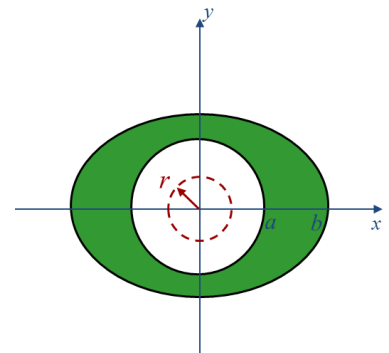15) Suppose that the cylinder is deformed as shown. The total current remains the same. Which of these statements about the interior of the cylinder (i.e.,  $r < a$ ) is FALSE?



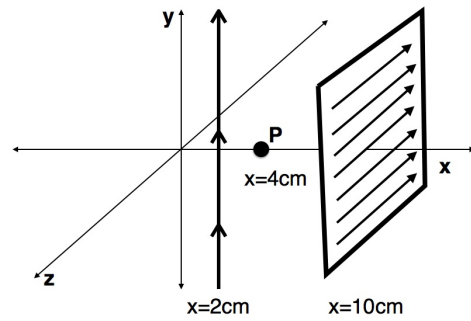- a. The integral  $\oint \vec{B} \cdot d\vec{\ell}$  over the dotted line to the right is equal to zero.
- b. The magnetic field is no longer zero for  $0 < r < a$ .
- c. Ampere's law can be used to determine the magnetic field.

A wire with current  $I_w = 1$  A in the y-direction is situated on the x-axis, a distance 2 cm from the origin. An infinite sheet of current with uniform current density  $J_s = 2$  A/m in the  $-z$  direction crosses the x-axis at a distance 10 cm from the origin. [Note that  $J \equiv nI$ , where  $n$  is the number of wires per unit length].





16) What is the value of the magnetic field at a point P on the x-axis 4 cm from the origin?

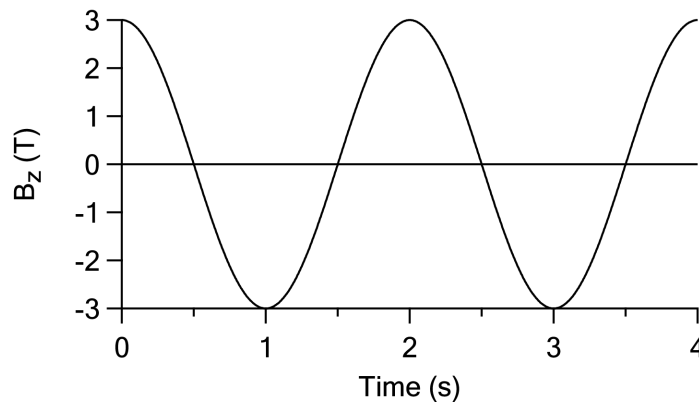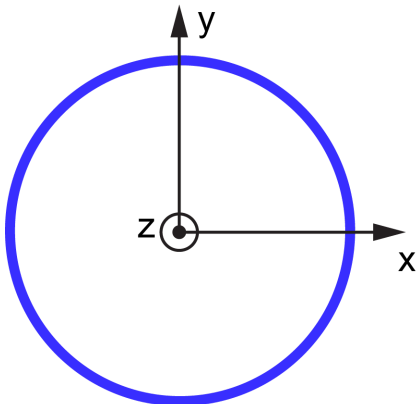- a.  $(-1 \times 10^{-6} \hat{y} + 1.26 \times 10^{-6} \hat{z})$  T
- b.  $(-2 \times 10^{-6} \hat{y} - 1 \times 10^{-7} \hat{z})$  T
- c.  $(1.26 \times 10^{-6} \hat{y} - 1 \times 10^{-5} \hat{z})$  T
- d.  $(-1.26 \times 10^{-6} \hat{y} + 1 \times 10^{-5} \hat{z})$  T
- e.  $(2 \times 10^{-6} \hat{y} + 1 \times 10^{-7} \hat{z})$  T

The next four questions pertain to the situation described below.

A circular conducting metal loop of radius 3 cm, lying in the xy-plane, is placed in a spatially uniform, but time-varying magnetic field  $B_z$ , which is oriented parallel to the z-direction (Note, the positive z-direction is pointed out of the page.) The loop has a resistance of  $5 \Omega$ . The magnetic field has the sinusoidal time dependence shown on the right:  $B_z(t) = B_0 \cos(2\pi ft)$ , where  $B_0 = 3$  T and  $f = 0.5$  Hz.



17) Which way is the current circulating in the loop at  $t = 0.5$  s?

- a. Clockwise
- b. There is no current at this time.
- c. Counter-clockwise

18) What is the magnetic flux through the loop at  $t = 2.0$  s?

- a.  $0.0054 \text{ T}\cdot\text{m}^2$
- b.  $0.00848 \text{ T}\cdot\text{m}^2$
- c.  $0.0027 \text{ T}\cdot\text{m}^2$

19) Which way is the current circulating in the loop at  $t = 1.0$  s?

- a. There is no current at this time.
- b. Clockwise
- c. Counter-clockwise


20) Calculate the magnitude of the circulating current at  $t = 0.8$  s. (Note: Make sure to either set your calculator to radians, or convert the phase into degrees.)

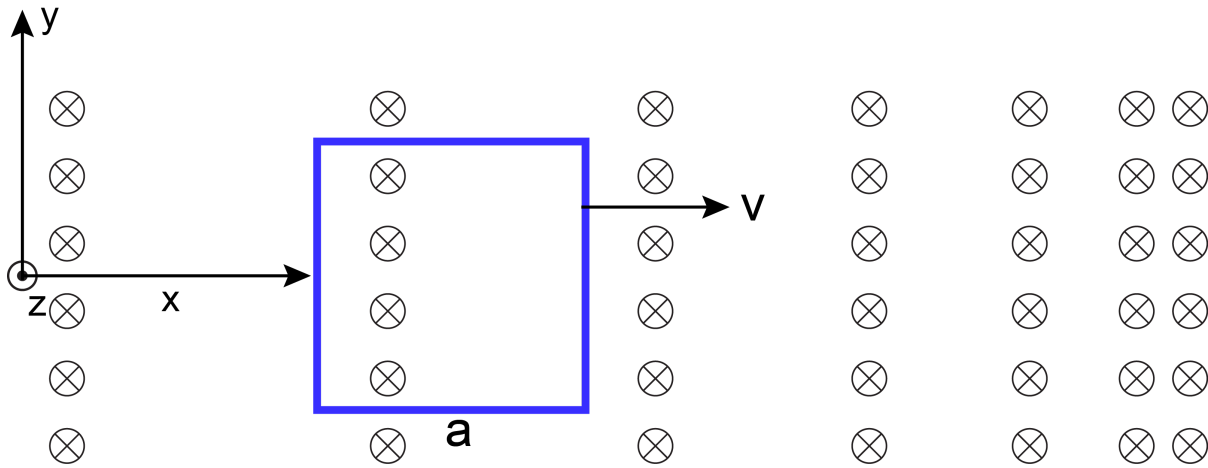- a.  $9.97 \times 10^{-4} \text{ A}$
- b.  $1.11 \text{ A}$
- c.  $0.00313 \text{ A}$
- d.  $0.0017 \text{ A}$
- e.  $0.00533 \text{ A}$



The next two questions pertain to the situation described below.

A square conducting metallic loop is moving in the x-direction through a region of space with a magnetic field pointing along the negative z-direction. The loop has dimension  $a = 20$  cm, and resistance of  $2 \Omega$ . The magnitude of the magnetic field increases linearly in the x-direction  $B_z = Ax$ , where  $A = 100$  T/m.



21) Calculate the flux through the loop when the left edge of the loop is located at  $x = 0.7$  m. Only consider the flux due to the external field.

- a.  $4 \text{ T}\cdot\text{m}^2$
- b.  $4.9 \text{ T}\cdot\text{m}^2$
- c.  $3.2 \text{ T}\cdot\text{m}^2$
- d.  $6.4 \text{ T}\cdot\text{m}^2$
- e.  $2.8 \text{ T}\cdot\text{m}^2$

22) Calculate the force on the loop when the left edge of the loop is located at  $x = 2.3$  m, and moving with velocity  $v = 3$  m/s.

- a.  $F = -24 \text{ N } \hat{x}$
- b.  $F = -1.2 \times 10^6 \text{ N } \hat{x}$
- c.  $F = -276 \text{ N } \hat{x}$
- d.  $F = -3170 \text{ N } \hat{x}$
- e.  $F = -48 \text{ N } \hat{x}$