

1 Single-cycle datapath control

The only difference between the instructions are that the `lwd` adds to registers together (`ALUSrc`) and writes back to register `$rd` (`RegDst`).


inst	PCSrc	ALUSrc	ALUOp	MemWrite	MemRead	MemToReg	RegDst	RegWrite
<code>lw</code>	0	1	ADD	0	1	1	0	1
<code>lwd</code>	0	0	ADD	0	1	1	1	1

2 Single-cycle datapath modifications


Implementing the `jal` requires a number of datapath additions. First a 26-bit immediate needs to be extracted and shifted 2 bits to the left to create a 28-bit number. To create a 32-bit PC, the top 4 bits of the current PC are merged in. The `PCSrc` multiplexor needs to be extended with a third input.

Second, the return address (`PC+4`) needs to be routed to the `Write data` port of the register file. This can be done by extending the `MemToReg` mux.

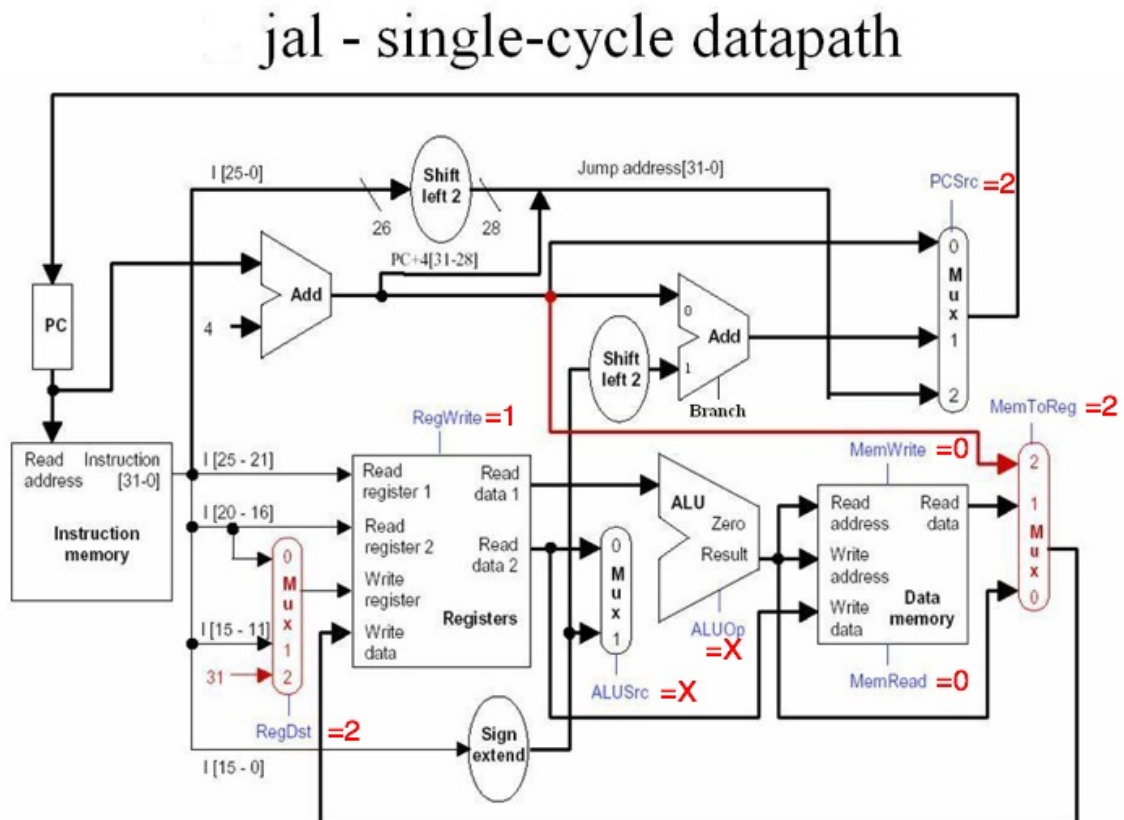Finally, the return address needs to be written to register 31, but there is no guarantee that the `rs`, `rt`, or `rd` fields will hold the value 31, so we have to have a “hard-coded” 31 and extend the `RegDst` mux to permit its selection.



 1. **Implementing jr:** Expand the PCsrc mux to take a third input (thus, it becomes a two-bit control signal). The third input will be from the Read data 1 line – see the diagram:



2. **Implementing lui:** Insert a “Shift Left by 16” unit which takes the 16-bit immediate as its input (it doesn’t matter whether this is before or after the “Sign Extend” unit). The resulting 32-bit signal is routed to the 3rd input of an extended MemToReg multiplexor.

