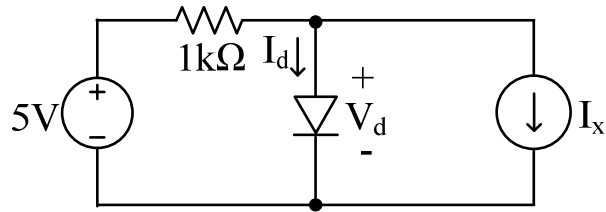


SP'11

Problem 1 (20 points)

The diode in the following circuit has a value for V_{ON} of 0.7 V.



(a) (10 pts) Determine I_d and V_d for $I_x = 7$ mA.

$$V_d = \boxed{-2} \text{ V}$$

$$I_d = \boxed{0} \text{ mA}$$

(b) (10 pts) Determine I_d and V_d for $I_x = 4$ mA.

$$V_d = \boxed{0.7} \text{ V}$$

$$I_d = \boxed{0.3} \text{ mA}$$

Problem 2 (20 points)

Multiple choice problem. Mark the box adjacent to the answer(s) that are correct.

(a) (5 pts) Mark all correct expressions for the F given in the truth table below.

X	Y	Z	F		
0	0	0	0	<input type="checkbox"/>	$F = \overline{X}Y\overline{Z} + \overline{X}YZ + X\overline{Y}Z + XYZ$
0	0	1	0	<input checked="" type="checkbox"/>	$F = \overline{X}Y\overline{Z} + \overline{X}YZ + XY\overline{Z} + XYZ$
0	1	0	1	<input type="checkbox"/>	$F = \overline{X}Y\overline{Z} + X\overline{Y}Z + XY\overline{Z} + XYZ$
0	1	1	1	<input checked="" type="checkbox"/>	$F = \overline{X}Y + YZ$
1	0	0	0	<input checked="" type="checkbox"/>	$F = Y\overline{Z} + YZ$
1	0	1	0	<input checked="" type="checkbox"/>	$F = \overline{X}Y + XY$
1	1	0	1	<input type="checkbox"/>	$F = X$
1	1	1	1	<input checked="" type="checkbox"/>	$F = Y$
				<input type="checkbox"/>	$F = Z$


(b) (5 pts) Determine the sum (expressed in binary) of $(101)_2$ and $(011)_2$.

- | | | |
|---|----------------------------------|----------------------------------|
| <input type="checkbox"/> 1 0 0 | <input type="checkbox"/> 1 1 0 | <input type="checkbox"/> 0 1 1 |
| <input checked="" type="checkbox"/> 1 0 0 0 | <input type="checkbox"/> 1 1 0 0 | <input type="checkbox"/> 1 1 1 0 |

(c) (5 pts) Considering X as the only input, check all of the following that can be used to yield \overline{X} .

- | | | |
|--|---|--|
| <input type="checkbox"/> XNOR gate | <input checked="" type="checkbox"/> NAND gate | <input type="checkbox"/> AND and OR gates |
| <input checked="" type="checkbox"/> OR and NOT gates | <input type="checkbox"/> AND and XOR gates | <input type="checkbox"/> None of the above |

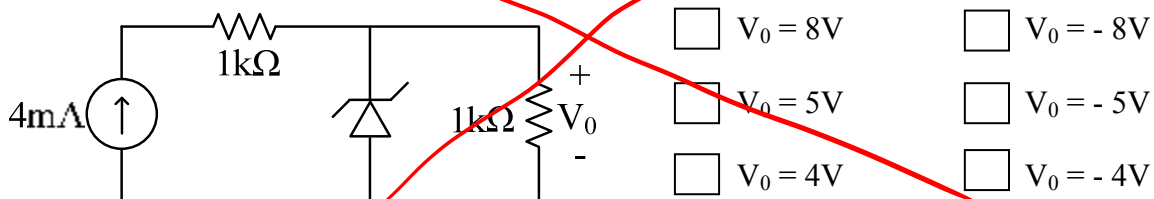
(d) (5 pts) Determine V_0 if the zener diode in the following circuit has a zener voltage, $V_Z = 5$ V.



- | | |
|-------------------------------------|--------------------------------------|
| <input type="checkbox"/> $V_0 = 8V$ | <input type="checkbox"/> $V_0 = -8V$ |
| <input type="checkbox"/> $V_0 = 5V$ | <input type="checkbox"/> $V_0 = -5V$ |
| <input type="checkbox"/> $V_0 = 4V$ | <input type="checkbox"/> $V_0 = -4V$ |

zener diodes no longer covered -

Problem 3 (20 points)

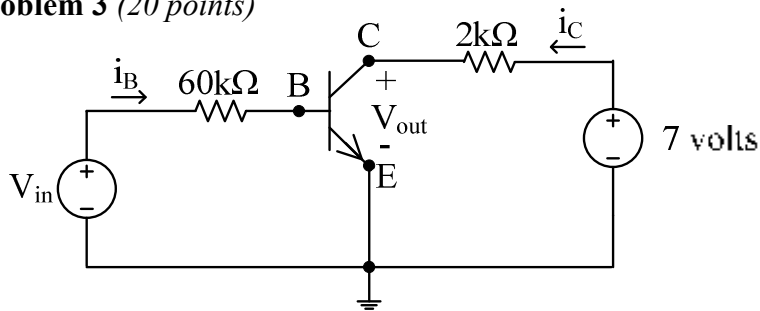

BJT parameters
 $V_{BEON} = 0.5\text{volts}$
 $V_{CESAT} = 0.3\text{volts}$
 $\beta = 100$

- (a) (14 pts) Fill out the table below for the value of V_{in} provided. For each part, show all of your work to justify your results.

V_{in}	i_B (μA)	i_C (mA)	V_{OUT} (volts)	BJT state
0.2	0	0	7	OFF
2	25	2.5	2	active
3	41.67	3.35	0.3	saturated



use space
for work

$V_{in} = 0.2\text{volts}$


$V_{in} = 2\text{volts}$

$V_{in} = 3\text{volts}$

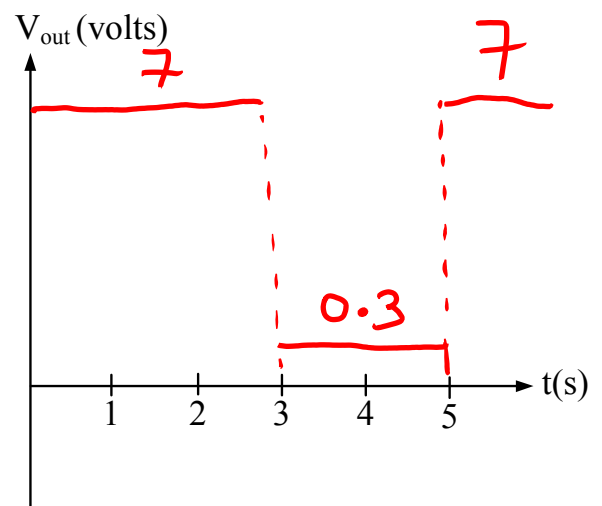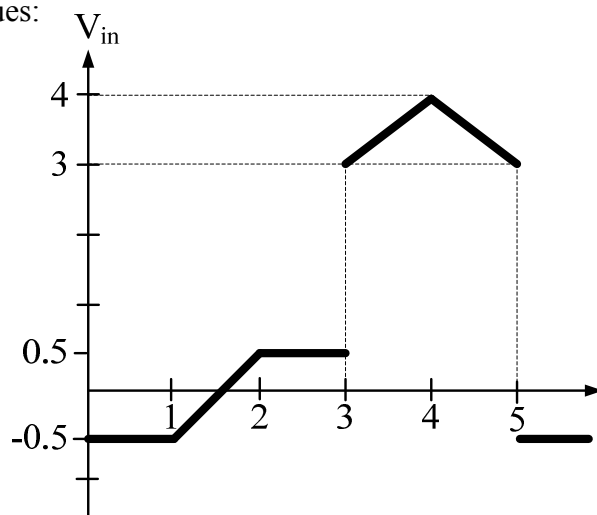- (b) (6 pts) For the given graph for V_{in} , draw the graph for V_{OUT} . Show work; label relevant values:



Problem 4 (20 points)

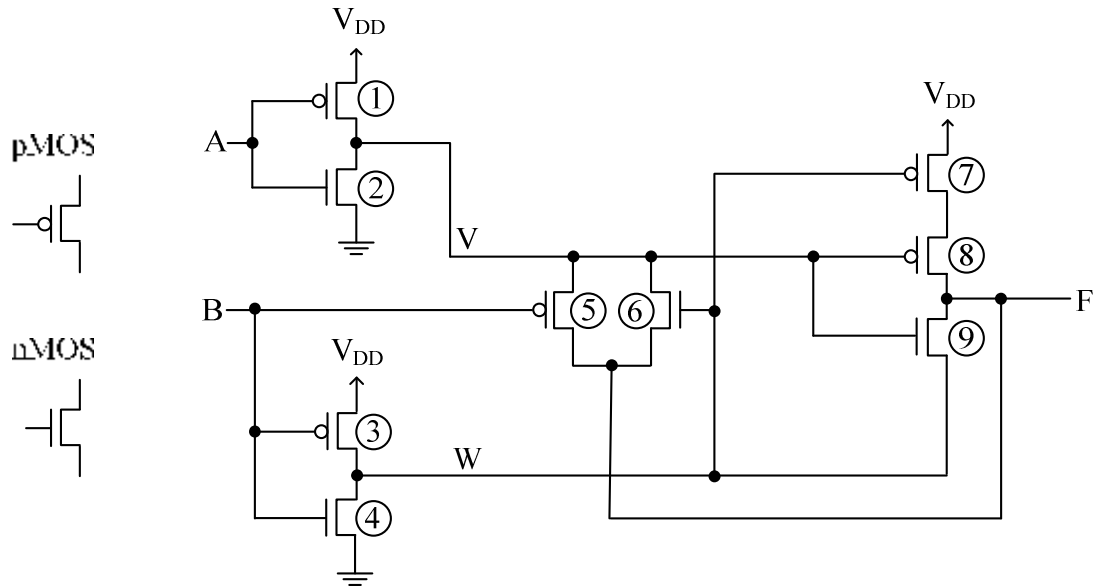

In this circuit, A and B are the inputs, F is the output. There are 9 transistors, labeled 1-9.

(a) (4 pts) Write the values for V and W in the table below.

A B	V W	pMOS Low	nMOS High
0 0	1 1	1 3 5	6 9
0 1	1 0	1 7	4 9
1 0	0 1	3 5 8	2 6
1 1	0 0	7 8	2 4


(b) (8 pts) In the right side of the table above, list all the pMOS transistors that have low values at their control input, and all the nMOS transistors that have high values at their control input. (Write the number of each transistor, they are labeled in the circuit.)

(c) (8 pts) The circuit implements an exclusive-nor gate. When $F=1$, F is connected to V_{DD} by one of two paths: either through pMOS transistors 1 and 5, or pMOS transistors 7 and 8. When $F=0$, F is connected to ground by one of two paths: either through nMOS transistors 2 and 6, or nMOS transistors 4 and 9. Complete the truth table below (fill in F), and also for each line on the truth table, put a checkmark in the column labeled with the two transistors that connect F to V_{DD} or ground.

A B	F	1 & 5	7 & 8	2 & 6	4 & 9
0 0	1	✓			
0 1	0				✓
1 0	0			✓	
1 1	1		✓		

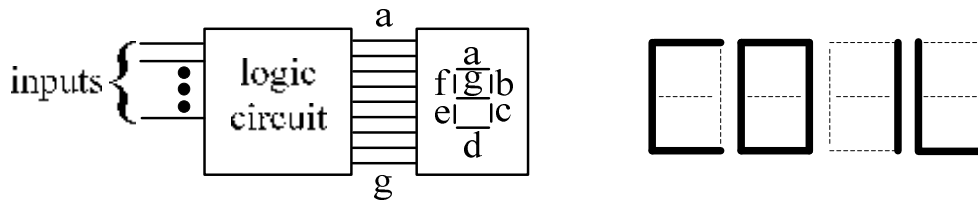Problem 5 (20 points)

In this problem, you will design a logic circuit that allows to eventually display $\square\square\square\square$.



(a) (2 pts) How many input lines are needed for the design? Justify answer.

2

(b) (4 pts) Fill out the truth tables below for your circuit. Make sure to name and include in the first column as many inputs as you claimed in (a).

inputs		outputs						
x	y	a	b	c	d	e	f	g
0	0	1	0	0	1	1	1	0
0	1	1	1	1	1	1	1	0
1	0	0	1	1	0	0	0	0
1	1	0	0	0	1	1	1	0


(c) (3 pts) From your table in (b), considering the design of the entire circuit (for all seven outputs), how many different circuits would you really need to design? Justify your answer.

4

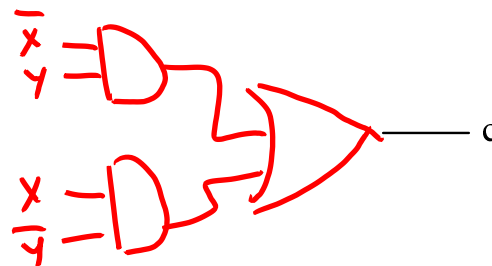(d) (7 pts) From your table in (b), give the canonical SOP for outputs c and d. Use input names you defined in part (b). Draw the non optimized AND OR circuit for output c below.

$$c = \bar{x}y + x\bar{y}$$

$$d = \bar{x}\bar{y} + \bar{x}y + x\bar{y}$$



(e) (4 pts) Assuming complemented inputs are available, suggest an implementation for c and d using at most one gate each. Give the corresponding Boolean expressions. Use input names you defined in part (b).

$$c = x \oplus y$$

$$d = \bar{x} + y$$