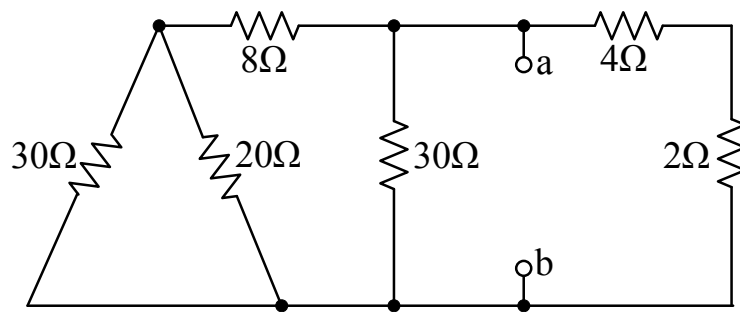



Problem 1 (9 points)

Determine the equivalent resistance between nodes a and b in the circuit below. **Show your work.**




$R_{ab} =$

Show your work.

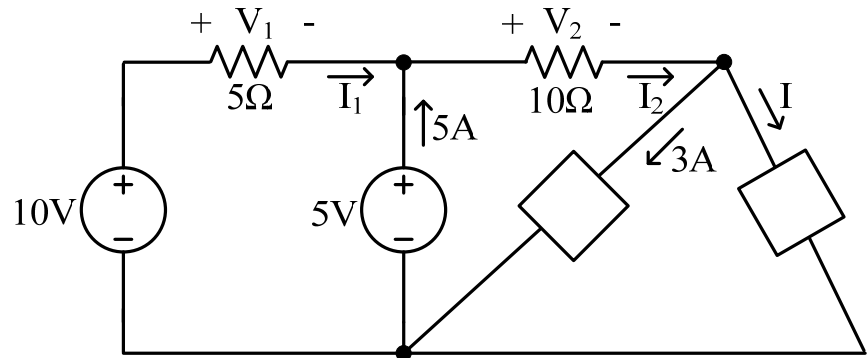

I =


We model a real voltmeter by an ideal voltmeter in parallel with a $3\text{ M}\Omega$ resistor. We wish to use the real voltmeter to measure voltages as large as 400 V by attaching a resistor R_0 in series with the real voltmeter, and scaling the reading. Use the Voltage Divider Rule to determine the minimum value of R_0 so that the voltage across the voltmeter remains less than or equal to 60 V , i.e., $V_m \leq 60\text{ V}$. **Show your work.**

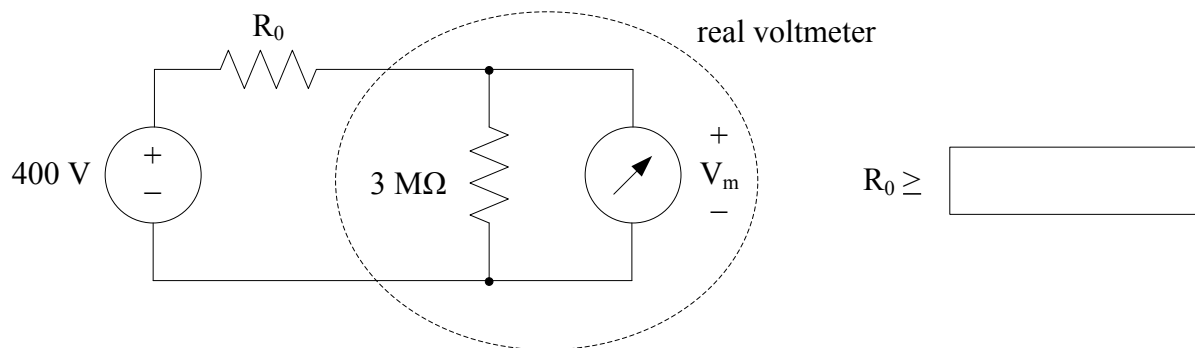

Problem 4 (20 points)


For all questions below, check the one correct answer.

(a) (3 pts)

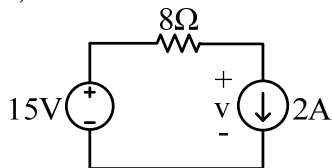


- ☐ $v < 0$
☐ $v = 0$
☐ $v > 0$

(b) (3 pts)

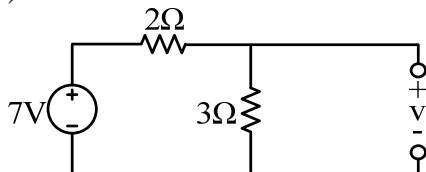


- ☐ $v = 7V$
☐ $v = 0$
☐ none of the above

(c) (3 pts)

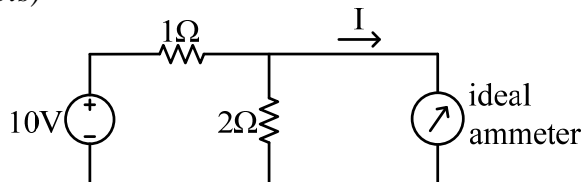

- ☐ $I = 20A$
☐ $I = 10A$
☐ none of the above

(d) (3 pts)

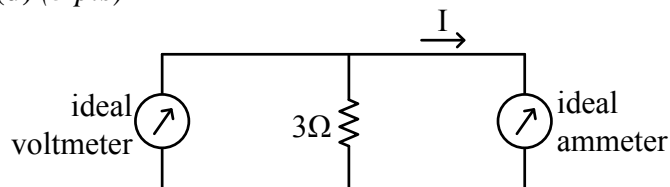

- ☐ $I < 0$
☐ $I = 0$
☐ $I > 0$

(e) (4 pts) A strand of copper wire whose circular diameter is 0.5 mm has a resistance of 0.9Ω . A copper wire of the same length whose diameter is 0.3 mm has a resistance of


- ☐ 0.324Ω ☐ 0.54Ω ☐ 1.5Ω ☐ 2.5Ω

(f) (4 pts) A voltage of $V_0(t)$ and current $I_0(t)$ at a resistor R_0 vary with time, and their average values are V_{avg} and I_{avg} . They are not in SRS. Which statement is true about the average power at resistor R_0 ?

- ☐ the resistor is a load ☐ the magnitude of the power is $|V_{avg} \times I_{avg}|$
☐ the resistor is a source ☐ none of these

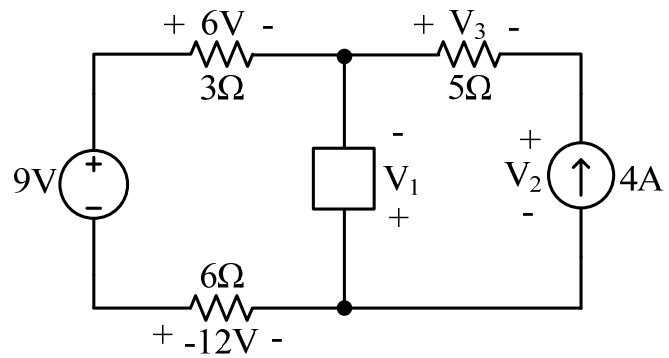Problem 5 (16 points)

Use the following circuit for this problem.



(a) (8 pts) Write a KVL equation involving V_1 as the only unknown and then solve for V_1 .


$$V_1 =$$

(b) (8 pts) Write a KVL equation involving V_2 as the only unknown and then solve for V_2 .

$$V_2 =$$

Problem 6 (15 points)

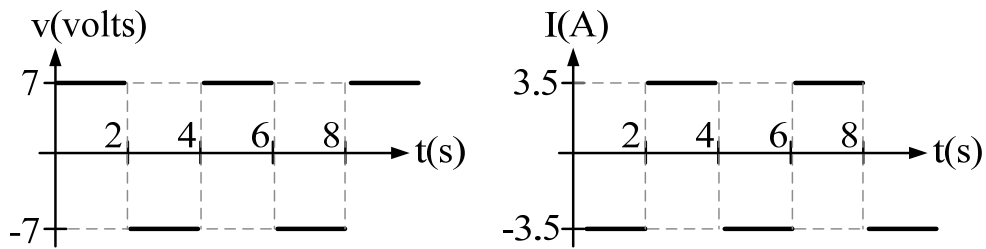(a) (10 pts) Assume the two following periodic time-varying signals:



(i) (2 pts) What is the frequency for the signals?

$f =$

(ii) (3pts) Compute V_{RMS} . **Show work.**

$V_{\text{RMS}} =$

(iii) (5 pts) Compute the time-averaged power over one period of time. **Show and explain work.**

$P_{\text{average}} =$



(b) (5 pts) Prove or disprove that, if $V(t) = -RI(t)$ for any t , then $P_{\text{average}} = -V_{\text{RMS}} \times I_{\text{RMS}}$.

☐ Proved

☐ Disproved

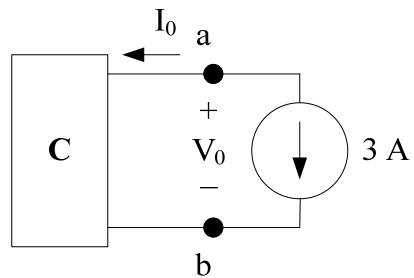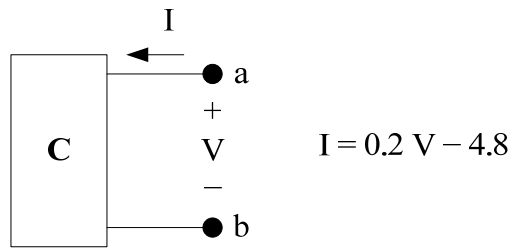Problem 7 (20 points)


A component **C** is defined by the I-V characteristic on the left below; the current I is in amps, the voltage V is in volts.



(a) (4 pts) Component **C** is connected to an ideal current source shown on the right above. Determine V_0 .

$V_0 =$

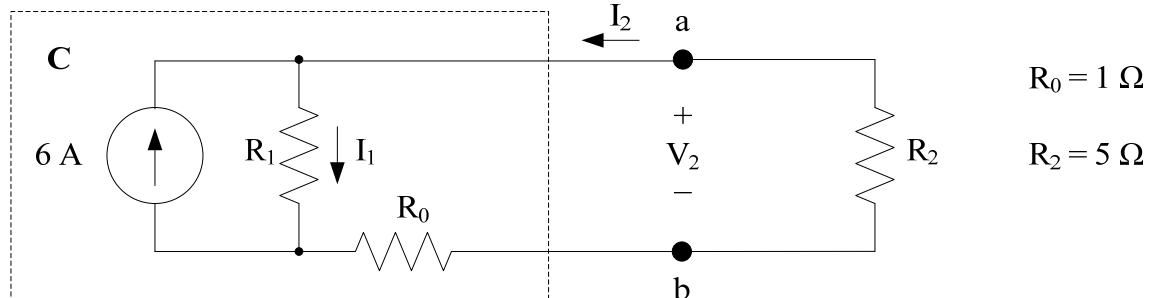(b) Suppose **C** has the structure shown on the left below, and **C** is connected to a resistance R_2 . The values of R_0 and R_2 are given. By KCL, $I_1 = I_2 + 6$.



(i) (8 pts) Show that $I_1 = 3.6$ A. Name the equations that you use.

(ii) (8 pts) Using (i) and the Current Divider Rule, determine the resistance R_1 . **Show your reasoning.**

$R_1 =$