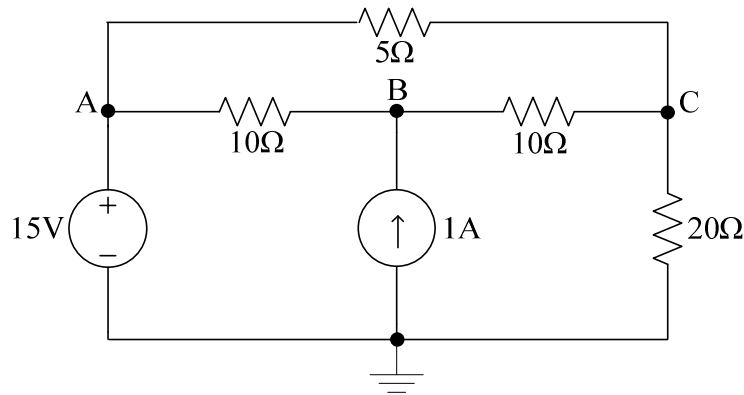


SP'11

Problem 1 (20 points)

Derive the three equations involving unknown voltages V_A , V_B and V_C that would result from applying the node voltage method to the following circuit.



Derive the appropriate equation for each node and enter the coefficients for each equation below.

Node A:

$$\boxed{} V_A + \boxed{} V_B + \boxed{} V_C = \boxed{}$$

Node B:

$$\boxed{} V_A + \boxed{} V_B + \boxed{} V_C = \boxed{}$$


Node C:

$$\boxed{} V_A + \boxed{} V_B + \boxed{} V_C = \boxed{}$$

Problem 2 (20 points)

Multiple Choice - no need to show work.

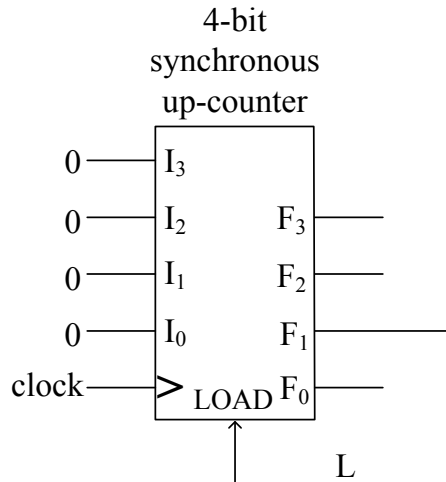
(a) (5 pts) What is the duty cycle of the signal “L”?



Pick one:

- | | |
|--------------------------------|------------------------------|
| <input type="checkbox"/> 100% | <input type="checkbox"/> 20% |
| <input type="checkbox"/> 50% | <input type="checkbox"/> 10% |
| <input type="checkbox"/> 33.3% | <input type="checkbox"/> 0% |
| <input type="checkbox"/> 25% | |


(b) (5 pts)

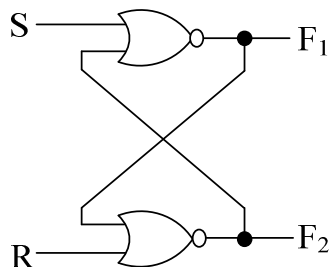

In this circuit, what is F_1 and F_2 while $S = 1$ and $R = 1$?

- | | |
|--------------------------------------------------|---------------------------------------------|
| <input type="checkbox"/> $F_1 = 0, F_2 = 0$ | <input type="checkbox"/> $F_1 = 1, F_2 = 0$ |
| <input type="checkbox"/> $F_1 = 0, F_2 = 1$ | <input type="checkbox"/> $F_1 = 1, F_2 = 1$ |
| <input type="checkbox"/> No way to know for sure | |

(c) (5 pts)

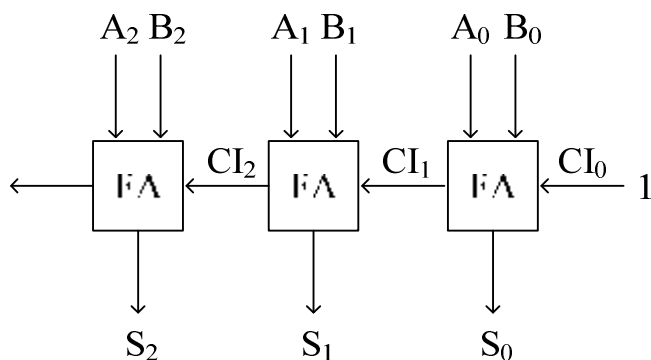

If $A = 3$, $B = 6$, $CI_0 = 1$, then

- | | |
|----------------------------------|----------------------------------|
| <input type="checkbox"/> $S = 0$ | <input type="checkbox"/> $S = 4$ |
| <input type="checkbox"/> $S = 1$ | <input type="checkbox"/> $S = 5$ |
| <input type="checkbox"/> $S = 2$ | <input type="checkbox"/> $S = 6$ |
| <input type="checkbox"/> $S = 3$ | <input type="checkbox"/> $S = 7$ |





A is $A_2 A_1 A_0$, B is $B_2 B_1 B_0$, S is $S_2 S_1 S_0$

(d) (5 pts) The following is a Morse Code message with prefixes (time gap between letters) removed. Mark all the possible data that might be encoded:

— • — •


<input type="checkbox"/> TEN	<input type="checkbox"/> KE	<input type="checkbox"/> NN
<input type="checkbox"/> C	<input type="checkbox"/> TETE	<input type="checkbox"/> NTE
<input type="checkbox"/> TAE	<input type="checkbox"/> TR	<input type="checkbox"/> SOS

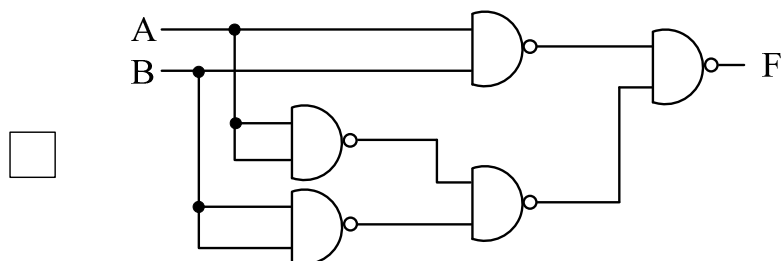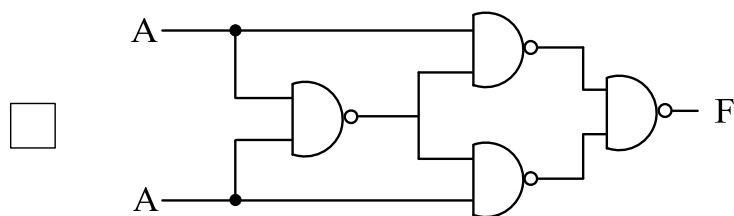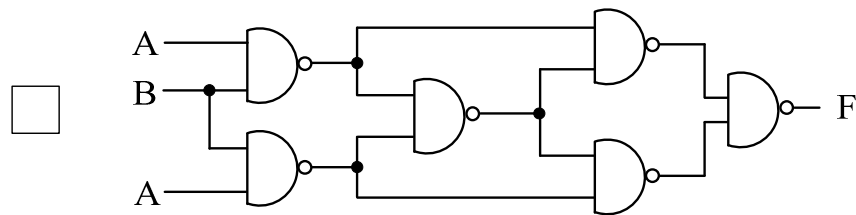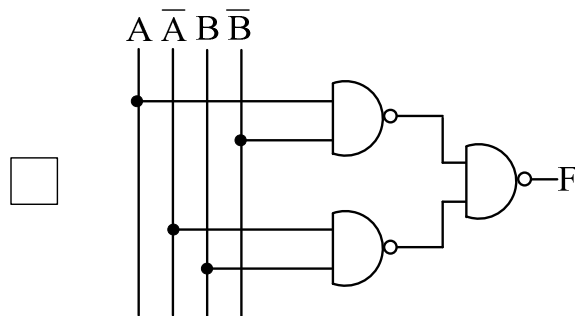(e) (5 pts) Which of the following circuits correctly implement XOR, i.e. $F = A \oplus B$? (more than one circuit may work)



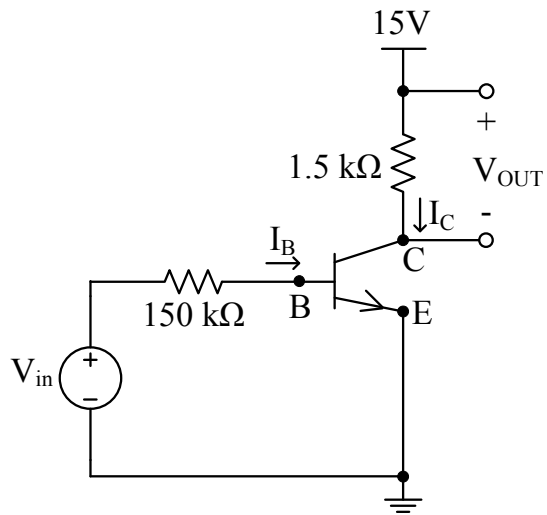Problem 3 (20 points)

The transistor in the following circuit has $\beta = 85$, $V_{BEON} = 0.7\text{ V}$, and $V_{CESAT} = 0.2\text{ V}$. **Show work.**



(a) (4 pts) Determine $I_{C\text{MAX}}$. (note labeling of V_{OUT})

$$I_{C\text{MAX}} = \boxed{} \text{ mA}$$

(b) (1 pt) Check the correct answer:


☐ $V_{\text{out}} = V_{\text{CE}}$

☐ $V_{\text{out}} \neq V_{\text{CE}}$

(c) (15 pts) Provide the missing values in the following table.

V_{IN} (V)	I_{B} (μA)	I_{C} (mA)	V_{OUT} (V)
2			
4			
20			

Problem 4 (20 points)

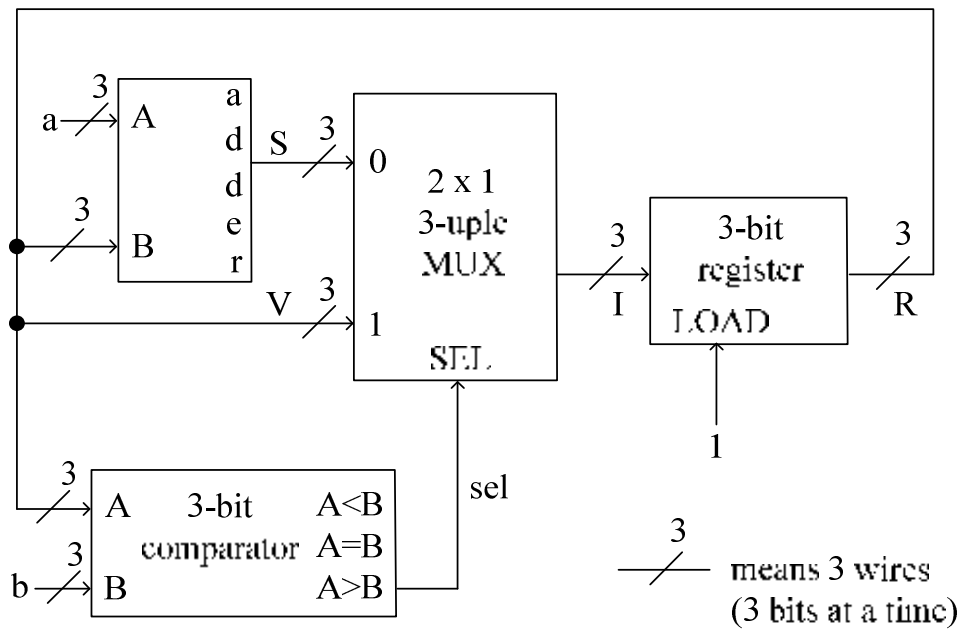


Notice that all binary numbers, except “sel” and “LOAD”, are coded on 3 bits.

Provide all values in decimal in the table below for consecutive clock pulses.

clock pulse	0	1	2	3
R	3			
a	1	5	3	2
b	5	2	6	7
S				
sel				
I				

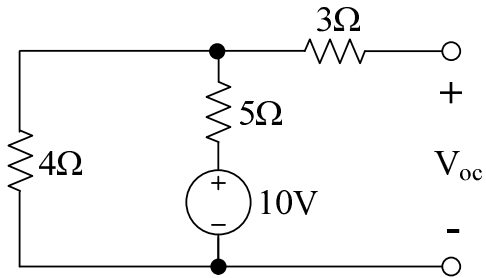Problem 5 (10 points)


Find V_{oc} in the following circuit using the voltage divider rule (VDR). You must show work and use VDR for credit.



$$V_{oc} = \boxed{} \text{ V}$$

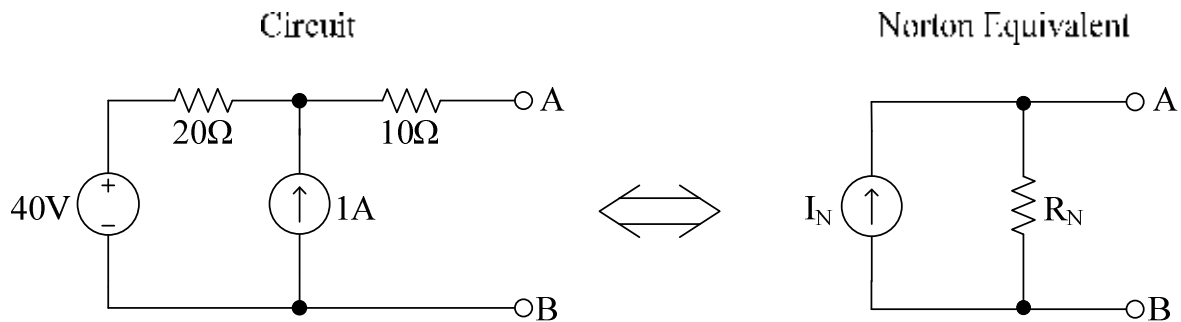Problem 6 (10 points)

Find the values (I_N and R_N) for the Norton equivalent for the circuit below.




$$I_N = \boxed{} \text{ A} \quad R_N = \boxed{} \Omega$$

Zener diodes no longer covered -

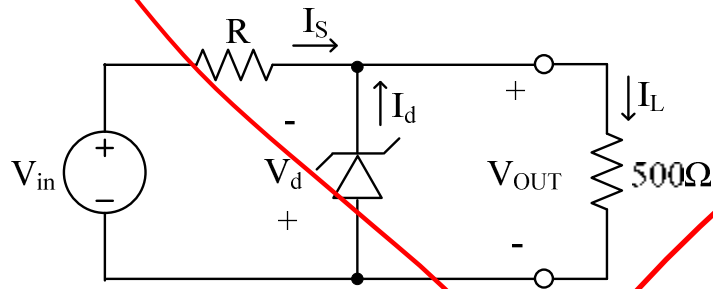Problem 7 (20 points)

The Zener diode in the following circuit has a value for V_Z of 5 V.



(a) (5 pts) Determine the value of I_L if the diode is in breakdown.

$$I_L = \boxed{} \text{ mA}$$

(b) (5 pts) Determine the value of I_L if the diode is off and $I_S = 3 \text{ mA}$.


$$I_L = \boxed{} \text{ mA}$$

(c) (10 pts) If V_{in} fluctuates between a low of 10 V and a high of 12 V, determine the maximum value for R that will allow the Zener diode to regulate the voltage V_{out} to the desired value of 5 V.

$$R_{MAX} = \boxed{} \Omega$$

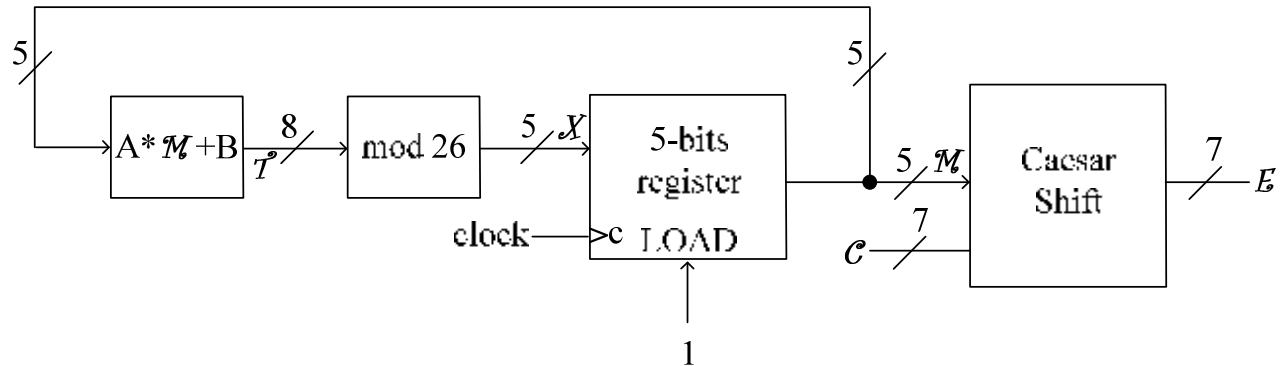Problem 8 (25 points)

The circuit “ENCRYPT” below encrypts an ASCII message by performing a pseudo-random sequence of Caesar Shifts on each character \mathcal{C} of a message; each clock pulse, one character gets treated (i.e. it is shifted by \mathcal{M} positions to the right to produce another letter of the alphabet).



- (a) (6 pts) Find the encrypted letter E for the two following independent cases (one example is given). The shift \mathcal{M} is given in decimal for convenience.

\mathcal{M}	1	15	10
\mathcal{C} (letter)	F	H	T
\mathcal{C} (ascii)	1000110		
E (letter)	G		
E (ascii)	1000111		

- (b) (9 pts) The two circuit portions on the left ($A*\mathcal{M}+B$ and mod 26) implement the pseudo-random generator:


$$\mathcal{X} = \mathcal{T} \bmod 26 \quad \text{with } \mathcal{T} = 7 * \mathcal{M} + 5$$

The message “MANDY” is encrypted by the circuit “ENCRYPT” one character at a time. Provide all numbers in decimal (\mathcal{M} , \mathcal{T} , \mathcal{X}) for each clock pulse, and the resulting encrypted message (one character E each clock pulse):

clock pulse	\mathcal{M}	\mathcal{C}	E	\mathcal{T}	\mathcal{X}
0	21	M			
1		A			
2		N			
3		D			
4		Y			

Problem 8 cont'd

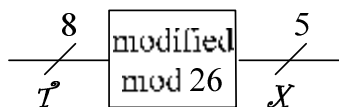(c) (10 pts) You will now implement a modified mod 26 circuit.



It still produces a number X between 0 and 25, but it is generated by the process:

- $\mathcal{Y} = T \bmod 32$ (\mathcal{Y} is coded on 5 bits)
- If $\mathcal{Y} \leq 25$, then $X = \mathcal{Y}$
If $26 \leq \mathcal{Y} \leq 31$, then $X = 31 - \mathcal{Y}$

To give you an idea on how to design this circuit, do the following examples:

Example 1: (give binary numbers)

$T = 44_{10}$

$\mathcal{Y} = 12_{10}$

$X = 12_{10}$

Example 2: (give binary numbers)

$T = 91_{10}$

$\mathcal{Y} = 27_{10}$

$X = 4_{10}$

Draw the two missing circuits (use wires, AND, OR, NOT gates only), and fill the two missing MUX inputs. **Justify your design!**

