
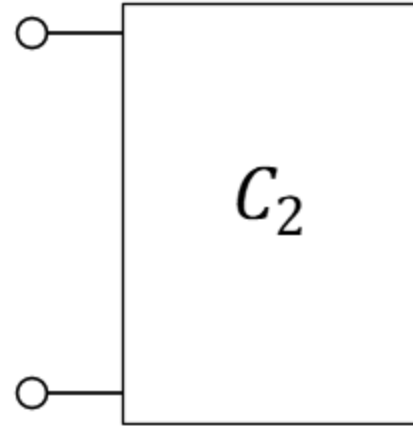




Lecture 11: IV Characteristics

- Measuring I-V Characteristics of Circuits
- Calculating I-V Characteristics of Linear Circuits
- Operating (I,V) point when Sub-circuits are Connected
- Power and the I-V Characteristics

What's in the Box?





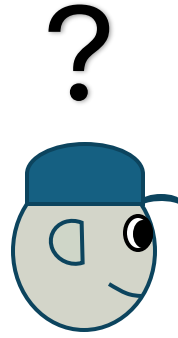


Can We Uncover the IV Behavior?

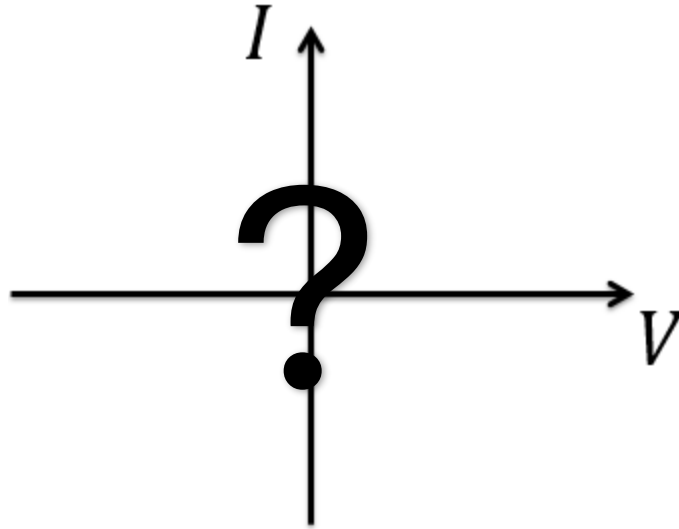
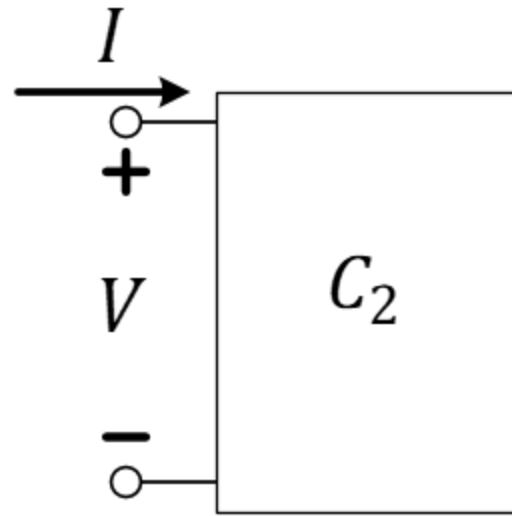


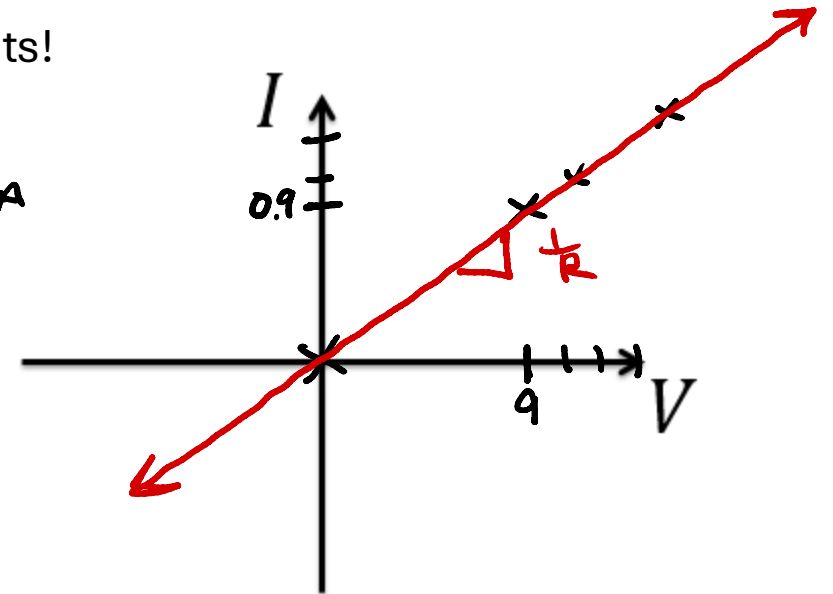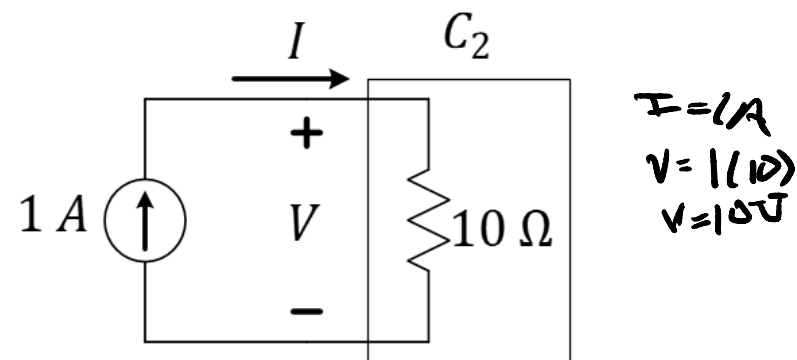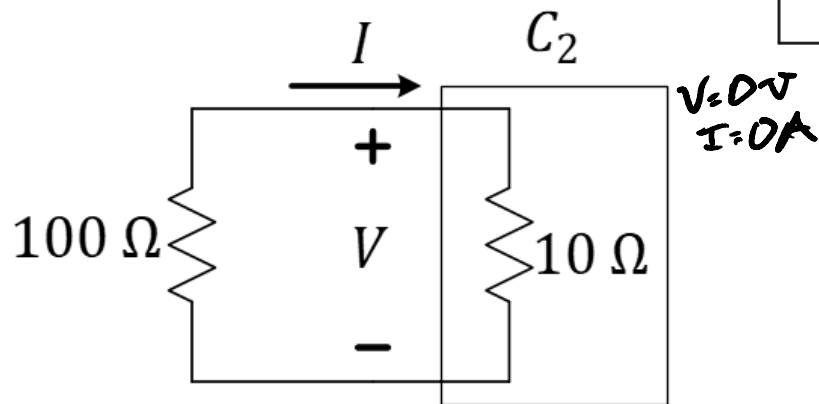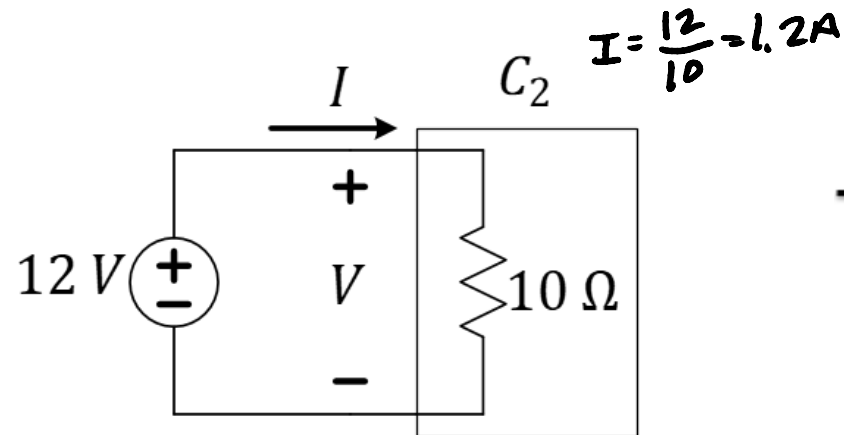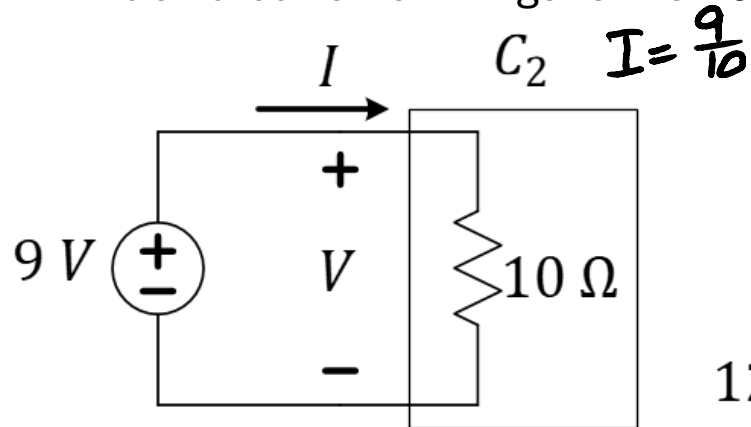Example: C2 is a $10\ \Omega$ Resistor

Attach a bunch of things to the $10\ \Omega$ and take current-voltage data points!




Measuring IV Data in the Lab

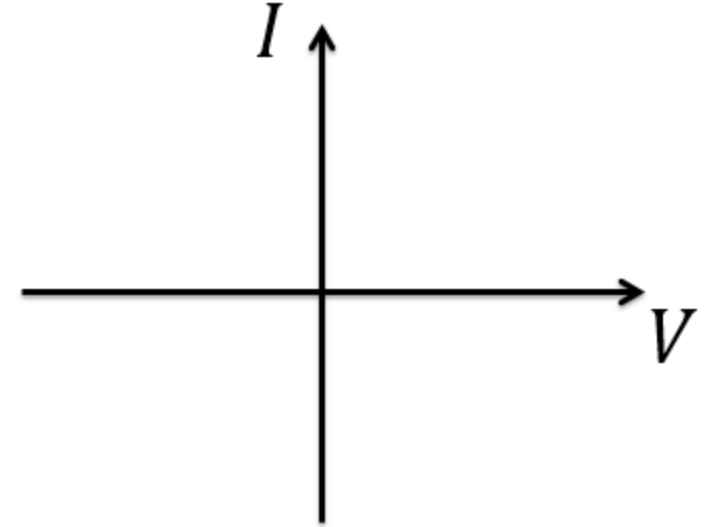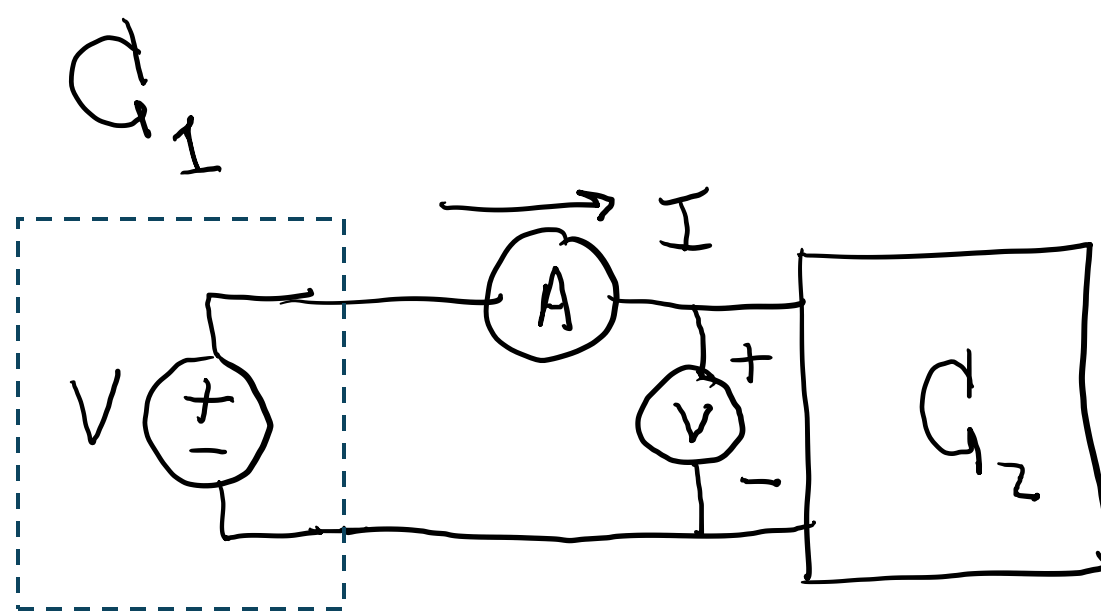

Q: What is the voltage drop across an ideal current-meter (ammeter)?

- A. 0 V
- B. 1 V
- C. Depends on the ammeter's internal resistance


Measuring IV Data

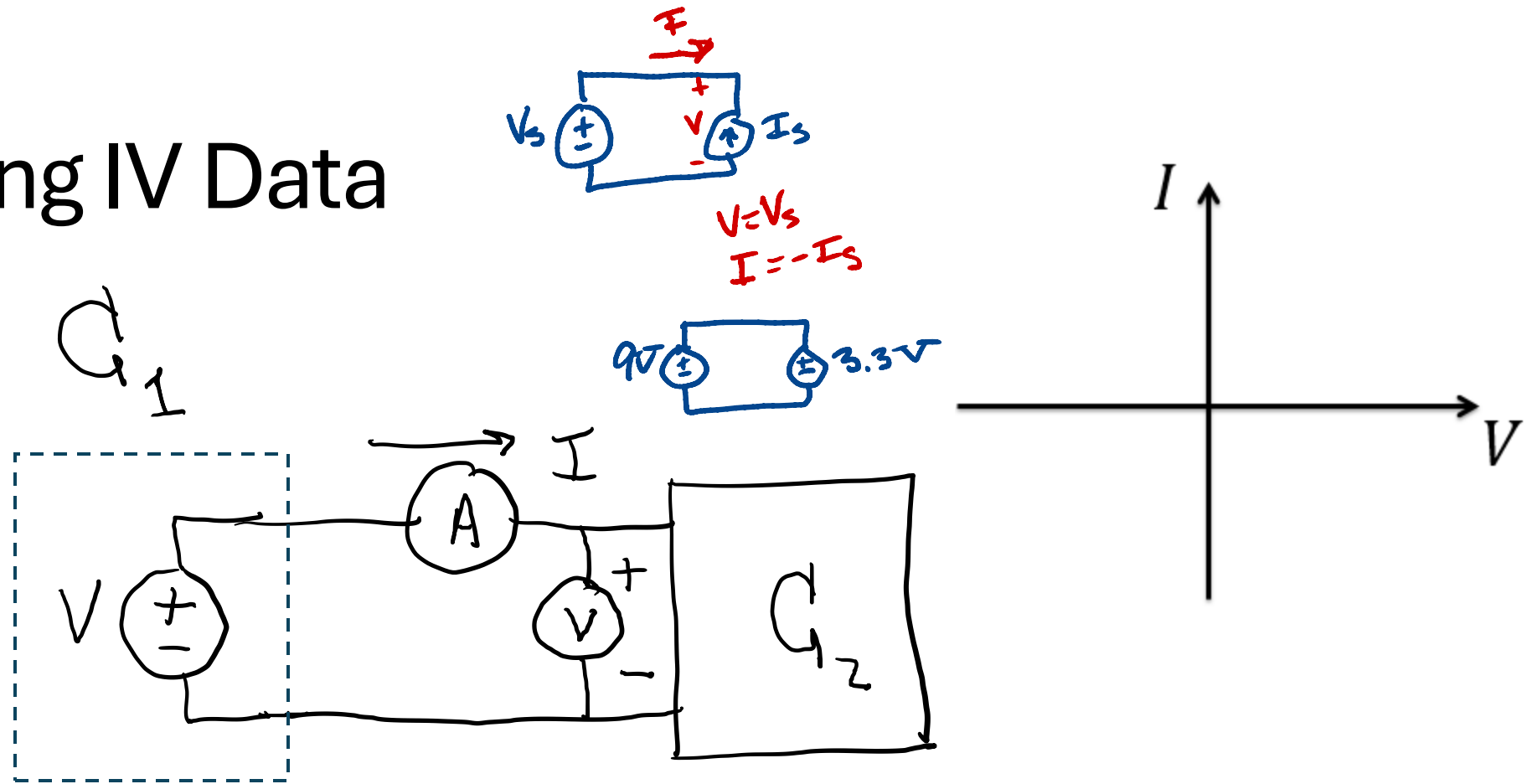

Q: When would this technique be a bad idea?

- A. When C_2 is another voltage source
- B. When C_2 is a current source
- C. When C_2 is a resistor


Measuring IV Data

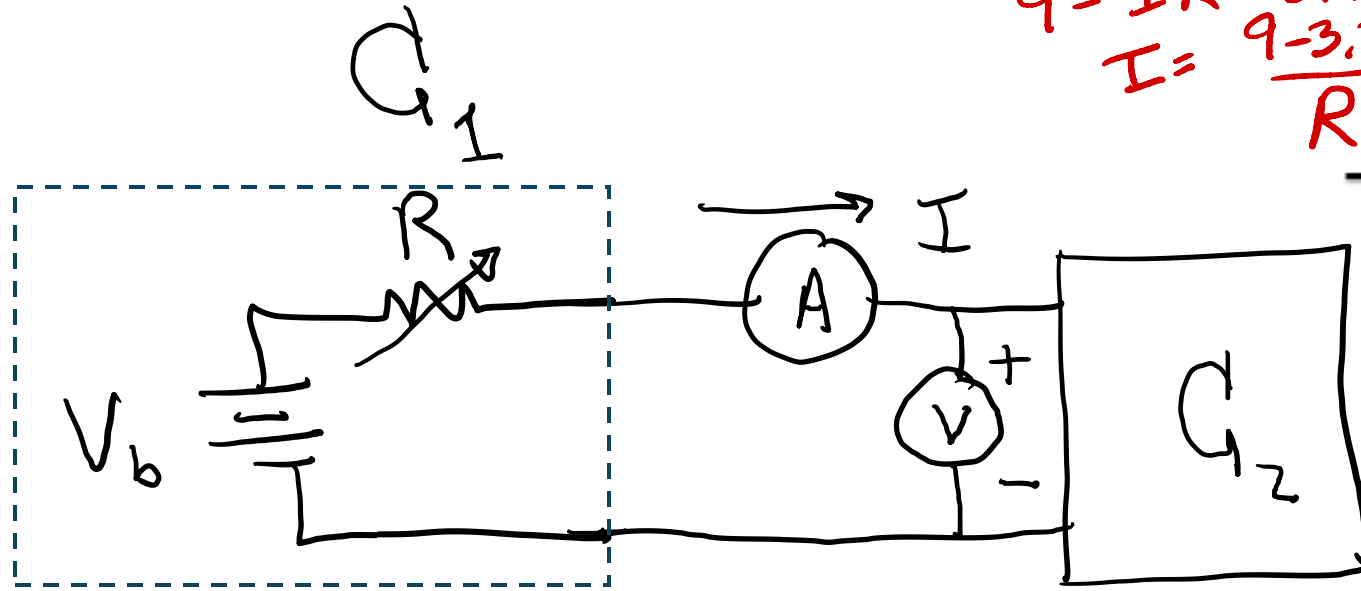

A small circuit diagram shows a 9V battery connected to a resistor R and a 3.3V source. The current I is indicated. Below the diagram, the following equations are written:

$$9 - IR - 3.3 = 0$$

$$I = \frac{9 - 3.3}{R}$$






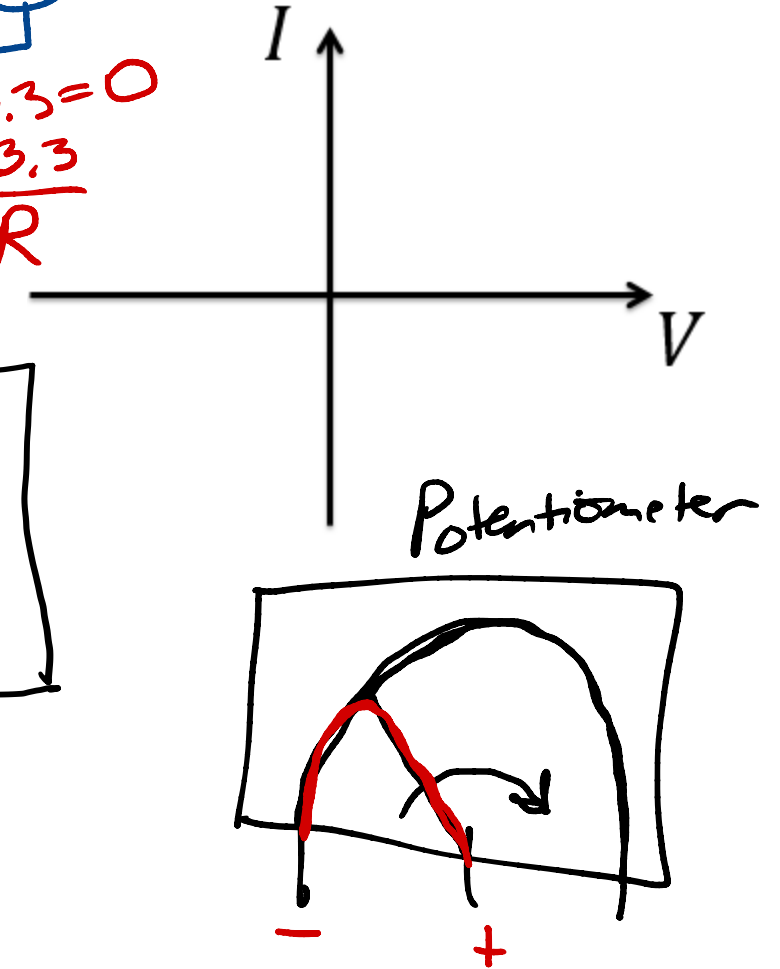


Q: Should this work to fix V_b and allow $0 < R < \infty \Omega$?

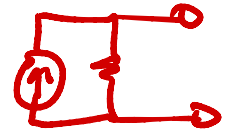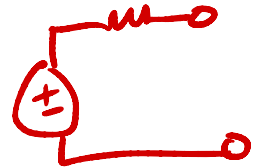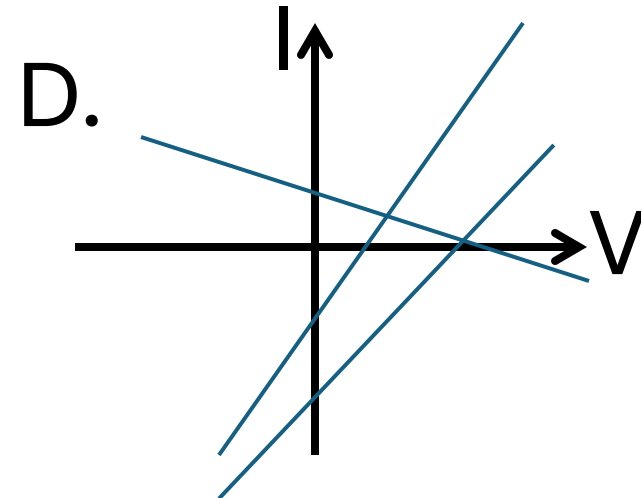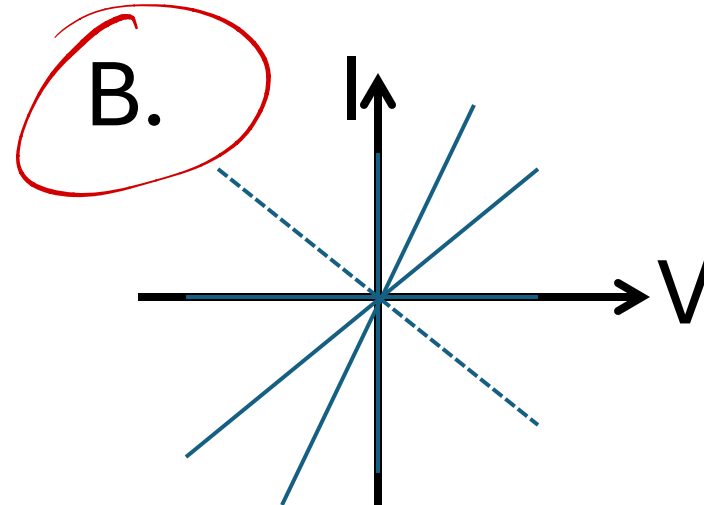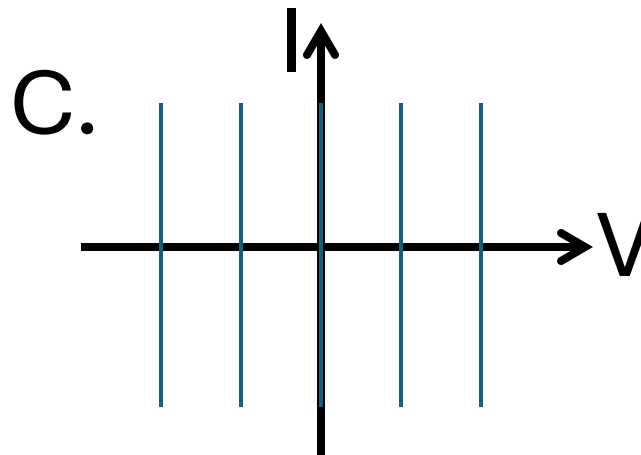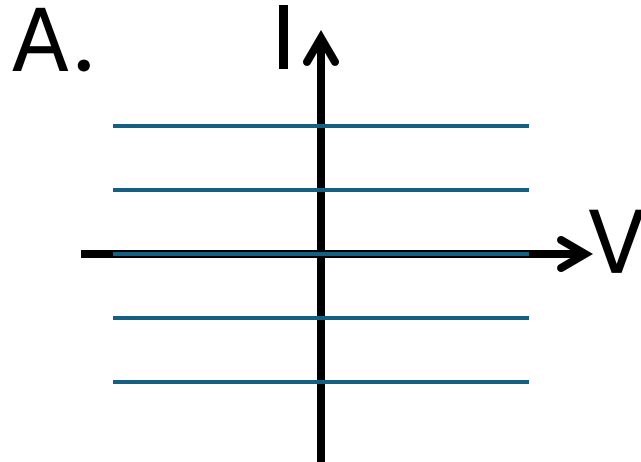- A. Yes
- B. No



Linear I-V curves

Q: Which set of graphs corresponds to pure resistances?



Simple Series Circuit

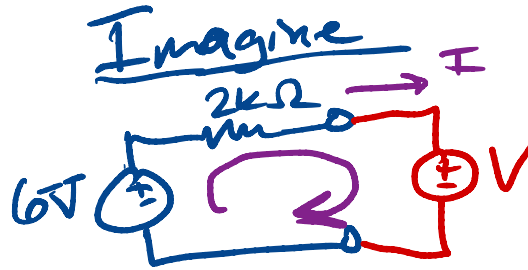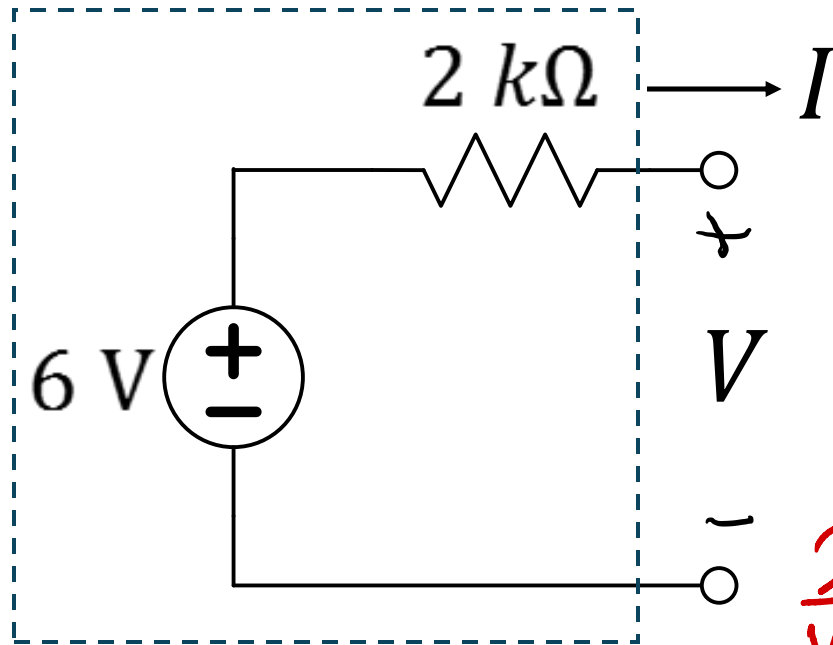
Show that the circuit has a linear IV characteristic by attaching a voltage source and analyzing it using your circuit-analysis toolbox.



$$6 - 2000I - V = 0$$

$$6 - V = 2000I$$

$$I = -\frac{V}{2000} + 3\text{mA}$$

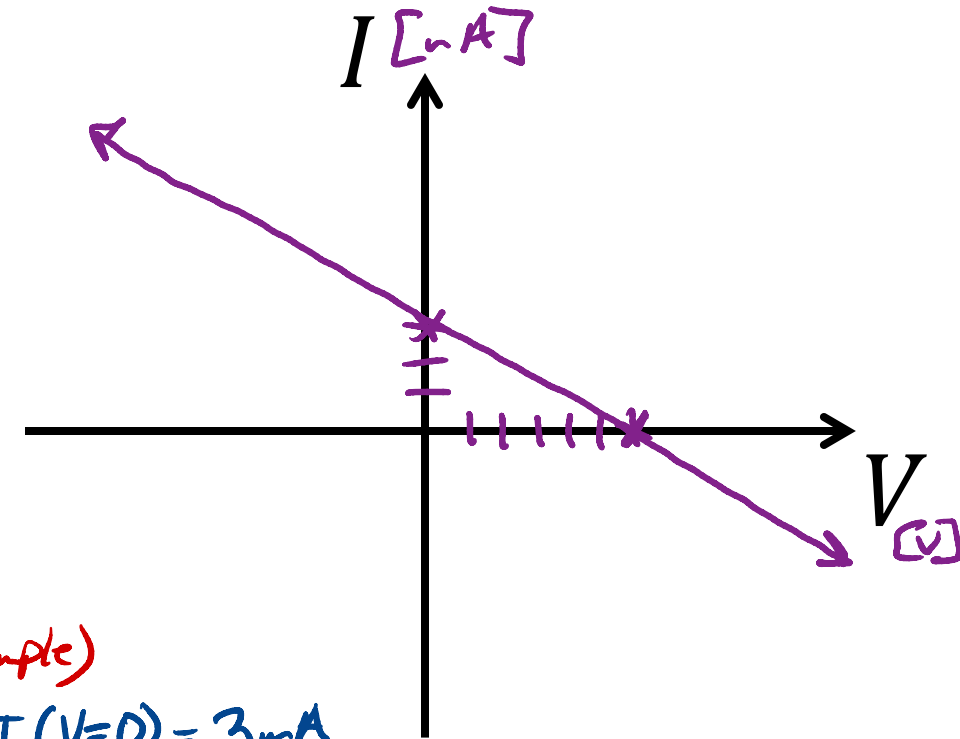

2 Points

$V_{oc} = V(I=0) = 6\text{V}$ (in this example)
Open circuit voltage





$I_{sc} = I(V=0) = 3\text{mA}$
short circuit current



Q: Find m and b such that $I = mV + b$ and then graph it.

Embedded Voltage Source

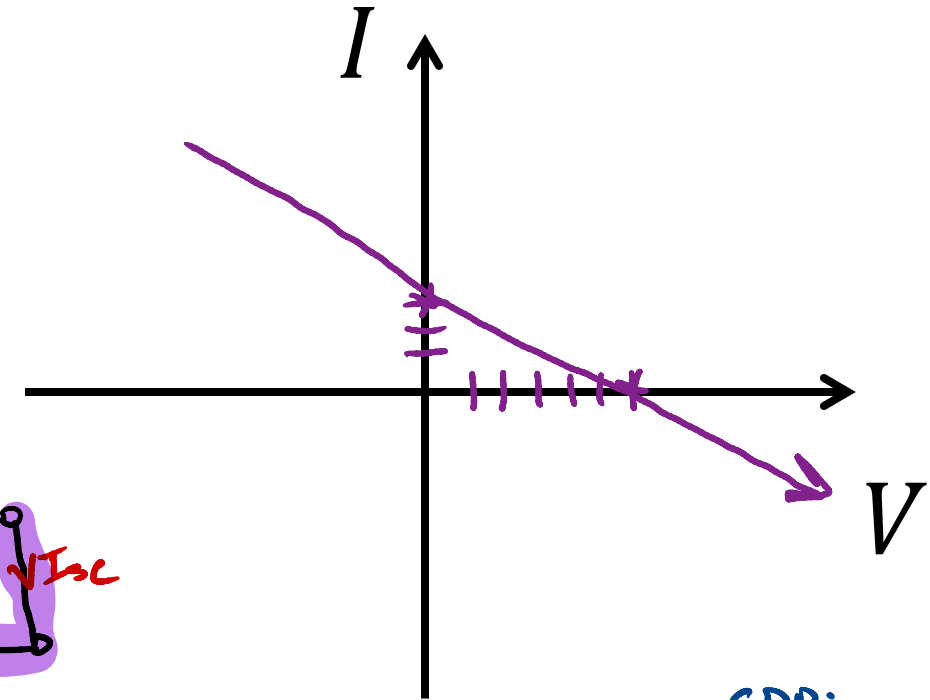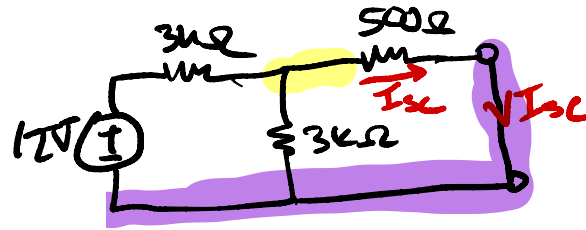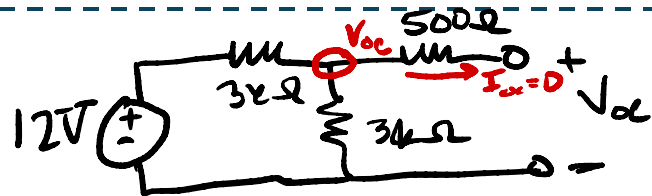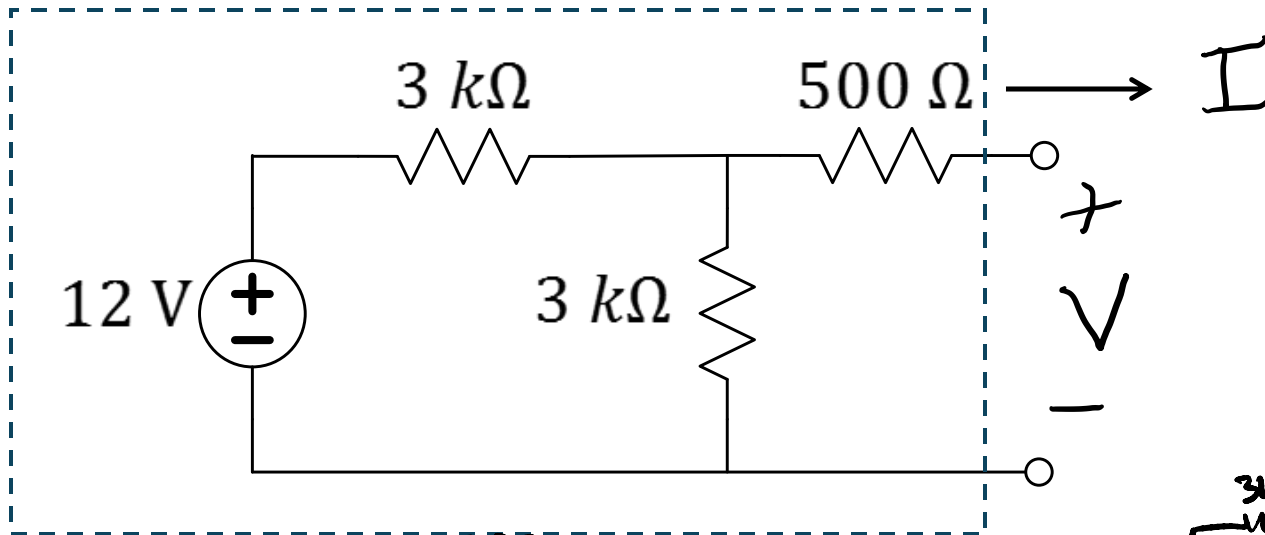Show that this circuit also has a linear IV characteristic.



Q: Find m and b such that $I = mV + b$ and then graph it.

$$V_{500} = 0$$

$$V_{3k} = \left(\frac{3k}{6k} \right) (12) = 6V = V_{OC}$$

$$R_{eq} = \left(\frac{1}{500} + \frac{1}{3000} \right)^{-1} = \left(\frac{6+1}{3000} \right)^{-1} = \frac{3}{7} k\Omega$$


$$I_+ = \frac{12}{3000 + \frac{3000}{7}} = 3.5mA$$

$$CDR: I_x = \left(\frac{\frac{3}{7} k\Omega}{500} \right) I_+$$

$$I_x = 3mA$$

Embedded Voltage Source

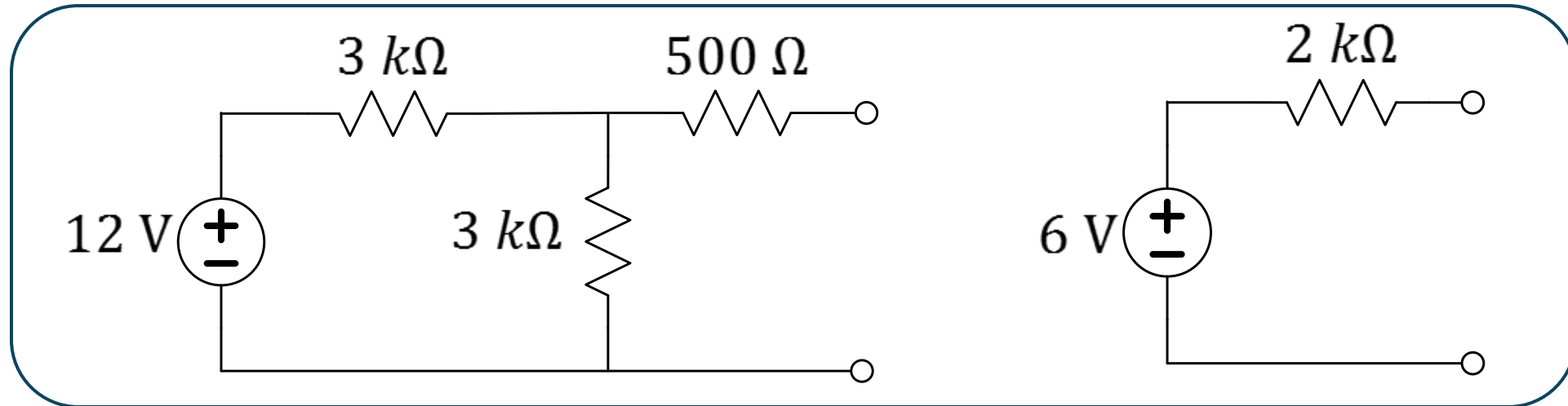Both these circuits have the SAME linear IV characteristic!



Q: If both circuits produce the same $I = mV + b$ plot, can the IV data be used to tell which of the two circuits is “in the box”?

- A. Yes
- B. No
- C. Other

L11 Learning Objectives

- a. Given one of the three sub-circuit descriptions (IV equation, IV line, diagram), find the other two

Note that more than one circuit diagram fits an IV description

- b. Quickly identify the IV representations of voltage and current sources, resistors, and combinations