
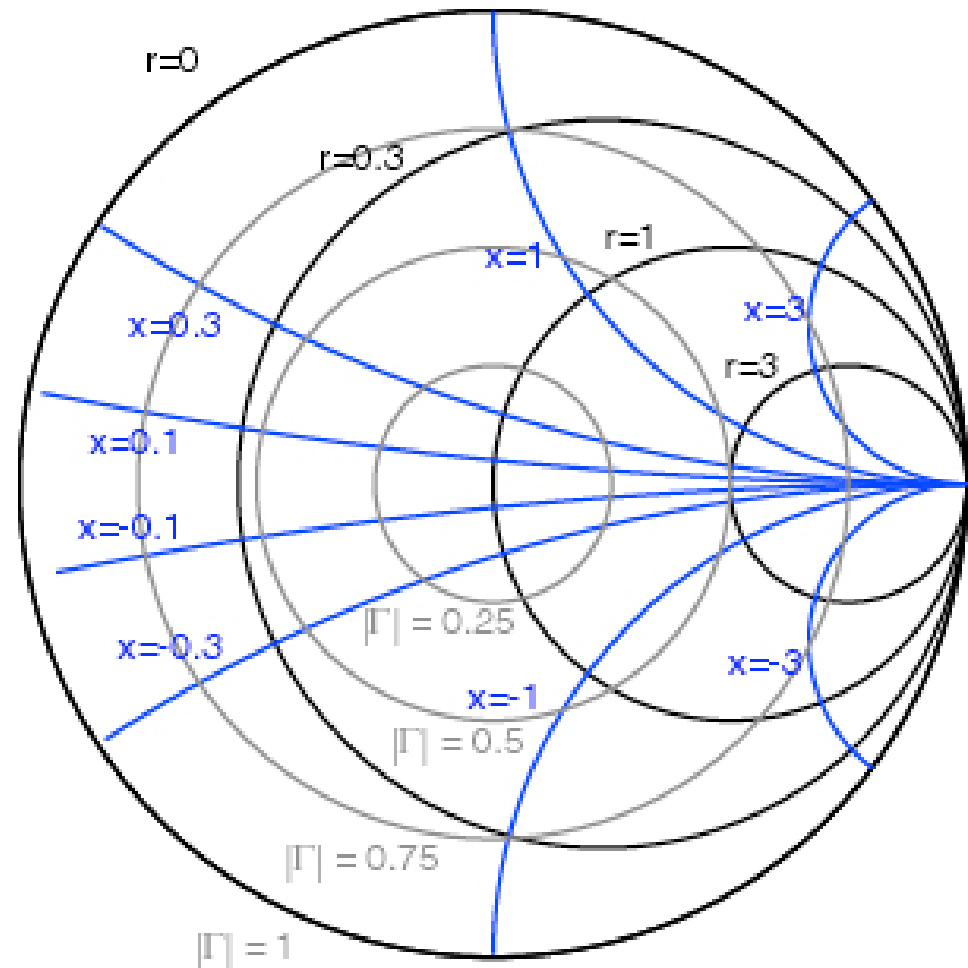


The Smith Chart

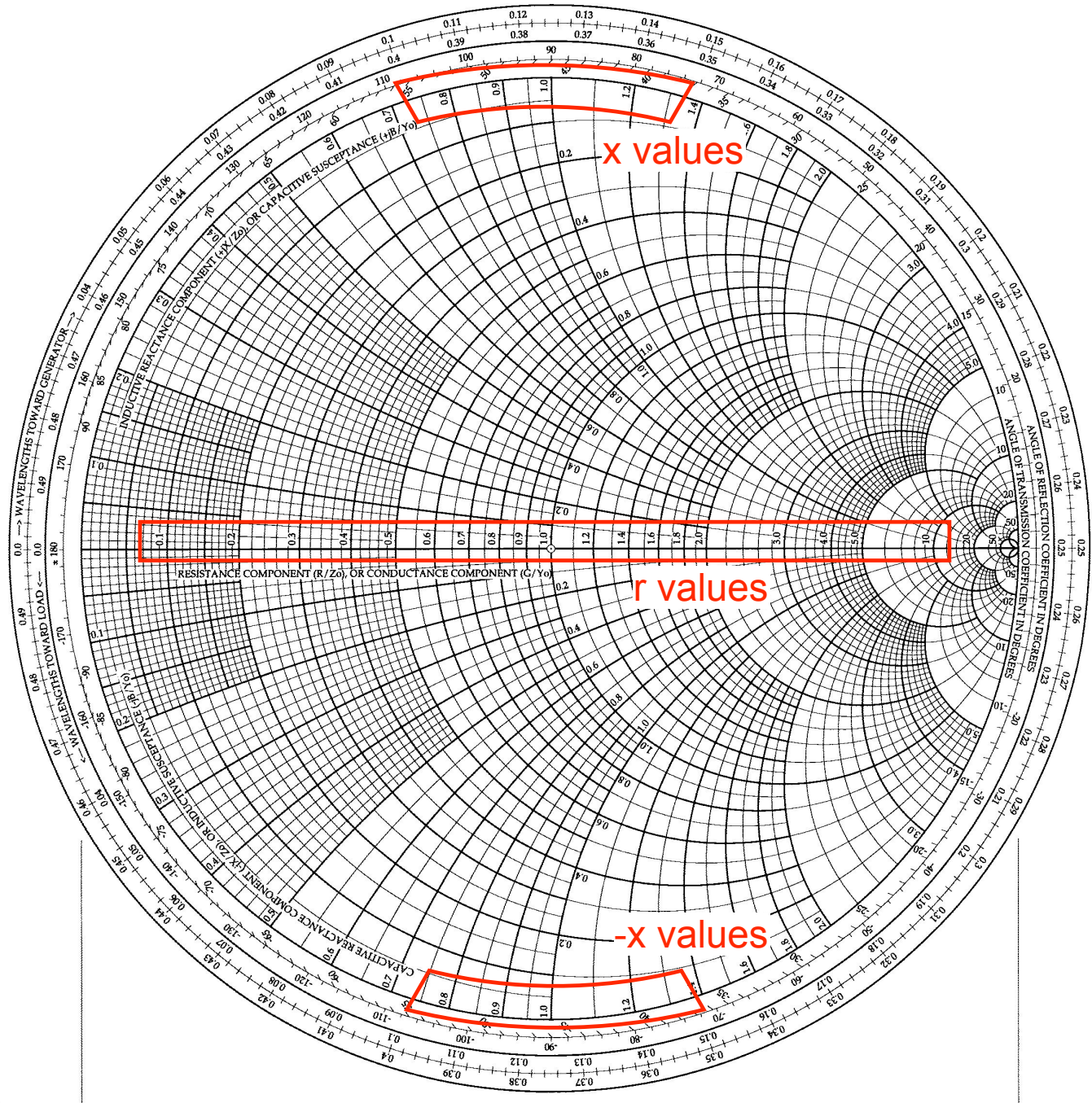
- Superimposes constant Γ , r and x circles
- We can quickly relate normalized line impedance to its corresponding reflection coefficient






$\Gamma(d)$ Transformations

- $\Gamma(d) = \Gamma_L e^{-2\beta d}$
- As d changes, we trace out a circle with radius $|\Gamma(d)| = |\Gamma_L|$
- A full circle is traced every
 - $2\beta d = 2\pi$
 - $d = \lambda/2$
- As d increases (towards generator) we move **counter-clockwise** along a constant Γ circle

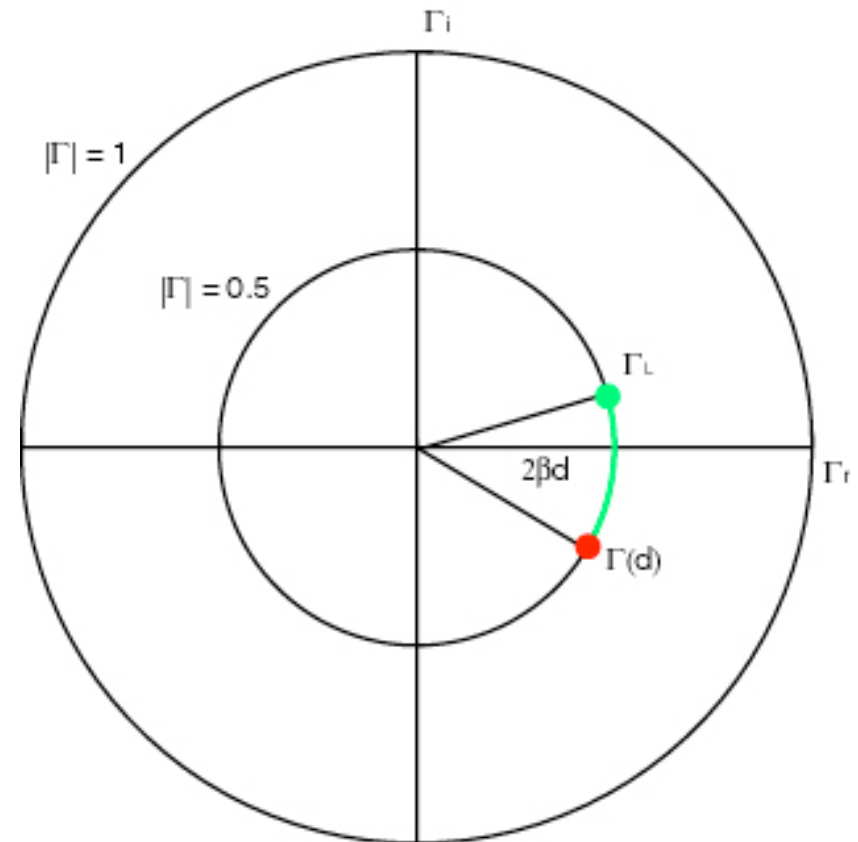


Distance (λ)
towards
generator

Distance (λ)
towards
load

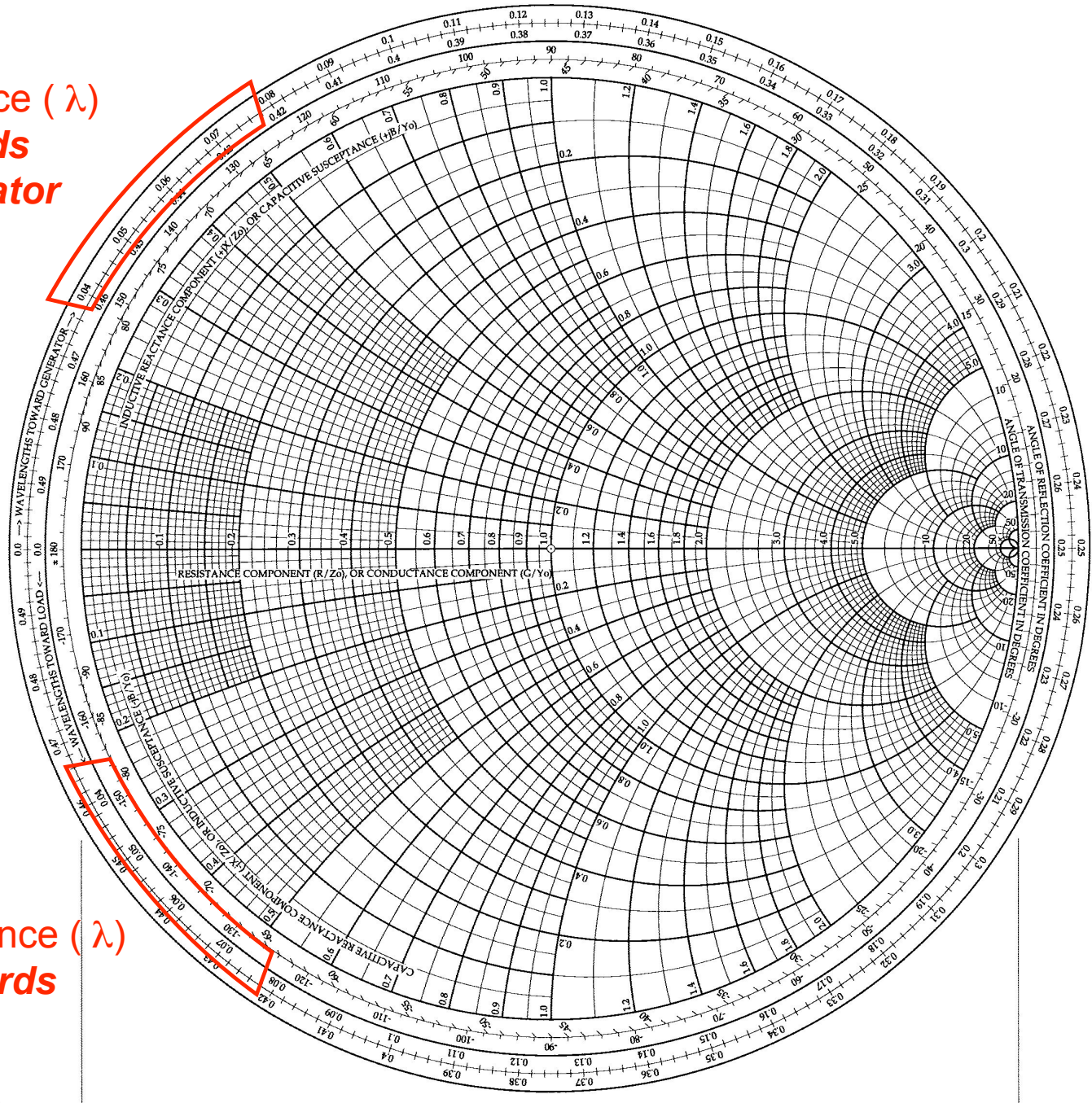

The standing wave ratio is read off of the chart by noting the r value where a constant Γ circle intersects the Γ_r axis

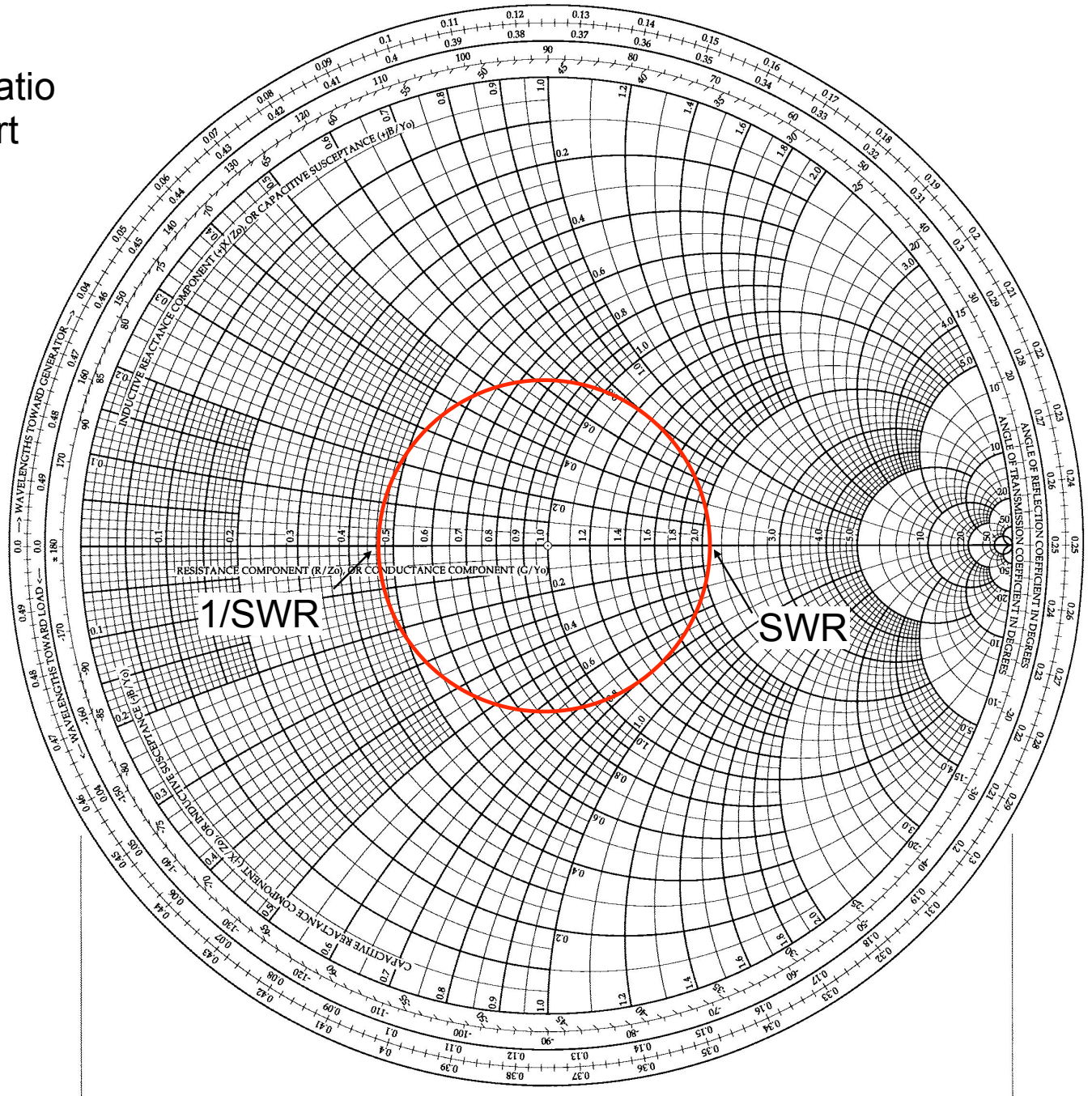
- 1) $SWR = Z_{max}/Z_0$
 $= z_{max}$
 $= r_{max}$
- 2) $SWR = Z_0/Z_{min}$
 $= 1/z_{min}$
 $= 1/r_{min}$



EXAMPLE:

If the effective reflection coefficient on a piece of $50\ \Omega$ line is $\Gamma = 0.4 + j0.2$, what is the corresponding line impedance at that point?

- 1) Find Γ on the Smith Chart

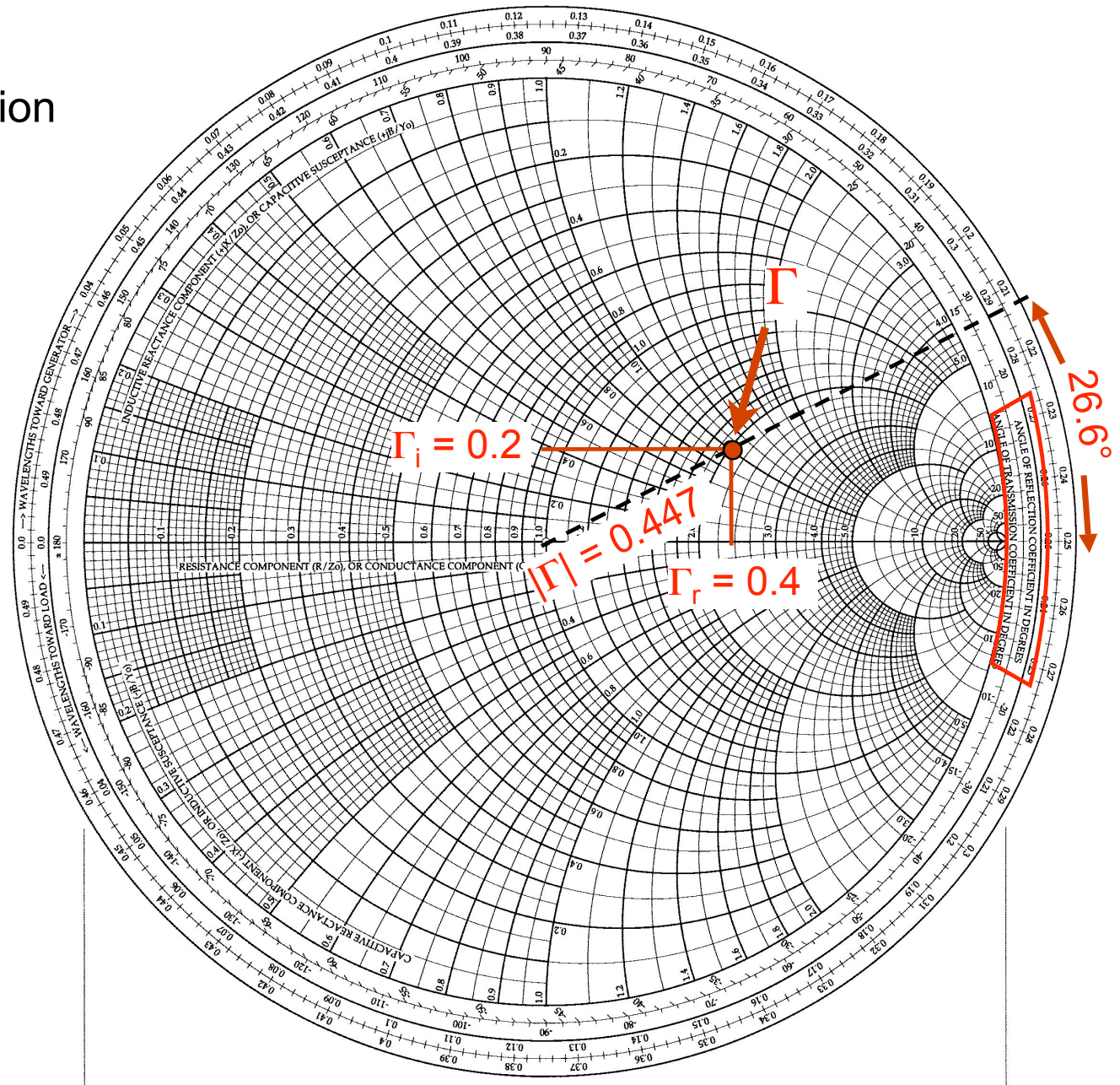


EXAMPLE:

If the effective reflection coefficient on a piece of 50Ω line is $\Gamma = 0.4 + j0.2$, what is the corresponding line impedance at that point ?

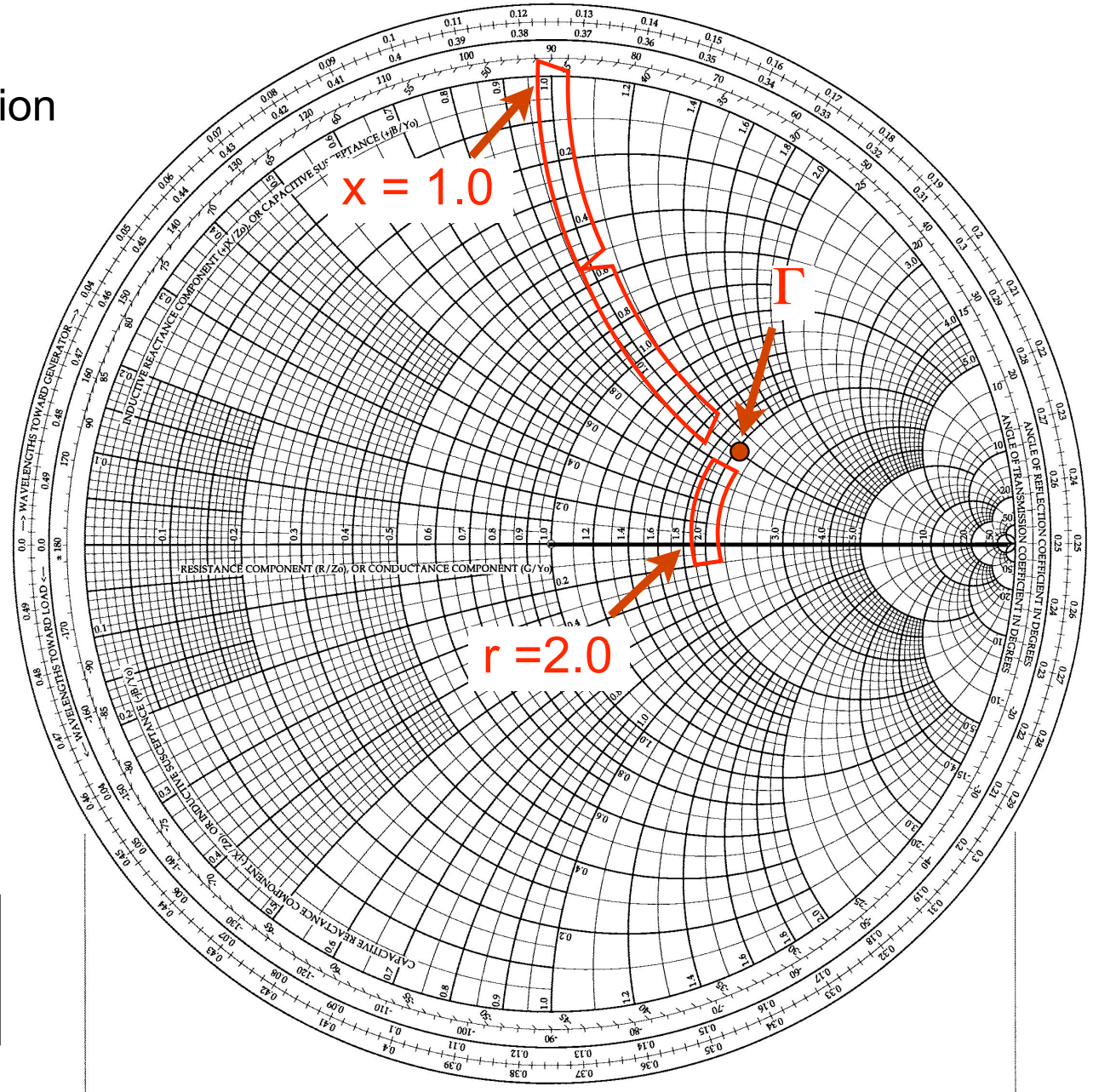- 1) Find Γ on the Smith Chart
- 2) Read r and x off of chart
- 3) Use Z_0 to re-normalize


$$Z = 50 (2.0 + j1.0) = 100.0 + j 50.0 \Omega$$



EXAMPLE:

A load with $Z_L = 50 - j25$ is attached to a lossless, 100Ω T-L. Find $Z(d)$ at $d = 0.4\lambda$

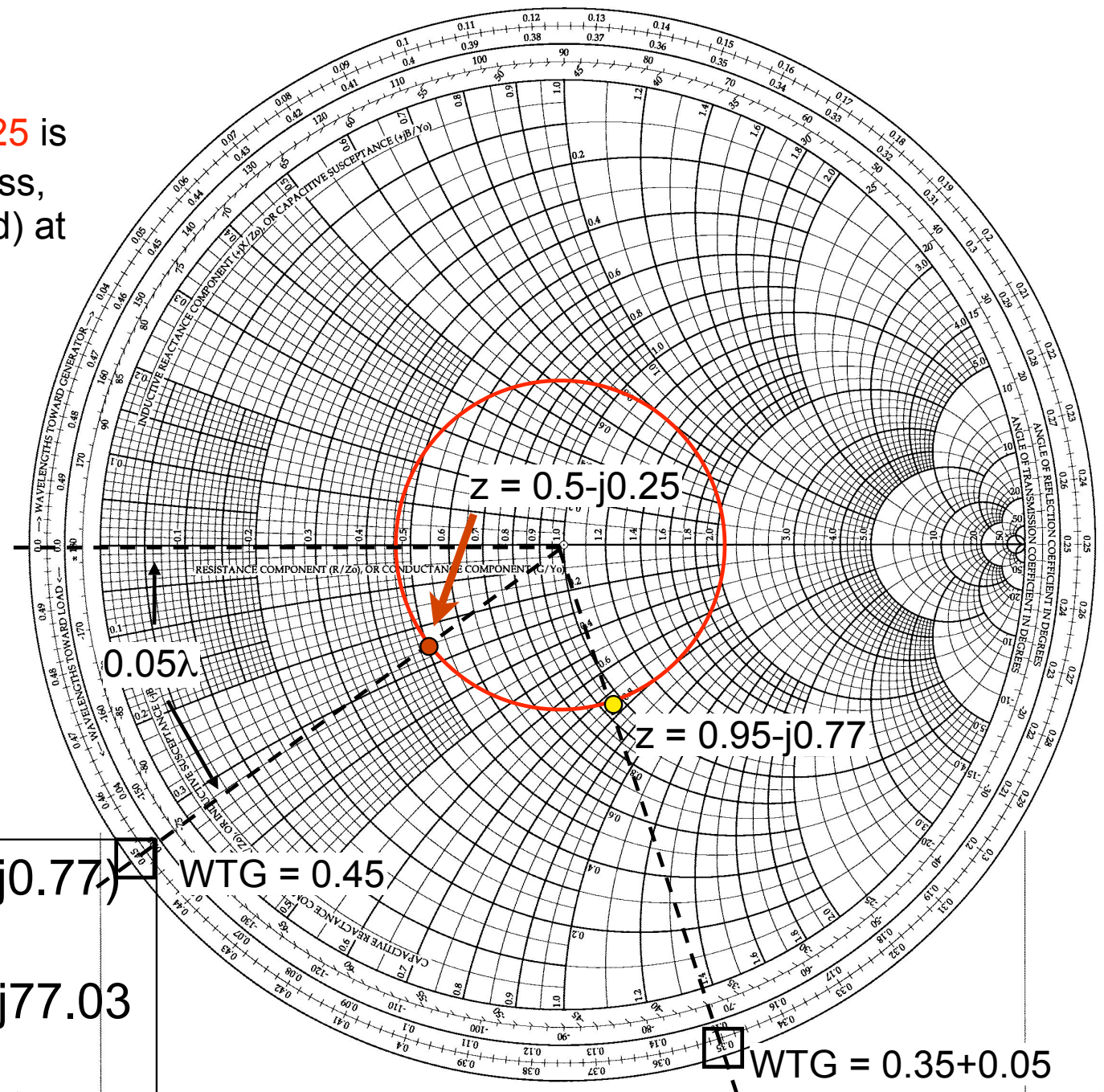- 1) Normalize Z_L
 $z = 0.5 - j0.25$
- 2) Find z on the Smith Chart
- 3) Rotate along constant Γ by 0.4λ
- 4) Read off new values of z
- 4) Use Z_0 to re-normalize



$$Z(d) = 100 (.95 - j0.77) \quad \text{WTG} = 0.45$$

$$= 95 - j77 \Omega$$

$$Z(d)_{\text{calc}} = 95.29 - j77.03$$

$$\% \text{error} \sim 0.2\%$$

$$\text{WTG} = 0.35 + 0.05$$

We can transform z into y by rotating z half way around a constant Γ circle

Given $Z = 95 + j20$ on a 50Ω line, find Y

- 1) Find z
 $z = 1.9 + j0.4$
- 2) Draw Γ circle
- 3) Draw line through origin
- 4) Find intersection with Γ circle
- 5) Read off y
 $y = 0.5 - j0.1$
- 6) Renormalize y
 $Y = y/Z_0$
 $= 10 - j2 \text{ mS}$
 $Y_{\text{calc}} = 10.1 - j2.12 \text{ mS}$

