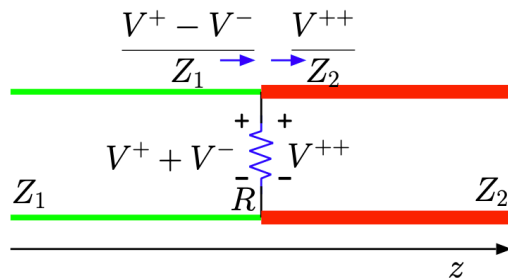


# Lecture 33

## 1 Multi-line circuits example with shunt resister

Two TL's with characteristic impedances  $Z_1$  and  $Z_2$  are joined at a junction that also includes a “shunt” resistance  $R$  as shown in the diagram in the margin. Determine the reflection coefficient  $\Gamma_{12}$  and transmission coefficient  $\tau_{12}$  at the junction.



For wave propagating from line 1 to line 2

- Find the equivalent impedance at the junction.

$$Z_{eq} = R \parallel Z_2$$

- Determine the  $\Gamma_{12}$  and  $\tau_{12}$ .

$$\Gamma_{12} = \frac{Z_{eq} - Z_1}{Z_{eq} + Z_1}, \text{ and } \tau_{12} = 1 + \Gamma_{12}$$

For wave propagating from line 2 to line 1


- Find the equivalent impedance at the junction.

$$Z_{eq} = R \parallel Z_1$$

- Determine the  $\Gamma_{21}$  and  $\tau_{21}$ .

$$\Gamma_{21} = \frac{Z_{eq} - Z_2}{Z_{eq} + Z_2}, \text{ and } \tau_{21} = 1 + \Gamma_{21}$$
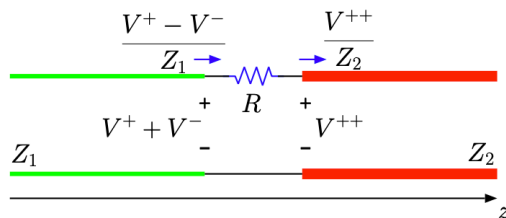
## 2 Multi-line circuits example with series resister



For wave propagating from line 1 to line 2

- Find the equivalent impedance at the junction.

$$Z_{eq} = R + Z_2$$

- Determine the  $\Gamma_{12}$  and  $\tau_{12}$ .

$$\Gamma_{12} = \frac{Z_{eq} - Z_1}{Z_{eq} + Z_1}$$

However,  $\tau_{12} \neq 1 + \Gamma_{12}$ , because  $\tau_{12} = \frac{Z_2}{R + Z_2} (1 + \Gamma_2)$

### 3 Oscillations in lossless TL ckts

If the transmission line ends are terminated with an open or short circuit, the TL (stub) becomes an oscillator, in analogous to a LC circuit.

#### 3.1 Open-open stub

When both ends of the stub are open, the reflection coefficient  $\Gamma = 1$ .

The standing wave on the stub is  $I(z, t) = \frac{f(t - \frac{z}{v})}{Z_o} - \frac{g(t + \frac{z}{v})}{Z_o}$

The boundary conditions at  $z = 0$  and  $z = l$  are current  $I(z, t) = 0$

From that we know, the forward going wave and the backward going wave are the same; and the function  $f(t)$  is a periodic function with

- Period  $T = \frac{2l}{v}$
- Fundamental frequency  $\omega_o = \frac{2\pi}{T} = \frac{\pi v}{l}$

Using Fourier series, the standing wave current is

$$I(z, t) = \sum_{n=1}^{\infty} \frac{2F_n}{Z_o} \underbrace{\sin(n\omega_o t + \theta_n) \sin(n\beta_o z)}_{\text{resonant modes}}$$

Where the fundamental wavenumber  $\beta_o \equiv \frac{\omega_o}{v} = \frac{\pi}{l}$

And the standing wave voltage is

$$I(z, t) = \sum_{n=1}^{\infty} 2F_n \underbrace{\cos(n\omega_o t + \theta_n) \cos(n\beta_o z)}_{\text{resonant modes}}$$

So the current and voltage on stub has infinite number of resonances.

- resonance frequency  $\omega = \frac{\pi v}{l} n$  rad/s or  $f = \frac{v}{2l} n$  Hz
- resonance wavelength  $\lambda = \frac{v}{f} = \frac{2l}{n}$
- length of the stub  $l = n \frac{\lambda}{2}$