

# Lecture 36


## 1 Smith Chart introduction

Download the Smith chart through this [link](#). You can print it in black.

Smith chart is the complex  $\Gamma$  plane. The outer periphery is  $\Gamma = 1$  unit circle. The origin is  $\Gamma = 0$ .


Möbius transformation above translate complex line impedance  $z = r + jx$  into the smith chart of  $\Gamma$  values.

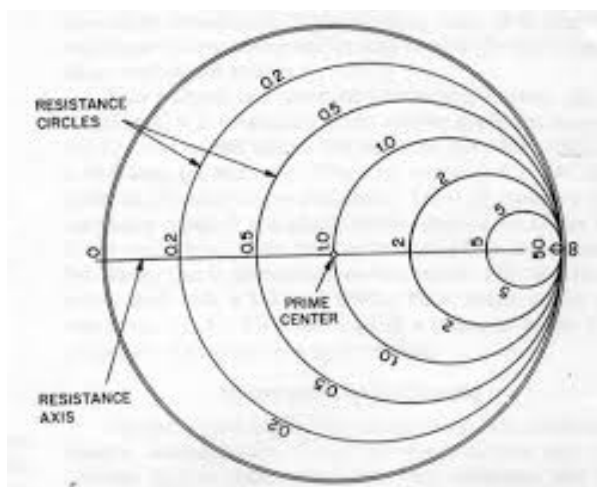- For  $r = \text{const}$  lines on complex  $z$  plane, they transform into smith chart as circles



- $z = 0$  (short)  $\rightarrow$  left side on center line
- $z = 1$  (matched)  $\rightarrow$  origin
- $z = \infty$  (open)  $\rightarrow$  right side on center line

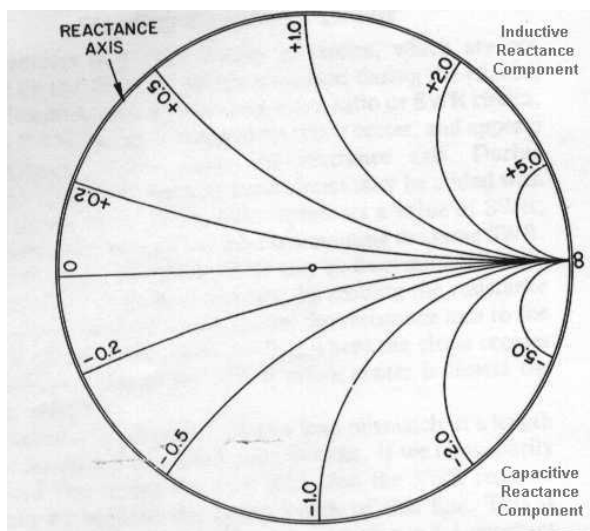- For  $x = \text{const}$  lines on complex  $z$  plane, they also transform into smith chart as circles, but we only care about the arcs inside the  $\Gamma = 1$  unit circle



- Arcs on upper half plane  $\rightarrow$  inductive reactance ( $x > 0$ )
- Arcs on lower half plane  $\rightarrow$  capacitive reactance ( $x < 0$ )

## 2 Examples using Smith Chart


Please watch the lecture to see the following examples on how to use Smith chart!

### 2.1 Example – From load impedance $Z_L$ to input impedance $Z_{in}$

### 2.2 Example – From $Z$ to $Y$
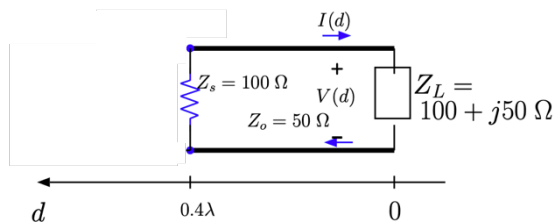
## 3 Example 1: From load to Input impedance and admittance

A load  $Z_L = 100 + j50 \Omega$  is connected across a TL with  $Z_o = 50 \Omega$  and  $l = 0.4 \lambda$ . At the generator end,  $d = l$ , the line is shunted by an impedance  $Z_s = 100 \Omega$ . What are the input impedance  $Z_{in}$  and admittance  $Y_{in}$  of the line, including the shunt connected element.



This example shows 2 ways of using Smith Chart.

- From load impedance  $Z_L$  to input impedance  $Z_{in}$


Rotate towards generator  $\rightarrow$  circle in clockwise direction

- From impedance  $Z$  to admittance  $Y$

Find the opposite position w.r.t. center.

## 1 Example 2: Average power

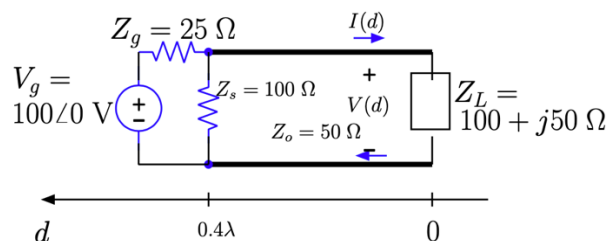Example 2: The TL network described in Example 1 is connected to a generator with open circuit voltage phasor  $V_g = 100\angle 0^\circ \text{ V}$  and internal impedance  $Z_g = 25 \Omega$ . What is the average power (a) input of the shunted line, (b) delivered to the shunt element, delivered to the load.



- a) Average power  $P_{in}$  at the input of the shunted line

$$P_{in} = \frac{1}{2} \text{Re}\{VI^*\}$$


Need  $V_{in}$  by voltage division.

- b) Average power  $P_L$  of the load  $Z_L$

Because TL is lossless, average power of the input  $P_{in}$  = average power of  $Z_s + P_L$

## 2 Example 3: From input to load

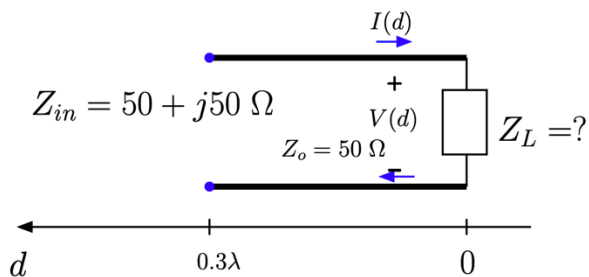Example 3: A TL of length  $l = 0.3 \lambda$  has an input impedance  $Z_{in} = 50 + j50 \Omega$ . Determine the load impedance  $Z_L = Z(0)$  and  $Y_L = Y(0)$  given that  $Z_o = 50 \Omega$  for the line.



- From input impedance  $Z_{in}$  to load impedance  $Z_L$

Rotate towards load  $\rightarrow$  circle in counterclockwise direction