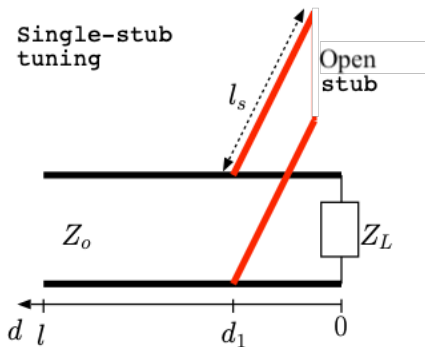


Lecture 39

1 Single-stub tuning with open ended stub



We can also use an open-ended red TL for the single-stub tuning and get a matched impedance.

- Find position d_1 where to insert the open-ended stub;
- Calculate normalized admittance $y(d_1)$ for the black TL.
- Calculate normalized admittance y_{stub} for the red TL.
- Find the length l_s of the red shorted-stub.

Part a-c will be exactly the same as the shorted-stub.


Part d). we need to rotate from open-ended load side to y_{stub} .

- For open terminal, the admittance $y_{LS} = 0$.
- Rotate y_{LS} towards generator to y_{stub} , to find the length of the red TL l_s .

Disadvantage of single-stub tuning:

- For different load impedance Z_L or frequency, the position d_1 and stub length l_s will be changing.
- It's very difficult to find the exact position d_1 on the original transmission line.

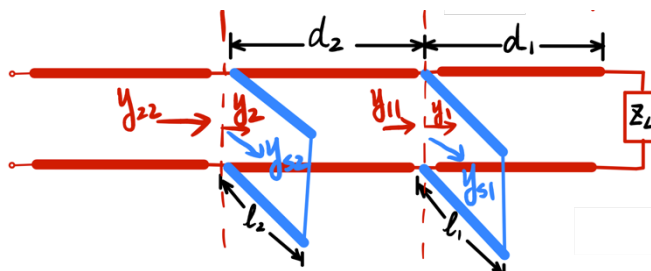2 Double-stub tuning with short ended stub



- Position d_1 and d_2 are fixed (easy to implement)

For example, $d_1 = 0$ or $\lambda/4$;

$d_2 = \lambda/8$, $\lambda/4$, or $3\lambda/8$

- Stub length l_{s1} and l_{s2} are varying with different Z_L

Step 1: normalize load impedance Z_L

Step 2: plot Z_L on Smith chart

Step 3: Find y_L on smith chart

Extend the z_L point through the center of the Smith Chart (in opposite direction, 180° , with same distance)

Step 4: Draw $(1 + jb)$ circle and rotate it with the distance d_2 chosen for the solution,

$$(d_2 = \quad \quad \quad)$$

Step 5: Move on constant real value circle, until it intersect the *rotated* $(1 + jb)$ circle

Step 6: Find the difference between y_1 (same as y_L for this example) point and y_{11}

$$y_{s2} = y_{11} - y_L$$

Step 7: Calculate the shunt line length l_1

From short circuit point for admittance to this susceptance value

Step8: find the corresponding point for y_{11} on the original $(1 + jb)$ circle

Step 9: find the susceptance of second stub

Step 10: calculate the shunt line length l_2