

# 35 Smith Chart examples

**Example 1:** A load  $Z_L = 100 + j50 \Omega$  is connected across a TL with  $Z_o = 50 \Omega$  and  $l = 0.4\lambda$ . At the generator end,  $d = l$ , the line is shunted by an impedance  $Z_s = 100 \Omega$ . What are the input impedance  $Z_{in}$  and admittance  $Y_{in}$  of the line, including the shunt connected element.

**Solution:** Normalized load impedance

$$z(0) = \frac{Z_L}{Z_o} = \frac{100 + j50}{50} = 2 + j1$$

is entered in the SC shown in the margin on the top. Clockwise rotation (from load toward generator) at fixed  $|\Gamma|$  (red circle) by

$$0.4\lambda \Leftrightarrow 0.8 \times 360^\circ = 288^\circ$$

takes us to

$$z(l) \approx 0.6 + j0.66 \quad \text{and} \quad y(l) \approx 0.75 - j0.83$$

as shown on the SC in the middle. Hence, including the shunt element with normalized input impedance  $z_{si} = 2$  and admittance  $y_{si} = \frac{1}{2}$ , we obtain


$$y_{in} = y(l) + y_{si} \approx 1.25 - j0.83$$

for the overall normalized input admittance of the shunted line as shown on the SC in the bottom — the corresponding normalized input impedance is

$$z_{in} = \frac{1}{y_i} \approx 0.56 + j0.37.$$

Hence, the unnormalized input impedance and admittance are

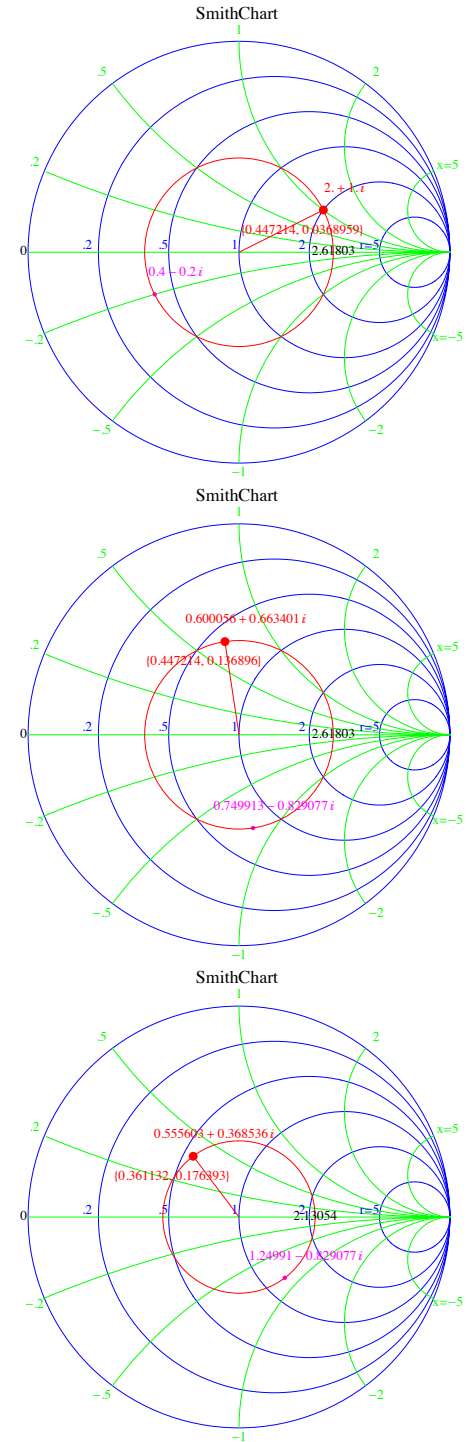
$$Z_{in} = Z_o z_{in} \approx 27.8 + j18.4 \Omega \quad \text{and} \quad Y_{in} = Y_o y_{in} \approx 0.025 - j0.017 \text{ S}.$$



$100\Omega$   
 $Z_s \parallel Z_0 = 50\Omega \parallel Z_L = 100 + j50\Omega$

$Z_{in} \cdot Y_{in}'$   
 $l = 0.4\lambda$

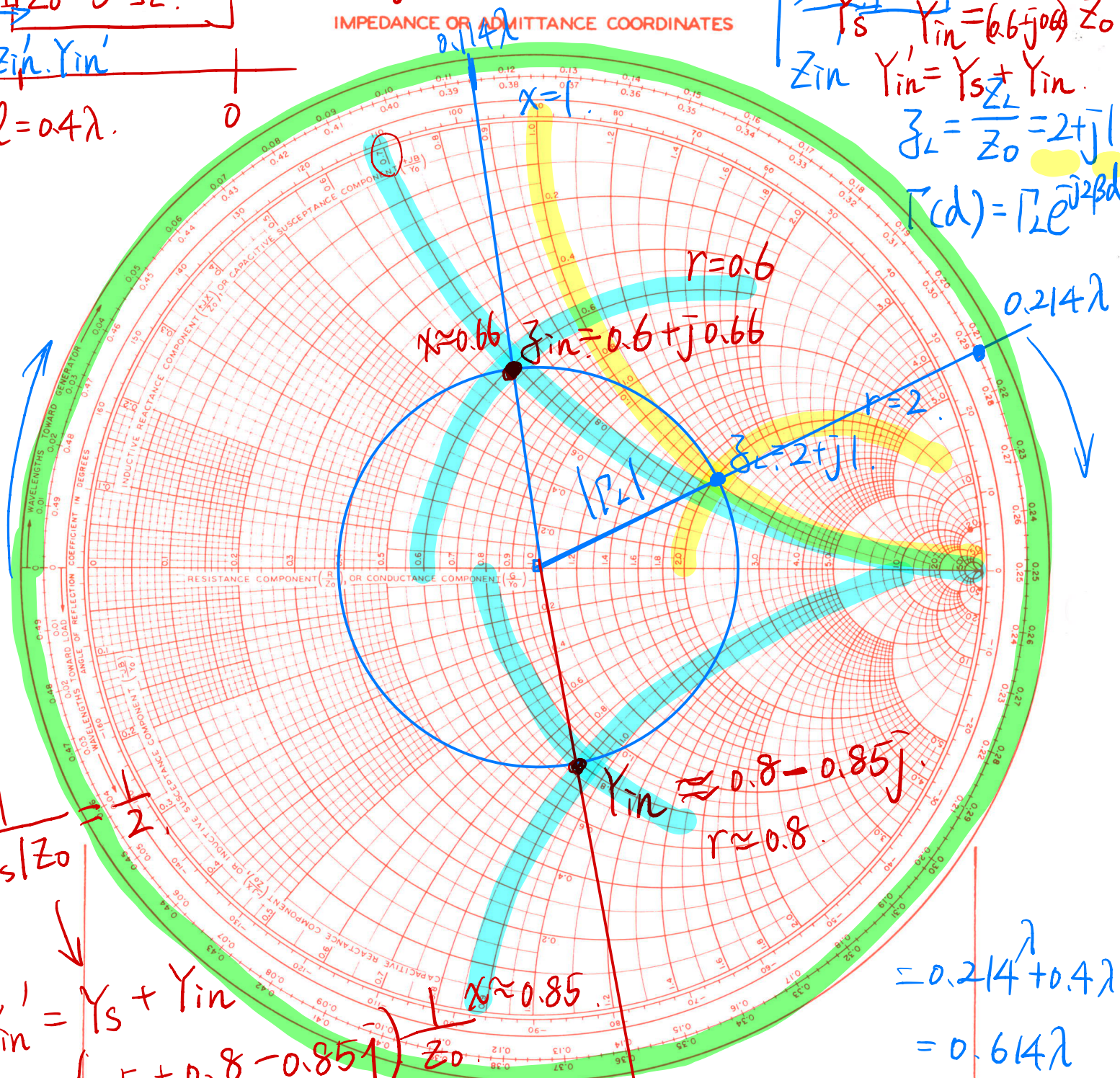$Z_s \parallel Z_{in}$   
 $Y_s \parallel Y_{in} = (6.5 + j0.6) Z_0$   
 $Y_{in}' = Y_s + Y_{in}$   
 $Z_L = \frac{Z_L}{Z_0} = 2 + j1$   
 $\Gamma(d) = \Gamma_L e^{j2\beta d}$




$\frac{1}{Z_s/Z_0} = \frac{1}{2}$

$Y_{in}' = Y_s + Y_{in}$

$= (6.5 + 0.8 - 0.85j) Z_0$   
 $= (1.3 - 0.85j) \cdot 50$

$Z_{in} = \frac{1}{Y_{in}'}$

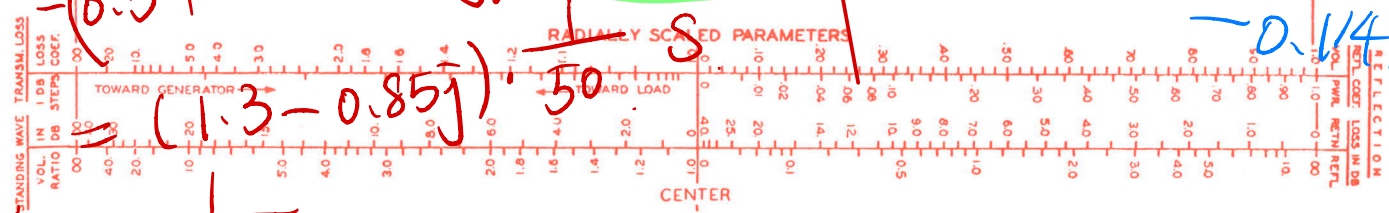$= 0.214\lambda + 0.4\lambda$   
 $= 0.614\lambda$   
 $- 0.114\lambda$



**Example 2:** The TL network described in Example 1 is connected to a generator with open circuit voltage phasor  $V_g = 100\angle 0$  V and internal impedance  $Z_g = 25\ \Omega$ . What is the average power (a) input of the shunted line, (b) delivered to the shunt element, delivered to the load.

**Solution:**

(a) Using the input impedance

$$Z_{in} \approx 27.8 + j18.4\ \Omega,$$

from Example 1, we can write

$$V_{in} = V_g \frac{Z_{in}}{Z_g + Z_{in}} \quad \text{and} \quad I_{in} = \frac{V_g}{Z_g + Z_{in}}.$$




Therefore, the average power input of the shunted line is

$$\begin{aligned} P &= \frac{1}{2} \text{Re}\{V_{in} I_{in}^*\} = \frac{1}{2} \text{Re}\left\{ \frac{V_g Z_{in}}{Z_g + Z_{in}} \left( \frac{V_g}{Z_g + Z_{in}} \right)^* \right\} \\ &= \frac{|V_g|^2}{2|Z_g + Z_{in}|^2} \text{Re}\{Z_{in}\} = \frac{100^2}{2|25 + 27.8 + j18.4|^2} 27.8 \approx 44.44 \text{ W}. \end{aligned}$$


(b) The shunt element  $Z_s = 100\ \Omega$  sees the same voltage  $V_{in}$  and conducts a current  $V_{in}/Z_s$ . Therefore it absorbs an average power of

$$\begin{aligned} P &= \frac{1}{2} \text{Re}\left\{ V_{in} \left( \frac{V_{in}}{Z_s} \right)^* \right\} = \frac{|V_{in}|^2}{2Z_s} = \frac{|V_g Z_{in}|^2}{2Z_s |Z_g + Z_{in}|^2} \\ &\approx \frac{|100 \cdot (27.8 + j18.4)|^2}{2 \cdot 100 \cdot |25 + 27.8 + j18.4|^2} \approx 17.78 \text{ W}. \end{aligned}$$

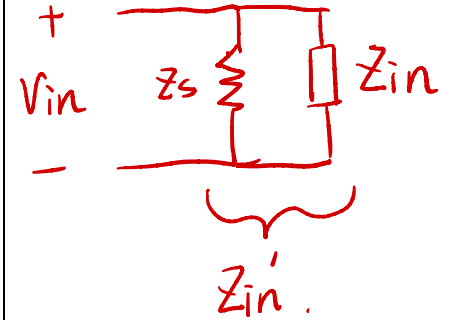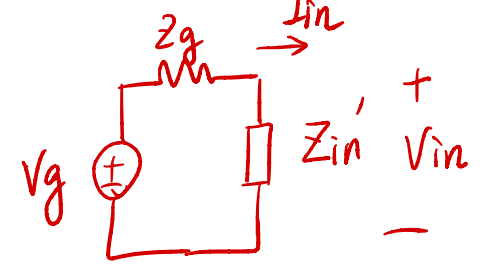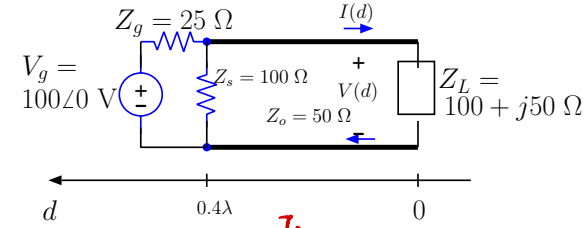The remainder of 44.44 W will be absorbed in  $Z_L$ .





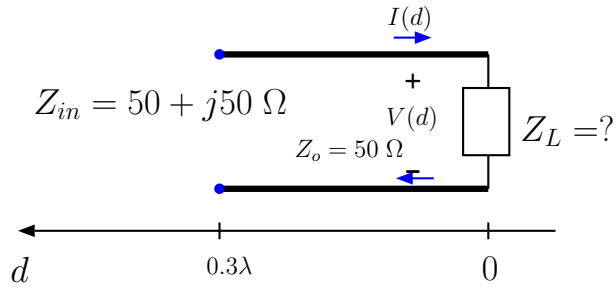

**Example 3:** A TL of length  $l = 0.3\lambda$  has an input impedance  $Z_{in} = 50 + j50 \Omega$ . Determine the load impedance  $Z_L = Z(0)$  and  $Y_L = Y(0)$  given that  $Z_o = 50 \Omega$  for the line.

**Solution:** First enter the normalized input impedance

$$z_{in} = \frac{Z_{in}}{Z_o} = \frac{50 + j50}{50} = 1 + j$$

in the SC as shown in the margin on the top. Counter-clockwise rotation (from generator toward load) at fixed  $|\Gamma|$  (red circle) by

$$0.3\lambda \Leftrightarrow 0.6 \times 360^\circ = 216^\circ$$

takes us to


$$z(0) \approx 0.76 - j0.84 \quad \text{and} \quad y(0) \approx 0.59 + j0.66$$

as shown on the next SC at the load point. Hence, we find

$$Z_L = Z_o z(0) \approx 50 \cdot (0.76 - j0.84) = 37.97 - j41.88 \Omega$$



and

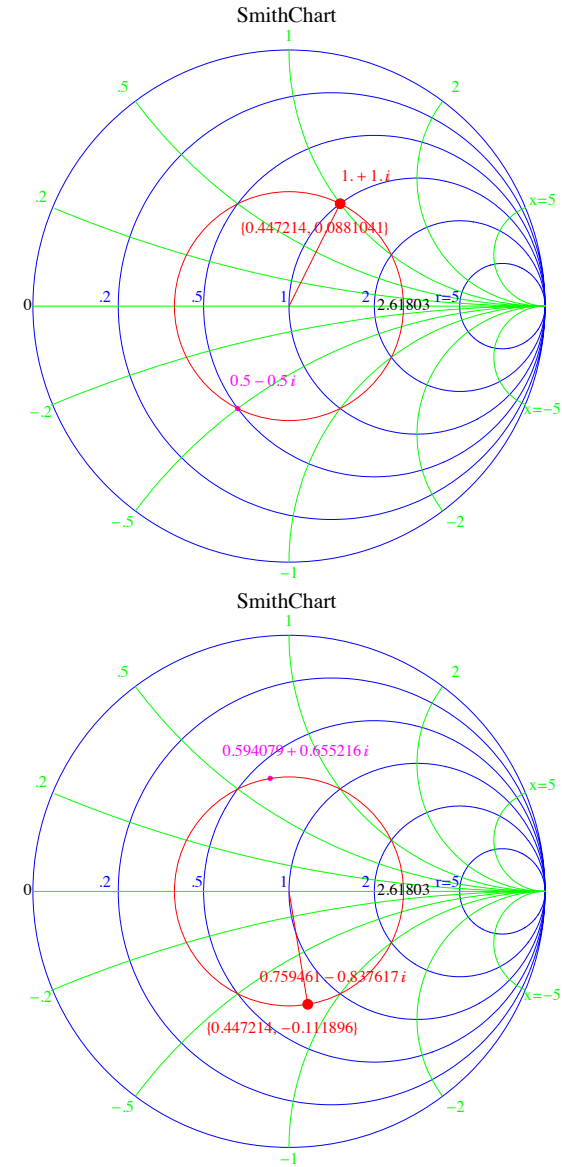
$$Y_L = Y_o y(0) \approx \frac{1}{50} (0.59 + j0.66) = 0.012 + j0.013 \text{ S}.$$



$$Z_{in} = \frac{Z_{in}}{Z_0} = 1 + j$$

# IMPEDANCE OR ADMITTANCE COORDINATES

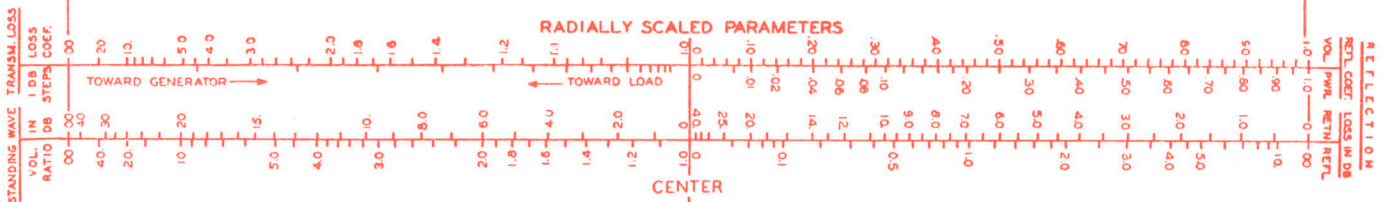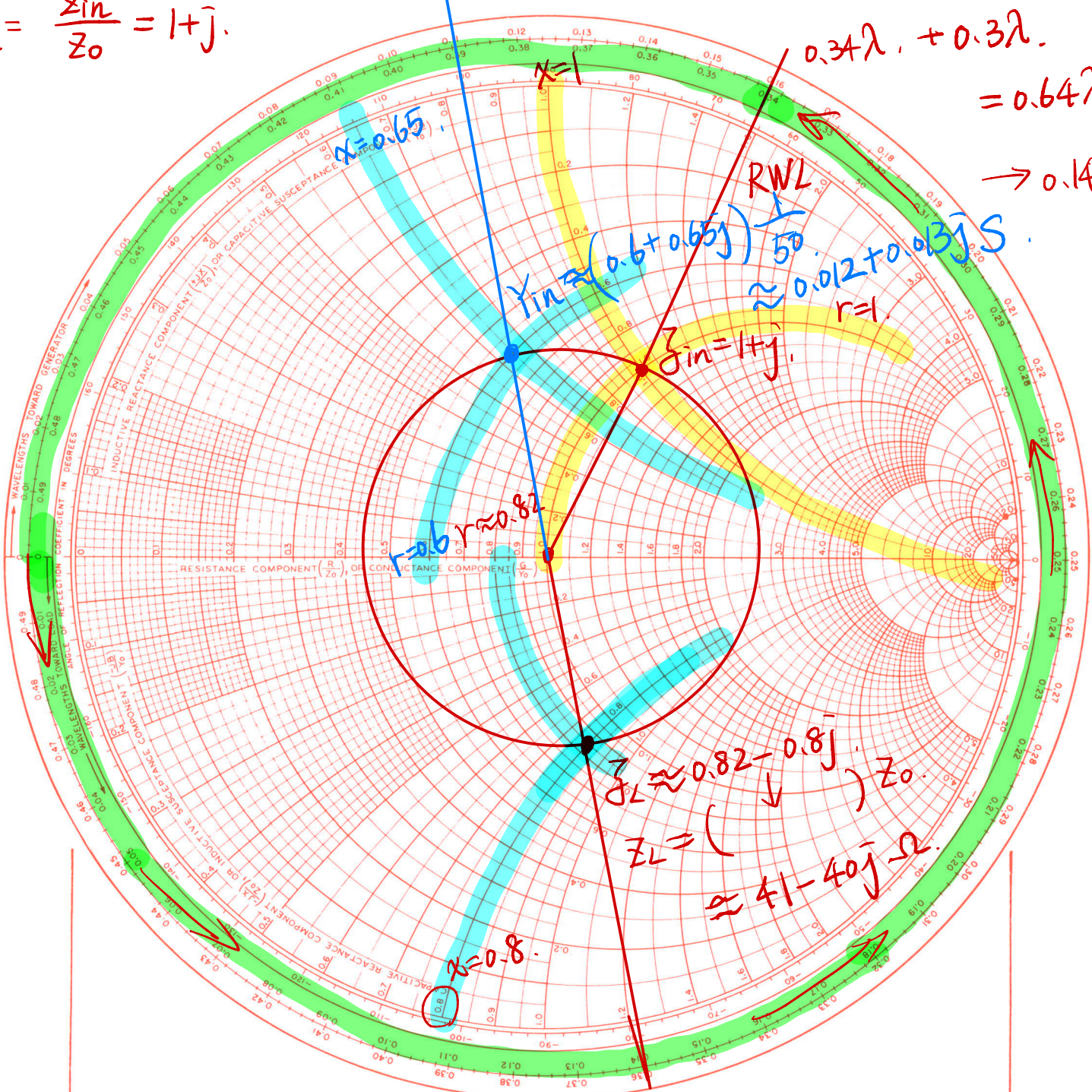

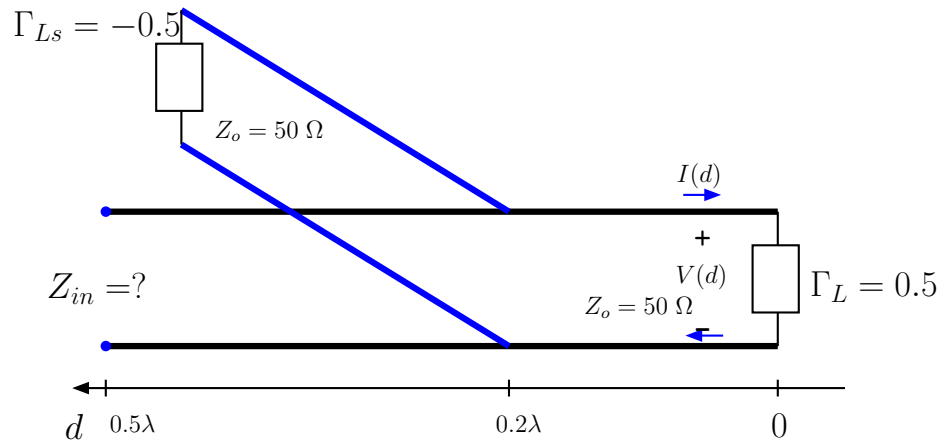

**Example 4:** A TL of length  $l = 0.5\lambda$  and  $Z_o = 50\Omega$  has a load reflection coefficient  $\Gamma_L = 0.5$  and **and** a shunt connected TL at  $d = 0.2\lambda$ . The shunt connected TL has  $l = 0.3\lambda$ ,  $Z_o = 50\Omega$ , and a load reflection coefficient  $\Gamma_L = -0.5$ . Determine the input impedance of the line.

**Solution:** Recall that the SC covers the unit circle of the complex plane and therefore the complex number

$$\Gamma_L = 0.5 + j0 = 0.5$$

can be entered directly in the SC as shown on the top SC in the margin. Clockwise rotation (from load toward generator) at fixed  $|\Gamma|$  (red circle) by




$$0.2\lambda \Leftrightarrow 0.4 \times 360^\circ = 144^\circ$$

takes us to

$$z(0.2\lambda) \approx 0.36 - j0.29 \quad \text{and} \quad y(0.2\lambda) \approx 1.7 + j1.33$$

as shown on the SC in the middle. Likewise, entering

$$\Gamma_{Ls} = -0.5 + j0 = -0.5$$

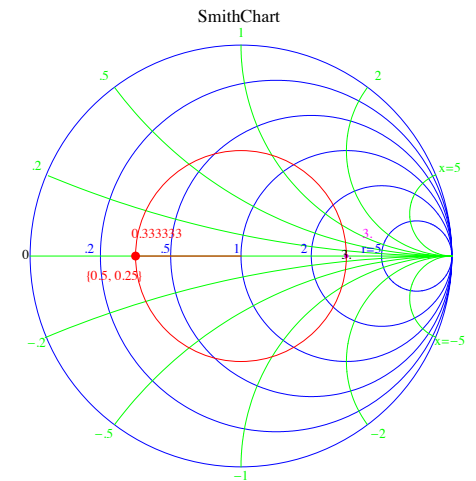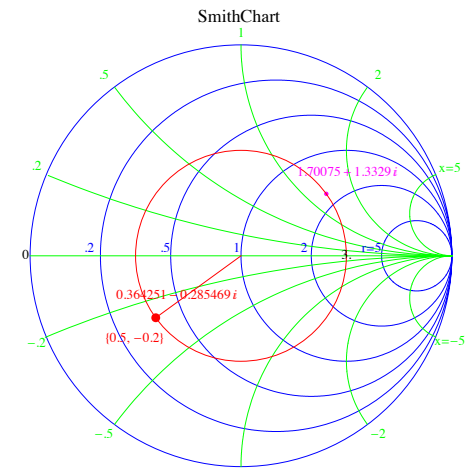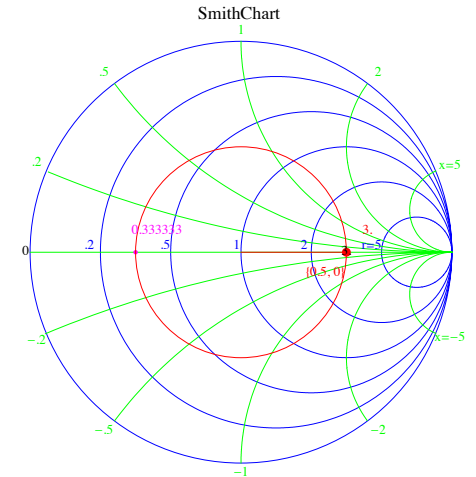

for the shunt connected stub in the third SC and rotating clockwise by

$$0.3\lambda \Leftrightarrow 0.6 \times 360^\circ = 216^\circ$$

we obtain

$$z_s(0.3\lambda) \approx 1.7 - j1.33 \quad \text{and} \quad y_s(0.3\lambda) \approx 0.36 + j0.29.$$

We proceed by combining the normalized admittances as


$$y_c = y(0.2\lambda) + y_s(0.3\lambda) \approx (1.7 + j1.33) + (0.36 + j0.29) = 2.065 + j1.61837,$$

and entering it in the next SC. Finally rotating clockwise once again by

$$0.3\lambda \Leftrightarrow 0.6 \times 360^\circ = 216^\circ$$

we obtain, from the last SC

$$z_{in} \approx 3.38 - j0.69 \quad \Rightarrow \quad Z_{in} = z_{in}Z_o \approx 169 - j34.4 \Omega.$$

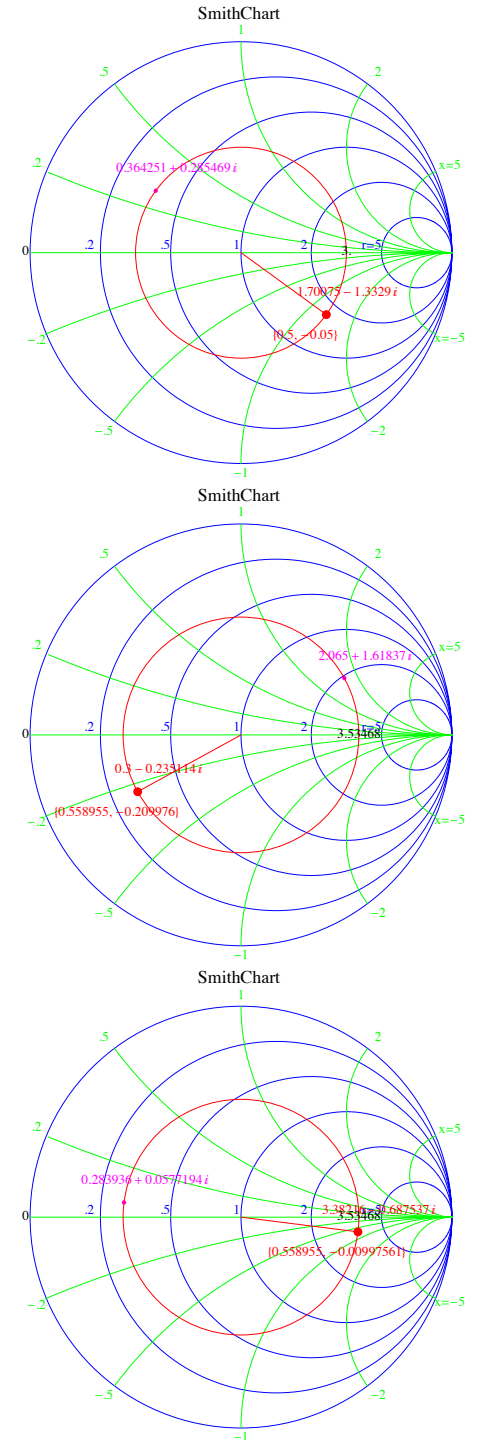



**Example 5:** What is the load impedance  $Z_{Ls}$  terminating the shunt connected stub in Example 4?

**Solution:** Given that the corresponding reflection coefficient is

$$\Gamma_{Ls} = -0.5,$$

it follows from the bilinear transformation linking  $z_{Ls}$  and  $\Gamma_{Ls}$  that

$$z_{Ls} = \frac{1 + \Gamma_{Ls}}{1 - \Gamma_{Ls}} = \frac{1 - 0.5}{1 + 0.5} = \frac{1}{3}.$$

Hence, the impedance is

$$Z_{Ls} = Z_o z_{Ls} = \frac{50}{3} \Omega.$$

**Example 6:** What is the load impedance  $Z_L$  in Example 4?

**Solution:** This is similar to Example 5. Given that the load reflection coefficient is

$$\Gamma_L = 0.5,$$

it follows from the bilinear transformation linking  $z_L$  and  $\Gamma_L$  that

$$z_L = \frac{1 + \Gamma_L}{1 - \Gamma_L} = \frac{1 + 0.5}{1 - 0.5} = 3.$$

Hence, the impedance is

$$Z_L = Z_o z_L = 150 \Omega.$$