

# 36 Smith Chart and VSWR

- Consider the general phasor expressions

$$V(d) = V^+ e^{j\beta d} (1 + \Gamma_L e^{-j2\beta d}) \quad \text{and} \quad I(d) = \frac{V^+ e^{j\beta d} (1 - \Gamma_L e^{-j2\beta d})}{Z_o}$$

describing the voltage and current variations on TL's in sinusoidal steady-state.

- Unless  $\Gamma_L = 0$ , these phasors contain reflected components, which means that voltage and current variations on the line “contain” standing waves.

In that case the phasors go through cycles of magnitude variations as a function of  $d$ , and in the voltage magnitude in particular (see margin) varying as

$$|V(d)| = |V^+| |1 + \Gamma_L e^{-j2\beta d}| = |V^+| |1 + \Gamma(d)|$$

takes maximum and minimum values of

$$|V(d)|_{max} = |V^+| (1 + |\Gamma_L|) \quad \text{and} \quad |V(d)|_{min} = |V^+| (1 - |\Gamma_L|)$$


at locations  $d = d_{max}$  and  $d_{min}$  such that

$$\Gamma(d_{max}) = \Gamma_L e^{-j2\beta d_{max}} = |\Gamma_L| \quad \text{and} \quad \Gamma(d_{min}) = \Gamma_L e^{-j2\beta d_{min}} = -|\Gamma_L|,$$


and

$$d_{max} - d_{min} \text{ is an odd multiple of } \frac{\lambda}{4}.$$
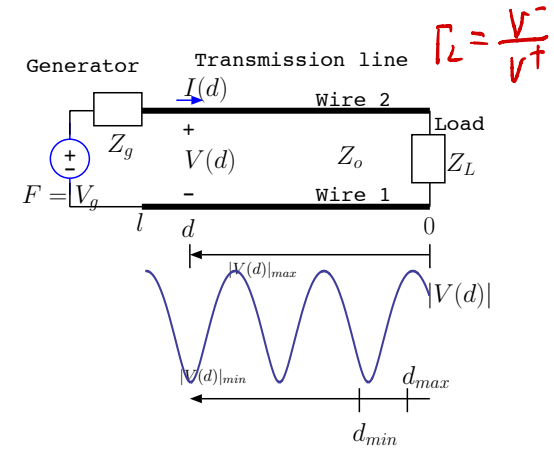
$$V^- e^{-j\beta d} \quad \uparrow \quad V^+ \Gamma_L e^{-j\beta d}$$



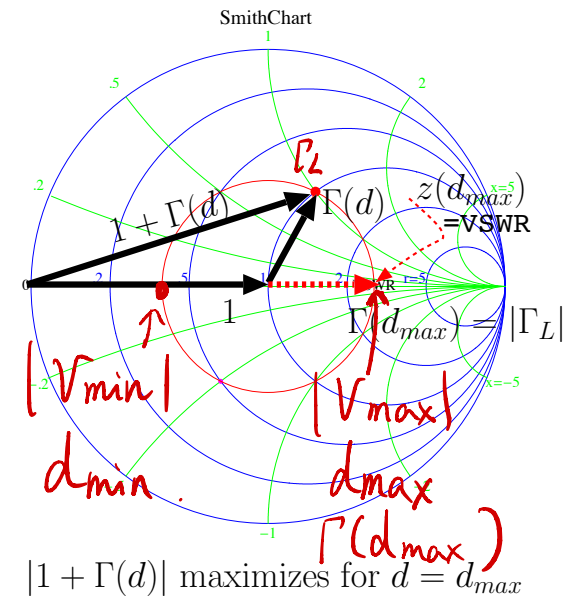Complex addition displayed graphically superposed on a Smith Chart



$|1 + \Gamma(d)|$  maximizes for  $d = d_{max}$

$|1 + \Gamma(d)|$  minimizes for  $d = d_{min}$   
such that  $\Gamma(d_{min}) = -\Gamma(d_{max})$

- These results can be most easily understood and verified graphically on a SC as shown in the margin.

- We define a parameter known as **voltage standing wave ratio**, or **VSWR** for short, by

$$\text{VSWR} \equiv \frac{|V(d_{max})|}{|V(d_{min})|} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \Leftrightarrow |\Gamma_L| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1}.$$

Notice that the VSWR and  $|\Gamma_L|$  form a **bilinear transform pair** just like

$$z = \frac{1 + \Gamma}{1 - \Gamma} \Leftrightarrow \Gamma = \frac{z - 1}{z + 1}.$$

$d_{max}$   
 $z(d_{max}) = \frac{1 + \Gamma(d_{max})}{1 - \Gamma(d_{max})}$

Since

$$\Gamma(d_{max}) = |\Gamma_L| \Rightarrow \text{VSWR} = \frac{1 + \Gamma(d_{max})}{1 - \Gamma(d_{max})},$$


this analogy between the transform pairs also implies that

★


$z(d_{max}) = \text{VSWR},$

as explicitly marked on the the SC shown in the margin . Consequently,

- the VSWR of any TL can be directly read off from its SC plot as the normalized impedance value  $z(d_{max})$  on constant- $|\Gamma_L|$  circle crossing the positive real axis of the complex plane.

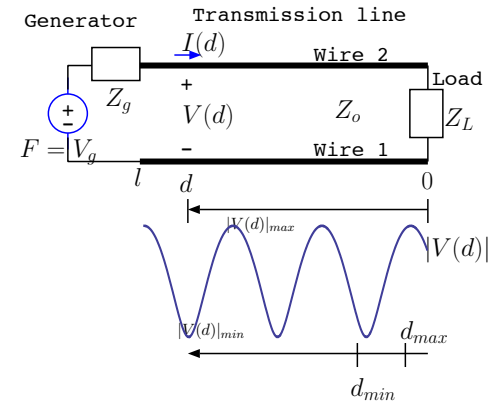

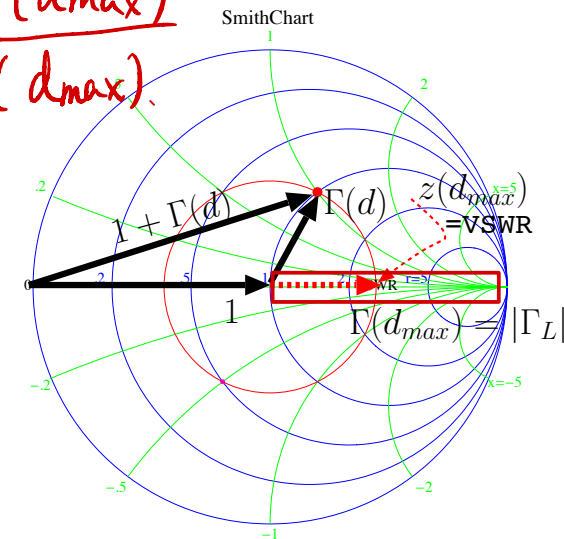Complex addition displayed graphically superposed on a Smith Chart



$|1 + \Gamma(d)|$  maximizes for  $d = d_{max}$

$|1 + \Gamma(d)|$  minimizes for  $d = d_{min}$   
such that  $\Gamma(d_{min}) = -\Gamma(d_{max})$

- The extreme values the VSWR can take are:

- VSWR=1 if  $|\Gamma_L| = 0$  and the TL carries no reflected wave.
- VSWR= $\infty$  if  $|\Gamma_L| = 1$  corresponding to having a short, open, or a purely reactive load that causes a total reflection.


Step 1: Find  $Z_L, \Gamma_L$  on SC.

$$\frac{Z_0}{Z_L} \left\} Z_L \right.$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Step 2: Draw a Circle  $|\Gamma_L|$

Step 3: Read VSWR

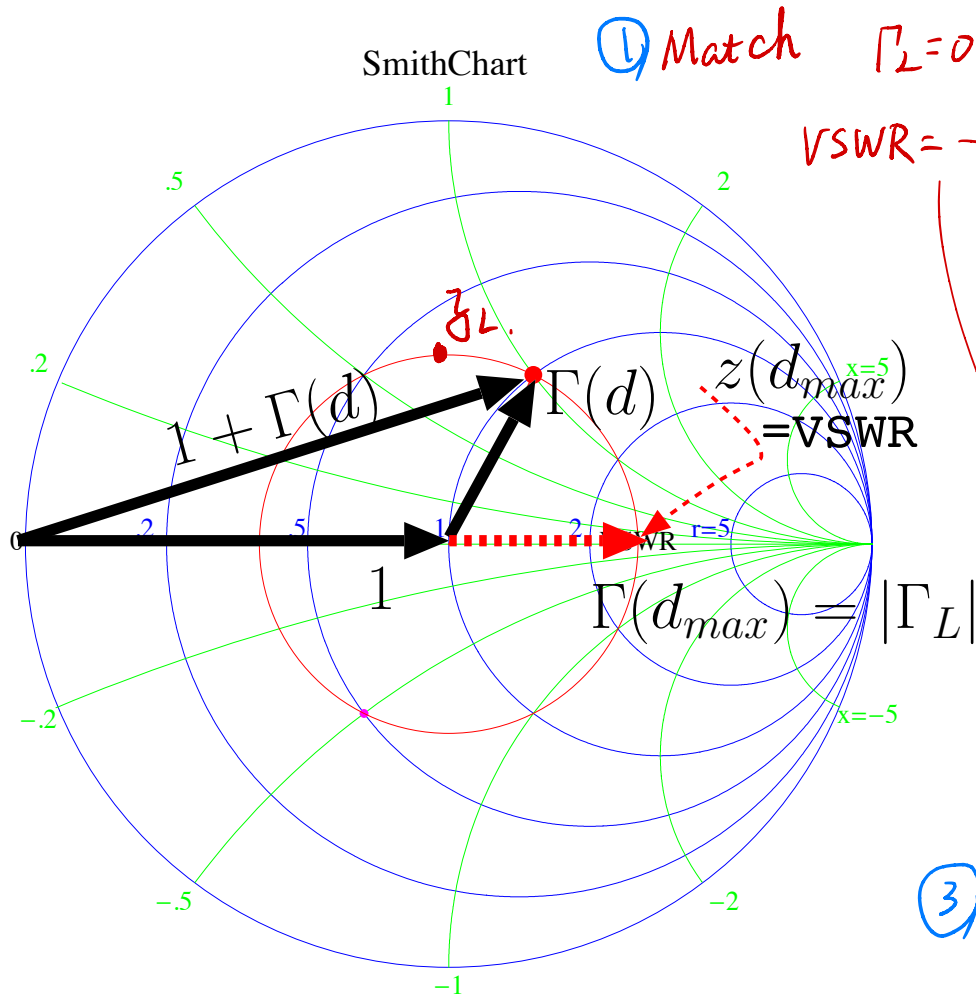

$|1 + \Gamma(d)|$  maximizes for  $d = d_{max}$

② open/short  $|\Gamma_L| = 1$

$$VSWR = \frac{1 + 1}{1 - 1} = \infty$$

$|1 + \Gamma(d)|$  minimizes for  $d = d_{min}$   
such that  $\Gamma(d_{min}) = -\Gamma(d_{max})$

③ reactive load  $Z_L = jX_L$ .  $|\Gamma_L| = 1$

$$VSWR = \infty$$



**Example 1:** An unknown load  $Z_L$  on a  $Z_o = 50 \Omega$  TL has

$$V(d_{min}) = 20 \text{ V}, \quad d_{min} = 0.125\lambda \quad \text{and} \quad \text{VSWR}=4.$$

Determine (a) the load impedance  $Z_L$ , and (b) the average power  $P_L$  absorbed by the load.

**Solution:**

- (a) As shown in the top SC in the margin,  $\text{VSWR}=4$  is entered in the SC as  $z(d_{max}) = 4 + j0$ , and constant  $|\Gamma_L|$  circle is then drawn (red circle) passing through  $z(d_{max}) = 4$ .

Right across  $z(d_{max}) = 4$  on the circle is  $z(d_{min}) = 0.25$ .

A counter-clockwise rotation from  $z(d_{min}) = 0.25$  by one fourth of a full circle corresponding to a displacement of  $d_{min} = 0.125\lambda$  (a full circle corresponds to a  $\lambda/2$  displacement) takes us to




$$z_L \approx 0.4706 - j0.8823$$

as shown in the second SC. Hence, this gives


$$Z_L = Z_o z_L = 50(0.4706 - j0.8823) = 23.53 - j44.12 \Omega.$$

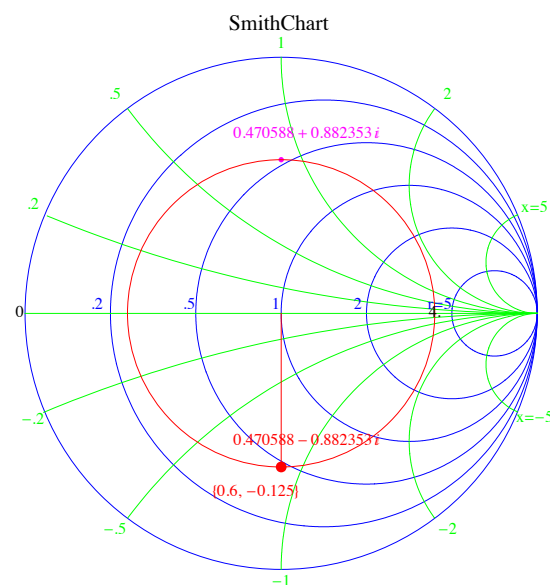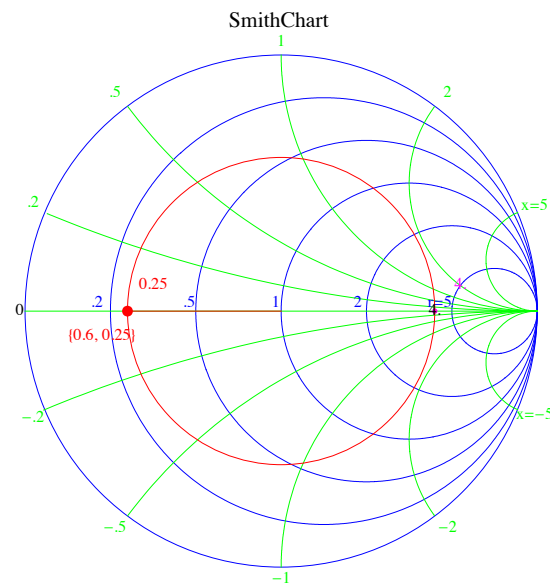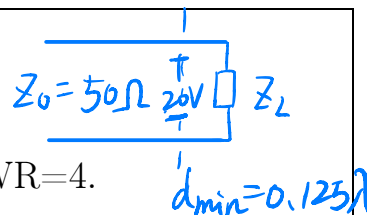- (b) We will calculate  $P_L$  by using  $V(d_{min})$  and  $I(d_{min})$ . Since

$$z(d_{min}) = 0.25 \quad \text{it follows that} \quad Z(d_{min}) = \frac{1}{4} 50 \Omega = 12.5 \Omega.$$





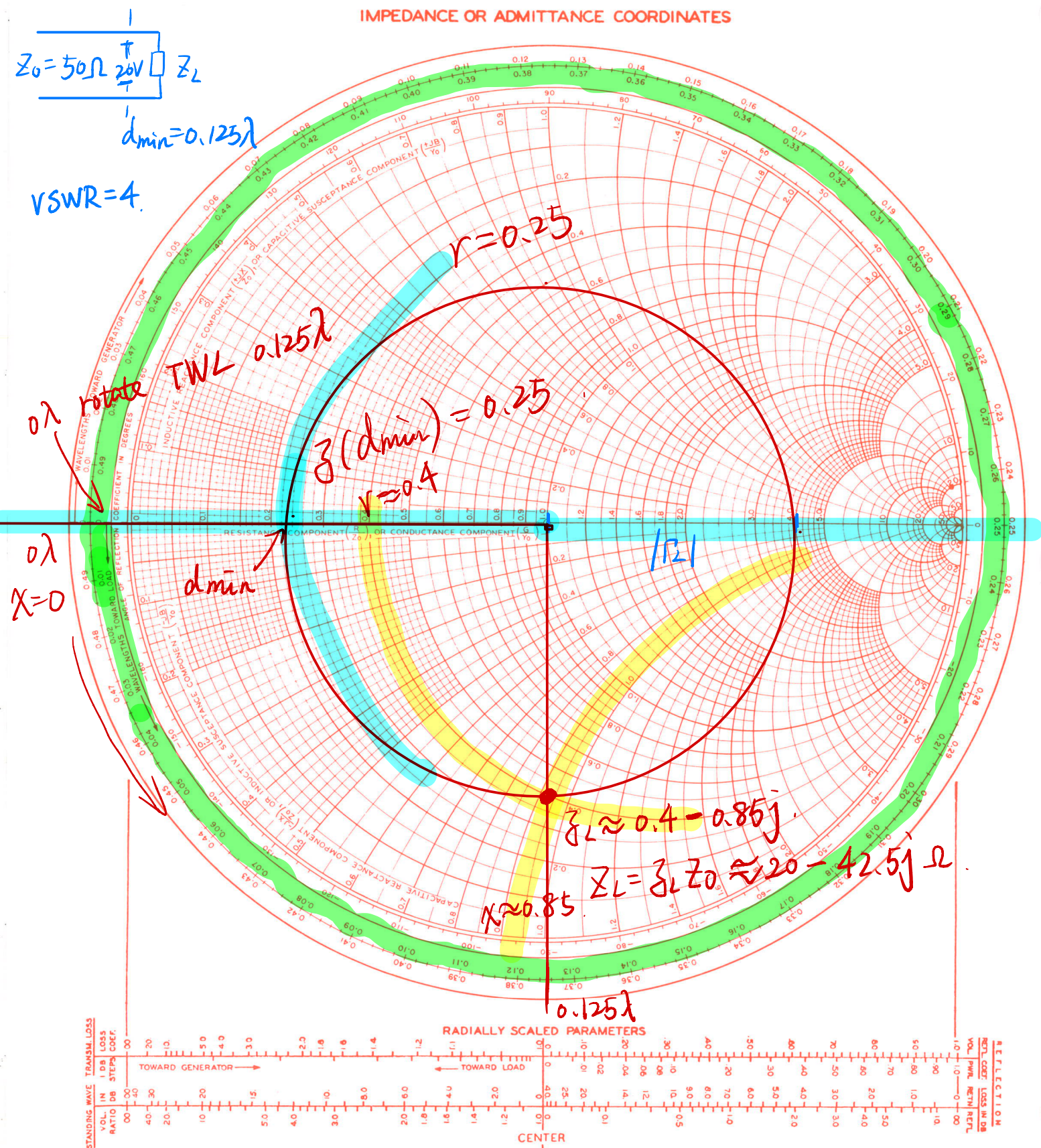

Therefore the voltage and current phasors at the voltage minimum location are


$$V(d_{min}) = 20 \text{ V} \quad \text{and} \quad I(d_{min}) = \frac{20 \text{ V}}{12.5 \Omega}.$$

Average power transported toward the load at  $d - d_{min}$  is, therefore,

$$P(d_{min}) = \frac{1}{2} \text{Re}\{V(d_{min})I(d_{min})^*\} = \frac{1}{2} \text{Re}\left\{20 \frac{20}{12.5}\right\} = \frac{400}{25} \text{ W} = 16 \text{ W}.$$

Since the TL is assumed to be lossless we should have

$$P_L = P(d_{min}) = 16 \text{ W}.$$

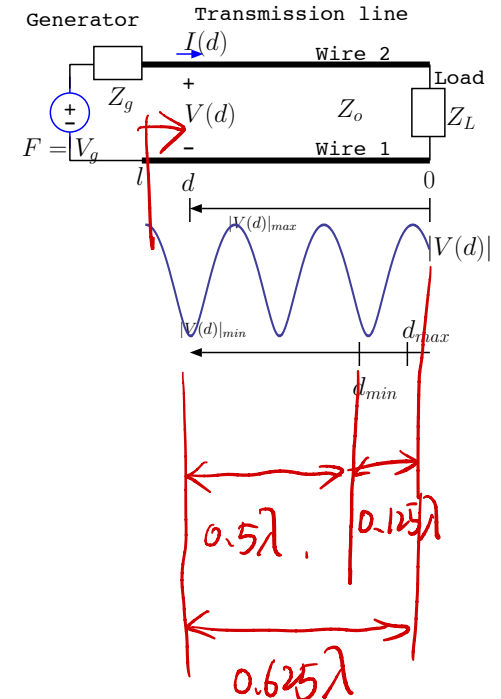

**Example 2:** If the TL circuit in Example 1 has  $l = 0.625\lambda$ , and a generator with an internal impedance  $Z_g = 50 \Omega$ , determine the generator voltage  $V_g$ .

**Solution:** Given that  $l = 0.625\lambda$  and  $d_{min} = 0.125\lambda$ , we note that there is just one half-wave transformer between  $l = 0.625\lambda$  and  $d_{min} = 0.125\lambda$ . Therefore

$$V_{in} = -V(d_{min}) = -20 \text{ V} \quad \text{and} \quad Z_{in} = Z(d_{min}) = 12.5 \Omega.$$

But also


$$V_{in} = V_g \frac{Z_{in}}{Z_g + Z_{in}}.$$

Consequently,

$$V_g = V_{in} \frac{Z_g + Z_{in}}{Z_{in}} = -20 \frac{50 + 12.5}{12.5} = -20 \frac{62.5}{12.5} = -100 \text{ V}.$$

$\frac{\lambda}{2}$  Transformer

$$\begin{cases} Z_{in} = Z_L \\ V_{in} = -V_L \end{cases}$$

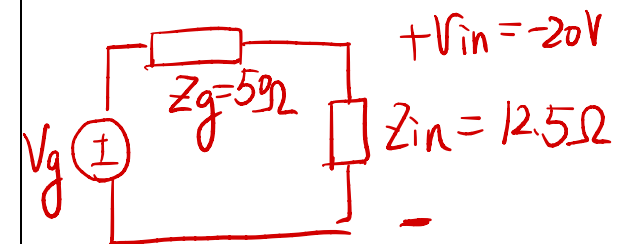

**Example 3:** Determine  $V^+$  and  $V^-$  in the circuit of Examples 1 and 2 above such that the voltage phasor on the line is given by

$$V(d) = V^+ e^{j\beta d} + V^- e^{-j\beta d}.$$

**Solution:** Looking back to Example 1 (also see the SC's in the margin), we first note that

$$|\Gamma_L| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1} = \frac{4 - 1}{4 + 1} = 0.6 = \Gamma(d_{\max}) = -\Gamma(d_{\min}).$$

Hence, evaluating  $V(d)$  at  $d = d_{\min}$ , we have

$$\begin{aligned} V(d_{\min}) &= V^+ e^{j\beta d_{\min}} (1 + \Gamma(d_{\min})) \\ &= V^+ (e^{j\frac{2\pi}{\lambda} \frac{\lambda}{8}}) (1 + (-0.6)) = 0.4 e^{j\frac{\pi}{4}} V^+ = 20 \text{ V}, \end{aligned}$$

from which

$$V^+ = 50 e^{-j\frac{\pi}{4}} \text{ V}.$$


$$\Gamma_L \equiv \frac{V^-}{V^+}.$$

Since

$$\Gamma_L = \Gamma(0) = \Gamma(d_{\min}) e^{j2\beta d_{\min}} = -0.6 e^{j\frac{\pi}{2}},$$

it follows that

$$V^- = \Gamma_L V^+ = -0.6 e^{j\frac{\pi}{2}} \times 50 e^{-j\frac{\pi}{4}} = -30 e^{j\frac{\pi}{4}} \text{ V}.$$

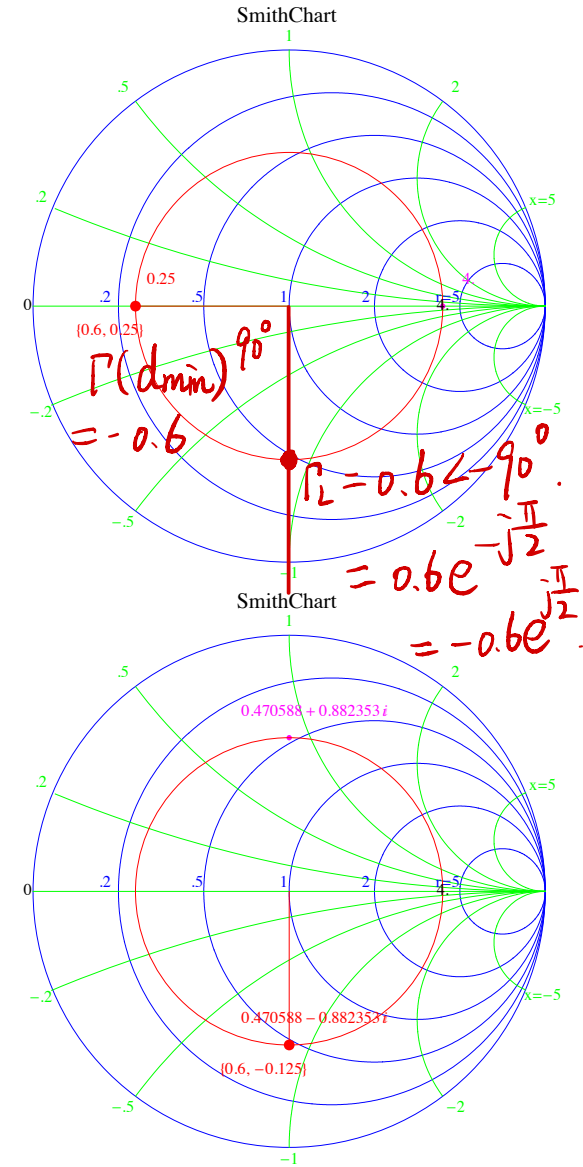



**Example 4:** Determine the load voltage and current  $V_L = V(0)$  and  $I_L = I(0)$  in the circuit of Examples 1-3 above.

**Solution:** In general,

$$V(d) = V^+ e^{j\beta d} - V^- e^{-j\beta d} \quad \text{and} \quad I(d) = \frac{V^+ e^{j\beta d} - V^- e^{-j\beta d}}{Z_o}.$$

Therefore,

$$V_L = V(0) = V^+ + V^- \quad \text{and} \quad I_L = I(0) = \frac{V^+ - V^-}{Z_o}.$$

Using  $Z_o = 50 \Omega$  and

$$V^+ = 50e^{-j\frac{\pi}{4}} \text{ V} \quad \text{and} \quad V^- = -30e^{j\frac{\pi}{4}} \text{ V}$$

from Example 3, we find that

$$V_L = 50e^{-j\frac{\pi}{4}} - 30e^{j\frac{\pi}{4}} \text{ V} \quad \text{and} \quad I_L = \frac{50e^{-j\frac{\pi}{4}} + 30e^{j\frac{\pi}{4}}}{50} = e^{-j\frac{\pi}{4}} + 0.6e^{j\frac{\pi}{4}} \text{ A}.$$

