

# ECE 329 Fields and Waves I

## Homework 14

Instructors: Chen, Goddard, Shao

Due May 4, 2023, 11:59 PM


### Homework Policy:

- Write your name and NetID on top of every page. This habit will help you in exams in the event of having loose page(s).
- Tag all the questions in Gradescope. Failure to do so results in a 5 points deduction.
- Cheating results in ZERO and 50% reduction in HW average on first offense. A 100% reduction in HW average on second offense.
- Please show detailed process for each problem instead of just an answer. No partial credits would be given otherwise. All answers should include units wherever appropriate.
- No late HW is accepted.
- Regrade requests are available one week following grade release.

**You are allowed to work with anyone else, but the work you submit should only belong to you. Note that if you have knowledge of a violation of the Honor Code, then you are obligated to report it. By submitting this homework, you are agreeing to the Honor Code: “I have neither given nor received unauthorized aid on this homework, nor have I concealed any violations of the Honor Code.”**

Question	Points	Score
1	8	
2	12	
3	10	
4	5	
5	15	
6	10	
7	10	
8	5	
Total:	75	

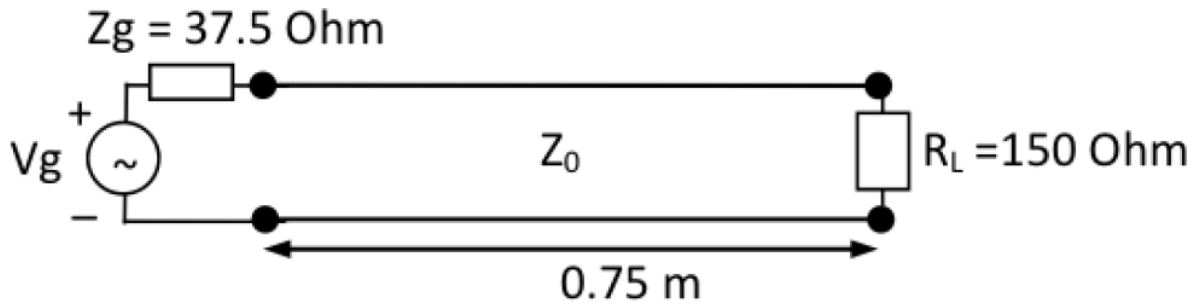1. In the transmission-line circuit shown below the voltage at the load is  $V_L = j15$  V. The operating frequency is 300 MHz. Given that the line is lossless of characteristic impedance of 75 Ohm with wave velocity  $3 \times 10^8$  m/s, calculate the following:
- (3 points) The time-average power dissipated at the load;
  - (5 points) The time-average power delivered by the generator.



2. A TL with characteristic impedance  $Z_o = 25 \Omega$  and length  $l = 0.45\lambda$  is terminated with a load  $Z_L = 100 \Omega$ .
- (5 points) Using a SC, determine (i) the load reflection coefficient  $\Gamma_L$ , (ii) the generalized reflection coefficient  $\Gamma(d)$  at  $d = l$ , and (iii) the input impedance  $Z(l)$  at the generator end. Hand in your S.C.  
**Hint:** you start by entering  $z_L = \frac{Z_L}{Z_o}$  in the SC. Express  $\Gamma_L$  and  $\Gamma(l)$  as complex numbers in polar form — i.e, as  $|\Gamma|\angle\theta$ .
  - (2 points) Using  $Z(l)$  from part (a), determine the voltage phasor  $V(l)$  at the generator end if the generator has an open circuit voltage phasor  $V_g = 10$  V and a Thevenin impedance  $Z_g = 50 \Omega$ .
  - (2 points) Given the result of (b), determine  $V^+$  such that  $V(d) = V^+(e^{j\beta d} + \Gamma_L e^{-j\beta d})$ .
  - (2 points) What is the load voltage phasor  $V(0)$  given the result of (c)?
  - (1 point) What is the corresponding load current  $I(0)$ ?
3. (10 points) A TL with characteristic impedance  $Z_o = 50 \Omega$  and length  $l = 0.4\lambda$  has an *open* termination at  $d = 0$  and a  $50 \Omega$  resistor connected between the TL conductors (a “shunt” connection) at  $d = 0.2\lambda$ . Use a SC to determine the input impedance and admittance of the line at the generator end, i.e.,  $Z(l)$  and  $Y(l)$ . Hand in your marked SC.  
**Hint:** first move by  $0.2\lambda$  from the load point (where you enter  $z(0)$  or  $y(0)$ ) toward generator on the SC, read off the corresponding  $y(d)$ , combine it in parallel with the shunt element, go back onto the SC with the normalized combined admittance, and move another  $0.2\lambda$  toward the generator...
4. (5 points) Two TL stubs of equal lengths  $l = 0.3\lambda$  and identical short terminations have unequal characteristic impedances of  $Z_o = 50 \Omega$  and  $100 \Omega$ . If the two stubs are connected in parallel at their input ports, what is the input admittance of the combined network. Use a SC to solve this problem and hand in your marked SC.

5. A transmission line having a characteristic impedance of  $50 \Omega$  is terminated by a load of unknown impedance  $Z_L$ . Measurements of the voltage amplitude  $|V(d)|$  along the line reveal a “standing wave pattern” with a maximum voltage of 8.4 V and a minimum voltage of 2.1 V.
- (2 points) What is the voltage standing wave ratio (SWR or VSWR) on the line?
  - (2 points) A voltage minimum is observed at distance  $d = 2.592\lambda$  from the load. What is then the distance  $d_{min}$  between the load and the first voltage minimum (closest to the load)? Hint: successive voltage minima are  $\frac{\lambda}{2}$  apart.
  - (3 points) Determine the magnitude and phase angle of the load reflection coefficient  $\Gamma_L$  using the S.C. and the results of parts (a) and (b). **Hint:** Given the VSWR, constant- $\Gamma$  circle passes through  $z = \text{VSWR} + j0$  on the S.C. The same location on the S.C. also correspond to the location of a voltage maximum on the line.
  - (2 points) Determine  $z_L$  using the S.C. and the value  $Z_L$  in  $\Omega$ 's.
  - (4 points) Determine  $|V^+|$  and  $|V^-|$ , the travelling wave amplitudes on the line.
  - (2 points) What is the average power (in W) delivered to the load?
6. We want to use a quarter-wave transformer to match a load  $Z_L$  to a T.L. with a characteristic impedance  $Z_o = 50 \Omega$ . The quarter wave transformer is to be inserted at a distance  $d_1$  away from the load.
- Determine  $d_1$  (in units of  $\lambda$ ) and the characteristic impedance  $Z_{qo}$  of the quarter wave transformer if
    - (2 points)  $Z_L = 100 \Omega$ ,
    - (2 points)  $Z_L = 100 + j100 \Omega$ .
  - For  $Z_L = 100 + j100 \Omega$ , what is VSWR in the region
    - (3 points)  $0 < d < d_1$ ,
    - (3 points)  $d_1 < d < d_1 + \frac{\lambda}{4}$ .
7. We want to use a single-stub tuner to match a load  $Z_L$  to a T.L. with a characteristic impedance  $Z_o = 50 \Omega$ . A shorted-stub is to be connected at a distance  $d_1$  away from the load.
- (6 points) Determine  $d_1$  (in units of  $\lambda$ ) and the length  $d_s$  of the shorted stub if  $Z_L = 100 + j100 \Omega$  and the characteristic impedance of the stub is  $50 \Omega$ .
  - (4 points) Repeat (a) if the characteristic impedance of the stub is  $100 \Omega$ .

8. (5 points) Please go to <https://tinyurl.com/33zam9rc> to fill out the informal early feedback form. Please take a screenshot that looks like the following picture and submit the screenshot as the solution.

