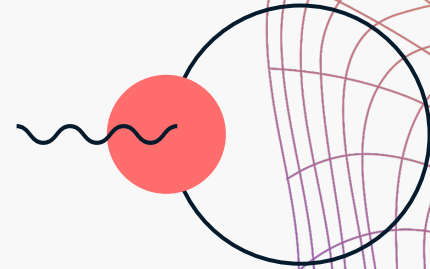





ECE329: Tutorial Session 13

December 3rd, 2024



Resonance

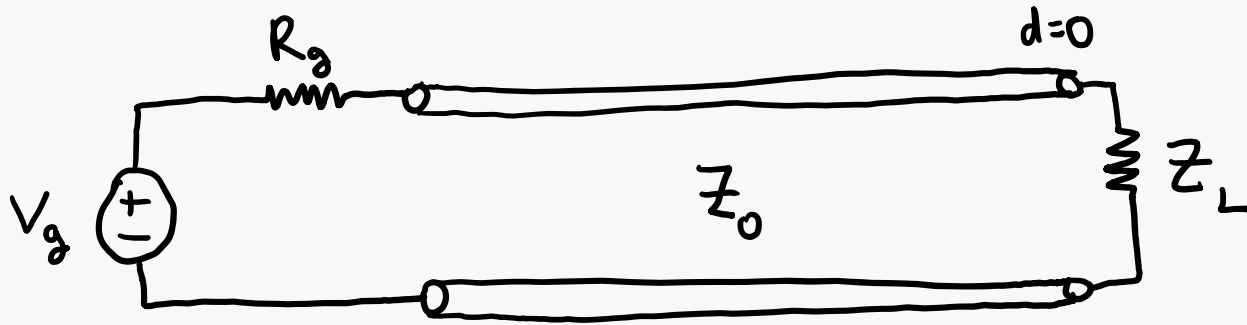

What if $Z_L = 0$?

What if $Z_L = \infty$?


Resonance

Type	Input	Output	T.L. Length
Series	Short	Short	$\frac{n\lambda}{2}$, n integer
Series	Short	Open	$\frac{n\lambda}{4}$, n odd integer
Parallel	Open	Short	$\frac{n\lambda}{4}$, n odd integer
Parallel	Open	Open	$\frac{n\lambda}{2}$, n integer

Problem 1: Resonance

Length of TL: 3m. $v = c$.

Load is shorted.

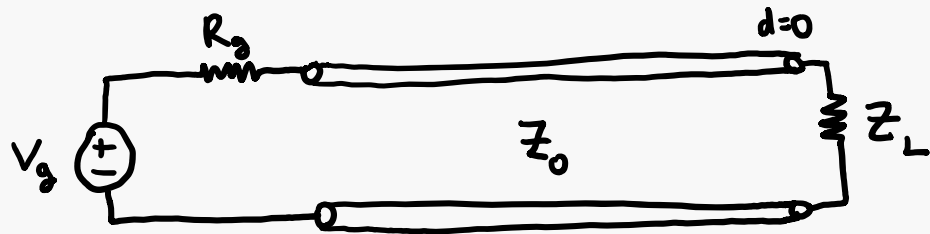


What input frequencies make Z_{in} equivalent to a short circuit?

What input frequencies make Z_{in} equivalent to an open circuit?

Problem 2: Resonance

$$v = c. f = 3 * 10^8 \text{ Hz.}$$


Load is open circuit.

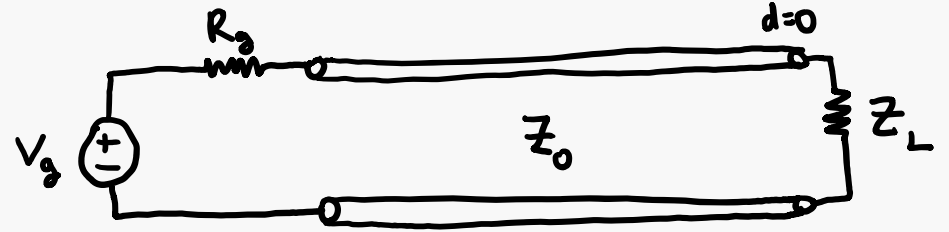

What lengths of TL make Z_{in} equivalent to a short circuit?

What lengths of TL make Z_{in} equivalent to an open circuit?

Last Week: Half -Wave Transformer

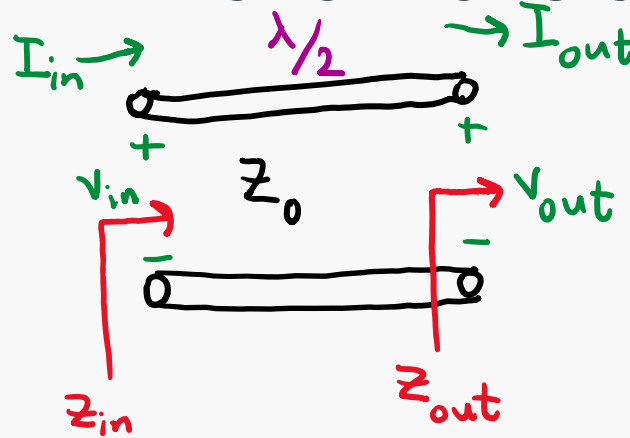


Allows you to 'crawl' up (or down) a TL in $\frac{\lambda}{2}$ steps.

$$V_{in} = -V_{out}$$

$$I_{in} = -I_{out}$$

$$Z_{in} = Z_{out}$$

Last Week: Quarter -Wave Transformer

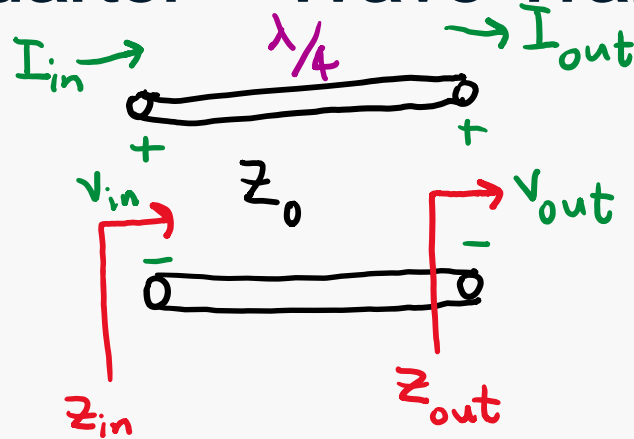


Allows you to 'crawl' up (or down) a TL in $\frac{\lambda}{4}$ steps.

$$V_{in} = jI_{out}Z_0$$

$$I_{in} = \frac{jV_{out}}{Z_0}$$


$$Z_{in} = \frac{Z_0^2}{Z_{out}}$$

This Week: Smith Charts!

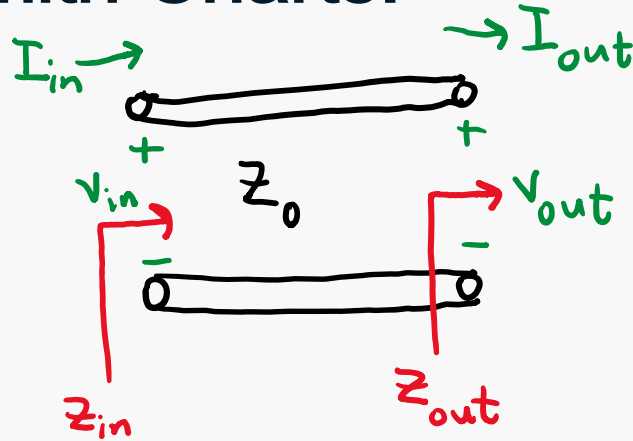


Allows you to 'crawl' up (or down) any TL of any length!


Smith Charts: Intro

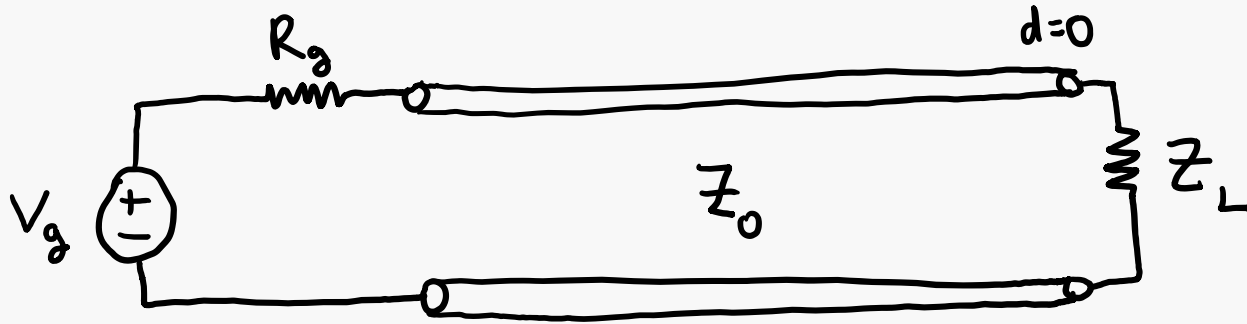


Smith Charts: Intro

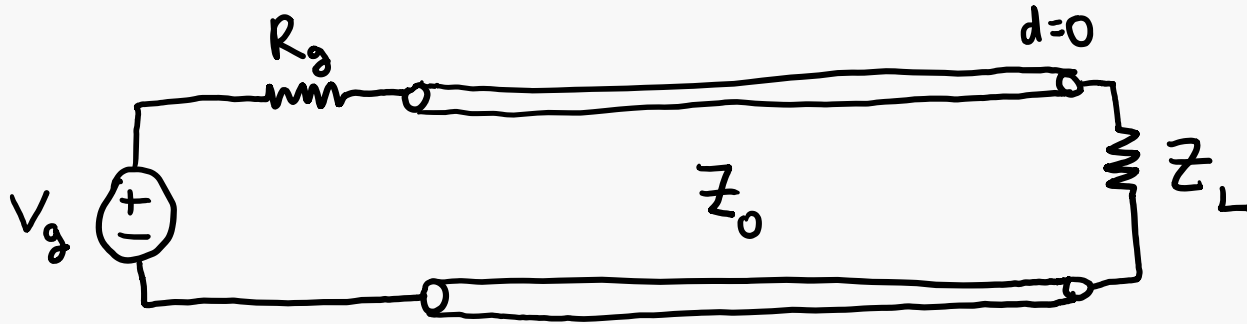

Smith Charts: Intro

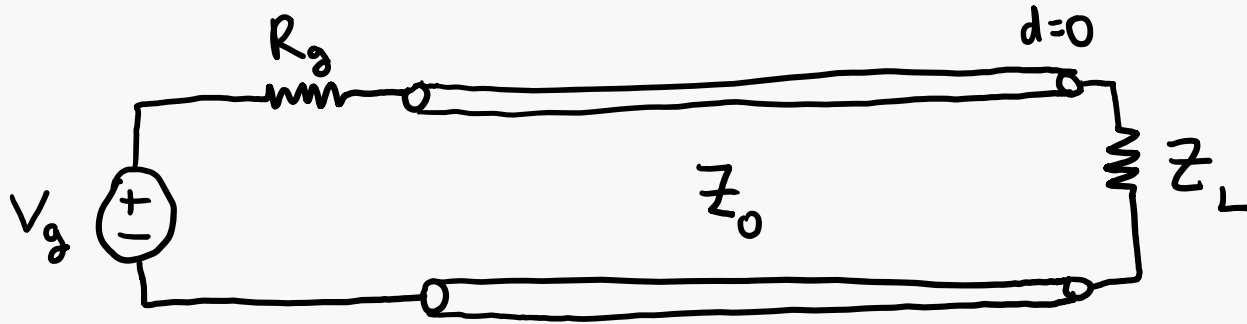

Smith Charts: Intro

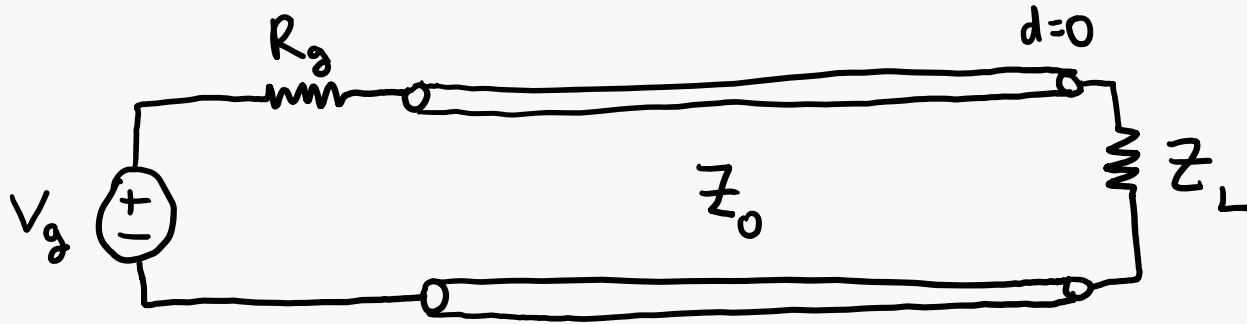




Problem 3

Eric protests – “I thought the ratio between the voltage and current on the transmission line was always the characteristic impedance of the transmission line, namely Z_0 !”


Is Eric wrong?



Smith Charts: Intro

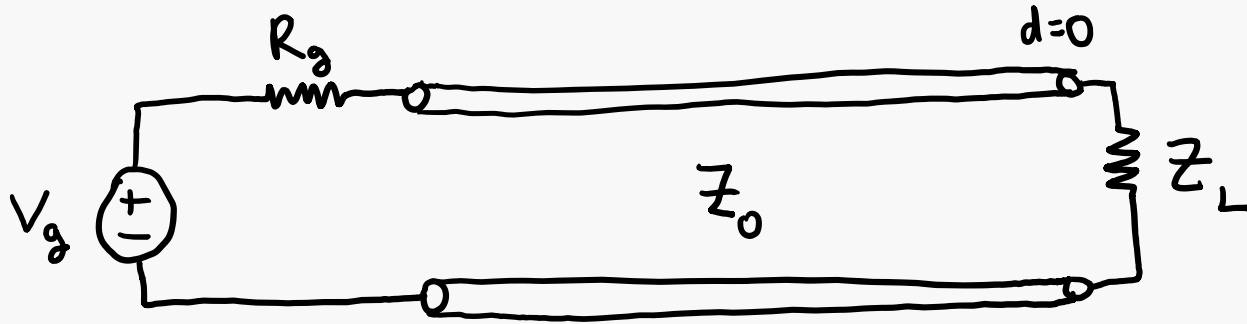

Smith Charts: Intro

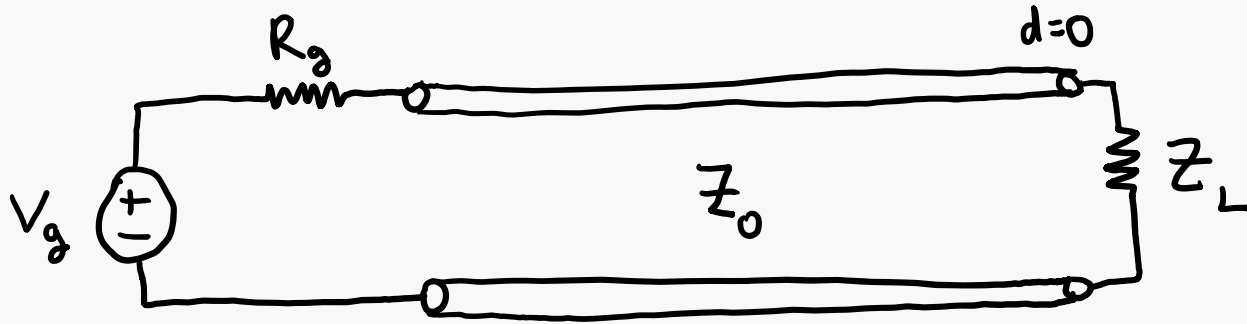



Problem 4: Pivotal Point 1

What does the origin of the Smith Chart correspond to in terms of Γ ?

What does the origin of the Smith Chart correspond to in terms of z ?

What does the origin of the Smith Chart correspond to as a load?





Problem 4: Pivotal Point 2

What does the leftmost point of the Smith Chart correspond to in terms of Γ ?

What does the leftmost point of the Smith Chart correspond to in terms of z ?

What does the leftmost point of the Smith Chart correspond to as a load?





Problem 4: Pivotal Point 3

What does the rightmost point of the Smith Chart correspond to in terms of Γ ?

What does the rightmost point of the Smith Chart correspond to in terms of z ?

What does the rightmost point of the Smith Chart correspond to as a load?





Problem 5: Devious Details 1

Evan tells you that at the load end of the transmission line he's at angle 0 on the Smith Chart. He then walks 3 meters toward the input and asks what angle we're at now.

What information are you missing to solve this problem?


Why is it important?





Problem 5: Devious Details 2

Evan starts at the load and walks $\lambda/2$ distance towards the input. How many degrees did he walkthrough on the Smith Chart? Why?






Problem 5: Devious Details 3


Sasha receives a transmission line problem with some load impedance and some intrinsic impedance. She first normalizes the load impedance, enters it on the Smith Chart, and then draws a constant Γ circle that passes through the origin and the point she drew.

Why did she do each of these three steps?



Problem 5: Devious Details 4

Eric finds the input impedance of some transmission line setup. He enters it on the Smith Chart and finds the phase and magnitude of Γ at that point. What is the significance of this Γ ?

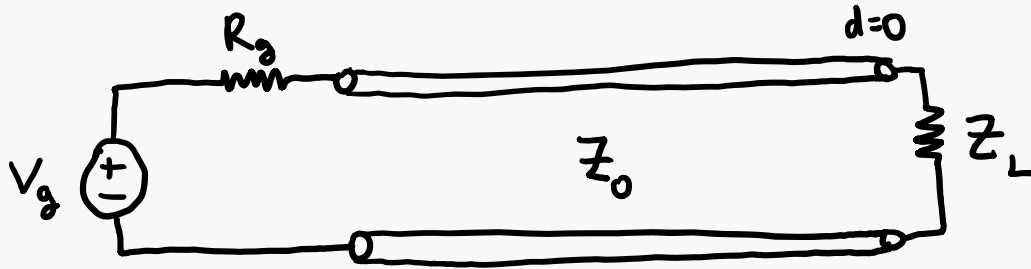




Problem 5: Devious Details 5

When travelling towards the source Sasha always rotates clockwise along the Smith Chart. Why?

If Sasha instead travels towards the load, then which direction should she rotate?





Problem 5: Devious Details 6

Does the Smith Chart yield steady state solutions, transient solutions, or both?



Problem 4: Example Smith Chart


TL length = 5m.

$v = c, f = 100\text{MHz}$.

$Z_L = 150 + j150\Omega, Z_0 = 50\Omega, R_g = 25\Omega.$

$V_g = 10e^{\frac{j\pi}{4}} \text{ V}$

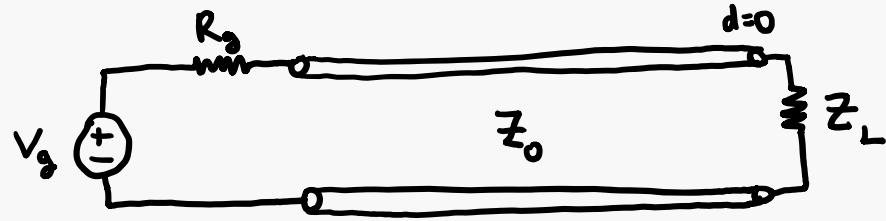Find $\Gamma_L, Z_{in}, V_{in}, I_{in}$. How would you find $V(0)$?



Midterm 1 equations, in one place

$$\vec{F} = \frac{q_1 q_2}{4\pi\epsilon_0 r^2} \hat{r}$$

$$\vec{F} = q_1 \vec{E} + q_1 (\vec{v}_1 \times \vec{B})$$

$$\vec{E} = \frac{q_2}{4\pi\epsilon_0 r^2} \hat{r}$$

$$\hat{n} \cdot (\vec{D}_1 - \vec{D}_2) = \rho_s$$

$$\hat{n} \times (\vec{E}_1 - \vec{E}_2) = 0$$

$$\hat{n} \cdot (\vec{P}_1 - \vec{P}_2) = -\rho_{b,s}$$

$$\epsilon \oint \vec{E} \cdot d\vec{S} = Q_{\text{enclosed}}$$

$$\oint \vec{D} \cdot d\vec{S} = Q_{\text{enclosed}}$$

$$\iiint \rho dV = Q_{\text{enclosed}}$$

$$\oint \vec{B} \cdot d\vec{S} = 0$$

$$I = \oint \vec{J} \cdot d\vec{S} = -\frac{\partial Q_{\text{enclosed}}}{\partial t}$$

$$\epsilon = \epsilon_0 (1 + \chi_e)$$

$$\vec{P} = \epsilon_0 \chi_e \vec{E}$$

$$\vec{D} = \epsilon_0 \vec{E} + \vec{P} = \epsilon \vec{E}$$

$$\vec{J} = \sigma \vec{E}$$

$$\rho_b = -\nabla \cdot \vec{P}$$

$$\nabla \cdot \epsilon_0 \vec{E} = \rho_f + \rho_b$$

$$\begin{aligned} \nabla \cdot \vec{D} &= \rho \\ \nabla \cdot \vec{J} &= -\frac{\partial \rho}{\partial t} \\ -\nabla^2 V &= \frac{\rho}{\epsilon} \end{aligned}$$

$$\nabla \times \vec{E} = 0$$

$$\vec{E} = -\nabla V$$

$$\oint \vec{E} \cdot d\vec{l} = 0$$

$$V_{ab} = V(b) - V(a) = -\int_a^b \vec{E} \cdot d\vec{l}$$

$$\oint \vec{D} \cdot d\vec{S} = \iiint \nabla \cdot \vec{D} dV$$

$$\oint \vec{E} \cdot d\vec{l} = \iint (\nabla \times \vec{E}) \cdot d\vec{S}$$

$$\int_a^b \nabla V \cdot d\vec{l} = V(b) - V(a)$$



Midterm 2 equations, in one place

$$\vec{B} = \frac{\mu I}{2\pi r} \hat{\phi}$$

$$d\vec{B} = \frac{\mu I d\vec{\ell} \times \hat{r}}{4\pi r^2}$$

$$\oint_C \vec{H} \cdot d\vec{\ell} = \iint_S \vec{J} \cdot d\vec{S}$$

$$\oint_C \vec{B} \cdot d\vec{\ell} = \mu I_{\text{encl}}$$

$$\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t}$$

$$\nabla \cdot \vec{B} = 0$$

$$\Psi = \iint_S \vec{B} \cdot d\vec{S}$$

$$-\frac{d}{dt} \iint_S \vec{B} \cdot d\vec{S} = \oint_C \vec{E} \cdot d\vec{\ell}$$

$$\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$$

$$\oint_C \vec{E} \cdot d\vec{\ell} = \varepsilon$$

$$\varepsilon = \frac{W}{q} = \oint_C \frac{\vec{F}}{q} \cdot d\vec{\ell}$$

$$\Psi = LI$$

$$\varepsilon = IR$$

$$v = \frac{\omega}{\beta} = \lambda f = \frac{1}{\sqrt{\mu\varepsilon}}$$

$$\omega = 2\pi f = \frac{2\pi}{T}$$

$$\eta = \frac{\sqrt{\mu}}{\sqrt{\varepsilon}}$$

$$\beta = \omega\sqrt{\mu\varepsilon}$$

$$\nabla^2 \vec{E} = \mu\varepsilon \frac{\partial^2 \vec{E}}{\partial t^2}$$

$$\vec{S} = \vec{E} \times \vec{H}$$

$$\vec{S} = \vec{E} \times \vec{H}^*$$

$$\langle \vec{S} \rangle = \frac{1}{2} \text{Re}\{\vec{E} \times \vec{H}^*\}$$

$$\frac{\partial}{\partial t} \left(\frac{1}{2} \varepsilon \vec{E} \cdot \vec{E} + \frac{1}{2} \mu \vec{H} \cdot \vec{H} \right) + \nabla \cdot \vec{S} + \vec{J} \cdot \vec{E} = 0$$

$$Q = CV$$

$$G = \frac{\sigma}{\varepsilon} C \quad R = \frac{1}{G}$$

$$\vec{J}_b = \frac{\partial \vec{P}}{\partial t} + \nabla \times \vec{M}$$

$$\vec{H} = \frac{\vec{B}}{\mu_0} - \vec{M}$$

$$\vec{M} = \chi_m \vec{H}$$

$$\vec{B} = \mu_0 \mu_r \vec{H} = \mu \vec{H}$$

$$\text{Acos}(\omega t - \beta x) \hat{z} \leftrightarrow A e^{-j\beta x} \hat{z}$$

$$\hat{n} \cdot (\vec{B}_1 - \vec{B}_2) = 0$$

$$\hat{n} \times (\vec{H}_1 - \vec{H}_2) = \vec{J}_s$$

$$\hat{n} \times (\vec{M}_1 - \vec{M}_2) = \vec{J}_{b,s}$$

Midterm 3 equations, in one place

Waves:

	Condition	β	α	$ \eta $	τ	$\lambda = \frac{2\pi}{\beta}$	$\delta = \frac{1}{\alpha}$
Perfect dielectric	$\sigma = 0$	$\omega\sqrt{\epsilon\mu}$	0	$\sqrt{\frac{\mu}{\epsilon}}$	0	$\frac{2\pi}{\omega\sqrt{\epsilon\mu}}$	∞
Imperfect dielectric	$\frac{\sigma}{\omega\epsilon} \ll 1$	$\sim \omega\sqrt{\epsilon\mu}$	$\beta\frac{1}{2}\frac{\sigma}{\omega\epsilon} = \frac{\sigma}{2}\sqrt{\frac{\mu}{\epsilon}}$	$\sim \sqrt{\frac{\mu}{\epsilon}}$	$\sim \frac{\sigma}{2\omega\epsilon}$	$\sim \frac{2\pi}{\omega\sqrt{\epsilon\mu}}$	$\frac{2}{\sigma}\sqrt{\frac{\epsilon}{\mu}}$
Good conductor	$\frac{\sigma}{\omega\epsilon} \gg 1$	$\sim \sqrt{\pi f\mu\sigma}$	$\sim \sqrt{\pi f\mu\sigma}$	$\sqrt{\frac{\omega\mu}{\sigma}}$	45°	$\sim \frac{2\pi}{\sqrt{\pi f\mu\sigma}}$	$\sim \frac{1}{\sqrt{\pi f\mu\sigma}}$
Perfect conductor	$\sigma = \infty$	∞	∞	0	-	0	0

$$\Gamma = \frac{\eta_2 - \eta_1}{\eta_2 + \eta_1} \quad \tau = \frac{2\eta_2}{\eta_2 + \eta_1} = 1 + \Gamma$$

$$v = \frac{\omega}{\beta} = \lambda f$$

$$\nabla^2 \vec{E} = (j\omega\mu)(\sigma + j\omega\epsilon)\vec{E}$$

TLs:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\tau_g = \frac{Z_0}{R_g + Z_0}$$

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0}$$

$$\Gamma_{jk} = \frac{Z_k - Z_j}{Z_k + Z_j}$$

$$\tau_{jk} = 1 + \Gamma_{jk}$$

Half-wave:

$$V_{in} = -V_{out}$$

$$I_{in} = -I_{out}$$

$$Z_{in} = Z_{out}$$

Quarter-wave:

$$V_{in} = jI_{out}Z_0$$

$$I_{in} = \frac{jV_{out}}{Z_0}$$

$$Z_{in} = \frac{Z_0^2}{Z_{out}}$$

$$\cos(\theta) = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$$\sin(\theta) = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$



Final exam equations, in one place

$$V(d) = V^+ e^{j\beta d} (1 + \Gamma_L e^{-j2\beta d})$$

$$\Gamma(d) = \Gamma_L e^{-j2\beta d}$$

$$z(d) = \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

$$y(d) = \frac{1}{z(d)}$$

$$z(d) = \frac{Z(d)}{Z_0}$$

Resonance:

Type	Input	Output	T.L. Length
Series	Short	Short	$\frac{n\lambda}{2}$, n integer
Series	Short	Open	$\frac{n\lambda}{4}$, n odd integer
Parallel	Open	Short	$\frac{n\lambda}{4}$, n odd integer
Parallel	Open	Open	$\frac{n\lambda}{2}$, n integer



Units

Charge Q : C

Current I : A

Electric field strength \vec{E} : N/C or V/m

Electric flux density \vec{D} : C/m²

Polarization field \vec{P} : C/m²

Electric potential V : V

Capacitance C : F

Magnetic flux density \vec{B} : T or Wb/m²

Magnetic field strength \vec{H} : A/m

Magnetic flux Ψ : Wb

Electromotive force ε : V

Inductance L : H

Electric permittivity ϵ : F/m

Magnetic permeability μ : H/m

Conductivity σ : Si/m

Charge density ρ : C/m³

Surface charge density ρ_s : C/m²

Current density \vec{j} : A/m²

Intrinsic impedance η : Ohm

Wave number β : rad/m

Characteristic impedance Z : Ohm



Office Hours

Any questions?

