

ECE 330 homework assignment #1 (In class quiz – Fri, Sep 8)

Text problem 2.1 (Partial answer: 0.707 leading)

Text problem 2.2 (Partial answers: -250, -500, 500, 0, 150, 1900, -150)

Text problem 2.8

Text problem 2.9

Text problem 2.10 (Partial answer: 100 Amps)

Text problem 2.11

Special problem #1

A single-phase source is supplying passive loads through two wires (typically called a feeder). The impedance of each wire is $0.05 + j 0.05$ Ohm. The load is connected between the two wires at the far end. The load current (which is also the feeder current) is 75 Amps (RMS).

- a) What is the source voltage that you need in order to have 120 Volts (RMS) across the load when the power factor of the load is unity? (Answer: 128V)
- b) Repeat for the case where the load power factor is 0.707 lagging (Answer: 131V).
- c) Repeat for the case where the load power factor is 0 leading (Answer: 113V).

Special problem #2

Three single-phase loads are connected in parallel across a 60Hz source of 240 Volts.

Load #1: 6 KVA at 0.8 power factor lag

Load #2: 4 KW at 0.9 power factor lag

Load #3: 13 Amps at unity power factor

- a) Find the total complex power consumed by these three loads.
- b) Find the source current magnitude (Answer: 54.76 Amps)
- c) Find the value of capacitive VARS that should be added in parallel to these three loads to make the overall power factor 0.95 lag. (Answer: 1,619 Vars)