

ECE330: Power Circuits & Electromechanics

Lecture 10. Ideal transformers

Prof. Richard Y. Zhang
Univ. of Illinois at Urbana-Champaign
ryz@illinois.edu



1

Schedule

*Mon 9/23: Coupled coils

- Wed 9/25: Ideal transformers
- **Friday 9/27: Review + Quiz 4**
- Mon 9/30: Review
- Wed 10/2: Review
- **Thursday 10/3: Mid-term Exam 1**
- Friday 10/4: No class

2


War of Currents (circa 1880-1900)



Edison



Westinghouse

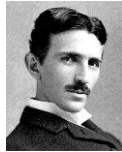


Tesla

- 1880 Edison receives patent for lightbulb, founds the Edison Illuminating Company. (Today: ConEd)
- 1888 Tesla joins Westinghouse to commercialize AC.
- 1888 Edison: "It will never be free from danger." IN MEMO CONCERNING THE WESTINGHOUSE AC SYSTEM.
- 1893 Westinghouse wins contract for Chicago World Fair.
- 1908 Edison: "Tell your father I was wrong." TO GEORGE STANLEY, THE SON OF WILLIAM STANLEY WHO HAD INVENTED AN AC TRANSFORMER FOR WESTINGHOUSE.



3

The Transformer: AC's secret weapon

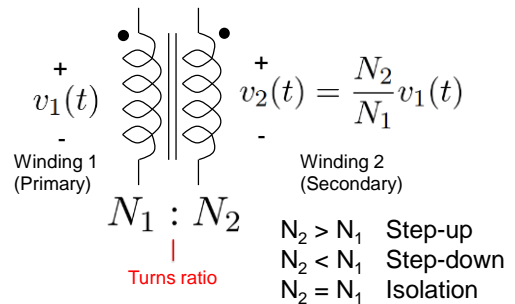

4

Transformers in the AC power system

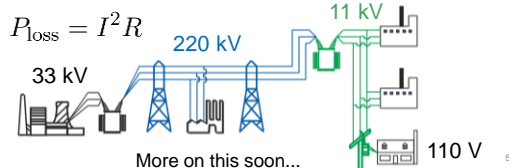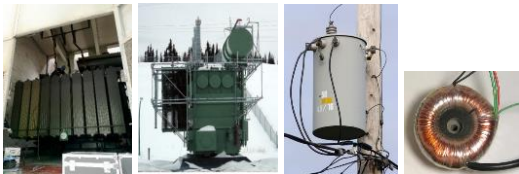

5

Genius is one percent inspiration and ninety-nine percent perspiration.

---Thomas Edison (c. 1903)



Just a little theory and calculation would have saved him ninety percent of his labor.

---Nikola Tesla (1931)


6

Today

- Ideal transformer model
- Apparent impedance
- Practical transformer model

7

Transformer (ideal)

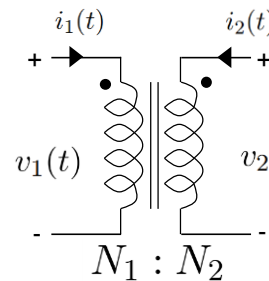

$$\text{Turns ratio} \\ a = N_1/N_2$$

Definition (ideal transformer)

$$\frac{v_1(t)}{v_2(t)} = \frac{N_1}{N_2} = a$$

(Transformation ratio)

$$P_{\text{in}} = P_{\text{out}} = 0$$

(Power conservation)

Implies current transformation

$$0 = v_1(t)i_1(t) + v_2(t)i_2(t)$$


$$= v_1(t) \left[i_1(t) + \frac{N_2}{N_1} i_2(t) \right]$$

$$= i_1(t) + \frac{N_2}{N_1} i_2(t) \quad \text{Minus sign!!}$$

$$\frac{i_1(t)}{i_2(t)} = -\frac{N_2}{N_1} = -\frac{1}{a}$$

8

Transformer (ideal)

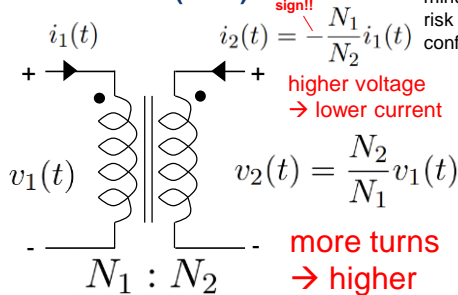

$$i_2(t) = -\frac{N_1}{N_2} i_1(t)$$

Minus sign!!

higher voltage
→ lower current


$$v_2(t) = \frac{N_2}{N_1} v_1(t)$$

more turns
→ higher voltage

Can reverse
minus sign at
risk of
confusion

9

Example 1. High voltage transmission

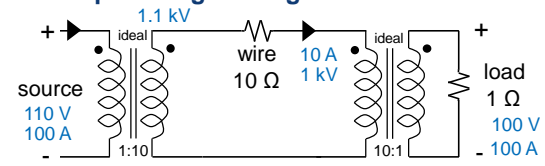

$$v_{\text{load}}(t) = \sqrt{2}(100) \cos \omega t \text{ [V]}$$

$$i_{\text{wire}}(t) = ? \text{ [A]}$$

$$v_{\text{source}}(t) = ? \text{ [V]}$$

$$i_{\text{source}}(t) = ? \text{ [A]}$$

~~A) $\sqrt{2} \cos \omega t$~~

~~A) $\sqrt{2}(100) \cos \omega t$~~

~~A) $\sqrt{2} \cos \omega t$~~

~~B) $\sqrt{2}(10) \cos \omega t$~~

~~B) $\sqrt{2}(110) \cos \omega t$~~

~~B) $\sqrt{2}(10) \cos \omega t$~~

~~C) $\sqrt{2}(100) \cos \omega t$~~

~~C) $\sqrt{2}(200) \cos \omega t$~~

~~C) $\sqrt{2}(100) \cos \omega t$~~

~~D) $\sqrt{2}(1000) \cos \omega t$~~

~~D) $\sqrt{2}(1100) \cos \omega t$~~


~~D) $\sqrt{2}(1000) \cos \omega t$~~

~~E) $\sqrt{2}(10000) \cos \omega t$~~

~~E) $\sqrt{2}(2000) \cos \omega t$~~


~~E) $\sqrt{2}(10000) \cos \omega t$~~

Why Edison lost the war (1890s)

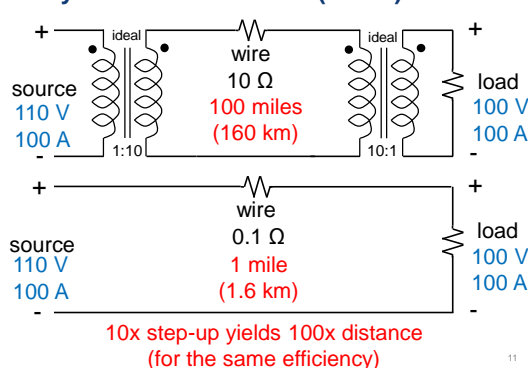

11

Why Edison lost the war (1960s)

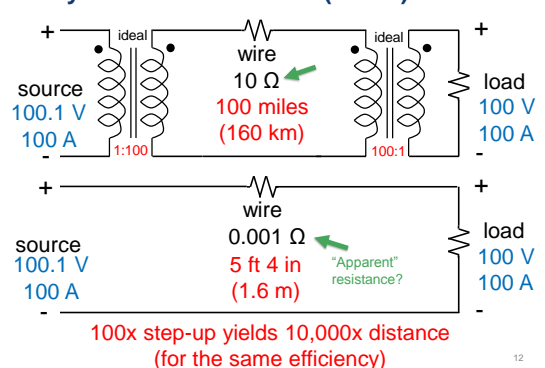


12

Today

- Ideal transformer model
- Apparent impedance
- Practical transformer model


13

Ideal transformer with resistance

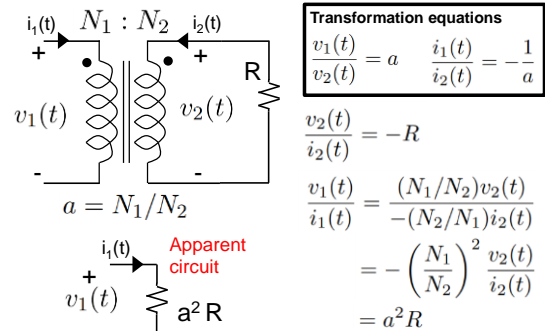


14

Ideal transformer with impedance

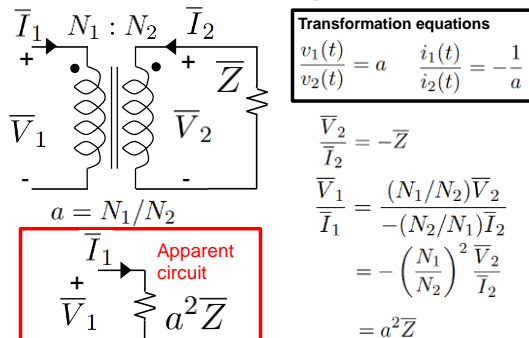


15


Example 2. Warm-up

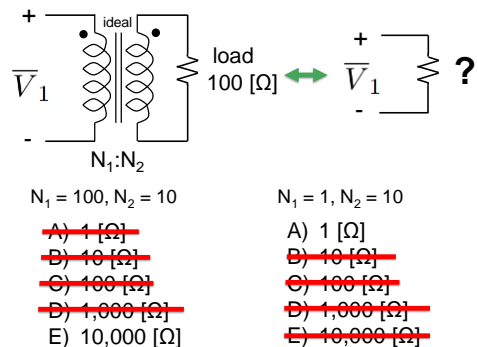Hint: $a = N_1/N_2$ 


Example 3. High voltage transmission

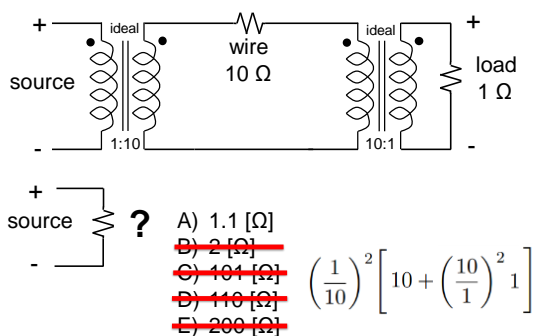


Example 4. Power transfer

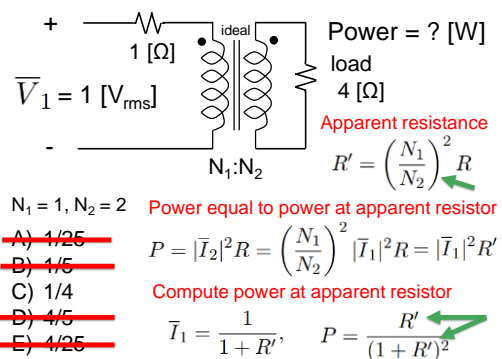

Maximum power transfer

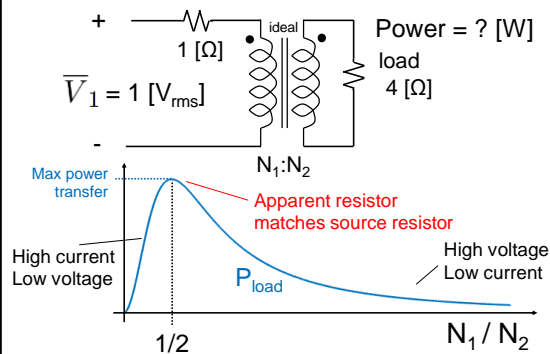

Impedance matching

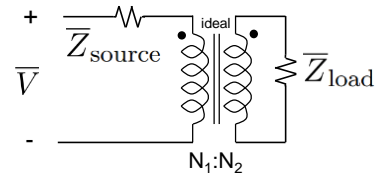

Theorem. Maximum power transfer if ratio $N_1:N_2$ satisfies

$$|\bar{Z}_{\text{source}}| = \left(\frac{N_1}{N_2} \right)^2 |\bar{Z}_{\text{load}}|$$


Apparent load impedance

Today

- Ideal transformer model
- Apparent impedance
- Practical transformer model

21


So far: Ideal transformers

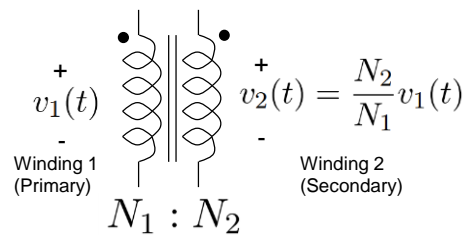


Real transformers far from ideal
Must use practical model





22

Mutual inductance

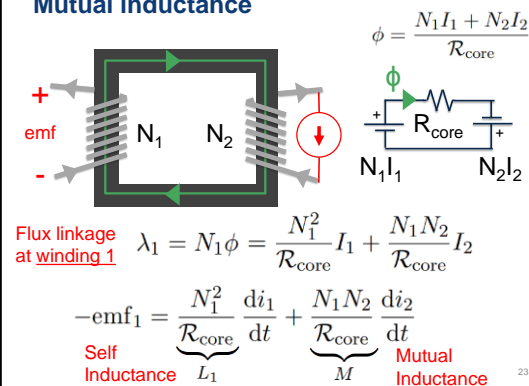

Circuit models of mutual inductance

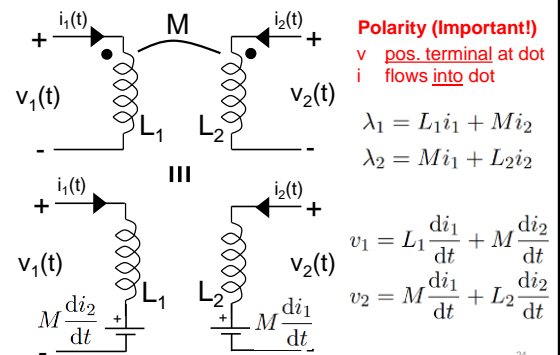

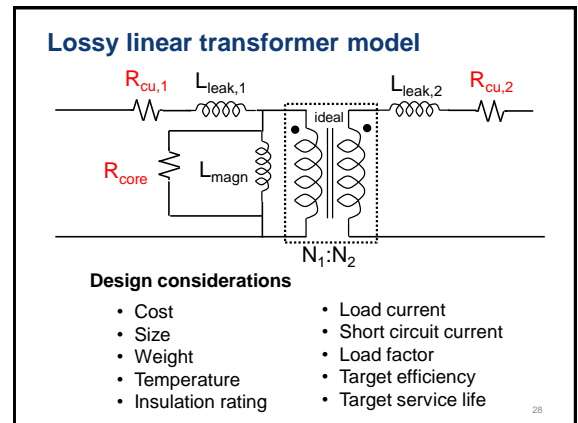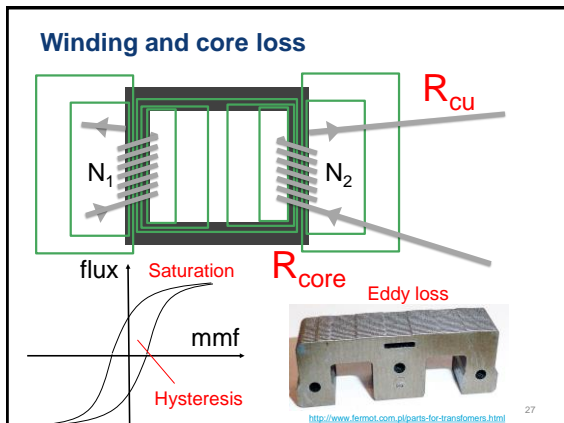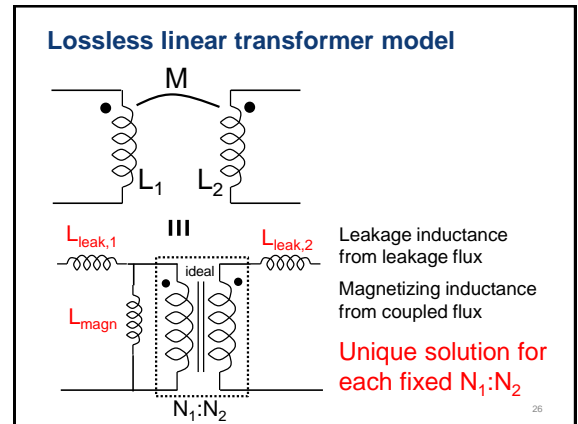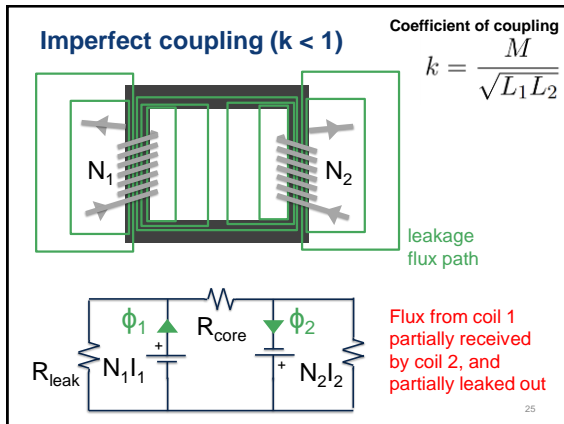

Schedule

- Mon 9/23: Coupled-coils
- Wed 9/25: Ideal transformers
- **Friday 9/27: Review + Quiz 4**
- Mon 9/30: Review
- Wed 10/2: Review
- **Thursday 10/3: Mid-term Exam 1**
- Friday 10/4: No class