

ECE 330: Power Circuits and Electromechanics

Lecture 2

2019-08-28

Last Time

- Review of Phasors
- Use RMS instead of peak
- Calculating average (real) power

Today

- What is complex power?
- How do we calculate it?

Reactive (Q) and Complex (S) Power

$$P = V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_v - \theta_i)$$

$$P = \operatorname{Re} \left\{ V_{RMS} I_{RMS} e^{j(\theta_v - \theta_i)} \right\}$$


$$Q = \operatorname{Im} \left\{ V_{RMS} I_{RMS} e^{j(\theta_v - \theta_i)} \right\}$$

$$P = \operatorname{Re} \left\{ V_{RMS} e^{j\theta_v} I_{RMS} e^{-j\theta_i} \right\} = \operatorname{Re} \left\{ \overline{VI}^* \right\}$$

$$Q = \operatorname{Im} \left\{ V_{RMS} e^{j\theta_v} I_{RMS} e^{-j\theta_i} \right\} = \operatorname{Im} \left\{ \overline{VI}^* \right\}$$

$$b = \operatorname{Re} \left\{ a e^{j\theta} \right\} = a \cos(\theta)$$
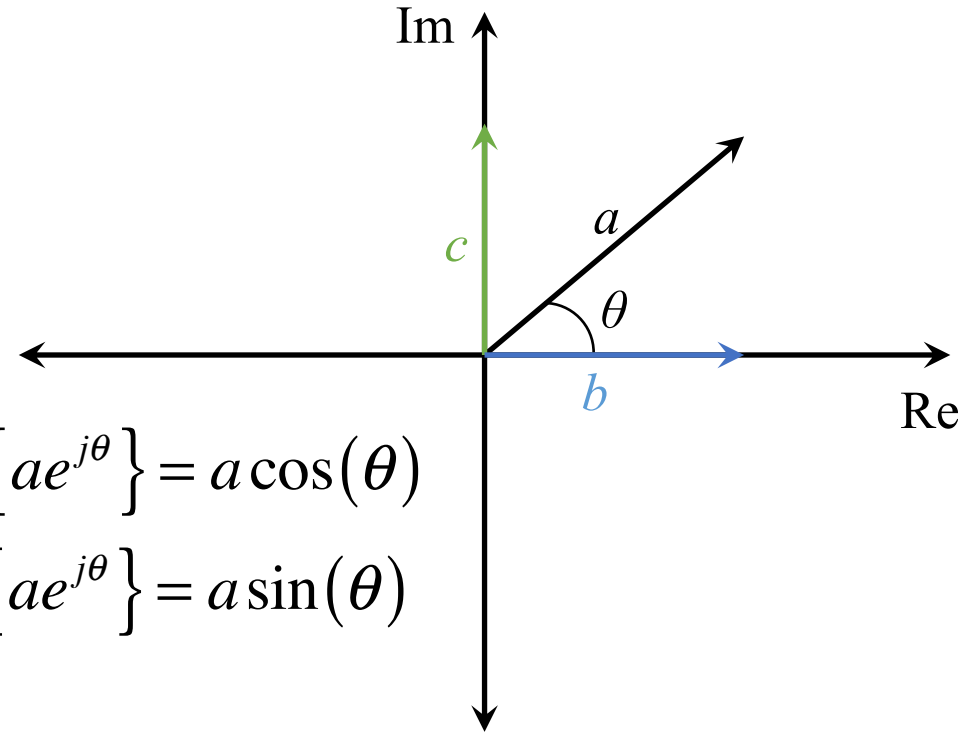
$$c = \operatorname{Im} \left\{ a e^{j\theta} \right\} = a \sin(\theta)$$



$$\overline{S} = \overline{VI}^* = P + jQ$$

Units and Nomenclature

$$[\bar{S}] = \text{VA}$$

$$[P] = \text{W}$$

$$[Q] = \text{VAR}$$

$$\|\bar{S}\| = S = VI : \text{apparent power}$$

$$\theta = \theta_v - \theta_i : \text{power factor angle}$$

$$\cos(\theta) = \cos(\theta_v - \theta_i) : \text{power factor}$$

Different units to distinguish
different meanings.

Examples

$$\bar{V} = 10 \angle 15^\circ \text{ V}, \bar{I} = 5 \angle -30^\circ \text{ A}$$

Find P :

A) 50 W

B) 35.355 W

C) 48.30 W

D) 70.71 W

Examples

$$\bar{V} = 10 \angle 15^\circ \text{ V}, \bar{I} = 5 \angle -30^\circ \text{ A}$$

Find P :

A) 50 W

B) 35.355 W

C) 48.30 W

D) 70.71 W

Examples

$$\bar{V} = 10 \angle 15^\circ \text{ V}, \bar{I} = 5 \angle -30^\circ \text{ A}$$

Find P :

A) 50 W

B) 35.355 W

C) 48.30 W

D) 70.71 W

$$\bar{V} = 10 \angle 15^\circ \text{ V}, \bar{I} = 5 \angle -30^\circ \text{ A}$$

Find Q :

A) 50 W

B) 35.355 W

C) -12.94 VAR

D) 35.355 VAR

Examples

$$\bar{V} = 10 \angle 15^\circ \text{ V}, \bar{I} = 5 \angle -30^\circ \text{ A}$$

Find P :

A) 50 W

B) 35.355 W

C) 48.30 W

D) 70.71 W

$$\bar{V} = 10 \angle 15^\circ \text{ V}, \bar{I} = 5 \angle -30^\circ \text{ A}$$

Find Q :

A) 50 W

B) 35.355 W

C) -12.94 VAR

D) 35.355 VAR

Example

$$v(t) = \sqrt{2}(10)\cos(\omega t + 15^\circ)$$

$$i(t) = \sqrt{2}(7)\sin(\omega t + 75^\circ)$$

Find \bar{S} :

A) $70+j0$ VA

B) $35-j60.62$ VA

C) $60.62+j35$ VA

D) $121.24+j70$ VA

Example

$$v(t) = \sqrt{2}(10)\cos(\omega t + 15^\circ)$$

$$i(t) = \sqrt{2}(7)\sin(\omega t + 75^\circ)$$

Find \bar{S} :

A) $70+j0$ VA


B) $35-j60.62$ VA

C) $60.62+j35$ VA


D) $121.24+j70$ VA

Recall: cosine is an even function

$$\cos(x) = \cos(-x)$$

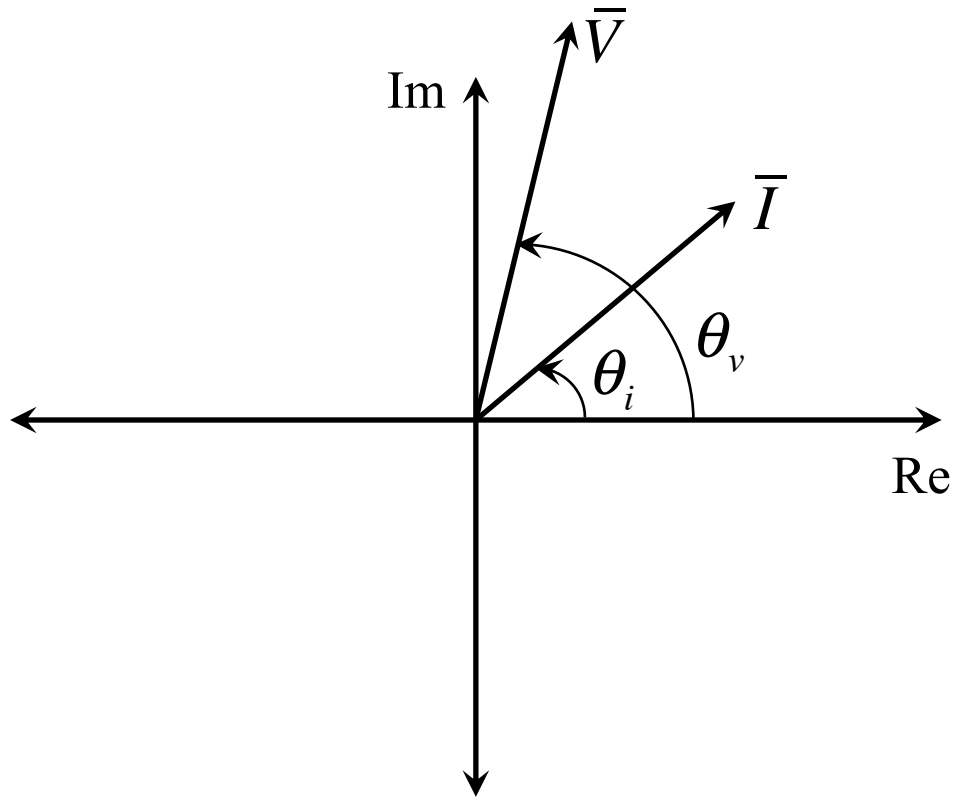

Current lags the voltage:
Lagging PF

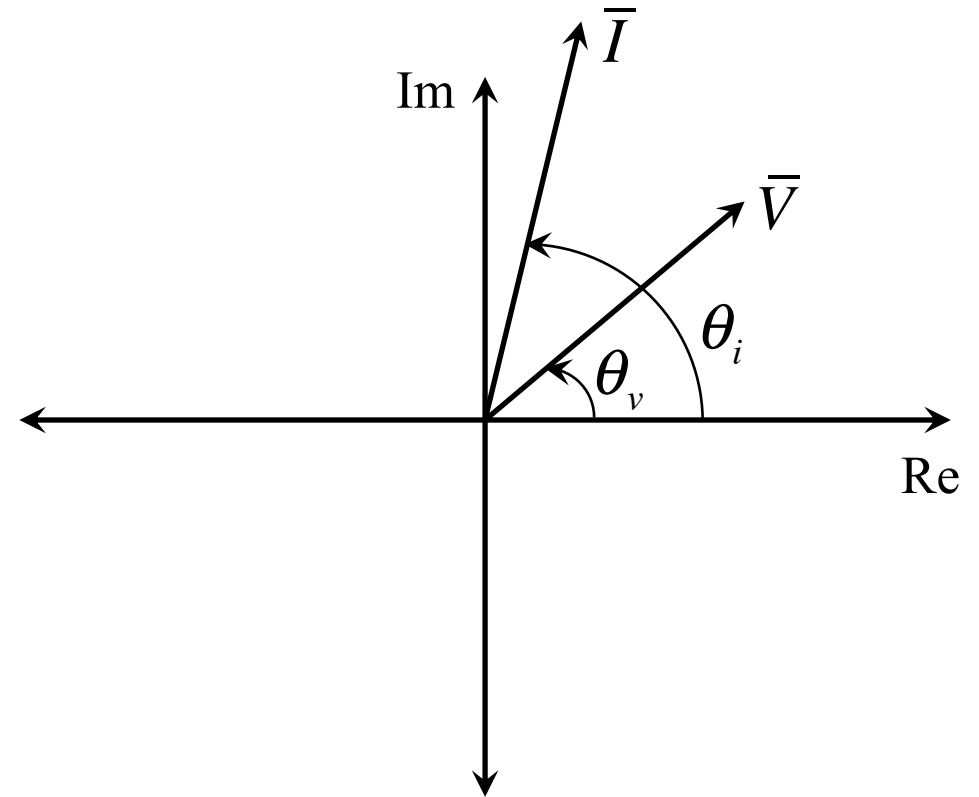


Current leads the voltage:
Leading PF

Note:

- PF is only defined for angles between -90 and $+90$ degrees
- Talking about the power consumed by the load
- If P is negative, this means power is generated by load, not consumed
- To correct, flip the direction for current definition.

Another way to view complex power

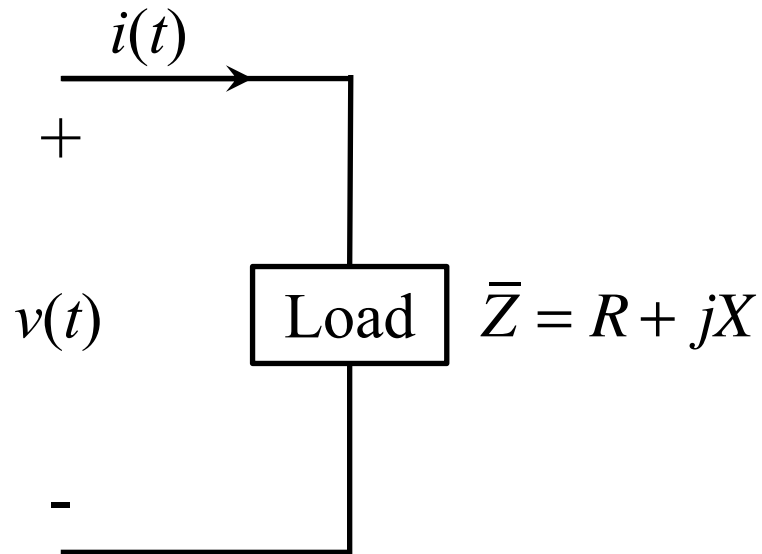

$$\bar{V} = \bar{Z}\bar{I}$$

$$\bar{S} = \bar{V}\bar{I}^* = \bar{Z}(\bar{I}^*) = \bar{Z}I^2$$

$$\bar{S} = I^2 R + jI^2 X = P + jQ$$

P is power dissipated by resistors

Q is power dissipated by reactances

Can also show that angle on
impedance is power factor angle

How do leading and lagging PF correspond to circuit?

$$v = L \frac{di}{dt}$$

$$v = \omega L I_m \left[-\sin(\omega t + \theta_i) \right]$$

$$v = \omega L I_m \sin(-\omega t - \theta_i)$$

$$v = \omega L I_m \cos\left(\omega t + \left[\theta_i + 90^\circ\right]\right)$$

$$\bar{V} = \omega L I_{RMS} \angle \theta_i + 90^\circ$$

$$\bar{S}_L = \omega L I_{RMS}^2 \angle 90^\circ$$

PF = 0 lag

$$i = C \frac{dv}{dt}$$

$$i = \omega C V_m \left[-\sin(\omega t + \theta_v) \right]$$

$$i = \omega C V_m \sin(-\omega t - \theta_v)$$

$$i = \omega C V_m \cos\left(\omega t + \left[\theta_v + 90^\circ\right]\right)$$

$$\bar{I} = \omega C V_{RMS} \angle \theta_v + 90^\circ$$

$$\bar{S}_C = \omega C V_{RMS}^2 \angle -90^\circ$$

PF = 0 lead

Plotting in Complex Plane

