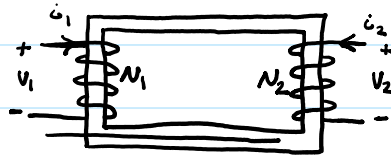


Last time: Mutually coupled coils



$$\lambda_1 = L_1 i_1 + M i_2$$


$$\lambda_2 = M i_1 + L_2 i_2$$

Today: 1) Dot convention


2) Circuits with Mutually coupled coils

* Very tedious to keep track of details of coupled windings

* To simplify use dot convention

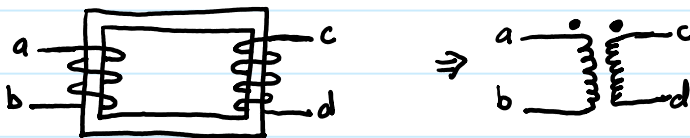


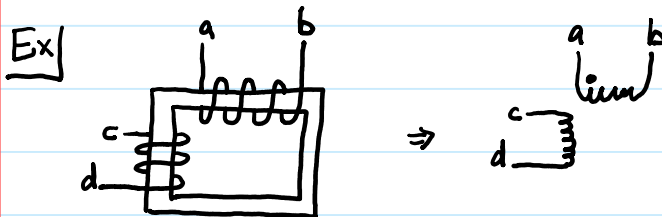* Dots are assigned so that current entering a dotted terminal on one winding produces a voltage with positive polarity on the dotted terminal of the second winding.





* where to put second dot?

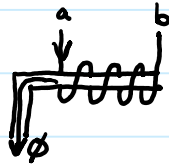
Steps: 1) Inject current into first dot and use RHR to find flux direction in iron



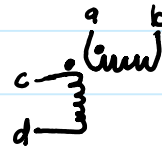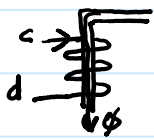2) Put second dot on terminal of second coil to give same flux direction




Ex

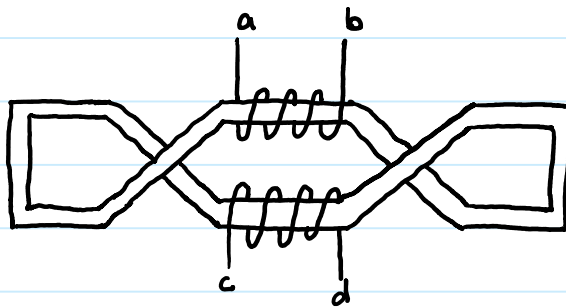

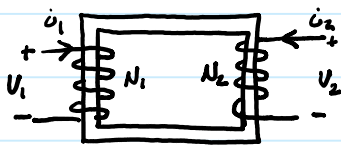- 1) Dot goes on a
- 2) Flux goes $\leftarrow$ through top coil
- 3) Flux goes $\rightarrow$ through bottom coil
- 4) Dot goes on d

Circuit Models for mutually coupled coils



$$\lambda_1 = L_1 i_1 - M i_2$$

$$\lambda_2 = -M i_1 + L_2 i_2$$




* Current entering dotted terminal is $-i_2$

* Voltage induced has negative sign

$$V_1 = i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$


Independent
of the dots

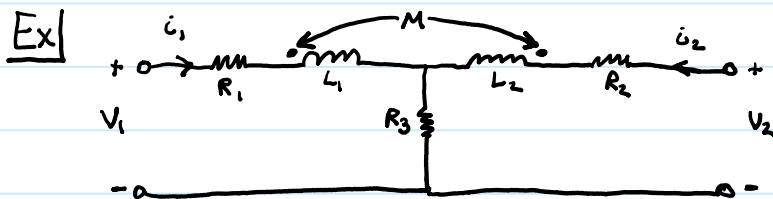

$$V_1 = i_1 R_1 + L_1 \frac{di_1}{dt} + R_3 (i_1 + i_2) + M \frac{di_2}{dt}$$



$$V_2 = i_2 R_2 + L_2 \frac{di_2}{dt} + R_3 (i_1 + i_2) + M \frac{di_1}{dt}$$

* i_2 direction reversed

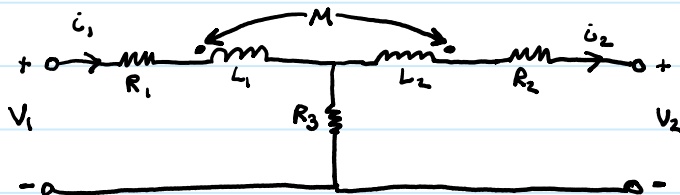

$$V_1 = i_1 R_1 + L_1 \frac{di_1}{dt} + R_3 (i_1 - i_2) - M \frac{di_2}{dt}$$

$$V_2 = -i_2 R_2 - L_2 \frac{di_2}{dt} + R_3 (i_1 - i_2) + M \frac{di_1}{dt}$$

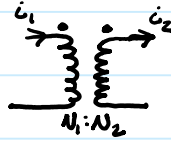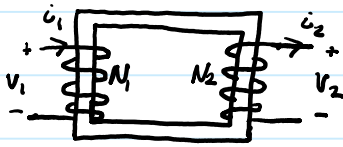Ideal transformers:Assume: 1) $\mu = \infty$

2) Lossless coils

3) No leakage flux ($\phi_1 = \phi_2$)

$$v_1 = N_1 \frac{d\phi}{dt}$$

$$v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_1}{N_1} = \frac{d\phi}{dt}$$

$$\frac{v_2}{N_2} = \frac{d\phi}{dt}$$

$$\frac{v_1}{N_1} = \frac{v_2}{N_2}$$

$$\Rightarrow \boxed{\frac{v_1}{v_2} = \frac{N_1}{N_2} = a}$$

a is the turn ratio

$$N_1 i_1 - N_2 i_2 = R\phi$$

$$\mu = \infty, R = 0$$

$$N_1 i_1 = N_2 i_2$$

$$\boxed{\frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{1}{a}}$$

* if direction of i changed, change sign of i * if polarity of v changed, change sign of v * if the dots are changed, change sign of v and i Power for ideal transformer: $\frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{v_2}{v_1}$

$$v_1 i_1 = v_2 i_2$$

$$P_1 = P_2$$

* No power stored in an ideal transformer