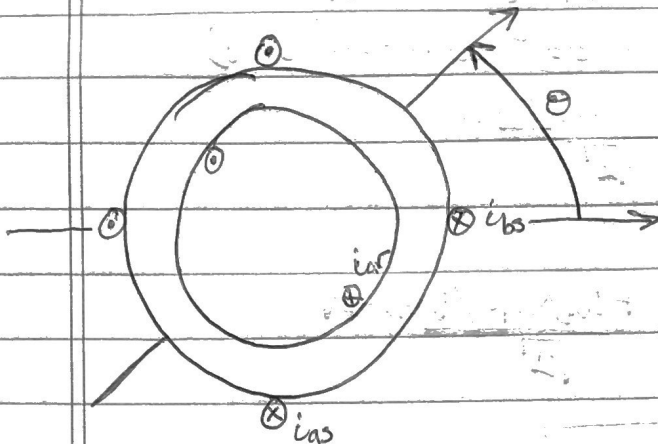


Frequency Condition: $\omega_m = \omega_s - \omega_r$

Synchronous machines: $\omega_m = \omega_s$

$\omega_r = 0$ (DC current for i_{ar} , $i_{br} = 0$)



λ_{as}	L_s	0	$M \cos(\theta)$	i_{as}
λ_{bs}	0	L_s	$M \sin(\theta)$	i_{bs}
λ_{ar}	$M \cos(\theta)$	$M \sin(\theta)$	L_r	i_{ar}

Assume: $i_{as} = I_s \cos(\omega_s t)$ $i_{ar} = I_r$

$i_{bs} = I_s \sin(\omega_s t)$ $\theta = \omega_m t + \gamma \Rightarrow \theta = \omega_s t + \gamma$

$$\lambda_{as} = L_s I_s \cos(\omega_s t) + M I_r \cos(\omega_s t + \gamma)$$

$$\lambda_{bs} = L_s I_s \sin(\omega_s t) + M I_r \sin(\omega_s t + \gamma)$$

$$\lambda_{ar} = M I_s (\cos(\omega_s t) + \sin(\omega_s t)) + L_r I_r$$

a phase Stator Voltage


$$V_{as} = i_{as} R_s + \frac{d\lambda_{as}}{dt}$$

$$V_{as} = I_s R_s \cos(\omega_s t) + (-L_s I_s \omega_s \sin(\omega_s t) - M I_r \omega_s \sin(\omega_s t + \gamma))$$

$$V_a \cos(\omega_s t + \theta_v) = I_s R_s \cos(\omega_s t) - \omega_s L_s I_s \sin(\omega_s t) - \omega_s M I_r \sin(\omega_s t + \gamma)$$

$$\Rightarrow \frac{V_a}{\sqrt{2}} \angle \theta_v = \frac{I_s R_s}{\sqrt{2}} \angle 0 + \frac{\omega_s L_s I_s}{\sqrt{2}} \angle 90^\circ + \frac{\omega_s M I_r}{\sqrt{2}} \angle \gamma + 90^\circ$$
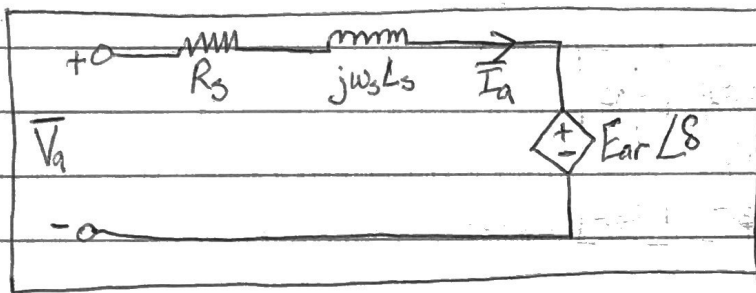
$$\frac{V_a}{\sqrt{2}} \angle \theta_v = R_s \left(\frac{I_s}{\sqrt{2}} \angle -\theta_v \right) + j\omega_s L_s \left(\frac{I_s}{\sqrt{2}} \angle -\theta_v \right) + \frac{\omega_s M I_r}{\sqrt{2}} \angle \gamma + 90^\circ - \theta_v$$



$$E_{ar} = \frac{\omega_s M I_r}{\sqrt{2}} \therefore \text{excitation voltage, dependent on } I_r$$

δ : torque angle

* Similar to per phase equivalent circuit from Chapter 2.

* Can use 1 ϕ power to calculate 3 ϕ power at synchronous machine.

$$\text{3 Phase Power: } P_{3\phi} = 3 P_{1\phi} \Rightarrow P_{3\phi} = 3 \operatorname{Re} \{ \bar{E}_{ar} \bar{I}_a^* \}$$

$$\bar{I}_a = \frac{\bar{V}_a - \bar{E}_{ar}}{R_s + jX_s}$$

$$P_{3\phi} = 3 \operatorname{Re} \left\{ \bar{E}_{ar} \frac{(\bar{V}_a - \bar{E}_{ar})^*}{R_s + jX_s} \right\} \Rightarrow P_{3\phi} = 3 \operatorname{Re} \left\{ \frac{\bar{E}_{ar} \bar{V}_a^*}{R_s + jX_s} - \frac{\bar{E}_{ar}^2}{R_s + jX_s} \right\}$$

$$P_{3\phi} = 3 \operatorname{Re} \left\{ \frac{\bar{E}_{ar} \bar{V}_a^*}{R_s(1 - j\frac{X_s}{R_s})} - \frac{\bar{E}_{ar}^2}{R_s(1 - j\frac{X_s}{R_s})} \right\} \Rightarrow P_{3\phi} = 3 \operatorname{Re} \left\{ \frac{\bar{E}_{ar} \bar{V}_a^*}{X_s(\frac{R_s}{X_s} - j)} - \frac{\bar{E}_{ar}^2}{X_s(\frac{R_s}{X_s} - j)} \right\}$$

$$\text{if } X_s \gg R_s: P_{3\phi} = 3 \operatorname{Re} \left\{ \frac{\bar{E}_{ar} \bar{V}_a^*}{-jX_s} - \frac{\bar{E}_{ar}^2}{jX_s} \right\} \Rightarrow P_{3\phi} = 3 \operatorname{Re} \left\{ \frac{j\bar{E}_{ar} \bar{V}_a^*}{X_s} - j \frac{\bar{E}_{ar}^2}{X_s} \right\}$$

$$P_{3\phi} = 3 \operatorname{Re} \left\{ j \frac{\bar{E}_{ar} \bar{V}_a^*}{X_s} \right\} \Rightarrow P_{3\phi} = 3 \operatorname{Re} \left\{ \frac{E_{ar} \angle 8 (V_a \angle 0) (\angle 90^\circ)}{X_s} \right\}$$

$$P_{3\phi} = 3 \operatorname{Re} \left\{ \frac{E_{ar} V_a \angle 8 + 90^\circ}{X_s} \right\}$$

$$P_{3\phi} = \frac{-3E_{ar} V_a \sin(8)}{X_s}$$

* This is power consumed by the synchronous machine.

$$P_m = T^e \omega_m \Rightarrow P_m = T^e \omega_s \Rightarrow$$

~~$$P_{3\phi} = \frac{-3E_{ar} V_a \sin(8)}{X_s}$$~~

$$T^e = \frac{P_{3\phi}}{\omega_s}$$

Motor: $8 < 0$

$$P_{3\phi} = \frac{3E_{ar} V_a \sin(8)}{X_s}$$

Generator: $8 > 0$

$$P_{3\phi} = \frac{-3E_{ar} V_a \sin(8)}{X_s}$$

$$\bar{S}_{3\phi} = 3V_L \bar{I}_L^*$$

$$\bar{S}_{3\phi} = P_{3\phi} + jQ_{3\phi}$$



if $Q_{3\phi} < 0$: overexcited (supply VARs)

if $Q_{3\phi} > 0$: underexcited (consume VARs)

Multiple Poles

* Everything up to now was a 2 pole system


2 poles: 1 + and 1 -

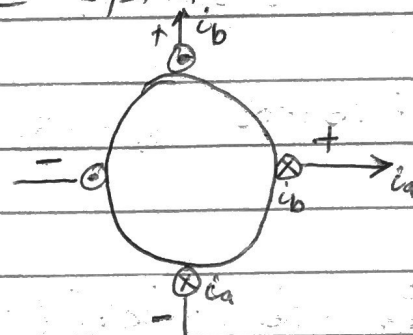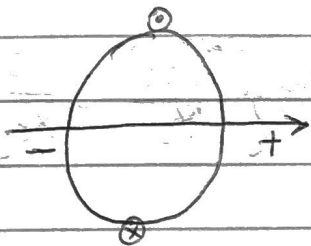


2 poles: 1 + and 1 - per phase

* The number of poles are the total + and - per phase

4 pole

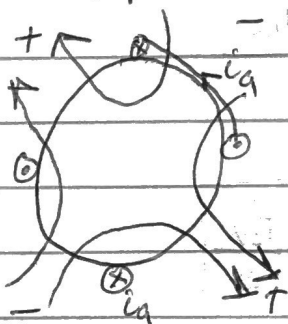

6 pole

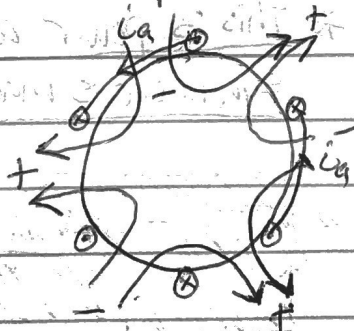

Changes to Equations for multi-pole systems

$p = \# \text{ of poles}$

$$\theta_e = \left(\frac{p}{2}\right) \theta_m$$

$$\omega_e = \left(\frac{p}{2}\right) \omega_m$$

* Don't have to travel as far in θ to switch current direction

θ_e : electrical angle

θ_m : mechanical angle

$$\omega_m = \frac{2\pi}{60} (\text{RPM})$$

$$\omega_e = 2\pi f$$

$$f = 60 \text{ Hz} \Rightarrow \omega_e = 120\pi$$

$$120\pi = \frac{2\pi}{60} (\text{RPM}) \left(\frac{p}{2}\right) \Rightarrow \boxed{\text{RPM} = \left(\frac{2}{p}\right) 3600}$$

p	RPM
2	3600
4	1800
6	1200
8	900
10	720

$$P = T^e \omega_m$$

$$P = T^e \left(\frac{2}{p}\right) \omega_e$$

$$\boxed{T^e = \frac{P}{\left(\frac{2}{p}\right) \omega_e}}$$

Ex 6.1 in textbook

3 ϕ , 60Hz, $V_L = 550$ V, 6 pole, wye connected generator

$P_{3\phi} = 1000$ kW generated

$E_{ar} = 460$ V/phase

$X_s = 2 \Omega$

Find: a) δ and T^e


b) $\bar{I}_a$, PF, Q generated

Solution: a) $P_{3\phi} = \frac{3 E_{ar} V_{an} \sin(\delta)}{X_s} \Rightarrow \sin(\delta) = \frac{X_s P_{3\phi}}{3 E_{ar} V_{an}}$

$$\sin(\delta) = \frac{2 \Omega (1000 \times 10^3 \text{ W})}{3 (460 \text{ V/phase}) \left(\frac{550 \text{ V}}{\sqrt{3}} \right)} \Rightarrow \sin(\delta) = 0.4564$$

$$\delta = 27.16^\circ$$

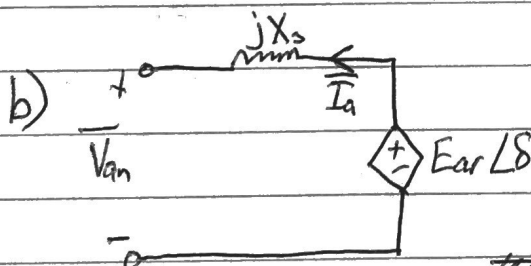~~$T^e = \frac{P_{3\phi}}{\omega_e}$~~ $\Rightarrow T^e = \frac{1000 \times 10^3 \text{ W}}{\left(\frac{2}{6} \right) 60 \text{ Hz} (2\pi)} \Rightarrow T^e = 795.77 \text{ Nm}$



$$E_{ar} \angle \delta = jX_s \bar{I}_a + V_{an} \angle 0$$

$$\bar{I}_a = \frac{E_{ar} \angle \delta - V_{an} \angle 0}{jX_s}$$

jX_s

$$\bar{I}_a = 114.57 \angle -23.60^\circ \text{ A}$$

PF = $\cos(23.60^\circ) \Rightarrow \text{PF} = 0.916$ lagging

$$S_{3\phi} = \frac{P_{3\phi}}{\text{PF}}$$

$Q = S_{3\phi} \sin(\theta) \Rightarrow Q = 43.706 \text{ kVAR}$