

ECE 330 Exam #1, Fall 2015 Name: Solution
 90 Minutes

Section (Check One) MWF 10am _____ TR 2:00pm _____

1. _____ / 25 2. _____ / 25
 3. _____ / 25 4. _____ / 25 Total _____ / 100

Useful information



$\sin(x) = \cos(x - 90^\circ)$ $\bar{V} = \bar{Z}\bar{I}$ $\bar{S} = \bar{V}\bar{I}^* = P + jQ$ $\bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$

$0 < \theta < 180^\circ$ (lag) $I_L = \sqrt{3}I_\phi$ (delta) $\bar{Z}_Y = \bar{Z}_\Delta / 3$ $\mu_0 = 4\pi \cdot 10^{-7}$ H/m
 $-180^\circ < \theta < 0$ (lead) $V_L = \sqrt{3}V_\phi$ (wye)


ABC sequence has A at zero, B at minus 120 degrees, and C at plus 120 degrees

$\int_C \mathbf{H} \cdot d\mathbf{l} = \int_S \mathbf{J} \cdot \mathbf{n} da$ $\int_C \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial}{\partial t} \int_S \mathbf{B} \cdot \mathbf{n} da$ $\mathfrak{R} = \frac{l}{\mu A}$ $MMF = Ni = \phi \mathfrak{R}$

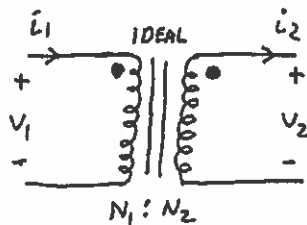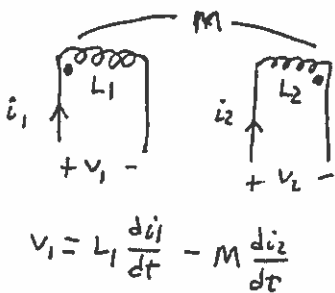$\phi = BA$ $\lambda = N\phi$ $k = \frac{M}{\sqrt{L_1 L_2}}$ 1 hp = 746 Watts



$a = \frac{N_1}{N_2}$ $N_1 i_1 = N_2 i_2$
 $\frac{v_1}{v_2} = \frac{N_1}{N_2}$

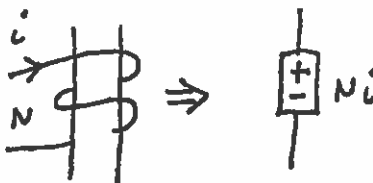

Problem 1. (25 points)

A single phase ac voltage source of 240 Volts RMS, 60 HZ supplies a load that draws 13 Amps RMS and a real power of 2,700 Watts.

- a) Find the power factor of the load – assume that it is lagging.

$$S = 240 \times 13 = 3120 \text{ VA} \quad \text{Pf} = \frac{2700}{3120} = 0.865 \text{ lag}$$

- b) If it really is lagging, how many VARS from a capacitor bank are required to improve the power factor to 0.95 lagging?

$$\bar{S} = 3120 \angle 30.07^\circ = 2700 + j1563$$

$$\bar{S}_{\text{new}} = \frac{2700}{0.95} \angle \cos^{-1} 0.95 = 2842 \angle 18.2^\circ = 2700 + j888$$

$$Q_{\text{adj}} = 1563 - 888 = 675 \text{ VARS}$$

- c) What is the magnitude of the current supplied by the source after the addition of the above capacitor bank if it really is lagging power factor?

$$I = \frac{2842}{240} = 11.8 \text{ A}$$

- d) What is the magnitude of the current supplied by the source after the addition of the above capacitor bank if the original load is actually leading power factor?

$$\bar{S}_{\text{new}} = 2700 - j1563 - j675 = 2700 - j2238$$

$$|\bar{S}| = 3507 \text{ VA} \quad I = \frac{3507}{240} = 14.6 \text{ A}$$

Problem 2. (25 points)

A 120 (L-N)/208 (L-L) Volts RMS, 3-phase, 4 wire, wye-connected, ABC sequence, 60 HZ source supplies the following two lagging power factor loads:

Load #1 14 Amps (line current) 3500 Watts (3-phase), wye-connected

Load #2 8 Amps (phase current) 0.8 power factor, delta connected

- a) What is the total line current (magnitude only) being supplied by the source?

$$|\bar{S}_1| = \sqrt{3} \times 14 \times 208 = 5043 \text{ VA} \quad \text{PF} = \frac{3500}{5043} = 0.694$$

$$\bar{S}_1 = 5043 \angle 46.05^\circ = 3500 + j3631 \text{ VA}$$

$$\bar{S}_2 = 3 \times 8 \times 208 \angle \cos^{-1} 0.8 = 3994 + j2995 \text{ VA}$$

$$\bar{S}_{\text{TOT}} = 7494 + j6626 = 10,003 \angle 41.5^\circ$$

$$I_L = \frac{10,003}{\sqrt{3} \times 208} = 27.8 \text{ A}$$

- b) How many capacitive VARS 3-phase need to be supplied at the load to reduce the total source line current to 25 Amps?

$$|\bar{S}| = \sqrt{3} \times 208 \times 25 = 9006.4$$


$$P = 7494 \quad \text{so} \quad \text{PF} = 0.832 \quad \theta = 33.69^\circ$$

$$Q = 9006.4 \sin 33.69^\circ = 4995 \text{ VARS}$$


$$\text{ADD } 6626 - 4995 = 1631 \text{ VARS}$$

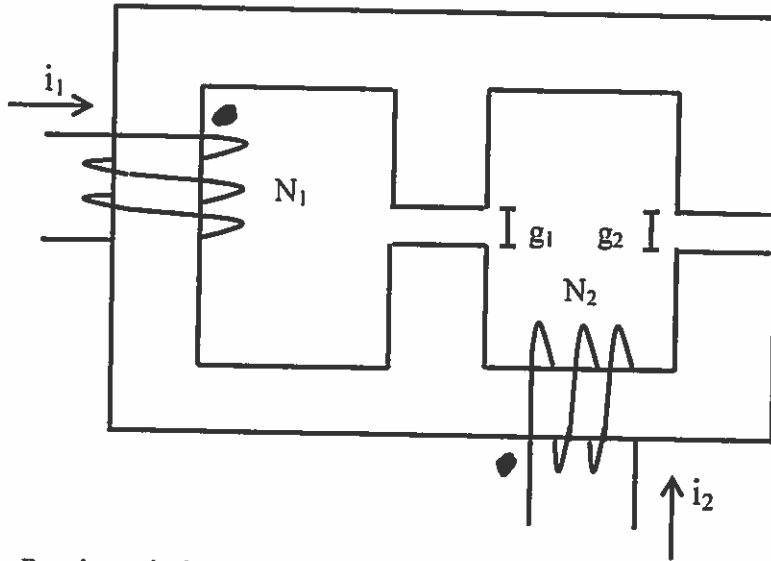Problem 3. (25 points)

Consider the iron core geometry given in the figure below. Neglect fringing in the air gaps and assume the iron core has infinite permeability. The gaps are $g_1 = 0.10$ cm, $g_2 = 0.12$ cm and $A_{\text{core}} = 2 \text{ cm}^2$, $N_1 = 100$, and $N_2 = 120$ turns.



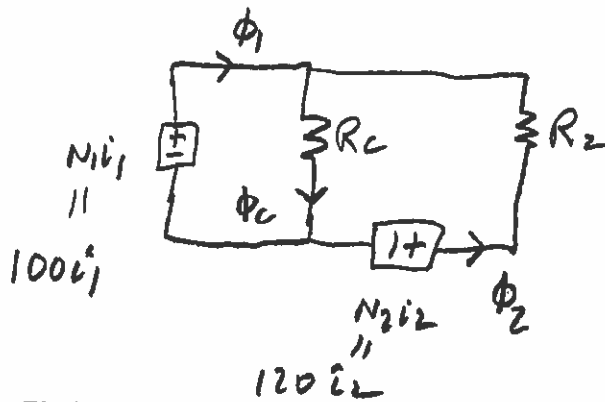- Put the polarity dots on the two coils.
See figure
- Draw the equivalent magnetic circuit and label everything you need to solve for the magnetic fluxes in the iron core segments.



$$R_c = \frac{0.001}{4\pi \times 10^{-7} \times 2 \times 10^{-4}} = 39.8 \times 10^5$$

$$R_2 = \frac{0.0012}{4\pi \times 10^{-7} \times 2 \times 10^{-4}} = 47.7 \times 10^5$$

- Find the positive mutual inductance (M) between the two coils

$$100 i_1 = 39.8 \times 10^5 \phi_c \quad \phi_c = 25 \times 10^{-6} i_1$$

$$100 i_1 = -47.7 \times 10^5 \phi_2 + 120 i_2 \quad \phi_2 = -21 \times 10^{-6} i_1 + 25.2 \times 10^{-6} i_2$$

Continued on the next page

$$\mathcal{F}_2 = 120\phi_2 = -0.00252i_1 + 0.00302i_2$$

$$m = 0.00252 \text{ H}$$

- d) Find the magnetic flux density in each of the three the iron core segments (left, center and right) when the currents are $i_1 = 7$ Amps (DC) and $i_2 = 6$ Amps (DC)


$$\begin{aligned}\phi_1 = \phi_c - \phi_2 &= 25 \times 10^{-6} i_1 + 21 \times 10^{-6} i_1 - 25.2 \times 10^{-6} i_2 \\ &= 46 \times 10^{-6} \times 7 - 25.2 \times 10^{-6} \times 6 \\ &= 322 \times 10^{-6} - 151.2 \times 10^{-6} = 170.8 \times 10^{-6} \text{ wb}\end{aligned}$$

$$B_1 = \frac{\phi_1}{2 \times 10^{-4}} = \frac{170.8 \times 10^{-6}}{2 \times 10^{-4}} = 0.854 \text{ T}$$

$$B_2 = \frac{\phi_2}{2 \times 10^{-4}} = \frac{-21 \times 10^{-6} \times 7 + 25.2 \times 10^{-6} \times 6}{2 \times 10^{-4}} = \frac{4.2 \times 10^{-6}}{2 \times 10^{-4}} = 0.021 \text{ T}$$


$$B_c = \frac{\phi_c}{2 \times 10^{-4}} = \frac{25 \times 10^{-6} \times 7}{2 \times 10^{-4}} = 0.875 \text{ T}$$

Problem 4. (25 points)

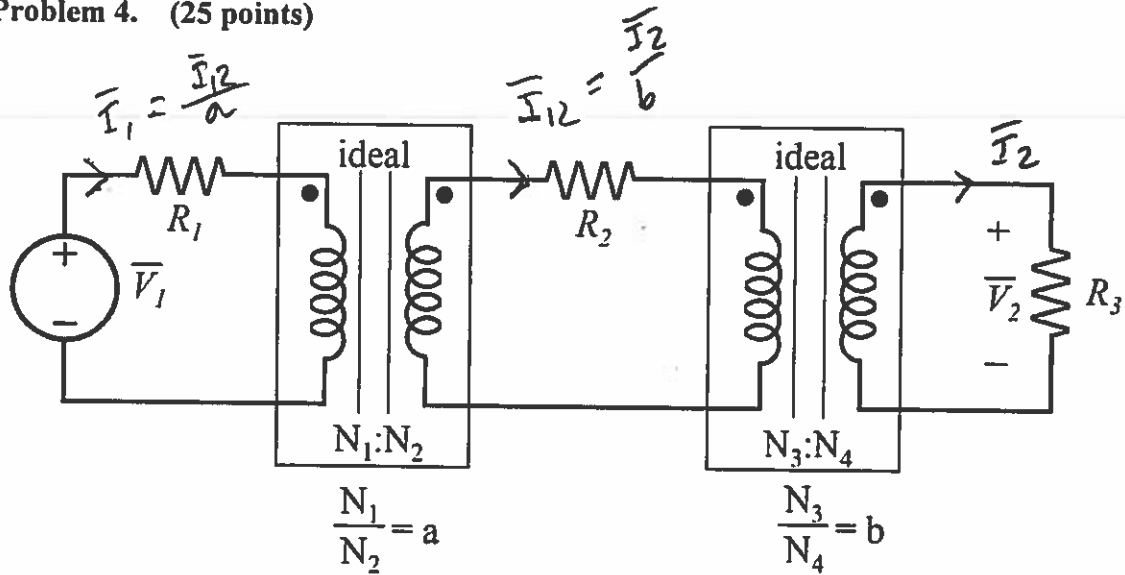

For the circuit showed above:

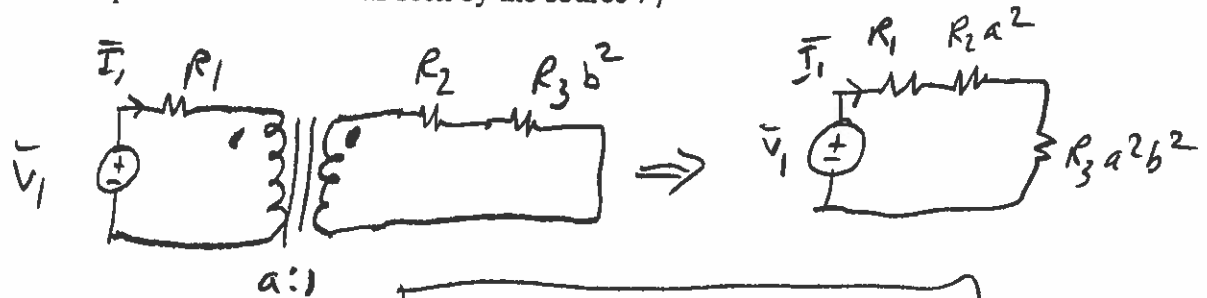- a) Find the equivalent resistance as seen by the source \bar{V}_1



$$\bar{V}_1 = \bar{I}_1 R_{eq}$$

$$R_{eq} = R_1 + R_2 a^2 + R_3 a^2 b^2$$

- b) Find the voltage \bar{V}_2 as a function of \bar{V}_1

$$\bar{V}_2 = \bar{I}_2 R_3 = b R_3 \bar{I}_{12} = ab R_3 \bar{I}_1 = ab R_3 \frac{\bar{V}_1}{R_{eq}}$$

$$= \frac{ab R_3}{R_1 + R_2 a^2 + R_3 a^2 b^2} \bar{V}_1$$