


ECE330: Power Circuits & Electromechanics
Lecture 20. Synchronous machines

Prof. Richard Y. Zhang
 Univ. of Illinois at Urbana-Champaign
 ryz@illinois.edu



1

Last time: The world of electric machines



Switching DC fields


- Brushed DC motor
- Reluctance machine
- Stepper motor
- Brushless DC motor

Rotating AC fields

- Synchronous machine
- Induction machine

Our focus in ECE 330

2

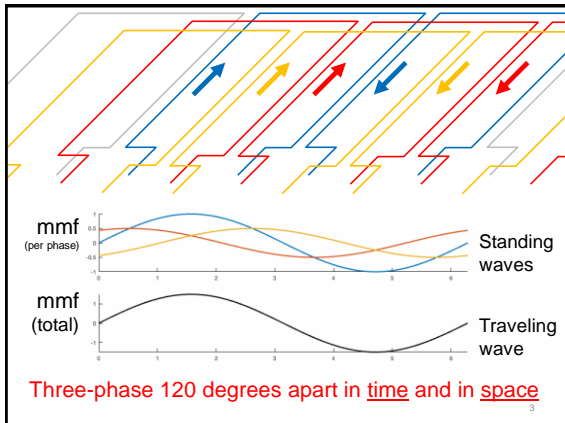

3

Recall: Rotating stator field

Balanced 3 ϕ stator currents

Rotating field spins at synchronous speed
 Drags rotor at same speed

Rotor construction?

- Magnetic material \rightarrow Reluctance machine
- Permanent magnet \rightarrow Brushless DC
- Electromagnet \rightarrow Synchronous machine

4

Recall: Multiple poles Important slide

2-pole @ 60 Hz
3600 rpm

4-pole @ 60 Hz
1800 rpm

Synchronous speed = 60π [rad/s] = 1800 rpm

Synchronous frequency = 120π [rad/s] = 60 [Hz]

$$\omega_m = \frac{2}{p} \omega_s$$


Mechanical speed ω_m # poles p Electrical frequency ω_s

5

Today: Synchronous machine model

Flux linkage equation
 $\lambda(t) = \lambda(i, \theta)$

Voltage of mechanical origin
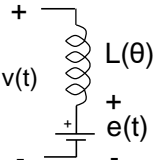
$$v(t) = \frac{d\lambda}{dt} = \underbrace{\frac{\partial \lambda}{\partial i} \frac{di}{dt}}_{L(\theta)} + \underbrace{\frac{\partial \lambda}{\partial \theta} \frac{d\theta}{dt}}_{e(t)}$$


Energy conversion in a loop

$$0 = \oint_C i(\lambda', \theta') d\lambda' + \oint_C -\tau(\lambda', \theta') d\theta'$$

Average power $EFE|_{\text{cycle}} \cdot \text{freq} = P_{\text{av}} = \text{Re}\{\bar{V} \bar{I}^*\}$

Average torque $EFM|_{\text{cycle}} = -\tau_{\text{av}} \cdot \text{dist}$

6

Today

- Mechanical model (torque vs speed)
- Electrical model (current vs voltage)
- Example analysis

7

Average torque from average power


$$0 = \oint_C \frac{i(\lambda', \theta') d\lambda'}{EFE|_{\text{cycle}}} + \oint_C \frac{-\tau(\lambda', \theta') d\theta'}{EFM|_{\text{cycle}}}$$

$$EFE|_{\text{cycle}} \cdot \text{freq} = P_{\text{av}}$$

$$EFM|_{\text{cycle}} = -\tau_{\text{av}} \cdot \text{dist}$$

Pav = 1 W, Tav = ? Nm

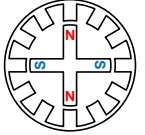A) $2\pi / 60$ B) $1 / 60\pi$ ←
 C) $2\pi / 60$ D) $1 / 120\pi$
 E) $1 / 240\pi$



4-pole @ 60 Hz
1800 rpm

Freq = 60 Hz (as usual)
Dist = half-rotation = π

8

Average torque from average power

$$EFE|_{\text{cycle}} \cdot \text{freq} = P_{\text{av}}$$

$$EFM|_{\text{cycle}} = -\tau_{\text{av}} \cdot \text{dist}$$

$$\tau_{\text{av}} = \frac{P_{\text{av}}}{\text{freq} \cdot \text{dist}} = \frac{P_{\text{av}}}{\text{freq} \cdot 2\pi \cdot (2/p)} = \frac{P_{\text{av}}}{\omega_m}$$

Average torque = $\frac{\text{Average power}}{\text{Mechanical rad/s}}$

Half the speed, same power, then twice the torque
Sacrifice speed to increase torque


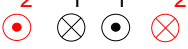
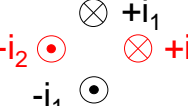
9

Today

- Mechanical model (torque vs speed)
- Electrical model (current vs voltage)
- Example analysis


10

Preliminary: Interlocking loops


$-i_2 \quad -i_1 \quad +i_1 \quad +i_2$ 	$\lambda_1 = +L_1 i_1 + M i_2$ $\lambda_2 = + M i_1 + L_2 i_2$
$-i_2 \quad +i_1 \quad -i_1 \quad +i_2$ 	$\lambda_1 = +L_1 i_1 - M i_2$ $\lambda_2 = - M i_1 + L_2 i_2$
$-i_2 \quad +i_1$ $-i_1$ 	$\lambda_1 = +L_1 i_1$ $\lambda_2 = \quad \quad \quad +L_2 i_2$

11

Inductance model

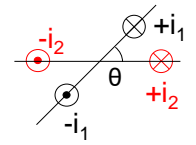

$$\lambda_1 = +L_1 i_1 + |M|\cos\theta i_2$$
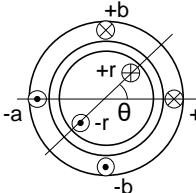
$$\lambda_2 = +|M|\cos\theta i_1 + L_2 i_2$$


$$\lambda_a = +L_a i_a + |M|\cos\theta i_r$$

$$\lambda_b = +L_b i_b + |M|\sin\theta i_r$$

$$\lambda_r = +L_r i_r + |M|\cos\theta i_a + |M|\sin\theta i_b$$

12

Per-phase circuit model

$\lambda_a = +L_a i_a + |M| \cos\theta i_r$
 $\lambda_b = +L_b i_b + |M| \sin\theta i_r$
 $\lambda_r = +L_r i_r + |M| \cos\theta i_a + |M| \sin\theta i_b$

fix $i_r(t) = I_r$, let $\theta = \omega t$

$v_a = L_a \frac{di_a}{dt} - \omega M I_r \sin \omega t$
 $v_b = L_b \frac{di_b}{dt} + \omega M I_r \cos \omega t$

90° shift

13

Per-phase phasor model

Time-domain

$v_b = L_b \frac{di_b}{dt} + \omega M I_r \cos \omega t$

Phasor representation

$\bar{V}_b = j\omega L_b \cdot \bar{I}_b + \bar{E}_b$

where $|\bar{E}| = \omega_s M I_r / \sqrt{2}$ ← Always true

4-pole, 60 Hz, M = 1 H, I_r = 1 A.

|E_b| = ? V

A) $2\pi / 60$ B) $60\pi / \text{sqrt}(2)$ C) 60π D) $120\pi / \text{sqrt}(2)$ E) 120π

electrical domain ignores number of poles

14

Per-phase phasor model

Phasor representation

$\bar{V}_b = j\omega L_b \cdot \bar{I}_b + \bar{E}_b$

where $|\bar{E}| = \omega_s M I_r / \sqrt{2}$

Circuit diagram of both phases

Same idea for 3φ but tedious math

15

Today

- Mechanical model (torque vs speed)
- Electrical model (current vs voltage)
- Example analysis

16

Example 6.4

Example 6.4 A two-pole, three-phase, 60 Hz, wye-connected synchronous machine has synchronous reactance $x_s = 2\Omega$ per phase. The machine is operating as a generator delivering power at a voltage of 1905 V per phase. The current is 350 A and the PF of the load is 0.8 lagging. Find \bar{E}_a , δ , and the torque of electric origin.

↓ Rephrase into a feeder problem

A three-phase source is serving a single load connected through a feeder with impedance $j2\Omega$. The load draws 350 A per phase at a lagging PF of 0.8. The voltage across the load is 1905V (phase-to-neutral).

a) Compute the source voltage as a complex phasor.

b) Compute the power consumed at the load and divide it by 120π , the mech speed of a 2-pole machine.

17

Example 6.4

A three-phase source is serving a single load connected through a feeder with impedance $j2\Omega$. The load draws 350 A per phase at a lagging PF of 0.8. The voltage across the load is 1905V (phase-to-neutral).

a) Compute the source voltage as a complex phasor.

b) Compute the power consumed at the load and divide it by 120π , the mech speed of a 2-pole machine.

18