


**ECE330: Power Circuits & Electromechanics**  
**Lecture 25. Efficiently generating a sine wave.**






Prof. Richard Y. Zhang  
 Univ. of Illinois at Urbana-Champaign  
 ryz@illinois.edu



1

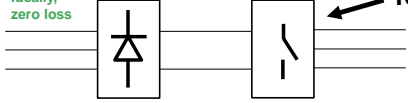
**Last time: Variable speed drive**

Ideally, zero loss

2


**What's wrong with this?**

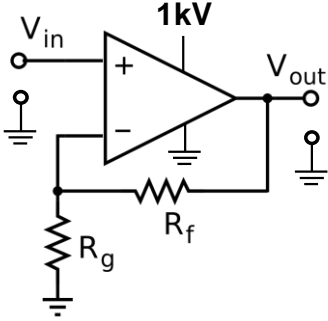

3

**Rules for high efficiency**

$I_{in} = I_{out}$

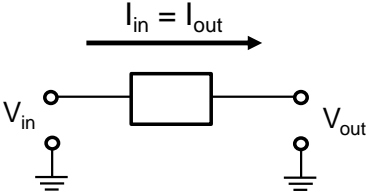


**100% Efficiency** Short circuit  $V_{in} = V_{out}$   
 Open circuit  $I_{in} = I_{out} = 0$

But  $V_{in} = 1kV$  DC and  $V_{out} = 500V$  AC ???

4



**Hypothetical one-switch inverter**

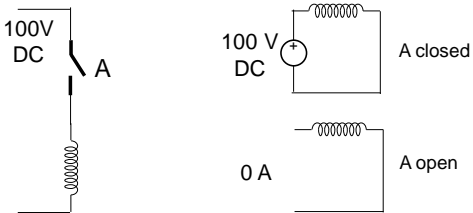

- Short-circuit with 100V vs open-circuit.
- Inductor doesn't like large di/dt.
- In practice will blow up the switch

5

**Basic two-switch inverter**

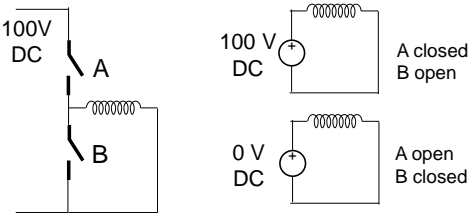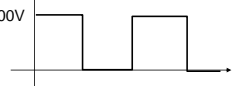- Switching voltage source 100V / 0V.
- But nonzero average voltage!

6

### Half-bridge inverter

- Finally, an AC waveform! (sort of)
- **No voltage control**

7

### Duty cycle (Pulse width) control

Slowly varying the average allows us to generate an arbitrary AC waveform

8

### Applying a low-pass filter recovers the underlying sine wave

Harmonic distortion ("Ripple")

9


10

### Full-bridge inverter


- Two levels of voltage supply
- But three levels of voltage output

11


12

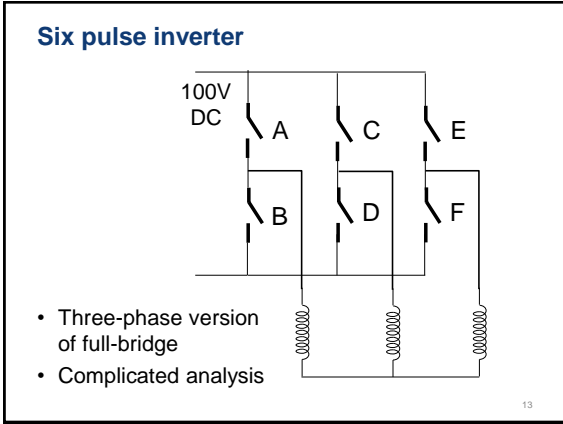


13

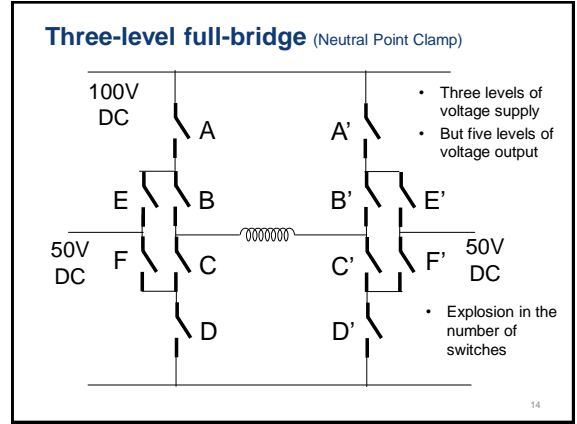


14

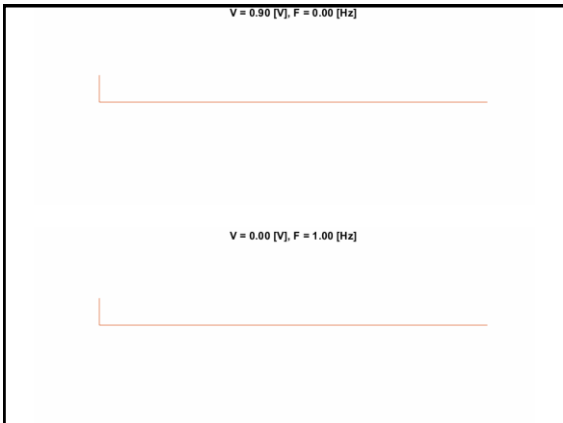

15

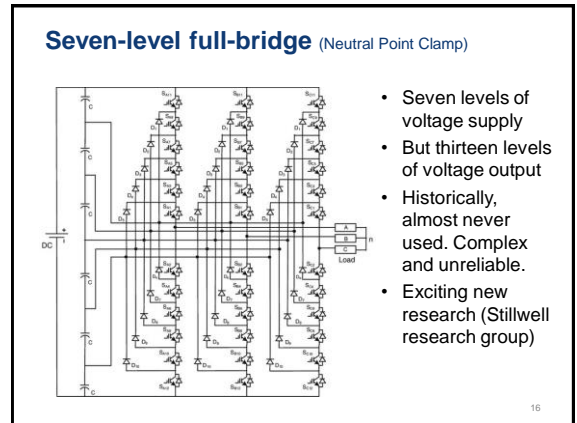

16

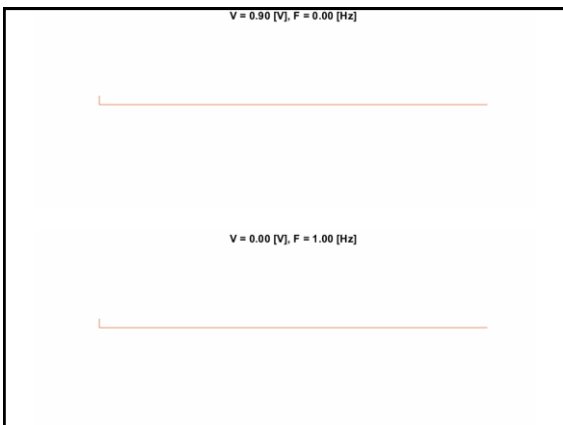

17

### Today: Inverters

Next time → → Ideally, zero loss

18