

ECE 330 Exam #1, Fall 2014 Name: Solution
 90 Minutes

Section (Check One) MWF 10am _____ MWF 2:00pm _____

1. _____ / 25 2. _____ / 25
 3. _____ / 25 4. _____ / 25 Total _____ / 100



Useful information

$\sin(x) = \cos(x - 90^\circ)$ $\bar{V} = \bar{Z}\bar{I}$ $\bar{S} = \bar{V}\bar{I}^* = P + jQ$ $\bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$
 $0 < \theta < 180^\circ$ (lag) $I_L = \sqrt{3}I_\phi$ (delta) $\bar{Z}_Y = \bar{Z}_\Delta / 3$ $\mu_0 = 4\pi \cdot 10^{-7}$ H/m
 $-180^\circ < \theta < 0$ (lead) $V_L = \sqrt{3}V_\phi$ (wye)


ABC sequence has A at zero, B at minus 120 degrees, and C at plus 120 degrees

$\int_C \mathbf{H} \cdot d\mathbf{l} = \int_S \mathbf{J} \cdot \mathbf{n} da$ $\int_C \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial}{\partial t} \int_S \mathbf{B} \cdot \mathbf{n} da$ $\mathfrak{R} = \frac{l}{\mu A}$ $MMF = Ni = \phi \mathfrak{R}$

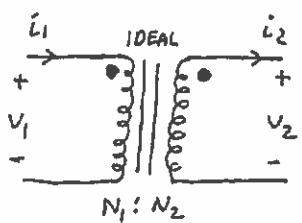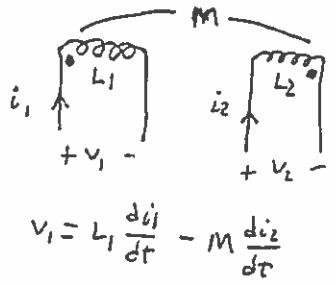$\phi = BA$ $\lambda = N\phi$ $k = \frac{M}{\sqrt{L_1 L_2}}$ 1 hp = 746 Watts



$a = \frac{N_1}{N_2}$ $N_1 i_1 = N_2 i_2$
 $\frac{v_1}{v_2} = \frac{N_1}{N_2}$

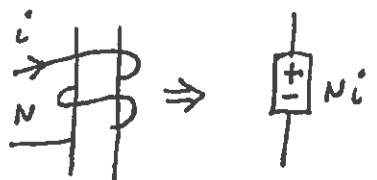

Problem 1. (25 points)

A single phase ac voltage source of 240 Volts RMS, 60 HZ supplies a 5 kVA, 0.7 pf lagging load.

- Find the complex power consumed by the load.
- Find the complex impedance of the load.
- Find the magnitude of the current supplied by the source.
- How many VARS from a capacitor bank are required to improve the power factor to 0.9 lagging?
- What is the magnitude of the current supplied by the source after addition of above capacitor bank?

$$\begin{aligned} \text{a) } \bar{S} &= 5000 \angle \cos^{-1}(0.7) = 5000 \angle 45.57^\circ \text{ VA} \\ &= 3500 + j3570 \text{ VA} \end{aligned}$$

$$\begin{aligned} \text{b) } \bar{Z} &= \frac{\bar{V}}{\bar{I}} = \frac{\bar{V}}{(\bar{S}/\bar{V})^*} = \frac{\bar{V} \cdot \bar{V}^*}{\bar{S}^*} = \frac{|\bar{V}|^2}{\bar{S}^*} = \frac{240^2}{5000 \angle -45.57^\circ} \Omega \\ &= 11.52 \angle 45.57^\circ \Omega \\ &= 8.064 + j8.227 \Omega \end{aligned}$$

$$\begin{aligned} \text{c) } \bar{I} &= (\bar{S}/\bar{V})^* = \left(\frac{5000 \angle 45.57^\circ}{240 \angle 0} \right)^* \\ &= 20.83 \angle -45.57^\circ \text{ A} \Rightarrow |\bar{I}| = 20.83 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{d) } \theta_{\text{new}} &= \cos^{-1}(0.9) = 25.84^\circ \\ Q_{\text{new}} &= (3570 - Q_{\text{cap}}) = P \tan(\theta) = 3500 \tan(25.84^\circ) \\ Q_{\text{cap}} &= 3570 - 1695 = 1875 \text{ Vars} \end{aligned}$$

$$\text{e) } \bar{S}_{\text{new}} = \frac{3500}{0.9} \angle \cos^{-1}(0.9) = 3889 \angle 25.84^\circ \text{ VA}$$

$$|\bar{I}| = \frac{|\bar{S}|}{|\bar{V}|} = \frac{3889}{240} = 16.2 \text{ A}$$

Problem 2. (25 pts)

A balanced three-phase, 480 Volt (line to line), 60 Hz, ABC sequence power system supplies the following two loads that are connected in parallel:

Load #1 is a four-wire, wye-connected load which draws 84 Amps and 21kW of real power per phase.

Load #2 is a three-wire delta-connected load which draws 150kVA (3-phase) of apparent power at a power factor of 0.88 lag.

$$PF_1 = \frac{21k \times 3}{\sqrt{3} \times 480 \times 84} = .902$$

a) What is the source line current if Load #1 is lagging power factor?

$$\bar{S}_1 = \sqrt{3} \times 480 \times 84 \angle \pm 25.56^\circ, \bar{S}_2 = 150k \angle \cos^{-1} 0.88 = 132k + j 71,246$$

$$\text{If } \theta > 0, \bar{S}_{TOT} = 132k + 63,000 + j 71,246 + j 30,130 \\ = 195,000 + j 101,376 = 219,777 \angle 27.417^\circ$$

$$219,777 = \sqrt{3} \times 480 \times I_L \quad I_L = 264 \text{ A}$$

b) What is the source line current if Load #1 is leading power factor?

$$\text{If } \theta < 0, \bar{S}_{TOT} = 132k + 63,000 + j 71,246 - j 30,130 \\ = 195,000 + j 41,160 = 199,296 \angle 11.92^\circ$$

$$199,296 = \sqrt{3} \times 480 \times I_L \quad I_L = 240 \text{ A}$$


c) What would the source line current be if power factor correction capacitors were used to make the total power factor of both loads 1.0?

$$\bar{S} = 132k + 63,000 = 195,000 = \sqrt{3} \times 480 \times I_L$$

$$I_L = 235 \text{ A}$$

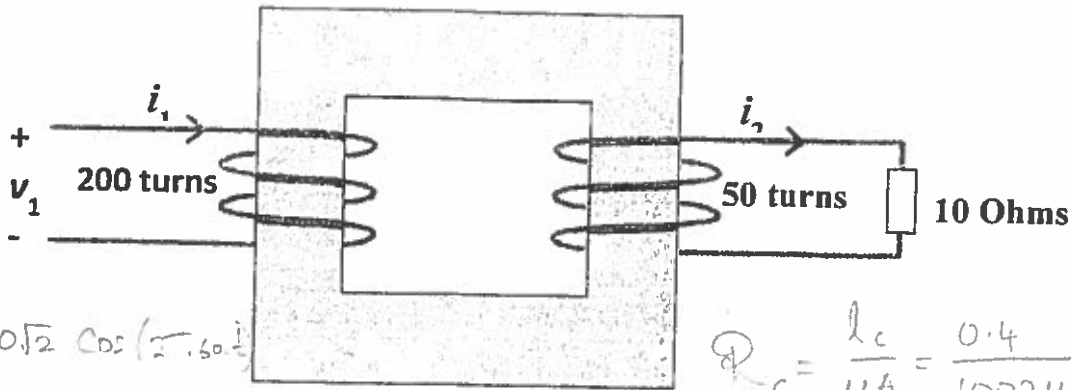Problem 3. (25 points)

The iron core in the following circuit has a relative permeability of 1000, cross-sectional area of 20cm^2 , and a mean length of 40cm . Neglect any leakage flux and all losses. $v_1 = 120\text{ V rms}$ at 60Hz (sinusoidal in time) is applied to the left coil.



$$v_1 = 120\sqrt{2} \cos(2\pi \cdot 60 \cdot t)$$

$$R_c = \frac{l_c}{\mu A} = \frac{0.4}{1000 \mu_0 \times 20 \times 10^{-4}} = 15915 \text{ A}^2/\text{Wb}^2$$

- What is the peak flux and the peak flux density in the iron core?
- How much current in the left coil (RMS magnitude) would be required to establish this flux?
- What is the current, i_2 , (RMS magnitude) through the 10 Ohm resistor?
- What is the total current, i_1 , (RMS magnitude) in the left coil?

$$\begin{aligned} \text{a) } v_1 &= \frac{d\lambda_1}{dt} \Rightarrow \lambda_1 = \int v_1 dt = \int 120\sqrt{2} \cos(2\pi \cdot 60 \cdot t) \\ &= \frac{120\sqrt{2}}{2\pi \cdot 60} \sin(2\pi \cdot 60 \cdot t) \end{aligned}$$

$$\Phi_{\text{peak}} = \frac{\lambda_{1\text{peak}}}{N_1} = \frac{120\sqrt{2}}{2\pi \cdot 60 \cdot 200} = 0.00225 \text{ Webers}$$

$$B_{\text{peak}} = \frac{\Phi_{\text{peak}}}{A_{\text{core}}} = \frac{0.00225}{20 \times 10^{-4}} = 1.125 \text{ T}$$

$$\begin{aligned} \text{b) } NI &= \oint H \Rightarrow I_{\text{magnetizing}} = \frac{\Phi_{\text{rms}} \cdot R_c}{N_1} = \frac{0.00225/\sqrt{2} \times 15915}{200} \\ &= 1.27 \text{ A rms} \end{aligned}$$

$$\text{c) } \text{No leakage} \Rightarrow \frac{V_1}{V_2} = \frac{N_1}{N_2} \Rightarrow V_2 = \frac{120 \times 50}{200} = 30 \text{ V}$$

$$I_2 = \frac{V_2}{Z_2} = \frac{30}{10} = 3 \text{ A}$$

d. I_2 referred to primary, $I_2' = \frac{N_2 I_2}{N_1} = \frac{50 \cdot 3}{200}$
 $= 0.75 \text{ A}$

$$I_{1 \text{ total}} = I_m + I_2'$$

↑
↑
 Current through inductor Current through resistor



$$I_1 = \sqrt{0.75^2 + 1.27^2} = 1.47 \text{ A}$$



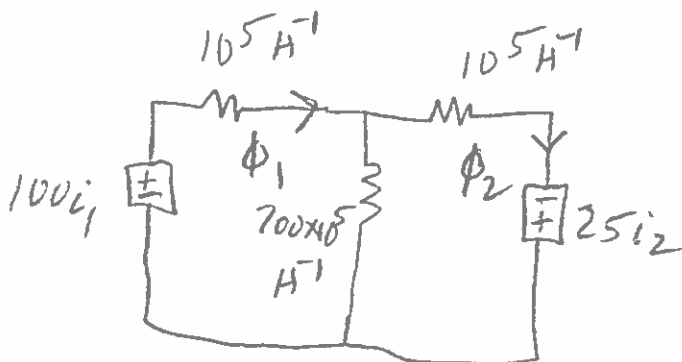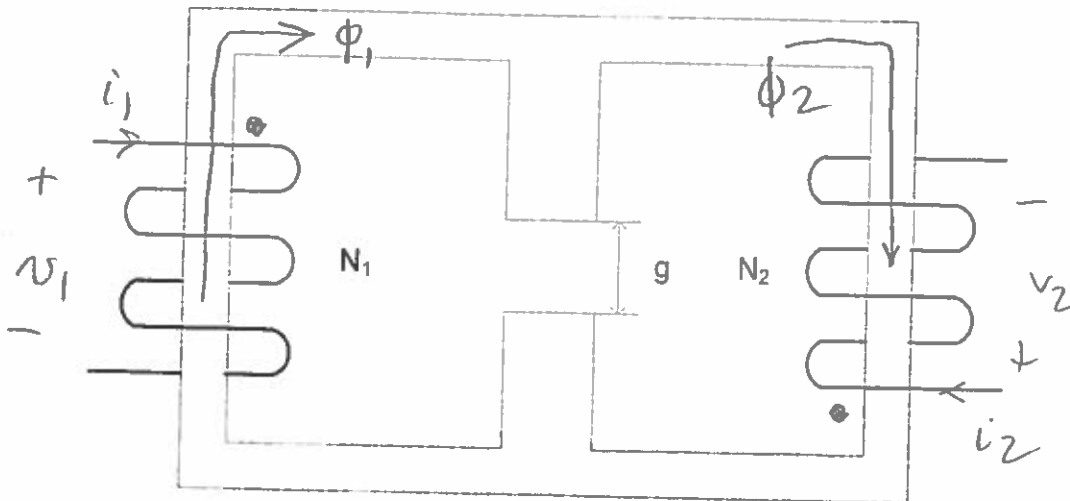Problem 4. (25 points)

In the figure below, $N_1 = 100$, $N_2 = 25$. The reluctances of the left and right branches of the core are each $1 \times 10^5 \text{ H}^{-1}$. The gap, g , in the center post is 1 cm, and the cross-sectional area of the center post is 4 cm^2 . Neglect fringing and the effect of the steel in the center post. The resistance of the left coil (primary) is 1 ohm and the resistance of the right coil (secondary) is 0.05 ohm.

- Label voltages v_1 and v_2 and currents i_1 and i_2 so that all self and mutual inductance terms are positive. Assign dot polarities. Assign v_1 and i_1 to the primary and v_2 and i_2 to the secondary.
- Find L_1 (self inductance of the primary), L_2 (self inductance of the secondary), and M (mutual inductance between coils).
- Treating this structure as a non-ideal transformer, draw the equivalent circuit with all impedances referred to the primary (assume a 60Hz supply and use the frequency domain).



$$R_{gap} = \frac{.01}{4\pi \times 10^{-7} \times 4 \times 10^{-4}} = 200 \times 10^5 \text{ H}^{-1}$$

$$\left. \begin{aligned} -100i_1 + 10^5\phi_1 + 200 \times 10^5(\phi_1 - \phi_2) &= 0 \\ -25i_2 + 10^5\phi_2 + 200 \times 10^5(\phi_2 - \phi_1) &= 0 \end{aligned} \right\} \begin{aligned} 201 \times 10^5 \phi_1 - 200 \times 10^5 \phi_2 &= 100i_1 \\ -200 \times 10^5 \phi_1 + 201 \times 10^5 \phi_2 &= 25i_2 \end{aligned}$$

$$\phi_2 = .1244 \times 10^{-5} i_2 + .995 \phi_1$$

$$201 \times 10^5 \phi_1 - 199 \times 10^5 \phi_1 = 100 i_1 + 24.88 i_2$$

$$2 \times 10^5 \phi_1 = 100 i_1 + 24.88 i_2$$

$$\phi_1 = .0005 i_1 + .000124 i_2$$

$$\mathcal{F}_1 = N_1 \phi_1 = .05 i_1 + .0124 i_2$$

$$\phi_2 = .1244 \times 10^{-5} i_2 + .995 (.0005 i_1 + .000124 i_2)$$

$$= .0004975 i_1 + .000125 i_2$$

$$\mathcal{F}_2 = N_2 \phi_2 = .0124 i_1 + .003125 i_2$$

$$L_1 = .05 \text{ H} \quad m = .0124 \text{ H} \quad L_2 = .003125 \text{ H}$$

$$L_{m1} = .0124 \times \frac{100}{25} = .0496 \text{ H}$$

$$L_{L1} = L_1 - L_{m1} = .0004 \text{ H}$$

$$L_{m2} = .0124 \frac{25}{100} = .0031 \text{ H} \quad \text{so } L_{L2} = L_2 - L_{m2} = .000025 \text{ H}$$

