

1. _____/25

2. _____/25

3. _____/25

4. _____/25

TOTAL _____/100

USEFUL INFORMATION

$$\sin(x) = \cos(x - 90^\circ) \quad \bar{V} = \bar{Z}\bar{I} \quad \bar{S} = \bar{V}\bar{I}^* = P + jQ \quad \bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$$

$$0 < \theta < 180^\circ \text{ (lag)} \quad I_L = \sqrt{3}I_\phi \text{ (delta)} \quad \bar{Z}_Y = \bar{Z}_\Delta/3$$



$$-180^\circ < \theta < 0 \text{ (lead)} \quad V_L = \sqrt{3}V_\phi \text{ (wye)} \quad \mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

ABC phase sequence has A at 0, B at -120°, and C at +120°

$$\int \underline{H} \cdot \underline{dl} = \int \underline{J_f} \cdot \underline{\hat{n}} dA \quad \int \underline{E} \cdot \underline{dl} = -\frac{d}{dt} \left(\int \underline{B} \cdot \underline{\hat{n}} dA \right) \quad \mathcal{R} = \frac{l}{\mu A} \quad Ni = \mathcal{R}\phi$$

$$\phi = BA \quad \lambda = N\phi = Li \text{ (if linear)} \quad v = \frac{d\lambda}{dt} \quad k = \frac{M}{\sqrt{L_1 L_2}}$$

$$1 \text{ hp} = 746 \text{ W}$$

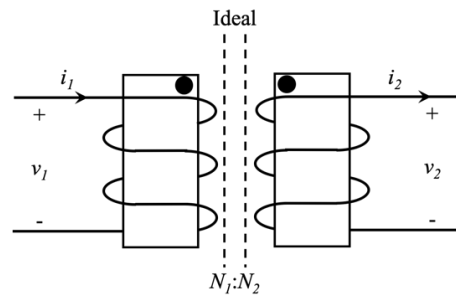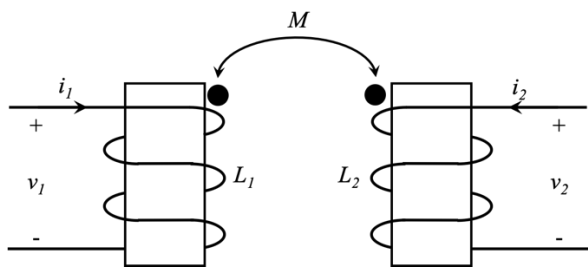


$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

$$a = \frac{N_1}{N_2} \quad N_1 i_1 = N_2 i_2$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

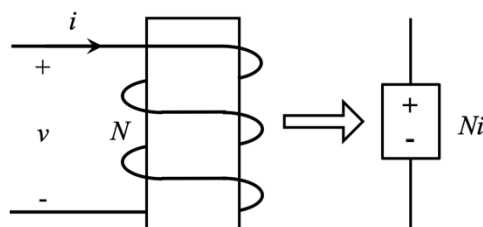

Problem 1 (25 Points)

4 single-phase loads are connected in parallel to a generator that supplies 480 V. The loads are given as:

- 1) A purely resistive load that consumes 50 kW
- 2) A load that consumes 10 kVA at a power factor of 0.707 leading
- 3) A load with impedance $Z = 120 + j50 \Omega$
- 4) A purely inductive load of 30 kVAR

- a) What is the total power supplied by the source? (12 points)

$$\begin{aligned}\bar{S}_1 &= 50 + j0 \text{ kVA} \\ \theta_2 &= -\cos^{-1}(0.707) = -45^\circ \\ \bar{S}_2 &= 10 \angle -45^\circ \text{ kVA} \\ &= 7.071 - j7.071 \text{ kVA}\end{aligned}$$

$$\begin{aligned}\bar{Z}_3 &= 120 + j50 \Omega \\ &= 130 \angle 22.620^\circ \Omega \\ \bar{S}_3 &= \frac{V^2}{\bar{Z}} \angle 22.620^\circ \\ \bar{S}_3 &= 1.772 \angle 22.620^\circ \text{ kVA} \\ &= 1.636 + j0.682 \text{ kVA} \\ \bar{S}_4 &= 0 + j30 \text{ kVA}\end{aligned}$$

$$\begin{aligned}\bar{S}_{tot} &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 + \bar{S}_4 \\ \bar{S}_{tot} &= 58.706 + j23.610 \text{ kVA} \\ &= 63.276 \angle 21.908^\circ \text{ kVA}\end{aligned}$$

- b) What is the source current? (5 points)

$$\begin{aligned}\bar{S}_{tot} &= V \bar{I}_s^* \\ \bar{I}_s &= \left(\frac{\bar{S}_{tot}}{V} \right)^* \\ \bar{I}_s &= 131.824 \angle -21.908^\circ \text{ A}\end{aligned}$$

- c) A capacitor is connected in parallel with the loads to make the power factor 0.995 lagging. What is the magnitude of the new source current? (8 points)

$$\begin{aligned}\theta_n &= \cos^{-1}(0.995) \\ &= 5.732^\circ \\ Q_n &= P \tan(\theta_n) \\ Q_n &= 5893 \text{ kVAR} \\ S_n &= \sqrt{P^2 + Q_n^2} \\ S_n &= 59.001 \text{ kVA} \\ I_n &= \frac{S_n}{V} \\ I_n &= 122.919 \text{ A}\end{aligned}$$

Problem 2 (25 points)

Three 3-phase loads are connected in parallel to a wye-connected source with 208 V line to line. The loads are given as:

- 1) A wye connected load consuming 10 kVA at a 0.95 leading power factor
- 2) A wye connected load consuming 80 kW at a 0.975 lagging power factor
- 3) A delta connected load with impedance $Z=15+j8 \Omega$


- a) What is the source line current? (13 points)

$$\begin{aligned}
 \theta_1 &= \cos^{-1}(0.95) \\
 \theta_1 &= -18.195^\circ \\
 \bar{S}_1 &= 10 \angle -18.195^\circ \text{ kVA} \\
 &= 9.5 - j3.123 \text{ kVA} \\
 \theta_2 &= \cos^{-1}(0.975) \\
 \theta_2 &= 12.837^\circ \\
 \bar{S}_2 &= \frac{80}{0.975} \angle 12.837^\circ \\
 \bar{S}_2 &= 80 + j18.232 \text{ kVA} \\
 \bar{Z}_{\Delta} &= 15 + j8 \Omega \\
 &= 17 \angle 28.073^\circ \Omega \\
 \bar{Z}_{\Delta Y} &= \frac{\bar{Z}_{\Delta}}{3} \angle 28.073^\circ \\
 \bar{Z}_{\Delta Y} &= 5.667 \angle 28.073^\circ \Omega \\
 \bar{S}_3 &= 3 \left(\frac{120^2}{5.667} \right) \angle 28.073^\circ \\
 \bar{S}_3 &= 7.635 \angle 28.073^\circ \text{ kVA} \\
 &= 6.737 + j3.593 \text{ kVA} \\
 \bar{S}_{tot} &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 \\
 &= 96.237 + j18.703 \text{ kVA} \\
 &= 98.037 \angle 10.998^\circ \text{ kVA} \\
 \bar{S}_{tot} &= \sqrt{3} \bar{V}_L \bar{I}_L^* \\
 \bar{I}_L &= \left(\frac{\bar{S}_{tot}}{\sqrt{3} \bar{V}_L} \right)^* \\
 \bar{I}_L &= 272.124 \angle -10.998^\circ \text{ A}
 \end{aligned}$$

- b) A delta connected capacitor bank is added in parallel to the three loads to make the overall power factor 0.995 lagging. What is the new source line current? (12 points)

$$\begin{aligned}
 \theta_n &= \cos^{-1}(0.995) \\
 \theta_n &= 5.732^\circ \\
 Q_n &= P \tan(\theta_n) \\
 Q_n &= 9.660 \text{ kVAR} \\
 \bar{S}_n &= 96.237 + j9.660 \text{ kVA} \\
 \bar{S}_n &= 96.720 \angle 5.732^\circ \text{ kVA} \\
 \bar{I}_L &= \left(\frac{\bar{S}_{tot}}{\sqrt{3} \bar{V}_L} \right)^* \\
 \bar{I}_L &= 268.468 \angle -5.732^\circ \text{ A}
 \end{aligned}$$

Problem 3 (25 Points)

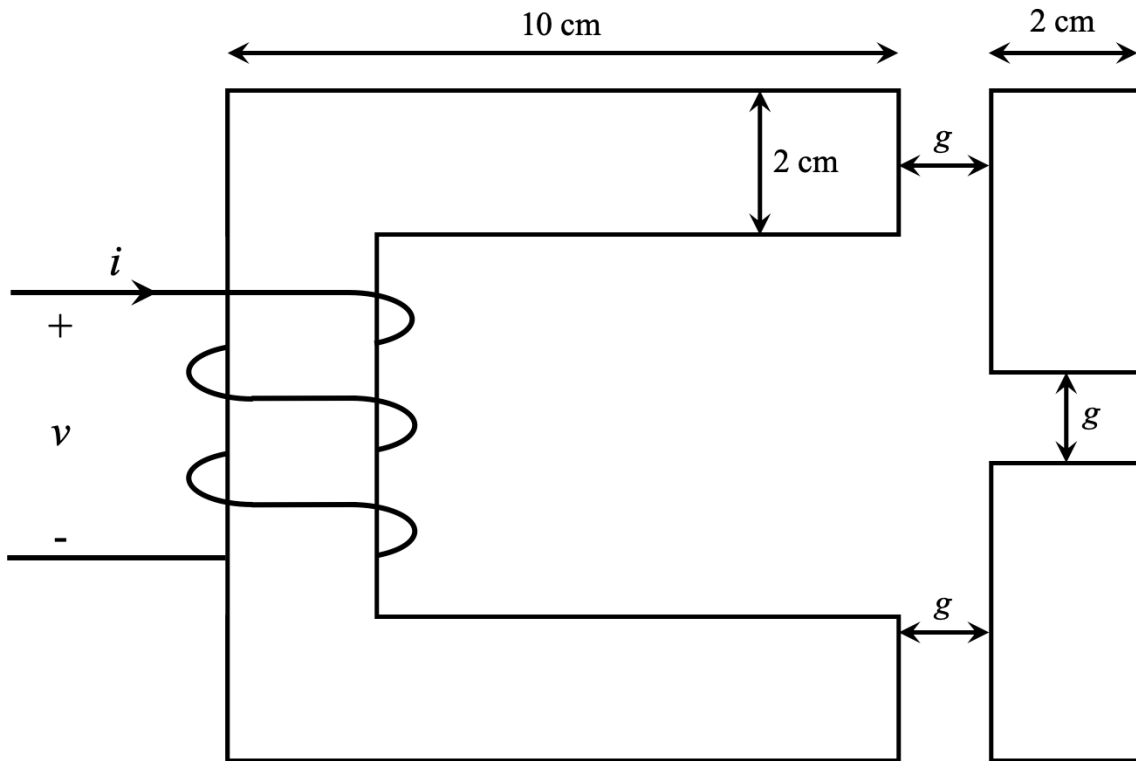

A coil is wound 250 times around an iron core with infinite permeability (dimensions given above) that has an air gap of 5 mm and a depth into the page of 3 cm. Fringing effects are included.


With the voltage polarity and current direction as defined above:

- a) What is the area of the air gap (include fringing)? (3 points)

$$A = (2\text{ cm} + 5\text{ mm})(3\text{ cm} + 5\text{ mm})$$

$$A = 0.000875\text{ m}^2$$

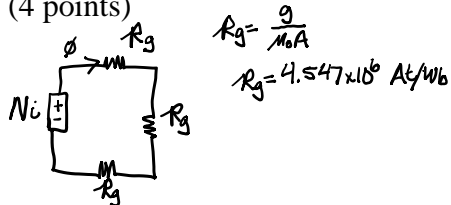- b) Draw the magnetic equivalent circuit and determine the reluctance values for the air gap. (4 points)



- c) What is the inductance of the coil? (10 points)

$$N\dot{L} = \oint (3R_g)$$

$$\phi = \frac{N}{3R_g} \dot{L}$$

$$\lambda = N\phi \Rightarrow \lambda = \frac{N^2}{3R_g} \dot{L} = L\dot{L}$$

$$L = \frac{N^2}{3R_g}$$

$$L = 0.00458 \text{ H}$$

- d) What is the inductance of the coil if fringing is neglected? (8 points)


$$A = 0.0006$$

$$R_g = \frac{l}{\mu_0 \mu_r A} = 6.631 \times 10^6 \text{ At/Wb}$$

$$L = \frac{N^2}{3R_g}$$


$$L = 0.00314 \text{ H}$$

Problem 4 (25 Points)

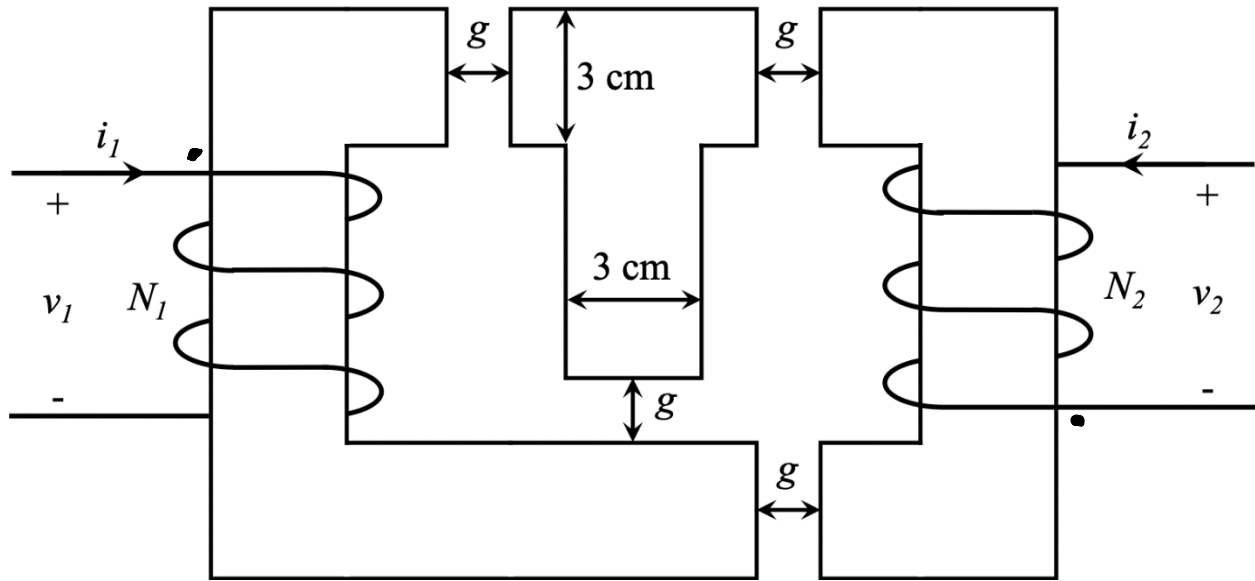

Two coils are wrapped around an iron core with infinite permeability as shown. Coil 1 has 400 turns while coil 2 has 100 turns. The air gap g is 2.5 mm and the depth into the page is 2 cm. Neglect fringing.

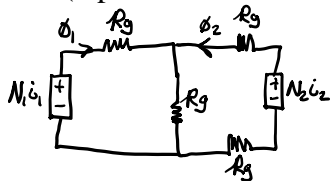- Put the dot markings on the two coils. (5 points)
- What is the self-inductance and the mutual inductance of the two coils? (5 points each=15 total points)



$$R_g = \frac{g}{\mu_0 \mu_r A}$$

$$A = 0.0006 \text{ m}^2$$

$$R_g = 3.316 \times 10^6 \text{ At/Wb}$$

$$N_1 i_1 = \phi_1 R_g + (\phi_1 + \phi_2) R_g$$

$$N_1 i_1 = 2\phi_1 R_g + \phi_2 R_g$$

$$\phi_2 = \frac{N_1 i_1 - 2\phi_1 R_g}{R_g}$$

$$\phi_2 = \frac{N_1 i_1 - 2(\frac{3}{5} N_1 i_1 - \frac{1}{5} N_2 i_2)}{R_g}$$

$$\phi_2 = -\frac{1}{5} \frac{N_1 i_1}{R_g} + \frac{2}{5} \frac{N_2 i_2}{R_g}$$

$$\lambda_1 = N_1 \phi_1 \Rightarrow \lambda_1 = \frac{3}{5} \frac{N_1^2}{R_g} i_1 - \frac{1}{5} \frac{N_1 N_2}{R_g} i_2$$

$$\lambda_2 = N_2 \phi_2 \Rightarrow \lambda_2 = -\frac{1}{5} \frac{N_1 N_2}{R_g} i_1 + \frac{2}{5} \frac{N_2^2}{R_g} i_2$$

$$L_1 = 0.02895 \text{ H}$$

$$L_2 = 0.001206 \text{ H}$$

$$M = 0.002413 \text{ H}$$

- c) What is the RMS magnitude of the open circuit voltage on coil 2 if $i_1(t) = 10\cos(377t)$?
(5 points)

$$V_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = \frac{d\lambda_2}{dt} = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

Open circuit: $i_2 = 0$

$$\begin{aligned} \frac{di_1}{dt} &= -10(377)\sin(377t) \\ &= 10(377)\sin(-377t) \\ &= 10(377)\cos(-377t - 90^\circ) \\ &= 10(377)\cos(377t + 90^\circ) \end{aligned}$$

$$V_2 = -M \frac{di_1}{dt}$$

$$\begin{aligned} V_2 &= -9.096 \cos(377t + 90^\circ) \text{ V} \\ &= 9.096 \cos(377t + 90^\circ - 180^\circ) \text{ V} \\ &= 9.096 \cos(377t - 90^\circ) \text{ V} \end{aligned}$$

$$V_{2\text{rms}} = \frac{9.096}{\sqrt{2}}$$

$$V_{2\text{rms}} = 6.432 \text{ V}$$

(Blank page for extra work)