
ECE 333 – Renewable Energy Systems

2. Power System Basics – AC Analysis

George Gross

**Department of Electrical and Computer Engineering
University of Illinois at Urbana-Champaign**

SINUSOIDAL VARIABLES


- ❑ In AC circuits, the basic current and voltage variables are considered to be sinusoidal functions
- ❑ A sinusoidal function is

$$x(t) = X_m \cos(\omega t + \theta)$$

time magnitude or amplitude angular frequency phase angle

SINUSOIDAL VARIABLES

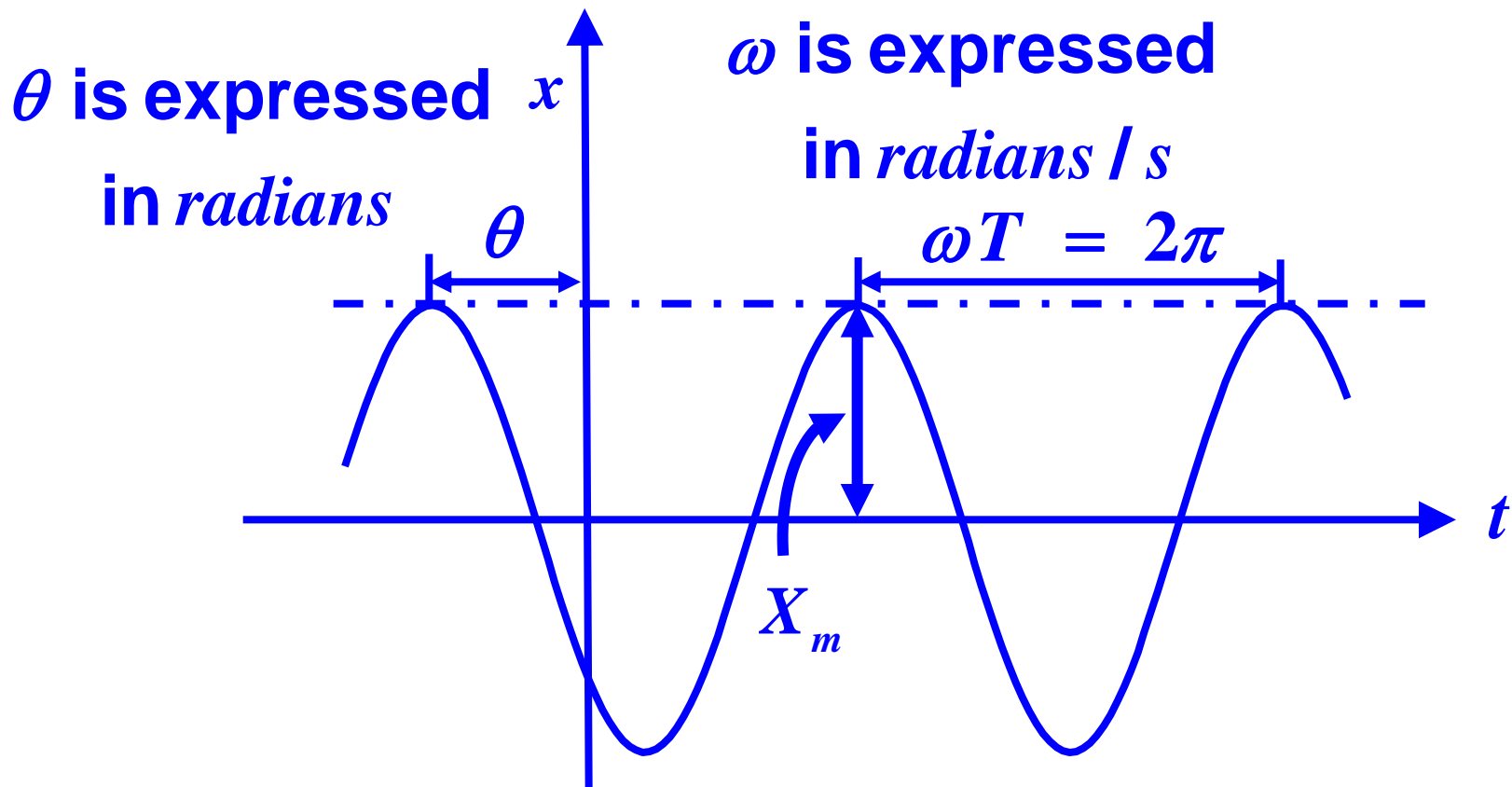- The argument of the sinusoidal function is radians and so:



ANGULAR FREQUENCY ω

- We can also express the argument of the sinusoidal function in terms of the frequency f given in Hz or cycles per second with

$$\omega = 2\pi f$$

radians/s *radians / cycle* *Hz*

ANGULAR FREQUENCY ω

- The periodic sinusoidal function has a period of T s, where

$$\textit{s/cycle} \longrightarrow T = \frac{1}{f} \longleftarrow \textit{cycles/s}$$

that is each cycle (or period) takes T s

- We may express $x(t)$ therefore as

$$\begin{aligned} x(t) &= X_m \cos(\omega t + \theta) = X_m \cos(2\pi f t + \theta) \\ &= X_m \cos\left(\frac{2\pi}{T} t + \theta\right) \end{aligned}$$

AC SYSTEM

- The current in the AC system is specified by

$$i(t) = I_m \cos(\omega t + \theta_i)$$

- The use of the cosine function is rather *arbitrary* since for arbitrary angle ϕ

$$\sin(\phi) = \cos\left(\frac{\pi}{2} - \phi\right)$$

or equivalently

$$\cos(\phi) = \sin\left(\frac{\pi}{2} - \phi\right)$$

AC SYSTEM

- The voltage is also sinusoidal

$$v(t) = V_m \cos(\omega t + \theta_v)$$

- The power is

$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_i) \cos(\omega t + \theta_v)$$

- Recall that

$$\cos \phi \cos \xi = \frac{1}{2} [\cos(\phi + \xi) + \cos(\phi - \xi)]$$

POWER EXPRESSION FOR NETWORK

□ We are interested in evaluating the average

value of $p(t)$: since we are focusing on two

periodic functions each with the **identical** period

T , the average value is the same as the average

value over a period

AC SYSTEM

□ Therefore

$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_0^T p(t) dt \\ &= \frac{V_m I_m}{2T} \int_0^T \left[\cos(2\omega t + \theta_i + \theta_v) + \cos(\theta_i - \theta_v) \right] dt \\ &= \frac{V_m I_m}{2T} \cos \left(\underbrace{\theta_i - \theta_v}_{\theta} \right) \cdot T \end{aligned}$$

AC SYSTEM

where we use the fact that the average value of a sinusoid is 0 , as the positive and negative areas cancel out

□ Therefore

$$P_{avg} = \frac{1}{2} V_m I_m \cos \theta$$

EFFECTIVE VALUE

□ The effective value of a periodic variable is the square root of the average of the squared value of the variable

□ For current

$$I \triangleq \left[\frac{1}{T} \int_0^T i^2(t) dt \right]^{\frac{1}{2}}$$

EFFECTIVE VALUE

□ We next evaluate I

$$I = \left[\frac{1}{T} \int_0^T I_m^2 \underbrace{\cos^2(\omega t + \theta_i)}_{\downarrow} dt \right]^{\frac{1}{2}}$$
$$\frac{1}{2} \left[\underbrace{\cos 2(\omega t + \theta_i) + \cos(\theta)}_{\downarrow} \right]$$
$$\frac{1}{2} \left[1 + \cos 2(\omega t + \theta_i) \right]$$
$$I = \frac{I_m}{\sqrt{2}}$$

EFFECTIVE VALUE

- ❑ The value I is referred to as the *r.m.s.* value
- ❑ The *r.m.s.* value of a sinusoid equals its amplitude divided by $\sqrt{2}$
- ❑ The 240-V 60-Hz voltage at which electricity is supplied to a dryer is understood to mean that

$$V = 240 \text{ V}$$

and so

$$V_m = 240\sqrt{2} = 339.41 \text{ V}$$

AC SYSTEM

$$V_m = 240\sqrt{2} = 339.41V$$

with the angular frequency

$$\omega = 2\pi \cdot 60 = 377 \text{ radians/s}$$


and so we have the sinusoid

$$v(t) = 339.41 \cos(377t + \theta_v)$$

- We henceforth adopt the **convention of treating incoming voltage as having $\theta_v = 0$** and we measure all other variables with respect to the **reference voltage**

r.m.s. VALUE OF A SQUARE WAVE

□ We consider the *square wave*

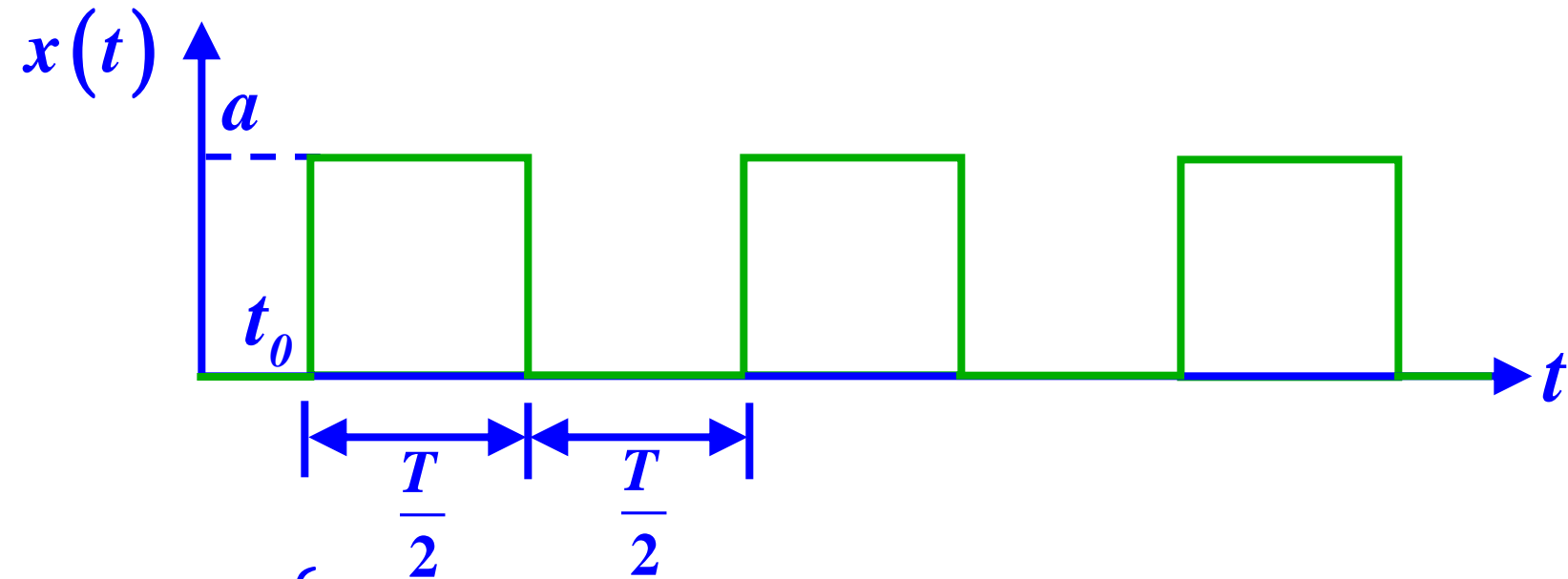


$$x(t) = \begin{cases} a & t_0 + (n-1)T \leq t \leq t_0 + (2n-1)\frac{T}{2} \\ 0 & t_0 + (2n-1)\frac{T}{2} < t < t_0 + nT \end{cases} \quad n = 1, 2, \dots$$

r.m.s. VALUE OF A SQUARE WAVE

- We compute the *r.m.s.* value of $x(t)$ by evaluating the average value over a cycle

$$\begin{aligned} X &= \left\{ \frac{1}{T} \int_{t_0}^{t_0+T} [x(t)]^2 dt \right\}^{\frac{1}{2}} = \left\{ \frac{1}{T} \int_{t_0}^{t_0+\frac{T}{2}} a^2 dt \right\}^{\frac{1}{2}} \\ &= \left[\frac{a^2}{T} \cdot \frac{T}{2} \right]^{\frac{1}{2}} \\ &= \frac{a}{\sqrt{2}} \end{aligned}$$

IDEAL RESISTOR IN AC NETWORKS

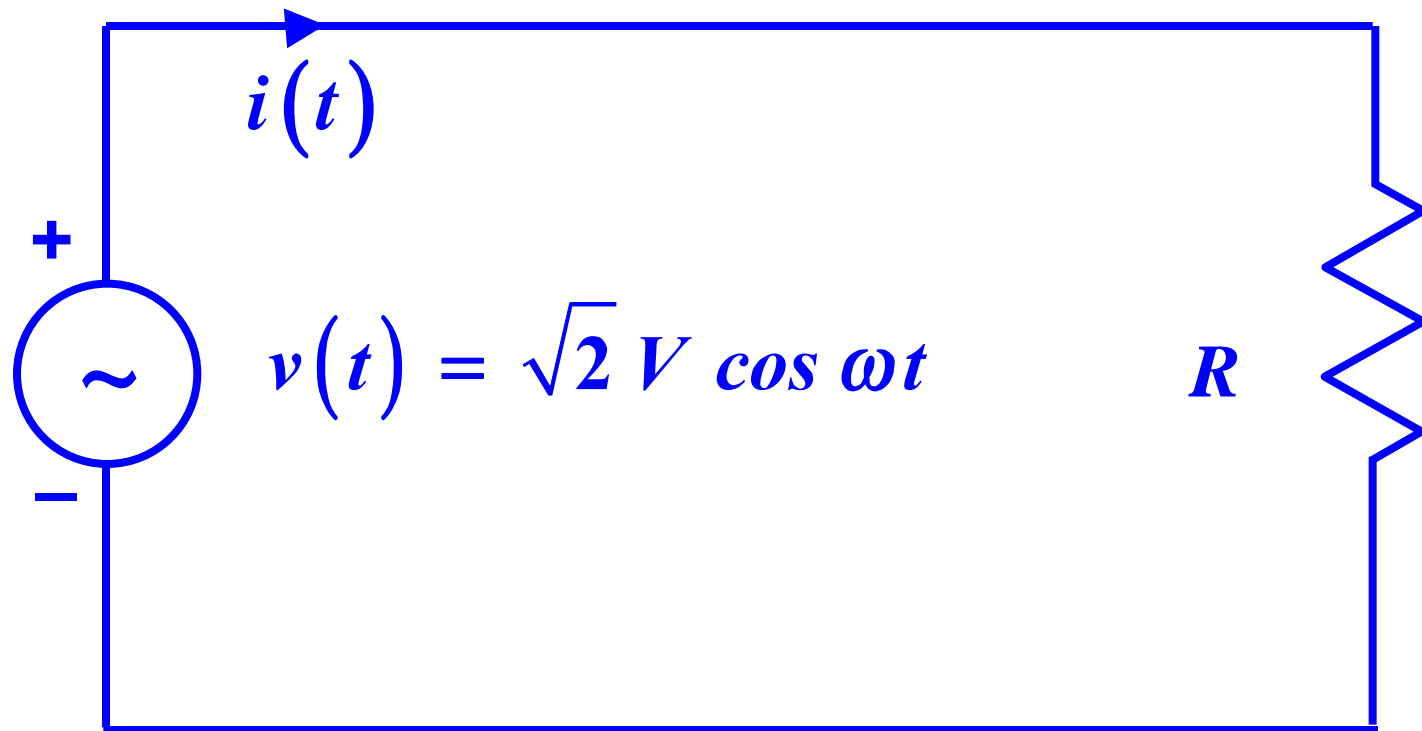

IDEAL RESISTOR IN AC NETWORKS

- We analyze the behavior of an ideal resistor in a circuit with a sinusoidal voltage source

$$v(t) = V_m \cos \omega t$$

or in the terms of the *r.m.s.* voltage V

$$v(t) = \sqrt{2} V \cos \omega t$$

- Now,

$$i(t) = \frac{v(t)}{R} = \sqrt{2} \frac{V}{R} \cos \omega t$$

IDEAL RESISTOR IN AC NETWORKS

is the current through the resistor with *r.m.s.*

value

$$I = \frac{V}{R}$$

□ Since there is a 0 angle phase difference

between the $v(t)$ and $i(t)$ sinusoids, we say that

the two sinusoids are *in phase* with each other

IDEAL RESISTOR IN AC NETWORKS

- The evaluation of the average power is

$$P_{avg} = VI \cos(\underbrace{\theta_v - \theta_i}_0) = VI = \frac{V^2}{R} = I^2 R$$

- In AC networks, power is always interpreted as average power and so we drop the *avg* subscript and write

$$P = VI = I^2 R = \frac{V^2}{R}$$

and P represents the average power

EXAMPLE: CUISINART TOASTER

- The two-slot Cuisinart toaster uses 1,500 W of power when plugged into a 120-V socket at 60 Hz; the appliance is modeled as a simple resistor
- We compute from

$$P = \frac{V^2}{R}$$

the value of the resistance

$$R = \frac{V^2}{P} = \frac{120 \cdot 120}{1,500} = \frac{14,400}{1,500} = 9.6 \Omega$$

EXAMPLE: CUISINART TOASTER

- The current is

$$I = \frac{V}{R} = \frac{120}{9.6} = 12.5 \text{ A}$$

- Now suppose there is a voltage spike of 125 V and so the dissipated power becomes


$$P = \frac{V^2}{R} = \frac{125 \cdot 125}{9.6} = 1627.6 \text{ W}$$

representing an increase of 127.6 W in the toaster consumption – an 8.5 % increase

IDEALIZED CAPACITOR IN AC NETWORKS

- Recall the *equation of motion* for a capacitor

$$i(t) = C \frac{dv}{dt}$$

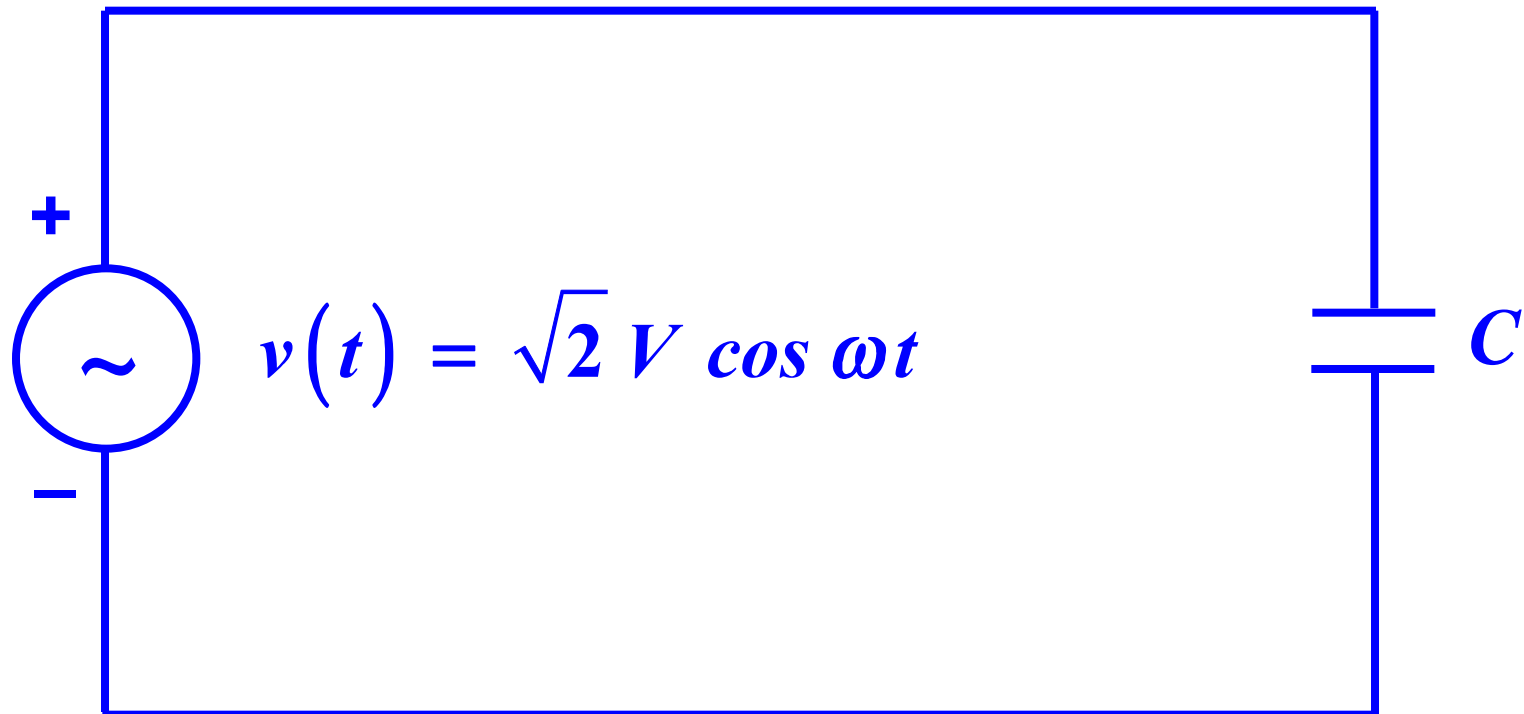

IDEALIZED CAPACITOR IN AC NETWORKS

- For a sinusoidal voltage in an AC network

$$i(t) = C \frac{d}{dt} \left[\sqrt{2} V \cos \omega t \right] = -\omega C \sqrt{2} V \sin \omega t$$

- We use the identity

$$\sin \phi = \cos \left(\frac{\pi}{2} - \phi \right) = -\cos \left(\frac{\pi}{2} - \phi - \pi \right) = -\cos \left(\phi + \frac{\pi}{2} \right)$$

- Thus

$$i(t) = \omega C \sqrt{2} V \cos \left(\omega t + \frac{\pi}{2} \right)$$

IDEALIZED CAPACITOR IN AC NETWORKS

□ Therefore, the voltage across the capacitor and the current through it are

- same frequency sinusoids

- there is a $\frac{\pi}{2}$ *radians* shift between the two

waveforms

- the current *leads* the voltage by $\frac{\pi}{2}$ and so

IDEALIZED CAPACITOR IN AC NETWORKS

□ Let

$$I = \omega CV$$

and so

$$i(t) = \sqrt{2}I \cos \left(\omega t + \frac{\pi}{2} \right)$$

IDEALIZED CAPACITOR IN AC NETWORKS

- We summarize

$$V = \left(\frac{1}{\omega C} \right) I \longleftarrow \begin{array}{l} \text{AC version of } \textit{Ohm's Law} \\ \text{for capacitors} \end{array}$$

- The power dissipated by the capacitor is

$$p(t) = v(t) i(t) = \sqrt{2} V \cos \omega t \sqrt{2} I \cos \left(\omega t + \frac{\pi}{2} \right)$$

and this simplifies to

IDEALIZED CAPACITOR IN AC NETWORKS

$$p(t) = 2VI \cdot \frac{1}{2} \left[\cos\left(2\omega t + \frac{\pi}{2}\right) \right] + \underbrace{\cos\left(-\frac{\pi}{2}\right)}_0$$
$$= VI \cos\left(2\omega t + \frac{\pi}{2}\right)$$

□ Since the average value of a sinusoid is 0

$$P_{avg} = 0$$

and so for a capacitor

$$P = 0$$

CAPACITOR EXAMPLE

- We consider the current through a $200 \mu F$ capacitor supplied by a $120\text{-V } 60\text{-Hz}$ source
- The voltage is given by

$$v(t) = \sqrt{2} 120 \cos \omega t$$

and the current is therefore

$$i(t) = \sqrt{2} I \cos \left(\omega t + \frac{\pi}{2} \right)$$


with

$$I = \sqrt{2} (2\pi 60)(120)(200 \cdot 10^{-6}) = 9.048 \text{ A}$$

IDEALIZED INDUCTOR IN AC NETWORKS

- Recall the equation of motion for an inductor

$$v(t) = L \frac{di}{dt}$$

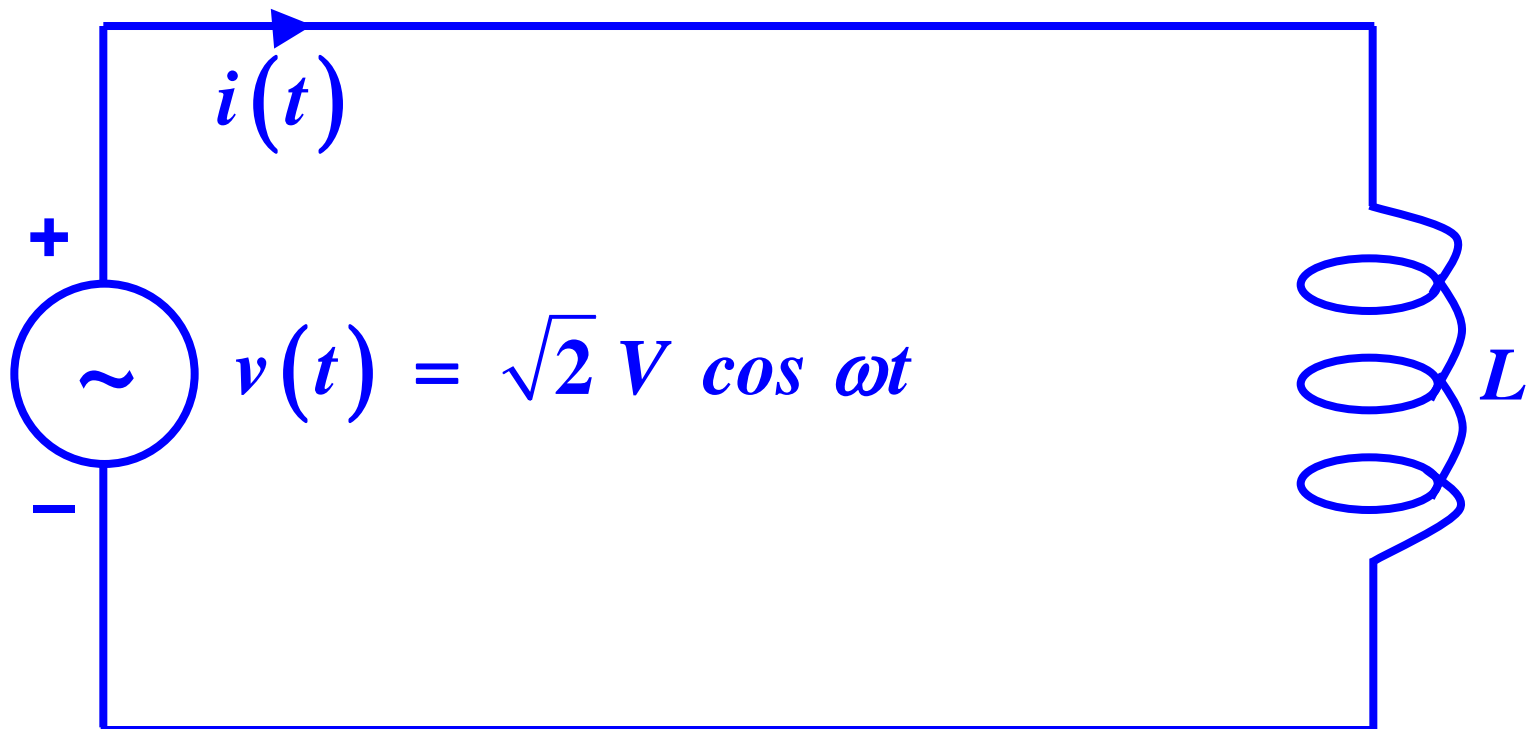

IDEALIZED INDUCTOR IN AC NETWORKS

and so

$$i(t) = \frac{1}{L} \int_0^t v(\xi) d\xi$$

□ For the sinusoidal voltage

$$v(t) = \sqrt{2} V \cos \omega t$$

we have

$$i(t) = \frac{1}{L} \int_0^t \sqrt{2} V \cos \omega \xi d\xi = \frac{\sqrt{2} V}{\omega L} \sin \omega t$$

□ We use the identity

$$\sin \phi = \cos \left(\phi - \frac{\pi}{2} \right)$$

IDEALIZED INDUCTOR IN AC NETWORKS

□ Thus

$$i(t) = \sqrt{2} \frac{V}{\omega L} \cos\left(\omega t - \frac{\pi}{2}\right)$$

□ Therefore, the voltage across the inductor and the current through it are

- same frequency sinusoids
- there is a $\frac{\pi}{2}$ radians shift between the two waveforms

IDEALIZED INDUCTOR IN AC NETWORKS

- the current *lags* behind the voltage by $\frac{\pi}{2}$

□ Let

$$I = \frac{1}{\omega L} V$$

and so

$$i(t) = \sqrt{2} I \cos\left(\omega t - \frac{\pi}{2}\right)$$

□ We summarize:

$$V = \omega L I$$

AC version of

Ohm's Law for

inductors

IDEALIZED INDUCTOR IN AC NETWORKS

- The power dissipated by the inductor is

$$p(t) = v(t) i(t) = \sqrt{2} V \cos \omega t \sqrt{2} I \cos \left(\omega t - \frac{\pi}{2} \right)$$

and this simplifies to

$$p(t) = 2VI \cdot \frac{1}{2} \left[\cos \left(2\omega t - \frac{\pi}{2} \right) + \underbrace{\cos \left(\frac{\pi}{2} \right)}_0 \right]$$
$$= VI \cos \left(2\omega t - \frac{\pi}{2} \right)$$

IDEALIZED INDUCTOR IN AC NETWORKS

- Clearly

$$p_{avg} = 0$$

and so

$$P = 0$$

- Neither capacitors nor inductors incur the consumption of real power

POWER FACTOR

- We may generalize the expressions for resistors capacitors and inductors for a sinusoidal

$$v(t) = \sqrt{2} V \cos \omega t$$

and a current

$$i(t) = \sqrt{2} I \cos(\omega t + \theta)$$

- Now, we have shown that

$$\theta = \begin{cases} 0 & \text{for a resistor} \\ \frac{\pi}{2} & \text{for a capacitor} \\ -\frac{\pi}{2} & \text{for an inductor} \end{cases}$$

POWER FACTOR

but for a network with an arbitrary combination of R , L and C components, θ is unknown

- We also showed earlier that the average value of power is

$$p_{avg} = V I \cos(\theta) \quad (*)$$

for

$$\theta = \theta_v - \theta_i$$

- Power engineers define the quantity $\cos \theta$ as the *power factor*

$$p f \triangleq \cos \theta$$

POWER FACTOR


- The expression in (*) is general and may apply to any circuit or circuit element, any combination of R , L and C elements and more importantly any component with sinusoidal voltage and current
- The interpretation of pf is the fraction that the real power represents of the total apparent power used by a particular component or system

EXAMPLE ON pf

- A small industrial customer is supplied by a $24\text{-kV } 60\text{-Hz}$ source to run a 1.5-MW real power load through a line with resistance R
- We compute the ratio of the real power line losses on the feeder line under two different pf values

$$S|_{pf_1} = 0.5 \quad \text{and} \quad S|_{pf_2} = \frac{\sqrt{3}}{2}$$

EXAMPLE ON pf

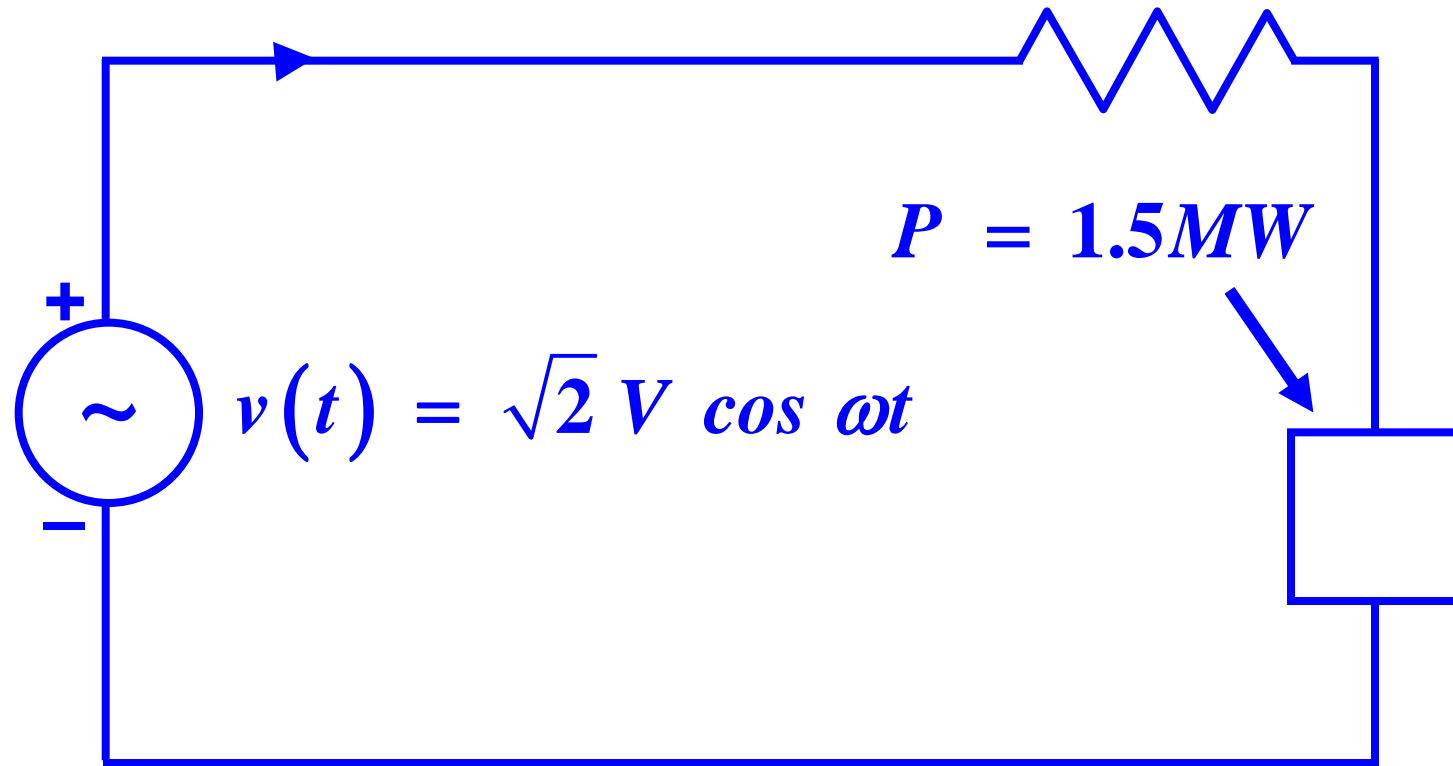

- **Basic assumption: the voltage drop through R is negligibly small**

EXAMPLE ON pf

□ Since

$$P = V I \cos \theta = 1.5 \text{ MW}$$

the *r.m.s.* value of the feeder current we compute under pf_1

$$I_1 = \frac{1.5 \text{ MW}}{\frac{1}{2}(24 \text{ kV})}$$

and also under pf_2

$$\frac{\text{MW}}{\text{kV}} = \text{kA}$$

$$I_2 = \frac{1.5 \text{ MW}}{\frac{\sqrt{3}}{2}(24 \text{ kV})}$$

EXAMPLE ON pf

□ The ratio of the losses is therefore

$$\frac{I_1^2 R}{I_2^2 R} = \left(\frac{I_1}{I_2} \right)^2 = \left(\frac{\frac{\sqrt{3}}{2}}{\frac{1}{2}} \right)^2 = (\sqrt{3})^2 = 3$$


□ There are 3 times higher losses under the poor

value pf_1 than the better value pf_2

THE POWER TRIANGLE

- There is an important relationship between the apparent power S , the real power P and the reactive power Q ; we represent this relationship by the so-called *power triangle* in the complex plane
- The power triangle is drawn as follows

THE POWER TRIANGLE

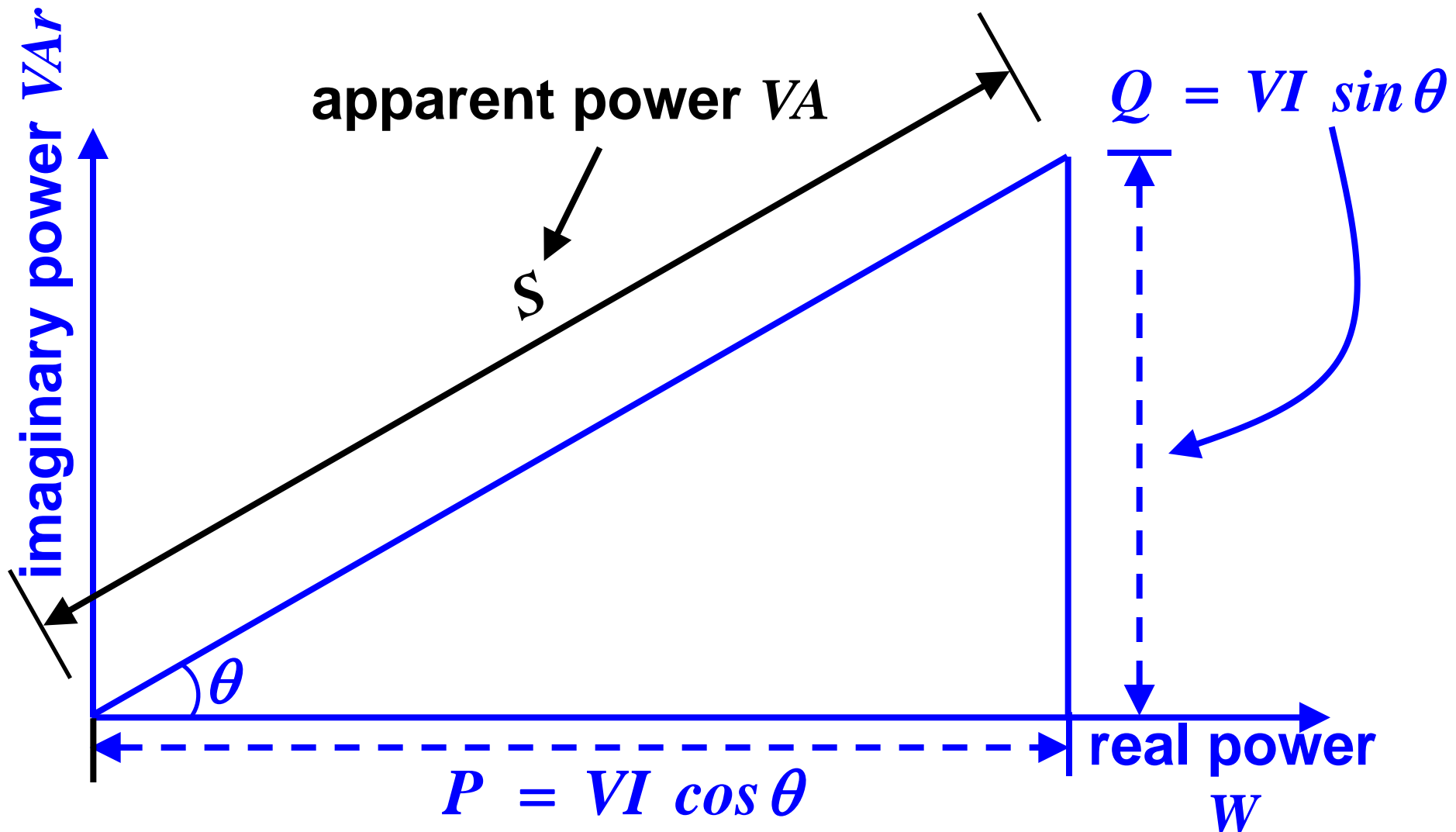

THE POWER TRIANGLE

$\theta > 0$ current *leads* voltage

$\theta < 0$ current *lags* voltage

$$S = VI$$

$$P = S \cos \theta \quad \leftarrow \text{real power}$$

$$Q = S \sin \theta \quad \leftarrow \text{reactive power}$$

$$S^2 = P^2 + Q^2 \quad \leftarrow \text{apparent power}$$

THE POWER TRIANGLE

- For an arbitrary consumptive load

$$P \geq 0$$

but

$$Q > 0 \quad \text{for an inductive load}$$

$$Q < 0 \quad \text{for a capacitive load}$$

- The actual power consumed by a load is the rate at which work is done and is measured in W
- The reactive power is incapable of doing work and its average is always 0 for either a capacitive or an inductive element

THE POWER TRIANGLE

- ❑ Power suppliers, typically, charge for P consumption but are impacted also by Q since the larger the Q the larger the line losses; in some cases charges are imposed on the basis of S or take into account the pf
- ❑ The presence of electric motors, which constitutes highly inductive loads, leads to increased losses on transmission lines

EXAMPLE: POWER TRIANGLE

- We consider a 250-V induction motor that draws 20 A of current to generate 4.33 kW of real power delivered to its shaft
- We draw the power triangle using

$$S = VI = 250 \cdot 20 = 5000 \text{ VA} = 5 \text{ kVA}$$


$$P = 4.33 \text{ kW}$$

$$\cos \theta = \frac{P}{S} = \frac{4.33}{5} = 0.866$$

$$\theta = \cos^{-1}(0.866) = \frac{\pi}{6}$$

$$Q = S \sin \theta = 2.5 \text{ kVAR}$$


EXAMPLE: POWER TRIANGLE

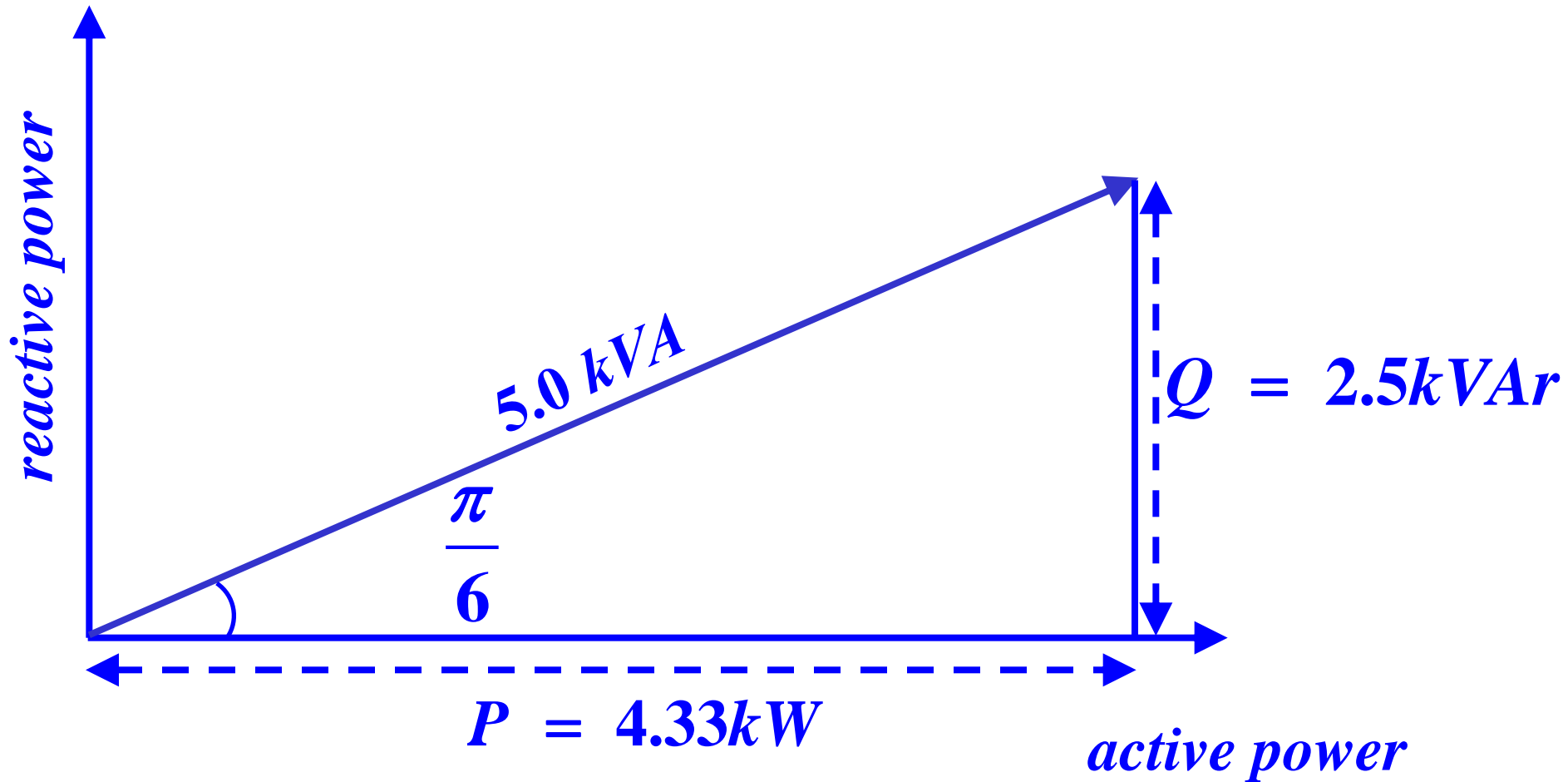

POWER FACTOR CORRECTION

- ❑ The smaller the pf the worse the utilization of power is; the ideal is to get **as near as possible** to the perfect pf of 1.0
- ❑ Sometimes it is desirable or necessary to use capacitors to correct the pf to offset the $VARs$ of the inductive elements
- ❑ A pf corrective action can lead to increased real power delivery to the loads

EXAMPLE: POWER FACTOR CORRECTION

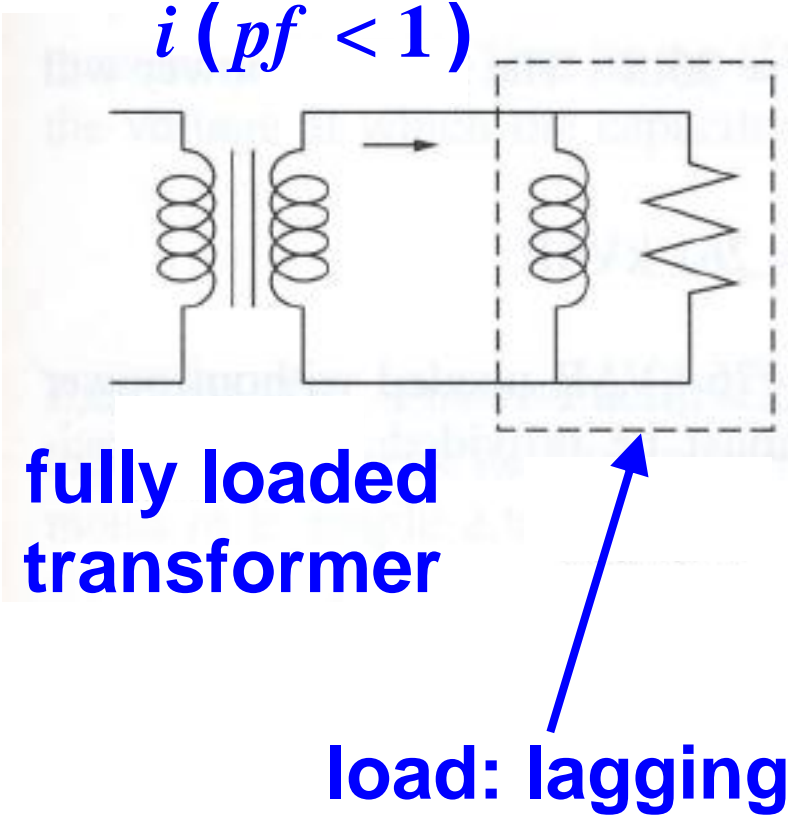

pf

EXAMPLE: POWER FACTOR CORRECTION

- ❑ A transformer is operating close to its kVA rating and is used to deliver 600 kVA at a 0.75 pf
- ❑ There is a 20% forecasted growth in the real power demand
- ❑ This growth needs to be accommodated without investing in a new transformer by installing capacitors for pf correction

EXAMPLE: POWER FACTOR CORRECTION

- The existing situation is characterized by

$$p f = 0.75 = \cos \theta$$

$$\theta = \cos^{-1}(0.75) = 0.72 \text{ radians}$$

$$P = 600 \cdot 0.75 = 450 \text{ kW}$$

$$Q = 600 \cdot 0.66 = 397 \text{ kVAR}$$

- The forecasted situation

$$P_{new} = 450(1.2) = 540 \text{ kW}$$

$$p f_{new} = \frac{540}{600} = 0.9$$

EXAMPLE: POWER FACTOR CORRECTION

$$\theta = \cos^{-1}(0.9) = 0.45 \text{ radians}$$

$$Q_{new} = 600(0.435) = 261 \text{ kVAr}$$


□ The difference between $Q = 476 \text{ kVAr}$ and

$Q_{new} = 261 \text{ kVAr}$ can be compensated by


capacitors

$$Q_c = 476 - 261 = 215 \text{ kVAr}$$

EXAMPLE: POWER FACTOR CORRECTION

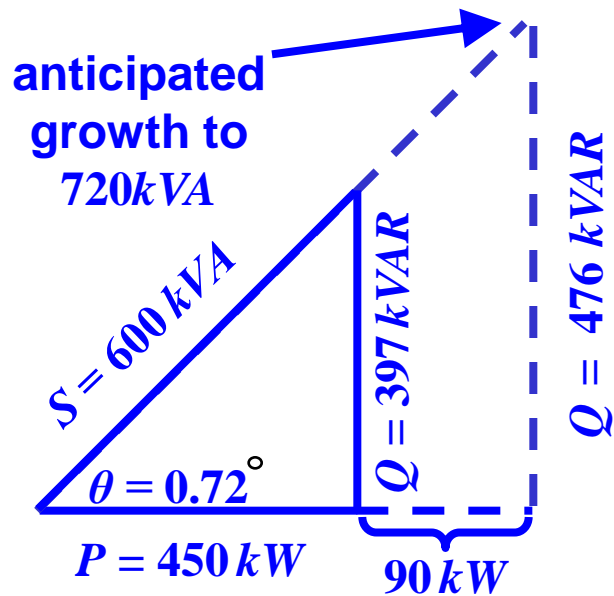

before correction

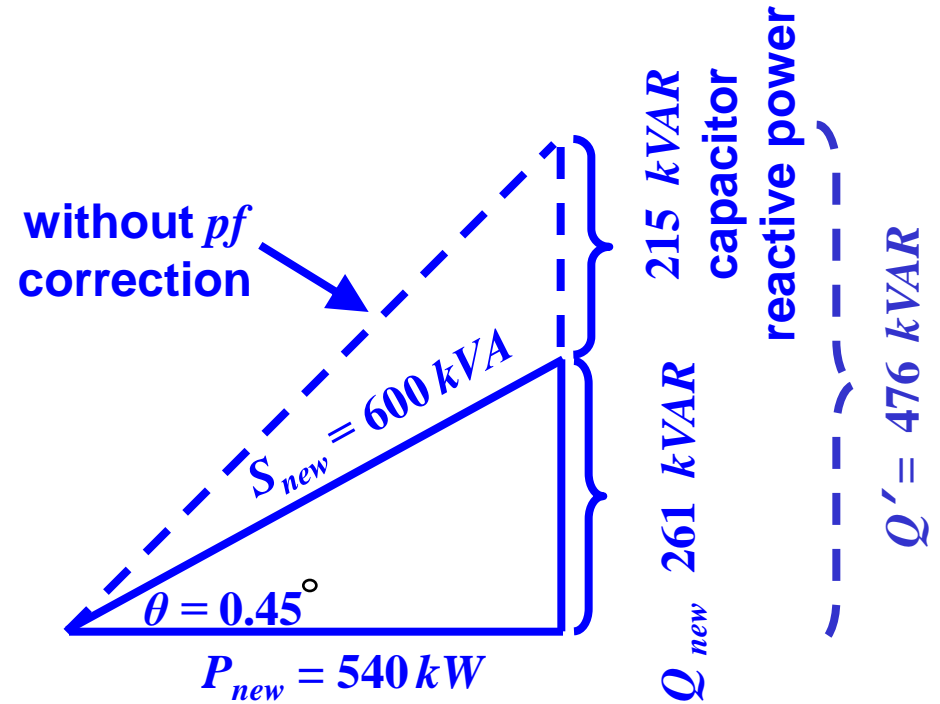

with 215-kVAR correction

EXAMPLE: POWER FACTOR CORRECTION

- We can determine the capacitance of the pf correcting capacitors

$$Q_c = V_c I_c = V_c (\omega C V_c)$$

$$C = \frac{Q_c}{\omega V_c^2}$$

- If we assume that the input voltage to the capacitors is at $12kV$, then

$$C = \frac{215 \text{ kVAr}}{(377)(12)^2 (\text{kV})^2} = (3.96) 10^{-3} \text{ F}$$

DISTRIBUTION SYSTEM CAPACITORS FOR pf CORRECTION




THE RESIDENTIAL ELECTRICITY SUPPLY

- In the U.S., residential service is typically provided from a 4.16 kV feeder line through a step-down transformer to the $120/240\text{ V}$ household voltage
 - all outlets provide 120 V
 - some outlets provide 240 V electricity (air conditioning, heavier duty appliances)

THE RESIDENTIAL ELECTRICITY SUPPLY

- The provision of 240 V service is done by
 - grounding the center tap of the secondary side of the transformer
 - using the other two ends of the windings at the $\pm 120\text{ V}$ supply to obtain the 240 V potential

THE RESIDENTIAL ELECTRICITY SUPPLY

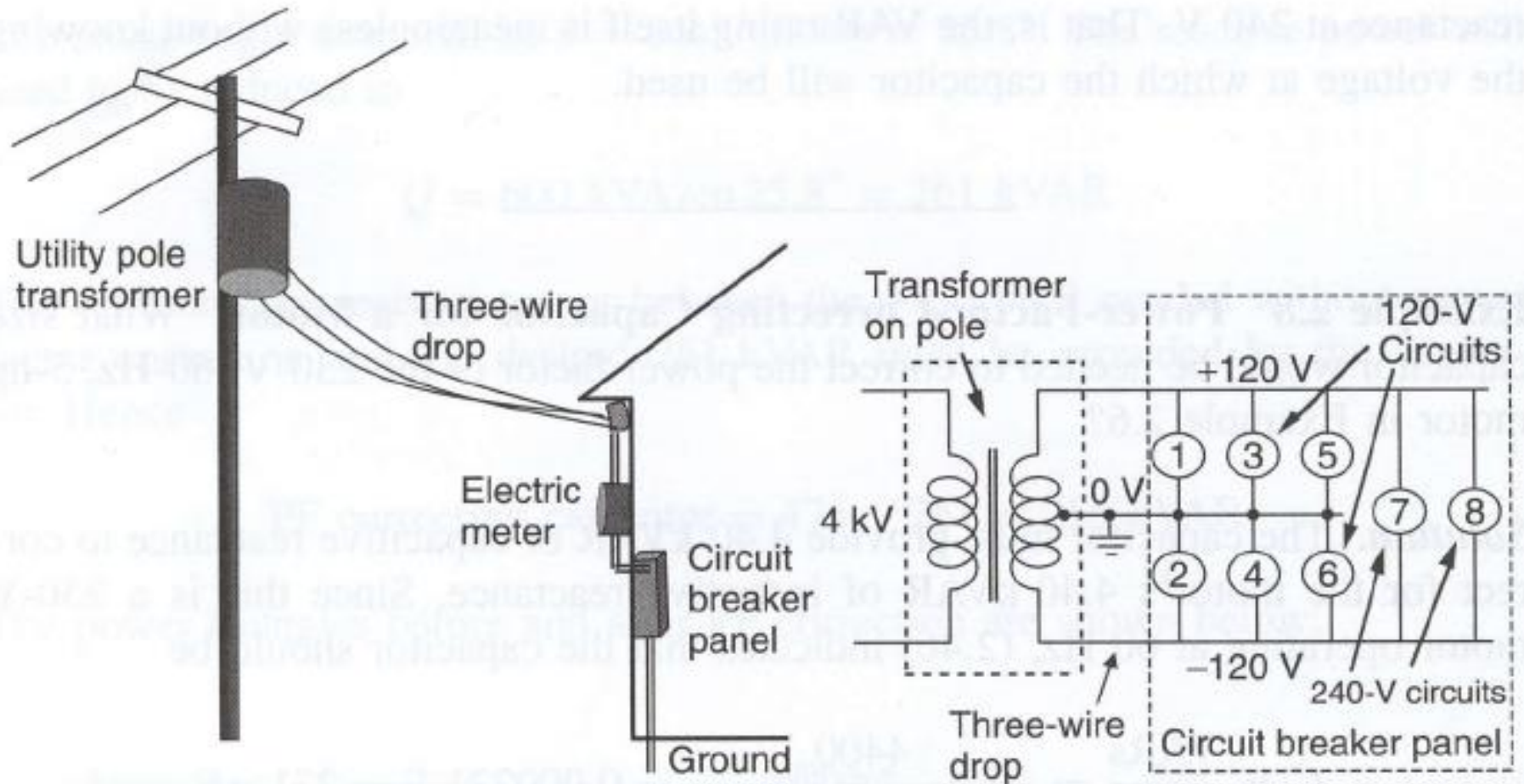


THE RESIDENTIAL ELECTRICITY SUPPLY

$$v_1 = 120\sqrt{2} \cos(377t)$$

$$v_2 = -120\sqrt{2} \cos(377t)$$

$$v_1 - v_2 = 240\sqrt{2} \cos(377t)$$

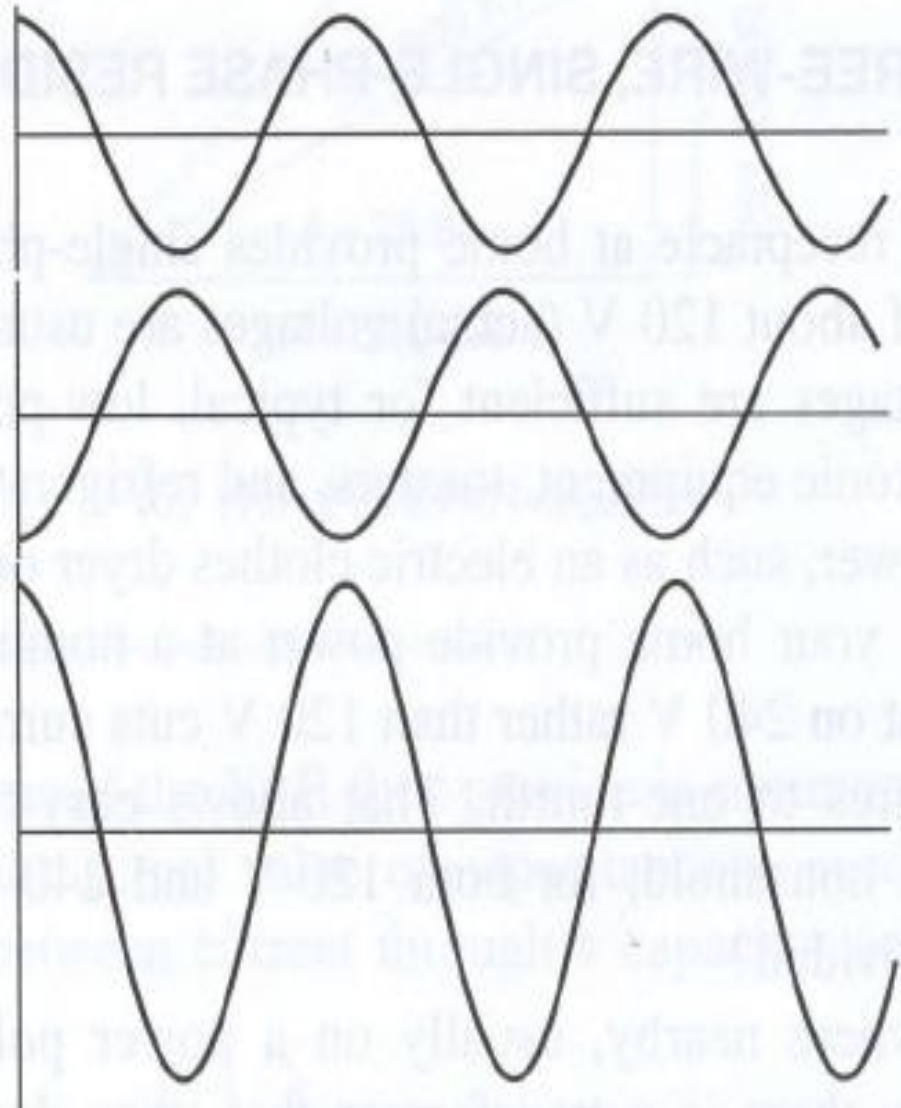

THE RESIDENTIAL ELECTRICITY SUPPLY

□ Analytically

$$v_1(t) = 120\sqrt{2} \cos 377t$$


$$v_2(t) = 120\sqrt{2} \cos(377t + \pi)$$

$$= -120\sqrt{2} \cos 377t$$

and therefore

$$v_1(t) - v_2(t) = 240\sqrt{2} \cos 377t$$

RESIDENTIAL LOAD EXAMPLE

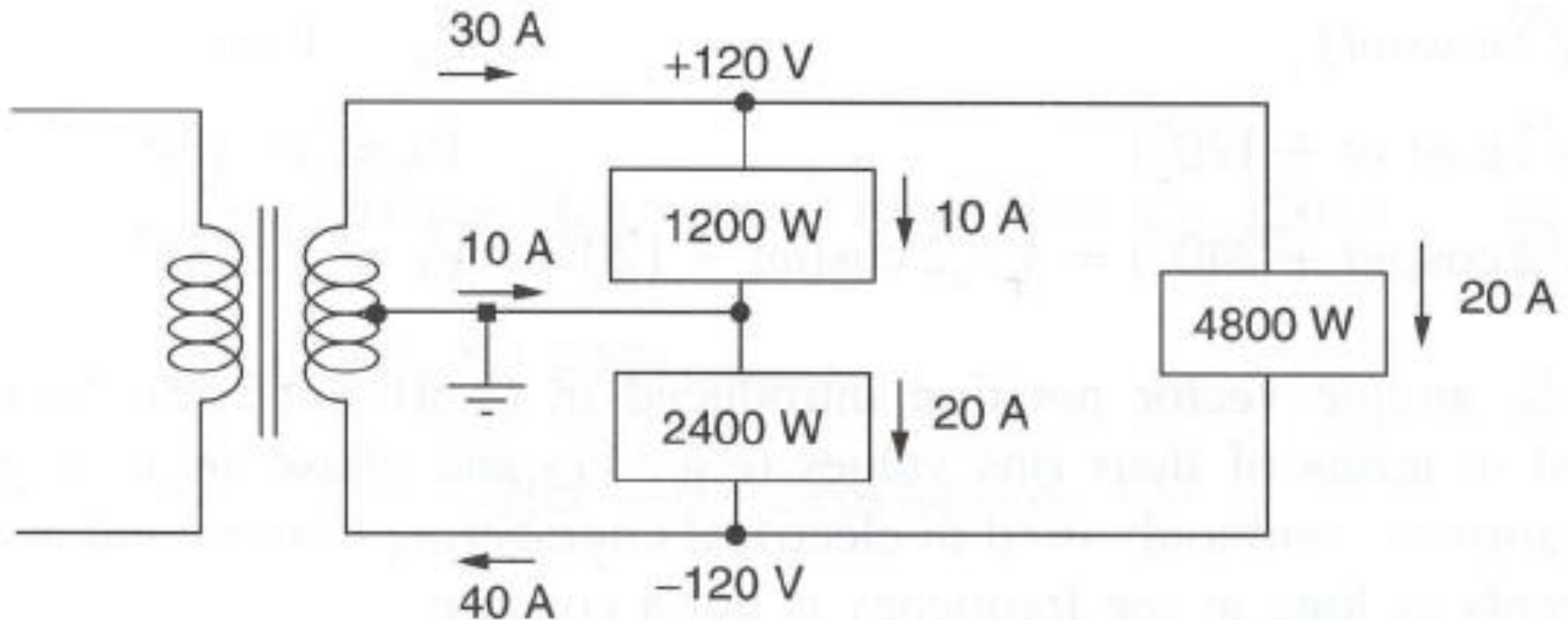

RESIDENTIAL LOAD EXAMPLE

- We consider the three loads served by a three-wire 120 / 240 V system with

1,200 W at 120 V on phase A, $pf = 1.0$

2,400 W at 120 V on phase B, $pf = 1.0$

4,800 W at 240 V, $pf = 1.0$

- We wish to compute the currents in the wires
- We start with the relationship

$$P = V I \cos \theta = V I$$

RESIDENTIAL LOAD EXAMPLE

□ For the 4,800 W load

$$I_{4,800} = \frac{4,800}{240} = 20 A$$

□ For the 2,400 W load

$$I_{2,400} = \frac{2,400}{120} = 20 A$$

□ For the 1,200 W load

$$I_{1,200} = \frac{1,200}{120} = 10 A$$


RESIDENTIAL LOAD EXAMPLE

- ❑ Note that *KCL* induces a current of $10A$ in the neutral leg and therefore the unbalanced load creates a nonzero current in the neutral
- ❑ This case differs from the typical balanced conditions we encounter in which each *hot* leg has current of the same magnitude and the neutral current vanishes

THREE – PHASE AC NETWORKS

- Today's systems use the three – phase (3ϕ) generators to produce electricity and 3ϕ transmission lines to “transport” it to various parts of the network
- The interconnection of network elements into a 3ϕ network is done typically using either the (Δ) delta or wye (Y) configuration
- We examine a Y -connected 3ϕ generator to a 3ϕ load

THREE – PHASE AC NETWORKS

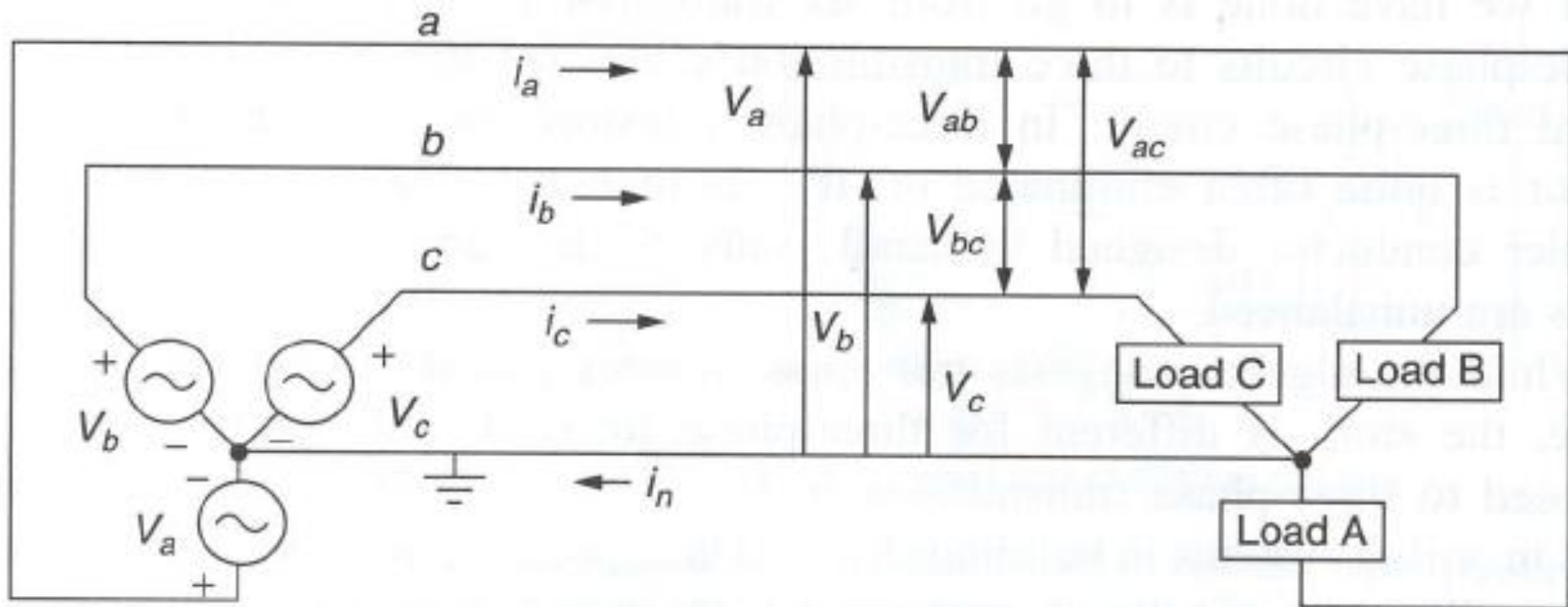

THREE – PHASE AC NETWORKS


- The phase voltages are measured with respect to the neutral

$$\begin{aligned}v_a(t) &= V\sqrt{2} \cos \omega t & \Leftrightarrow & \vec{V}_a = Ve^{j^0} \\v_b(t) &= V\sqrt{2} \cos\left(\omega t + \frac{2\pi}{3}\right) & \Leftrightarrow & \vec{V}_b = Ve^{j\frac{2\pi}{3}} \\v_c(t) &= V\sqrt{2} \cos\left(\omega t - \frac{2\pi}{3}\right) & \Leftrightarrow & \vec{V}_c = Ve^{-j\frac{2\pi}{3}},\end{aligned}$$

with the entities on the right representing the phasor notation for the voltages

THREE – PHASE AC NETWORKS

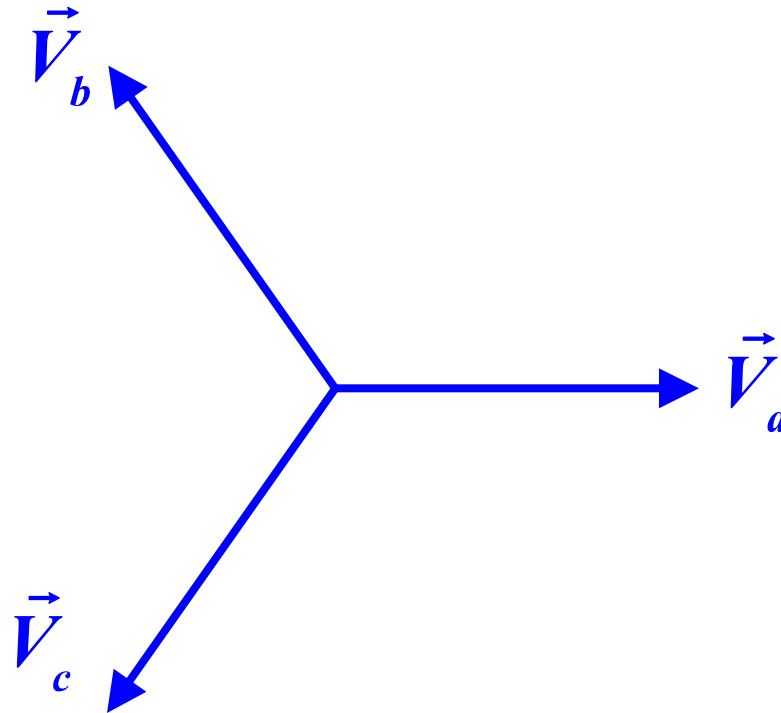- Note that the voltages are equal in magnitude and exactly $\pm \frac{2\pi}{3}$ from another (*balanced voltages*)



THREE – PHASE AC NETWORKS

□ Consequently,

$$\vec{V}_a + \vec{V}_b + \vec{V}_c = 0$$

□ The voltage between two-phases are typically called line voltages; for example the line a to the line b voltage is

$$v_{ab}(t) = v_{a0}(t) + v_{0b}(t) = v_{a0}(t) - v_{b0}(t)$$

and so

$$v_{ab}(t) = V\sqrt{2} \cos \omega t - V\sqrt{2} \cos \left(\omega t + \frac{2\pi}{3} \right)$$

THREE – PHASE AC NETWORKS

- Now, for a balanced network, the phase voltage *r.m.s.* values are equal

$$V_a = V_b = V_c = V_p \longleftarrow \textit{r.m.s. phase voltage}$$

- Therefore

$$v_{ab}(t) = V_p \sqrt{2} \cos \omega t - V_p \sqrt{2} \cos \left(\omega t + \frac{2\pi}{3} \right)$$

- We make use of the identity

$$\cos \phi - \cos \xi = -2 \sin \left[\frac{1}{2} (\phi + \xi) \right] \sin \left[\frac{1}{2} (\phi - \xi) \right]$$

THREE – PHASE AC NETWORKS

□ So we obtain

$$\begin{aligned}v_{ab}(t) &= V_p \sqrt{2} \cdot (-2) \sin\left(\omega t + \frac{\pi}{3}\right) \cdot \sin\left(-\frac{\pi}{3}\right) \\&= V_p \sqrt{2} \cdot 2 \sin\frac{\pi}{3} \cdot \sin\left(\omega t + \frac{\pi}{3}\right) \\&= \underbrace{\sqrt{3} V_p}_{V_\ell} \sqrt{2} \sin\left(\omega t + \frac{\pi}{3}\right) \\&= V_\ell \sqrt{2} \sin\left(\omega t + \frac{\pi}{3}\right)\end{aligned}$$

THREE – PHASE AC NETWORKS

- The relationship of importance for the *r.m.s.* value of line-to-line voltage V_ℓ relative to that of the phase voltage V_p is

$$V_\ell = \sqrt{3} V_p$$

- Examples of typical values

<i>service type</i>	V_ℓ	V_p
<i>buildings</i>	202 V	120 V
<i>commercial</i>	480 V	277 V
<i>residential</i>	416 V	240 V

THREE – PHASE AC NETWORKS

- Each phase has apparent power

$$S_{\phi} = I_p V_p$$

and so the 3ϕ system has apparent power

$$\begin{aligned} S_{3\phi} &= 3I_p V_p \\ &= \sqrt{3} I_p \sqrt{3} V_p \\ &= \sqrt{3} I_p V_{\ell} \end{aligned}$$

- Therefore,

$$P_{3\phi} = S_{3\phi} \cos \theta$$

$$Q_{3\phi} = S_{3\phi} \sin \theta$$

THREE – PHASE AC NETWORKS


with θ being the phase angle between phase current and voltage and is the same for each phase under balanced conditions

□ In fact, we can show that

$$p_a(t) + p_b(t) + p_c(t) = 3P_\phi$$

and is constant and such a smooth constant level of power constitutes a key advantage of 3ϕ systems in contrast to 1ϕ where $p(t)$ is sinusoidal

THREE – PHASE AC NETWORKS

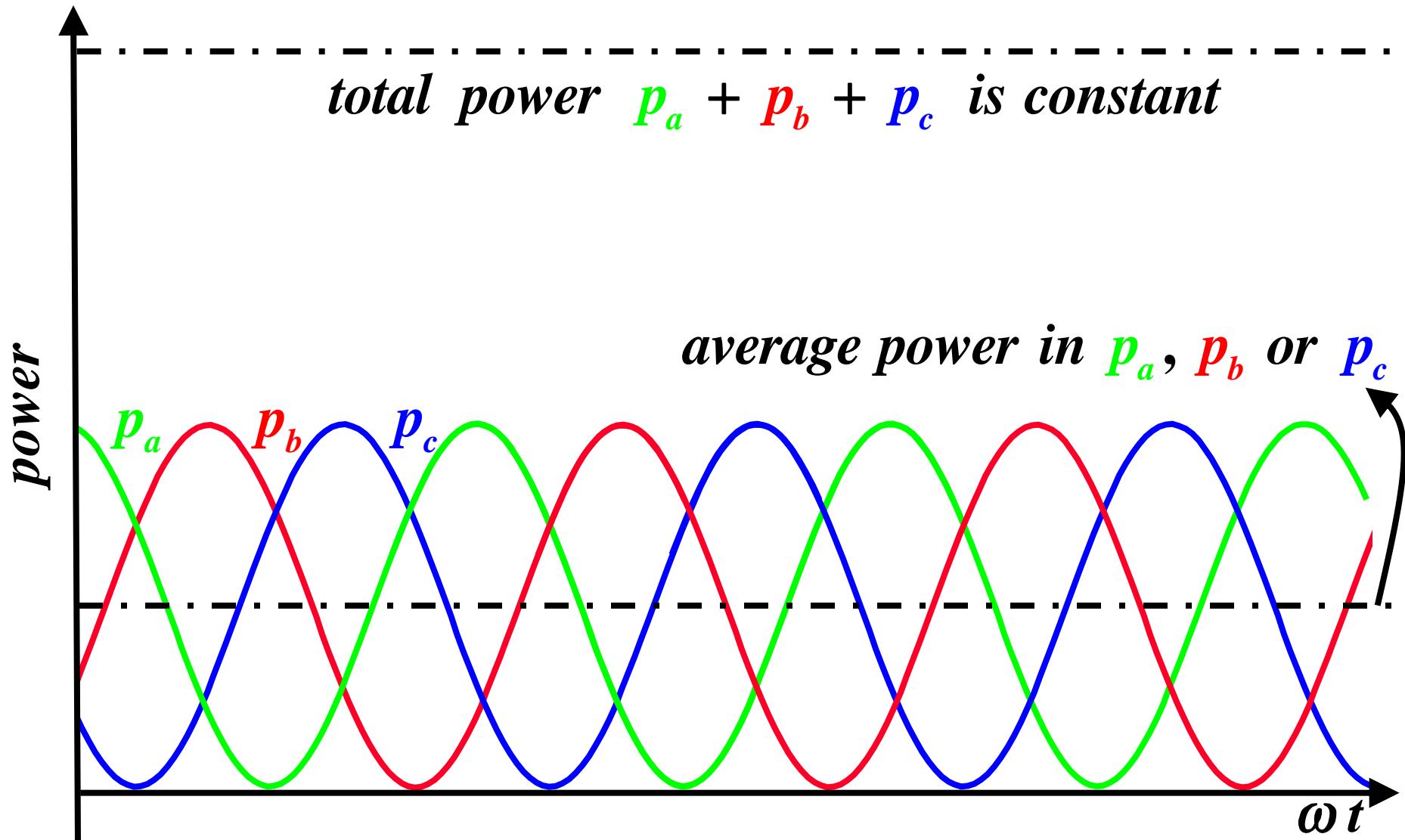

EXAMPLE: 3ϕ NETWORK pf CORRECTION

- The 1ϕ motors in a small enterprise are supplied using a 3ϕ $208V$ transformer
- The real power demand is $80kW$ with a $pf = 0.5$ and incurs losses of $4kW$
- We compute $S_{3\phi}$ using

$$P_{3\phi} = \sqrt{3} V_{\ell} I_p \cos\theta = S_{3\phi} 0.5 = 80 kW$$

so that

$$S_{3\phi} = 160 kVA$$

EXAMPLE: 3 ϕ NETWORK pf CORRECTION

□ We also evaluate

$$I_p = \frac{S_{3\phi}}{\sqrt{3} V_\ell} = \frac{160}{\sqrt{3} 208} = .444 \text{ kA}$$

□ Next consider a pf correction to 0.9 and so

$$S'_{3\phi} = \frac{80}{0.9} = 88.9 \text{ kVA} \ll 160 \text{ kVA}$$

EXAMPLE: 3 ϕ NETWORK pf CORRECTION

□ Also


$$I'_p = \frac{88.9}{\sqrt{3} 208} = .247 \text{ kA}$$

□ We also evaluate the losses under corrected pf

$$R \left(I'_p \right)^2 = \frac{4}{\left(.444 \right)^2} \left(.247 \right)^2 = 1.24 \text{ kW}$$

THE 3 ϕ DELTA CONNECTION

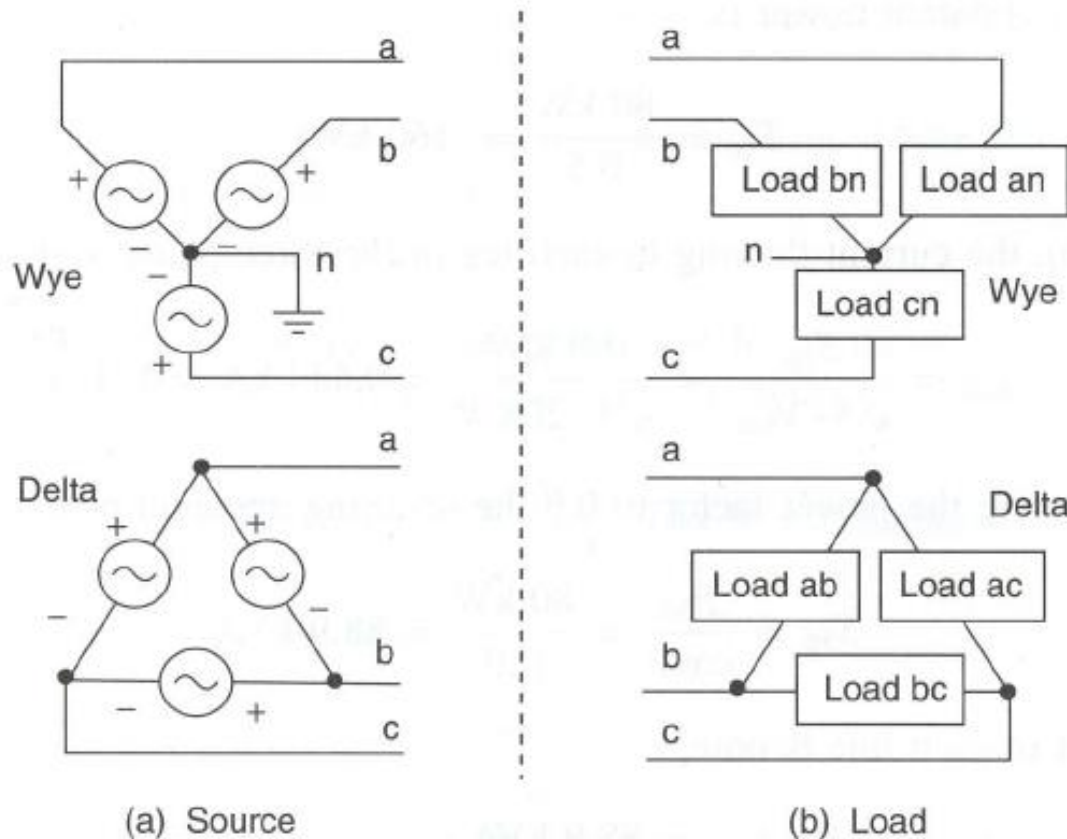- The other way to connect 3 ϕ elements in the Δ connection which has no neutral line



THE 3ϕ DELTA CONNECTION

- The comparison of the key characteristics of the two connection schemes is summarized by the table

<i>variable</i>	<i>Y – connection</i>	<i>Δ – connection</i>
<i>r.m.s. current</i>	$I_\ell = I_p$	$I_\ell = \sqrt{3} I_p$
<i>r.m.s. voltage</i>	$V_\ell = \sqrt{3} V_p$	$V_\ell = V_p$
<i>3ϕ power</i>	$P_{3\phi} = \sqrt{3} V_p I_p \cos\theta$	$P_{3\phi} = \sqrt{3} V_\ell I_\ell \cos\theta$