

Problem: P310-5.2

Equation 5.10: $i = I_{sc} - I_0 (e^{38.9V} - 1)$

$$= 64 - 4 \times 10^{-11} (e^{38.9V} - 1) \quad V.$$

Equation 5.11: $V_{oc} = 0.0257 \ln\left(\frac{I_{sc}}{I_0} + 1\right)$


$$= 0.0257 \ln\left(\frac{64}{4 \times 10^{-11}} + 1\right)$$

$$\approx 0.71V$$

b) $i(V=0.55) = 64 - 4 \times 10^{-11} (e^{38.9 \times 0.55} - 1)$
 $\approx 6.32A$




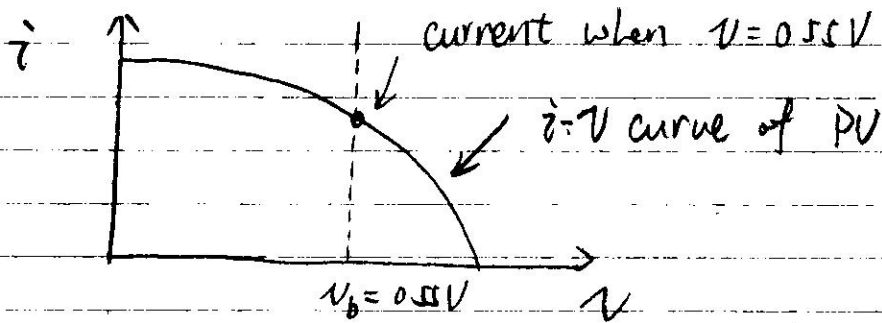
c) skip part c)

In this problem, if you're given the $i-v$ curve instead of the equation, how can you determine the current in problem b)?



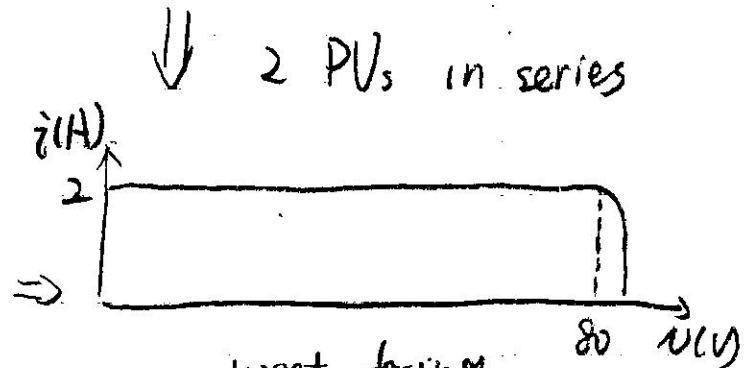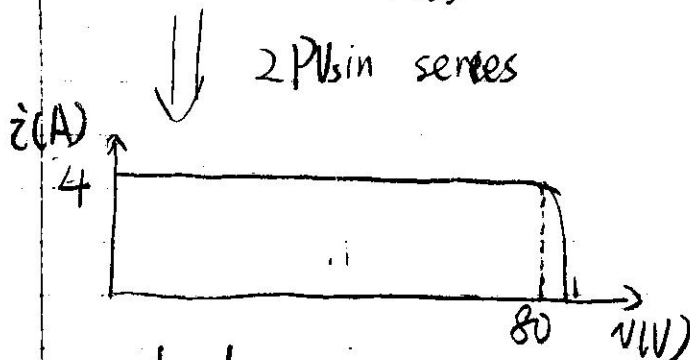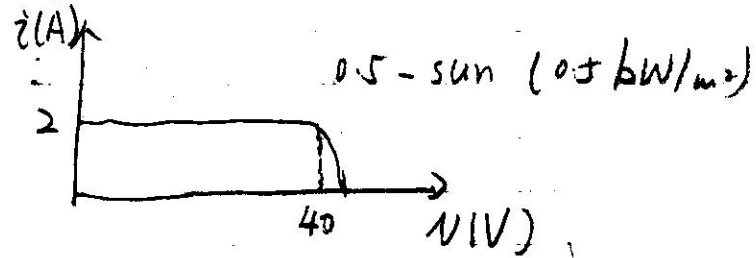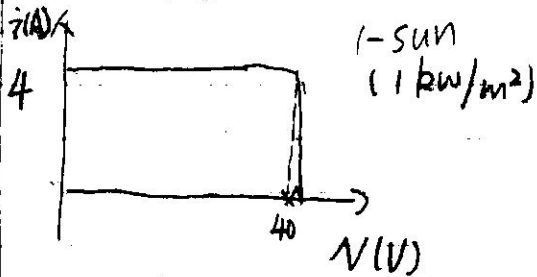
Problem B12 - J.J.

Please pay attention to the Figure in P219



South-facing

west-facing
put them in parallel

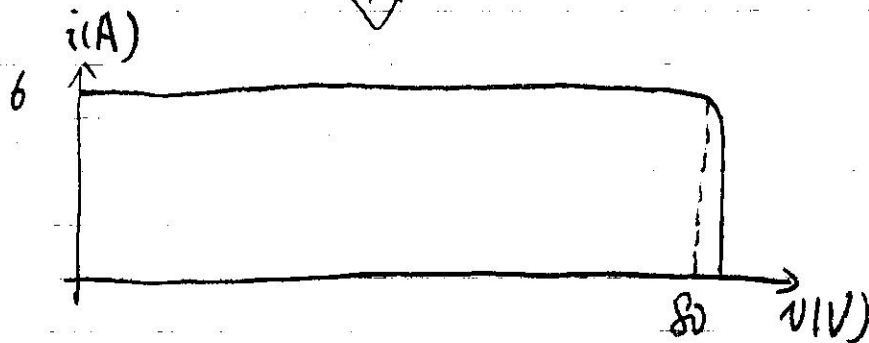

MPP: $v = 80 \text{ V}$, $i = 6 \text{ A}$
 $P_{\text{max}} = 480 \text{ W}$

In this problem, you're required to know how to derive the $i-v$ curve of a PV array based on the $i-v$ curves of smaller PV components.

Problem

for a PV, $i = f(v)$

for a resistor, $i = r \cdot v$

If you wanna solve the above equations graphically,

① draw the $i-v$ curve of PV

② draw the $i-v$ curve for the resistor.

③ the point where the above two curves intersect is the operating point of the PV

