

ECE 342

2. PN Junctions and Diodes

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jschutt@emlab.uiuc.edu

Definitions

B : material dependent parameter = 5.4×10^{31} for Si

E_G : Bandgap energy = 1.12 eV

k : Boltzmann constant = 8.62×10^{-5} eV/K

n_i : intrinsic carrier concentration

At $T = 300$ K, $n_i = 1.5 \times 10^{10}$ carriers/cm³

J_p : current density A/m²

q : electron charge

D_p : Diffusion constant (diffusivity) of holes

μ_p : mobility for holes = 480 cm² /V sec

μ_n : mobility for electrons = 1350 cm² /V sec

N_D : concentration of donor atoms


n_{no} : concentration of free electrons at thermal equilibrium

N_A : concentration of acceptor atoms

p_{po} : concentration of holes at thermal equilibrium

Einstein Relation: $\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = \frac{kT}{q} = V_T$: thermal voltage

PN Junction

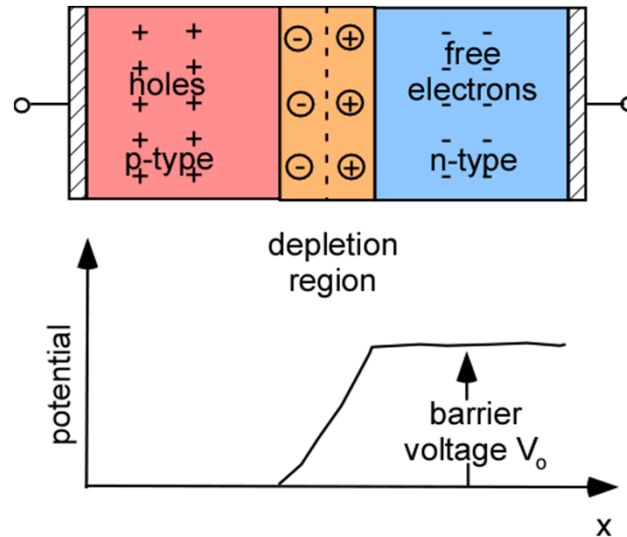

- **When a p material is connected to an n-type material, a junction is formed**
 - Holes from p-type diffuse to n-type region
 - Electrons from n-type diffuse to p-type region
 - Through these diffusion processes, recombination takes place
 - Some holes disappear from p-type
 - Some electrons disappear from n-type

A depletion region consisting of bound charges is thus formed
Charges on both sides cause electric field \rightarrow potential = V_0

PN Junction

- Potential acts as barrier that must be overcome for holes to diffuse into the n-region and electrons to diffuse into the p-region
- Open circuit: No external current

Junction built-in voltage

From principle of detailed balance and equilibrium we get:

$$V_o = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

For Si, V_o is typically 0.6V to 0.8V

Charge equality in depletion region gives:

$$qx_p AN_A = qx_n AN_D$$

A: cross-section of junction

x_p : width in p side

x_n : width in n side

ϵ_s : silicon permittivity

$$\epsilon_s = 11.7\epsilon_o = 1.04 \times 10^{-8} \text{ F/m}$$

$$\frac{x_n}{x_p} = \frac{N_A}{N_D}$$

$$W_{dep} = x_n + x_p = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) V_o}$$

Example

Find the barrier voltage across the depletion region of a silicon diode at $T = 300$ K with $N_D = 10^{15}/\text{cm}^3$ and $N_A = 10^{18}/\text{cm}^3$.

Use
$$V_o = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$


@ 300K,
 $n_i = 1.5 \times 10^{10} / \text{cm}^3$
 $V_T = 0.026$ V

$$V_o = \psi_o = 0.026 \ln\left(\frac{10^{18} \cdot 10^{15}}{(1.5)^2 \times 10^{20}}\right) = 0.026 \ln\left[\frac{10^{13}}{2.25}\right]$$

$$V_o = \psi_o = 0.026 \times 29.12 = 0.7571 \text{ volts}$$

$$V_o = \psi_o = 0.7571 \text{ volts}$$

PN Junction under Reverse Bias

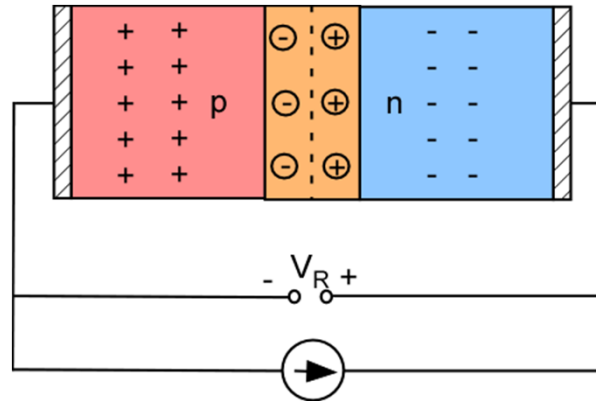

- **When a reverse bias is applied**
 - Transient occurs during which depletion capacitance is charged to new bias voltage
 - Increase of space charge region
 - Diffusion current decreases
 - Drift current remains constant
 - Barrier potential is increased
 - A steady state is reached
 - After transient: steady-state reverse current = $I_S - I_D$ (I_D is very small) → reverse current $\sim I_S \sim 10^{-15}$ A

Under reverse bias the current in the diode is negligible

Depletion Layer Stored Charge

$$q_j = q_N = qN_D x_n A$$

A : cross section area

q_j : stored charge

Let W_{dep} = depletion-layer width

$$q_j = q \frac{N_A N_D}{N_A + N_D} A W_{dep}$$

The total voltage across the depletion layer is $V_o + V_R$

$$W_{dep} = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) (V_o + V_R)}$$

Depletion Capacitance

$$C_j = \left. \frac{dq_j}{dV_R} \right|_{V_R=V_Q}$$

Q is bias point
 V_R is reverse voltage

$$C_j = \frac{\epsilon_s A}{W_{dep}} = \frac{C_{jo}}{\sqrt{1 + \frac{V_R}{V_o}}}$$


$$C_{jo} = A \sqrt{\frac{\epsilon_s q}{2} \left(\frac{N_A N_D}{N_A + N_D} \right) \left(\frac{1}{V_o} \right)} \quad C_j = \frac{C_{jo}}{\left(1 + \frac{V_R}{V_o} \right)^m}$$

m is the grading coefficient and depends on how the concentration varies from the p side to the n side

$$1/3 < m < 1/2$$

For an abrupt junction, $m=0.5$

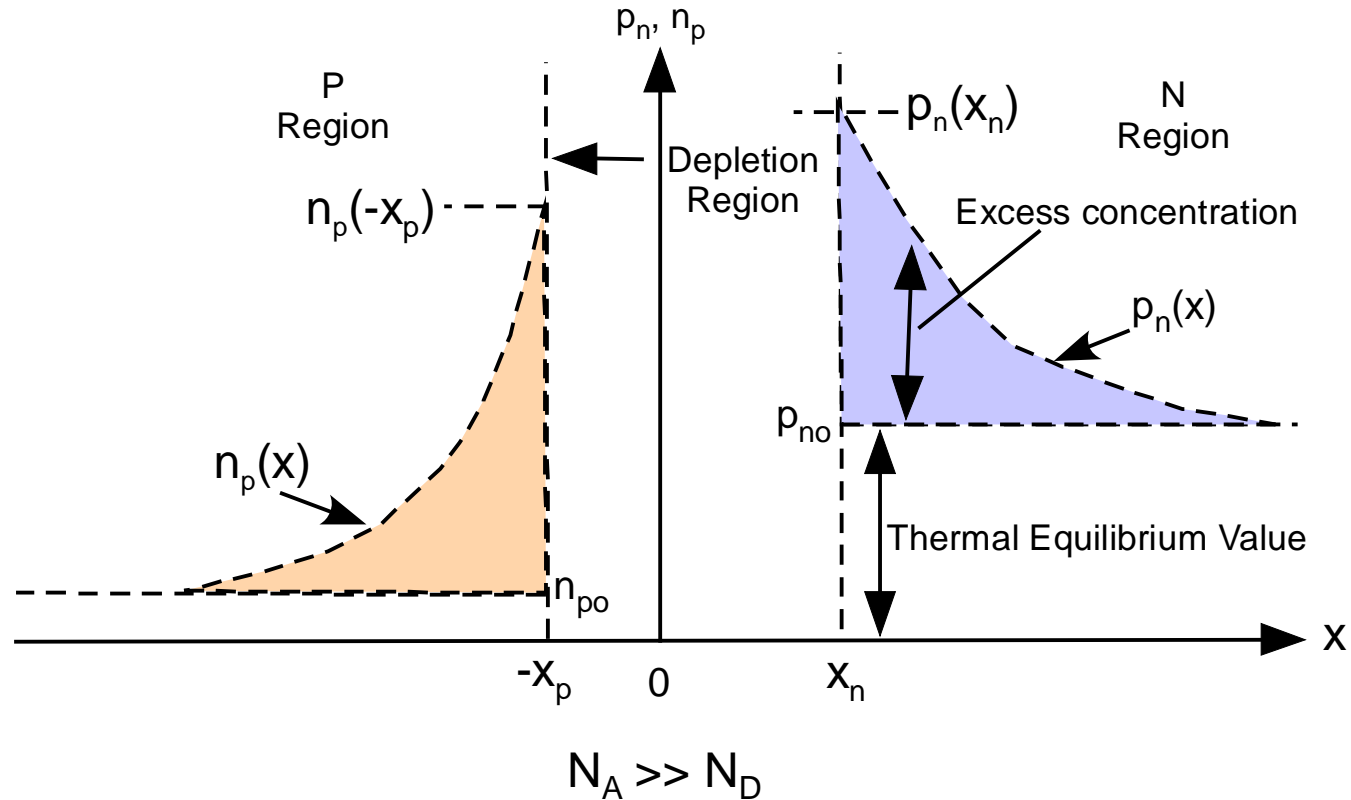Forward-Biased Junction Carrier Distribution



Barrier voltage is now lower than V_0

In steady state, concentration profile of excess minority carriers remains constant

Forward-Biased PN Junction

Diode equation: $I_D = I_S (e^{V/nV_T} - 1)$

$$I_S = Aqn_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$


since n_i^2 is a strong function of temperature; thus I_S is a strong function of temperature

n has a value between 1 and 2. Diodes made using standard IC process have $n=1$; discrete diodes have $n=1$

In general, assume $n=1$


If $V \gg V_T$, we can use $I_D \approx I_S e^{V/V_T}$

Diode Characteristics

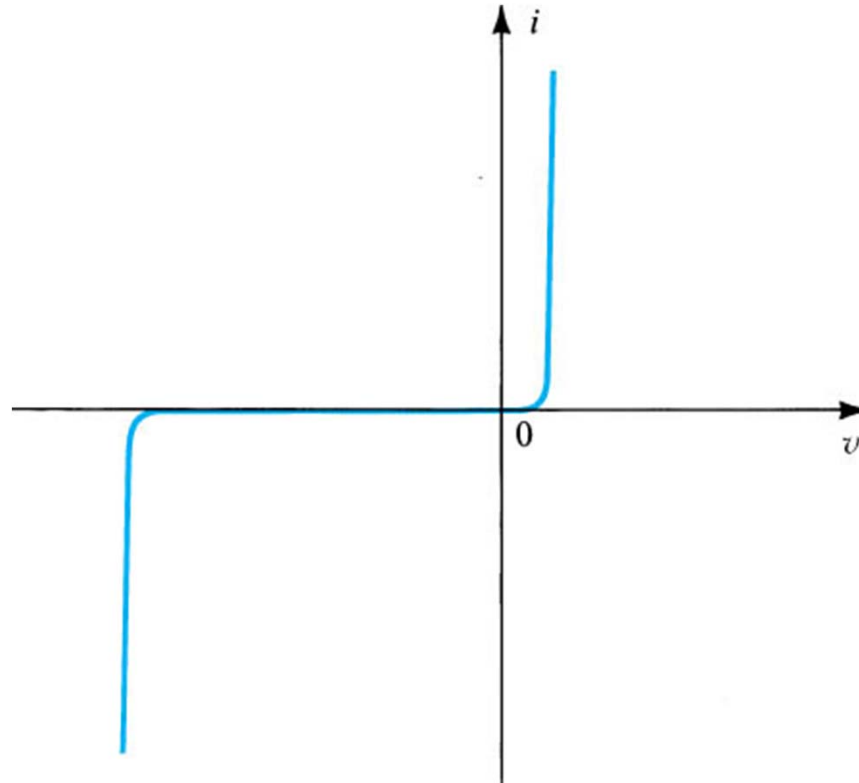

- **Three distinct regions**
 - The forward-bias region, determined by $v > 0$
 - The reverse-bias region, determined by $v < 0$
 - The breakdown region, determined by $v < -V_{ZK}$


Diode I-V Relationship

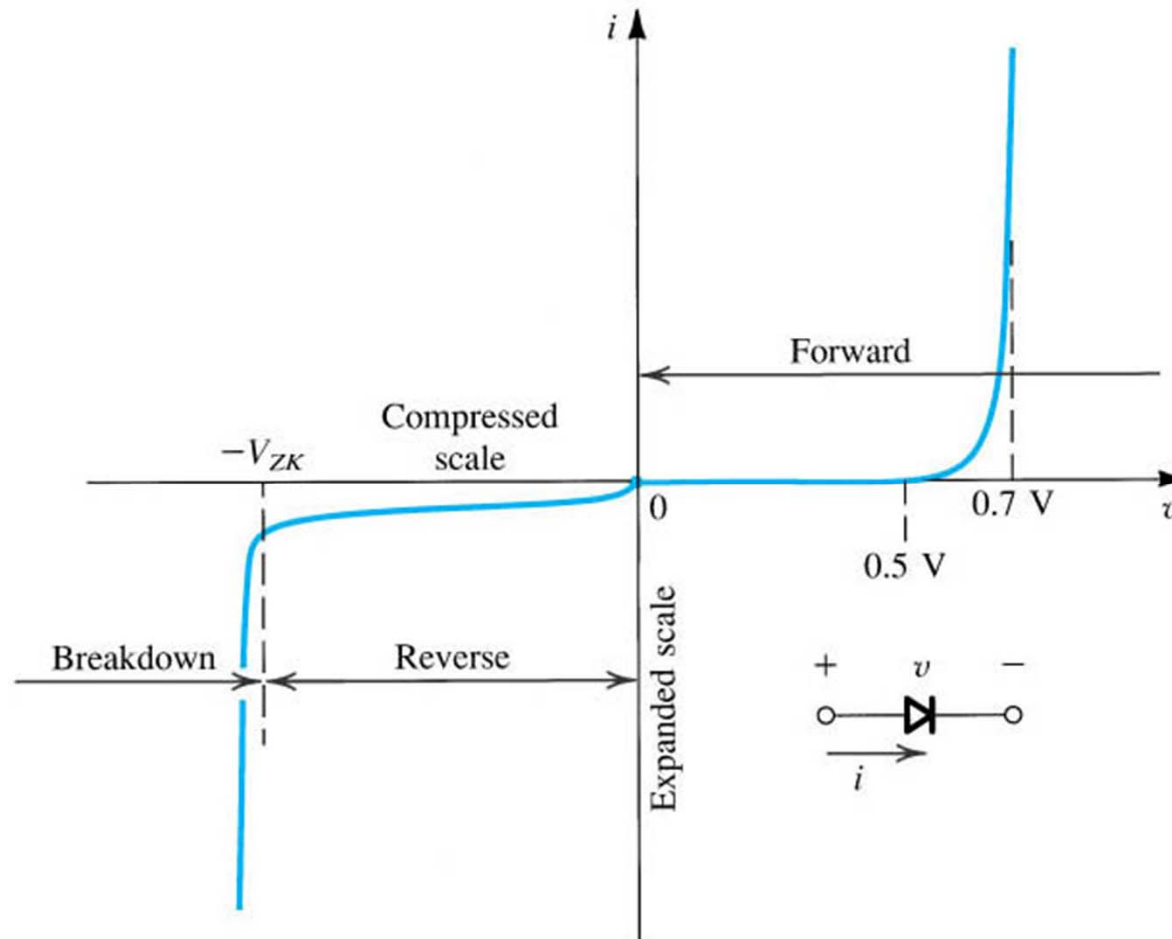

Breakdown

- Electric field strong enough in depletion layer to break covalent bonds and generate electron-hole pairs. Electrons are then swept by E-field into the n-side. Large number of carriers for a small increase in junction voltage





The Diode

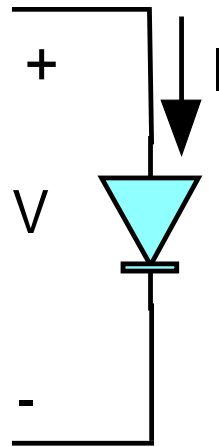


- **Diode Properties**

- Two-terminal device that conducts current freely in one direction but blocks current flow in the opposite direction.
- The two electrodes are the anode which must be connected to a positive voltage with respect to the other terminal, the cathode in order for current to flow.

Ideal Diode Characteristics

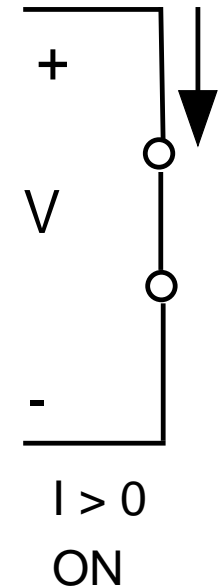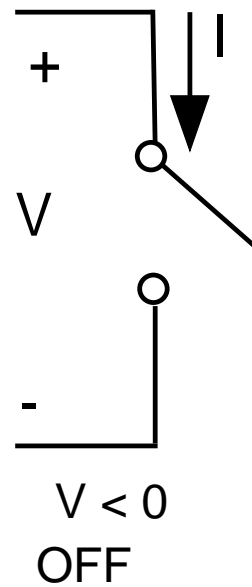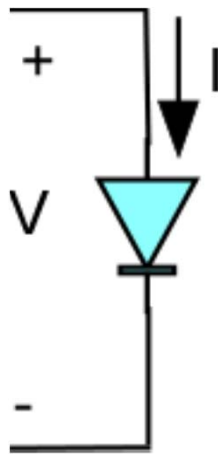
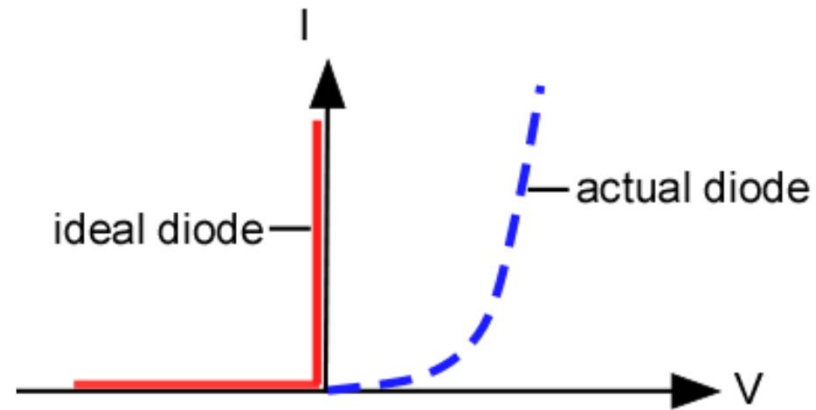


Ideal Diode Characteristics


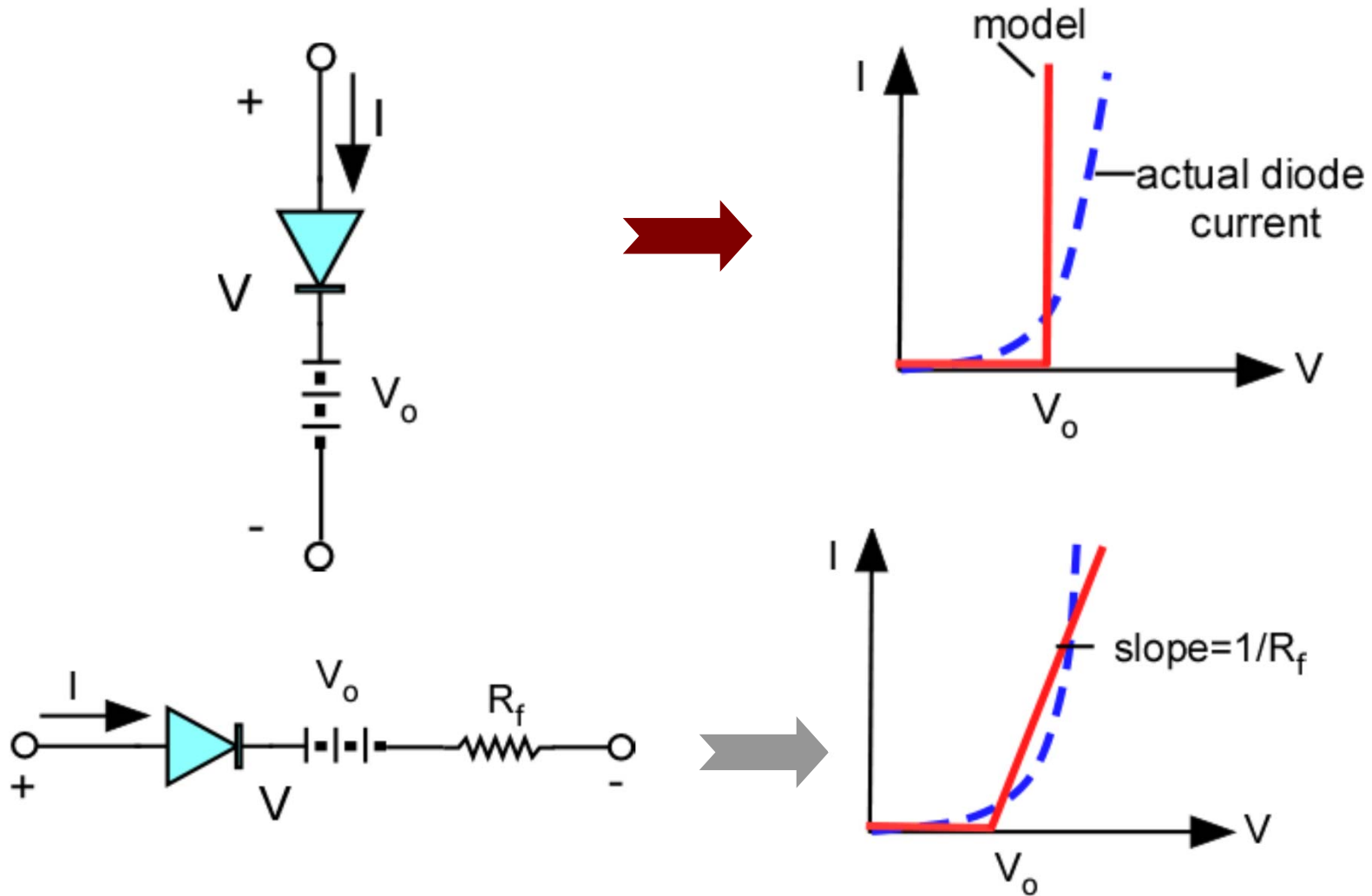


Diode Models



Exponential

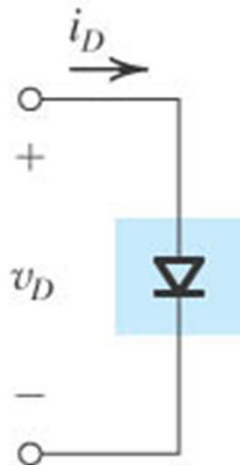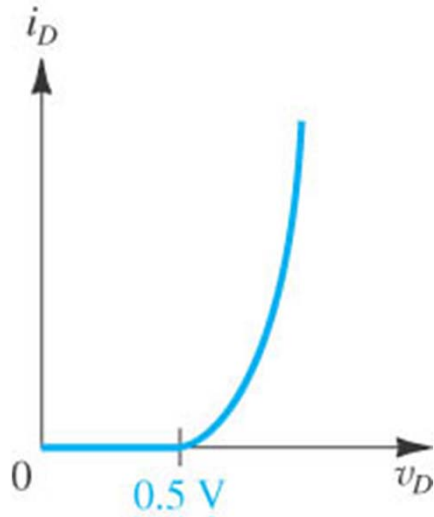





Piecewise Linear

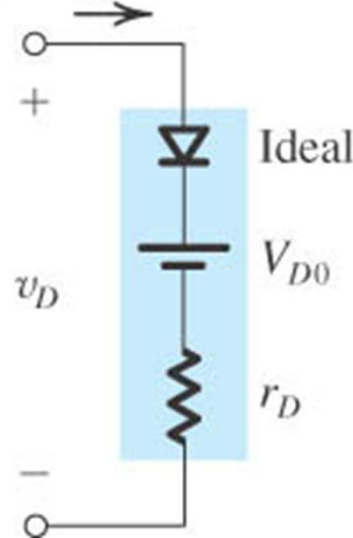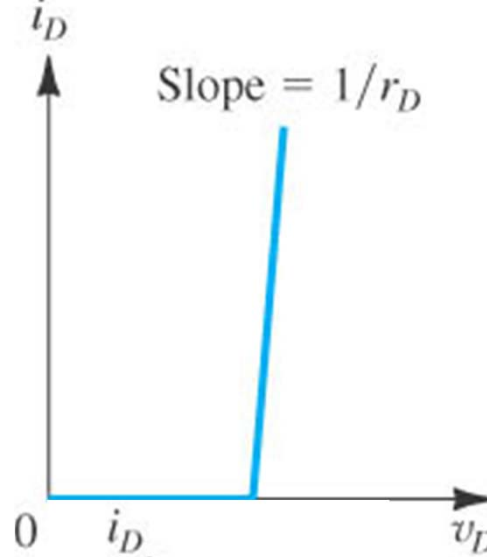

Constant-Voltage-Drop

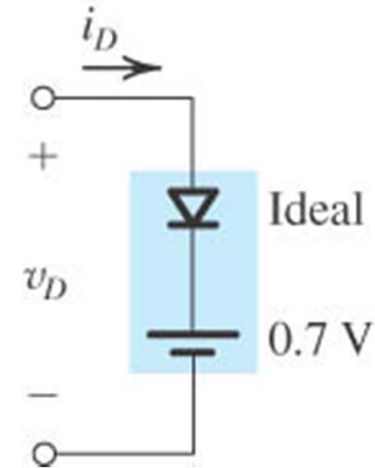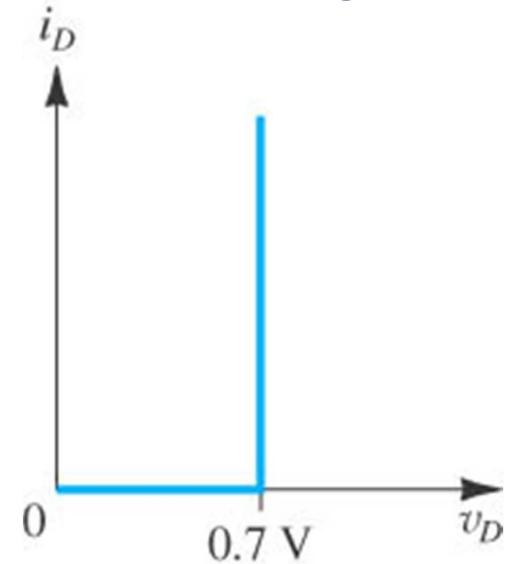


Diode Models

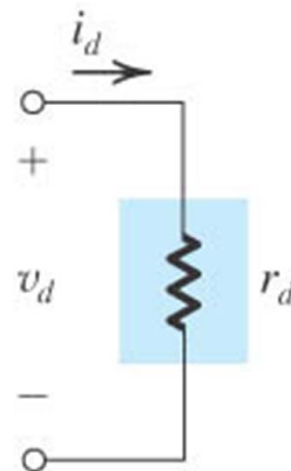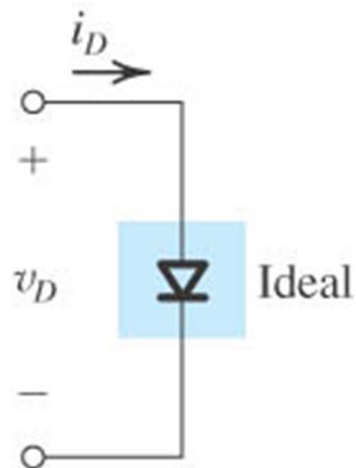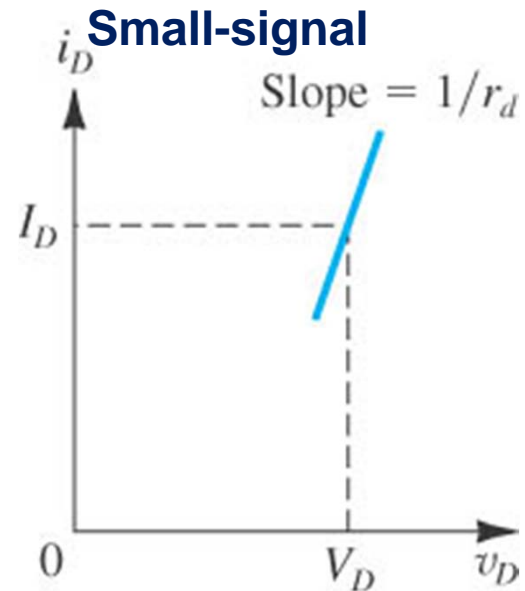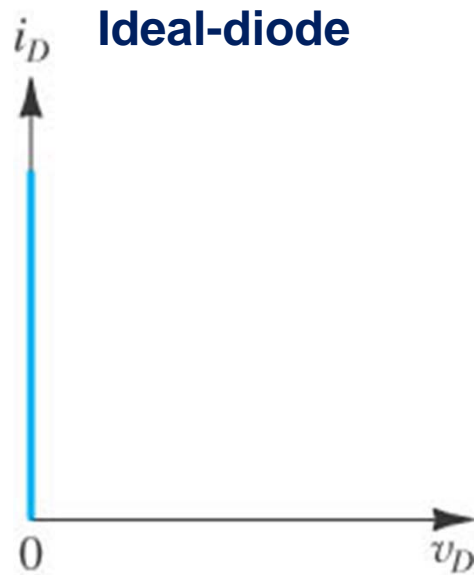


Piecewise-Linear Model

$$\text{for } v_D \leq V_{D0} : i_D = 0$$
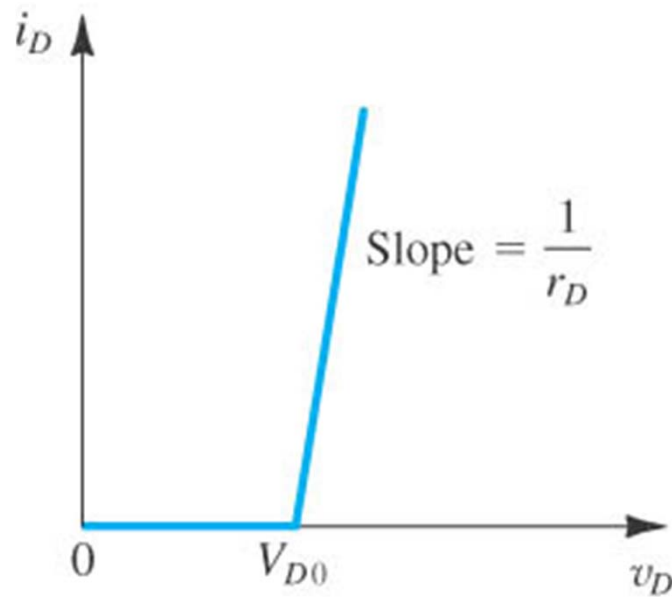
$$\text{for } v_D \geq V_{D0} : i_D = \frac{1}{r_D} (v_D - V_{D0})$$




(a)

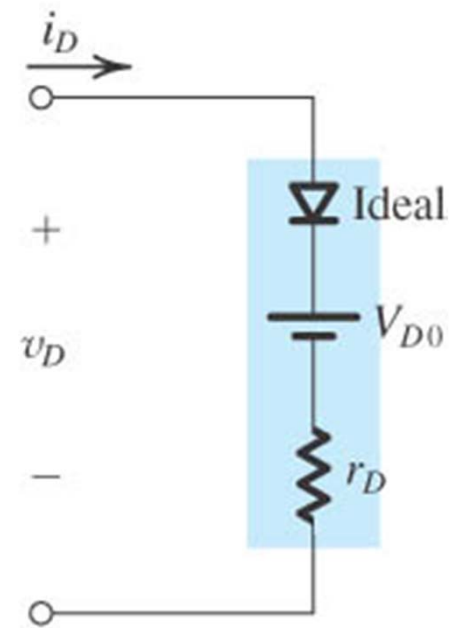



(b)

Piecewise-Linear Model

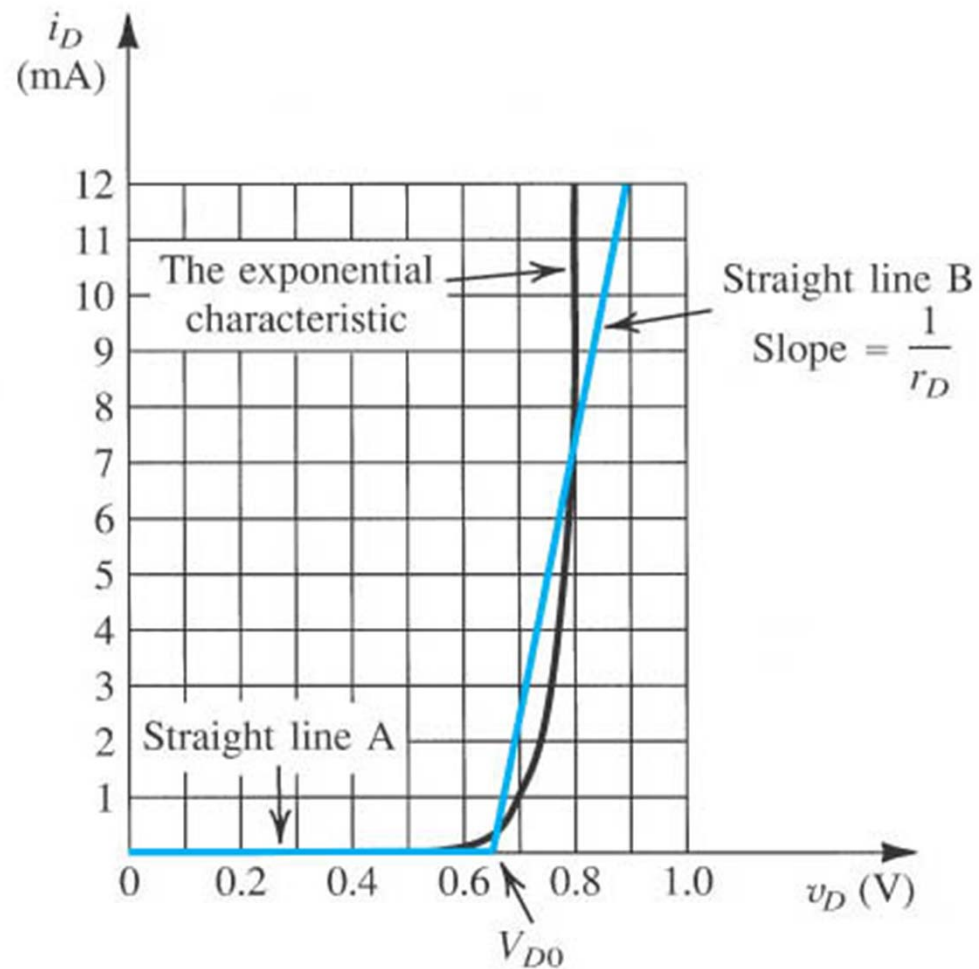


Constant-Voltage-Drop Model


for $i_D > 0$: $v_D = 0.7 \text{ V}$

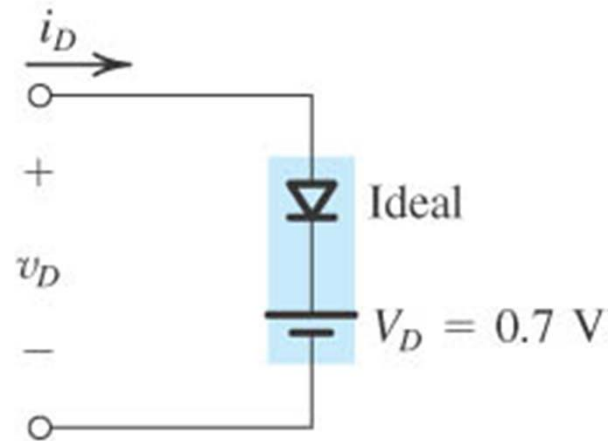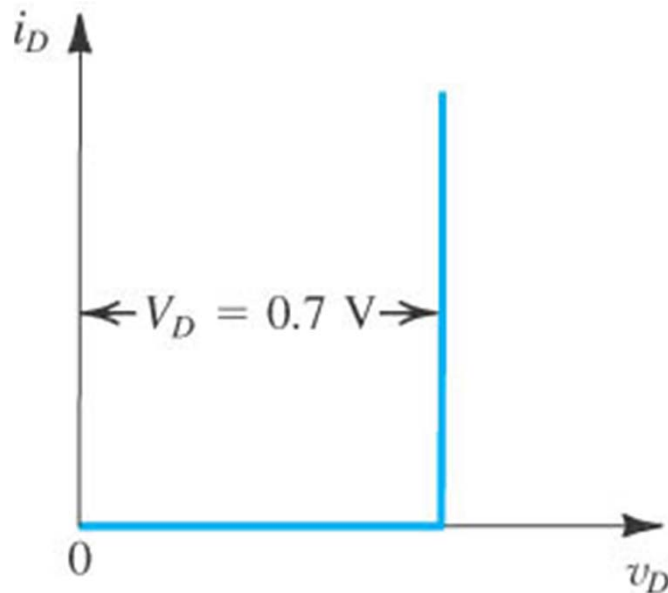

Constant-Voltage-Drop Model

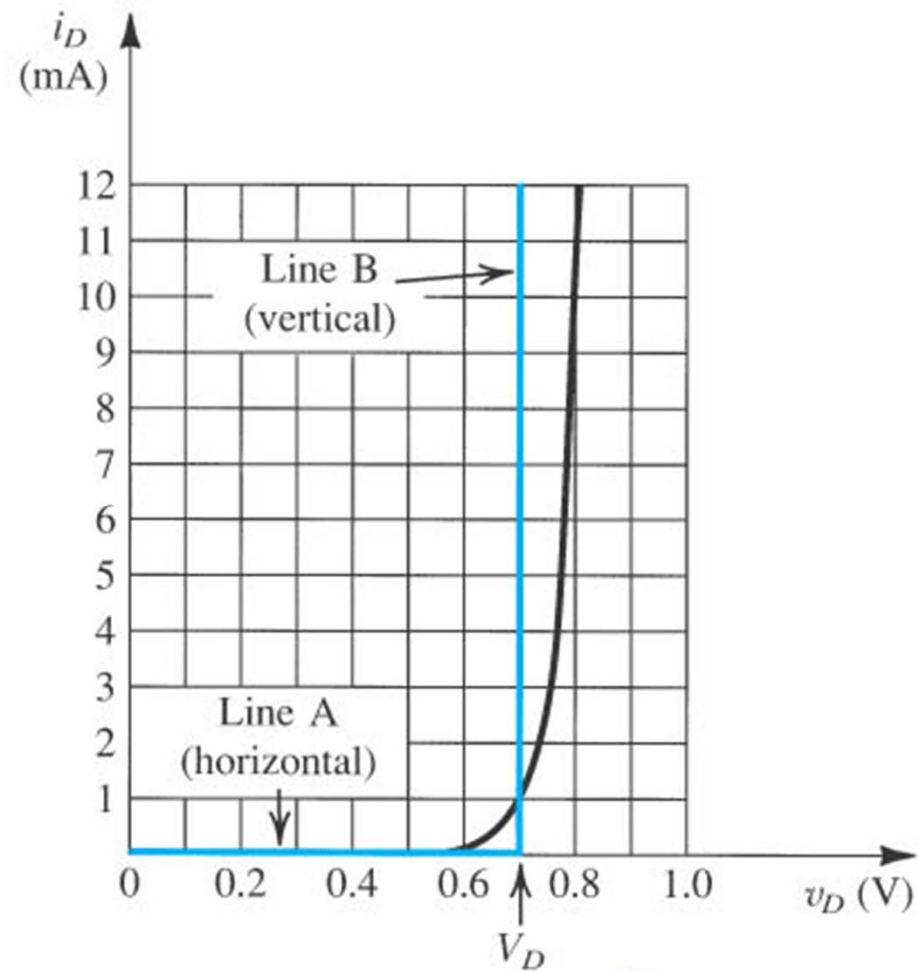


Diodes Logic Gates

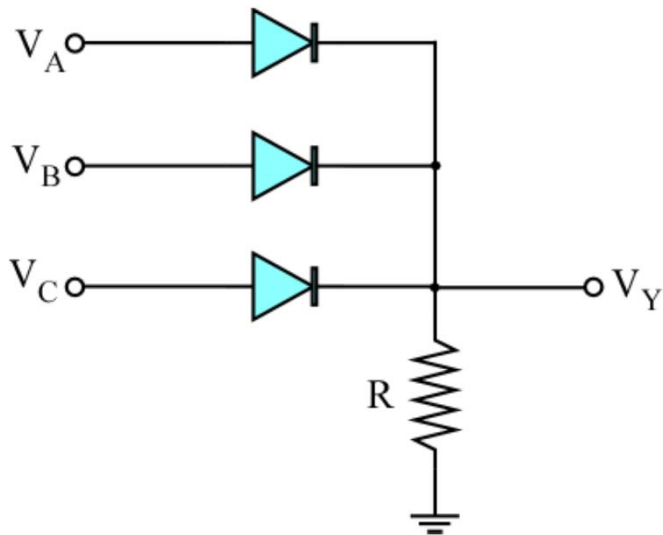

OR Function

$$Y = A + B + C$$

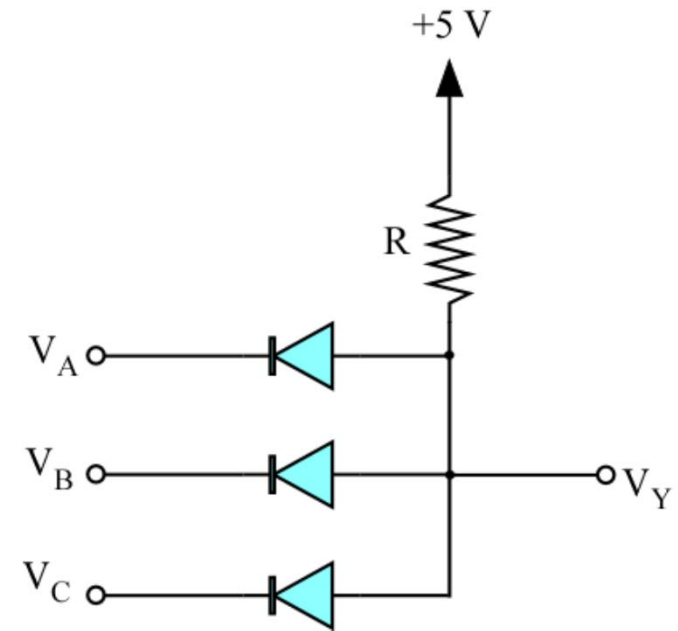

AND Function

$$Y = A \cdot B \cdot C$$

Diode Circuit Example 1

IDEAL Diodes

Assume both diodes are on; then


$$V_B = 0 \quad \text{and} \quad V = 0$$

$$I_{D2} = \frac{10 - 0}{10} = 1 \text{ mA}$$

At node B


$$I + 1 = \frac{0 - (-10)}{5} \Rightarrow I = 1 \text{ mA}, V = 0 \text{ V}$$

D₁ is conducting as originally assumed

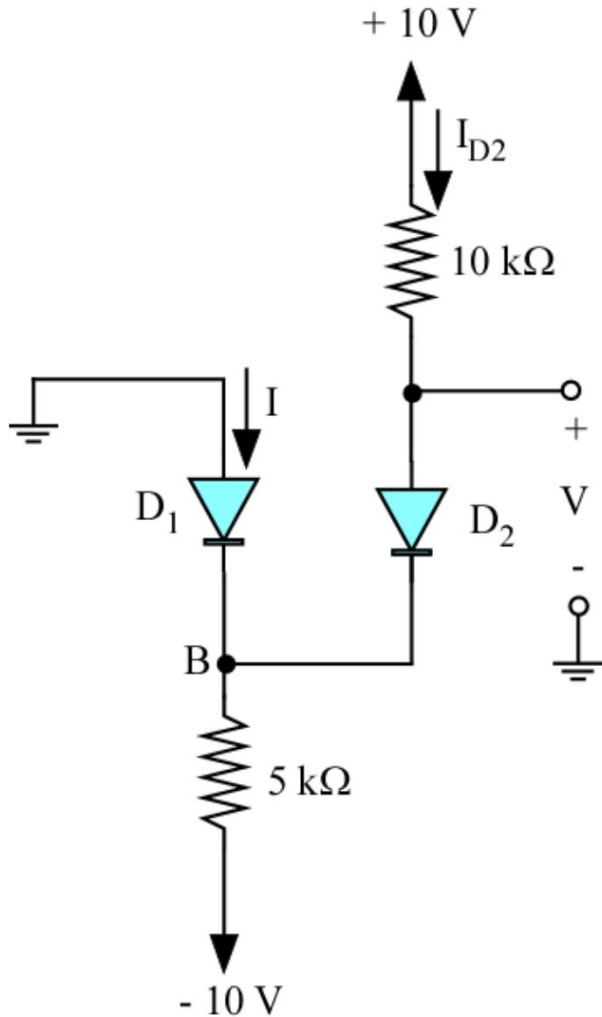

Diode Circuit Example 2

IDEAL Diodes

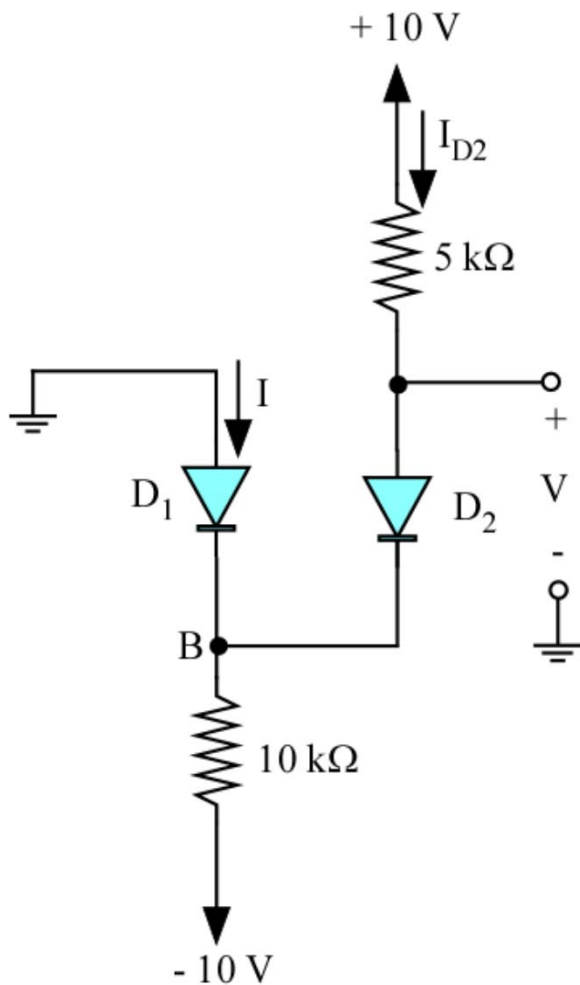

Assume both diodes are on; then

$$V_B = 0 \quad \text{and} \quad V = 0$$

$$I_{D2} = \frac{10 - 0}{5} = 2 \text{ mA}$$

At node B

$$I + 2 = \frac{0 - (-10)}{10} \Rightarrow I = -1 \text{ mA} \Rightarrow \text{wrong}$$

**original assumption is not correct ...
assume D_1 is off and D_2 is on**

$$I_{D2} = \frac{10 - (-10)}{15} = 1.33 \text{ mA}$$

$$V_B = -10 + 10 \times 1.33 = +3.3 \text{ V}$$

D_1 is reverse biased as assumed

Example

The diode has a value of $I_S = 10^{-12}$ mA at room temperature (300° K)

- (a) Approximate the current I assuming the voltage drop across the diode is 0.7V
- (b) Calculate the accurate value of I
- (c) If I_S doubles for every 6° C increase in temperature, repeat part (b) if the temperature increases by 40° C


(a) The resistor will have an approximate voltage of $6 - 0.7 = 5.3$ V. Ohm's law then gives a current of

$$I = \frac{5.3}{2} = 2.65 \text{ mA}$$

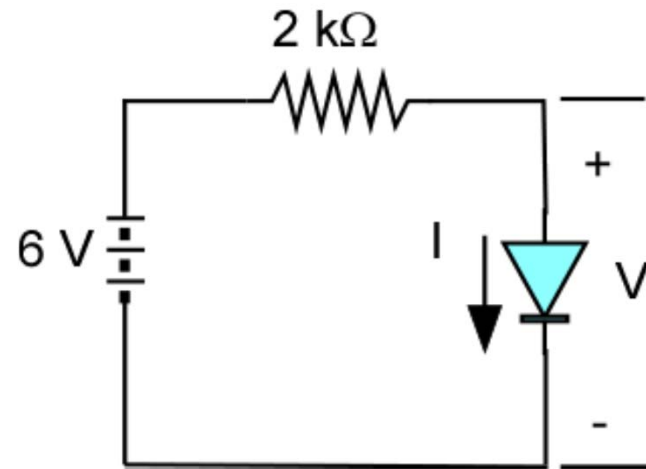(b) The current through the resistor must equal the diode current; so we have

$$I = \frac{6 - V}{2} \text{ (resistor current)}$$

$$I = I_S e^{V/V_T} \text{ (diode current)}$$



Example (cont'd)

$$\frac{6-V}{2} = 10^{-12} e^{V/0.026}$$

Nonlinear equation → must be solved iteratively

Solution: $V = 0.744 \text{ V}$

Using this value of the voltage, we can calculate the current

$$I = \frac{6-V}{2} = \frac{6-0.744}{2} = 2.63 \text{ mA}$$

When the temperature changes, both I_s and V_T will change. Since $V_T = kT/q$ varies directly with T , the new value is:

$$V_T(340) = V_T(300) \times \frac{340}{300} = 0.0295$$

Example (cont'd)

The value of I_s doubles for each 6° C increase, thus the new value of I_s is

$$I_s(340) = I_s(300) \times 2^{40/6} = 1.016 \times 10^{-10} \text{ mA}$$

The equation for I is then


$$I = \frac{6 - V}{2} = 1.016 \times 10^{-10} \times e^{V/0.0295}$$

Solving iteratively, we get

$$V = 0.640 \text{ V} \quad \text{and} \quad I = 2.68 \text{ mA}$$

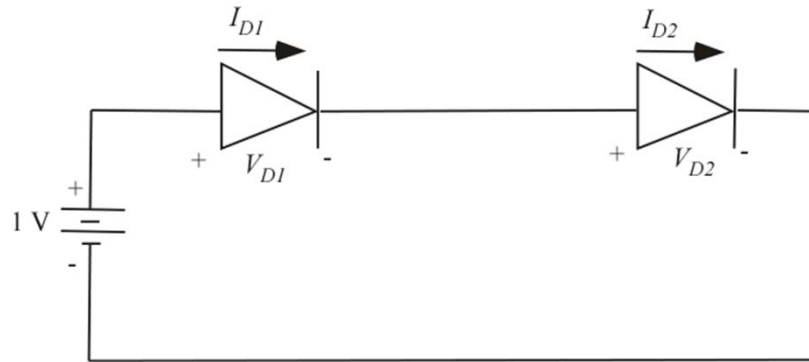Example

Two diodes are connected in series as shown in the figure with $I_{s1} = 10^{-16}$ A and $I_{s2} = 10^{-14}$ A. If the applied voltage is 1 V, calculate the currents I_{D1} and I_{D2} and the voltage across each diode V_{D1} and V_{D2} .



The diode equations can be written as:

$$I_{D1} = I_{S1} e^{V_{D1}/V_T} \quad I_{D2} = I_{S2} e^{V_{D2}/V_T} \quad \frac{I_{S1}}{I_{S2}} e^{\frac{V_{D1}-V_{D2}}{V_T}} = \frac{I_{D1}}{I_{D2}} = 1$$

$$\text{from which } V_{D1} - V_{D2} = -V_T \ln \left(\frac{I_{S1}}{I_{S2}} \right) = -0.12$$

$$\text{Using KVL, we get } V_{D1} + V_{D2} = 1 \quad \text{from which } V_{D2} = 0.44 \text{ V and } V_{D1} = 0.56 \text{ V}$$

$$I_{D1} = 10^{-16} e^{0.56/0.026} = 0.22 \mu\text{A} = I_{D2}$$

Small Signal Model

Approximation - valid for small fluctuations about bias point


$$i_D = I_D e^{v_d/nV_T}$$

$$r_d = \left[\frac{\partial i_D}{\partial v_D} \right]_{i_D=I_D} = \frac{nV_T}{I_D}$$

$$i_D = I_D + i_d$$

↑ Total ↑ DC ↑ applied (small)


$$v_D = V_D + v_d$$

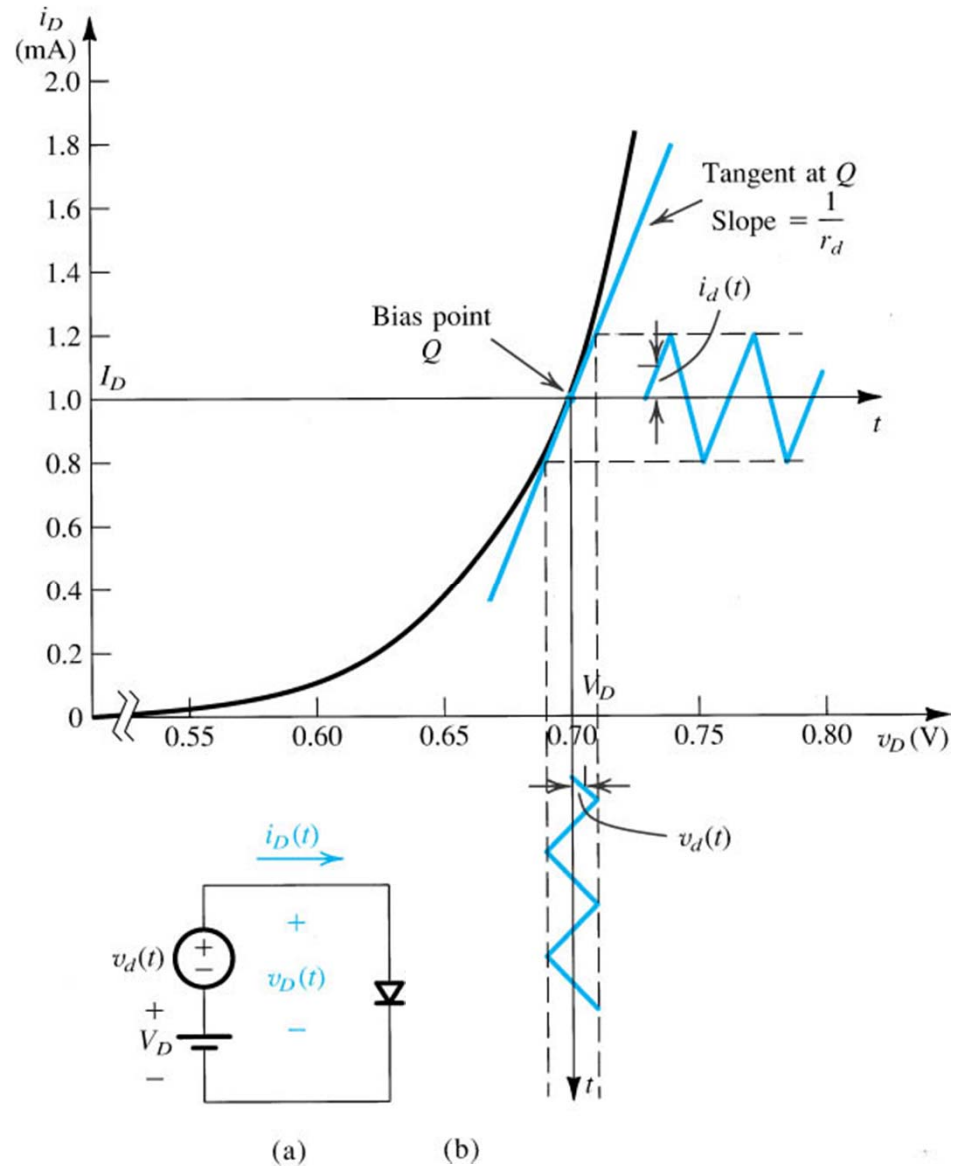

Diodes as Voltage Regulators

- **Objective**

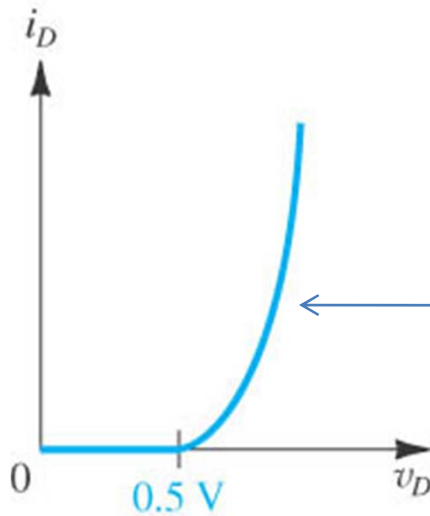- Provide constant dc voltage between output terminals
- Load current changes
- Dc power supply changes
- Take advantage of diode I-V exponential behavior



**Big change in current
correlates to small
change in voltage**

Voltage Regulator - Example

Assume $n=2$ and calculate % change caused by a $\pm 10\%$ change in power-supply voltage (a) with no load (b) with 1-k Ω load

Nominal value of current is:

$$I = \frac{10 - 2.1}{1} = 7.9 \text{ mA}$$

Incremental resistance for each diode:


$$r_d = \frac{nV_T}{I} = \frac{2 \times 25}{7.9} = 6.3 \Omega$$

Resistance for all 3 diodes:

$$r = 3r_d = 18.9 \Omega$$

Voltage change
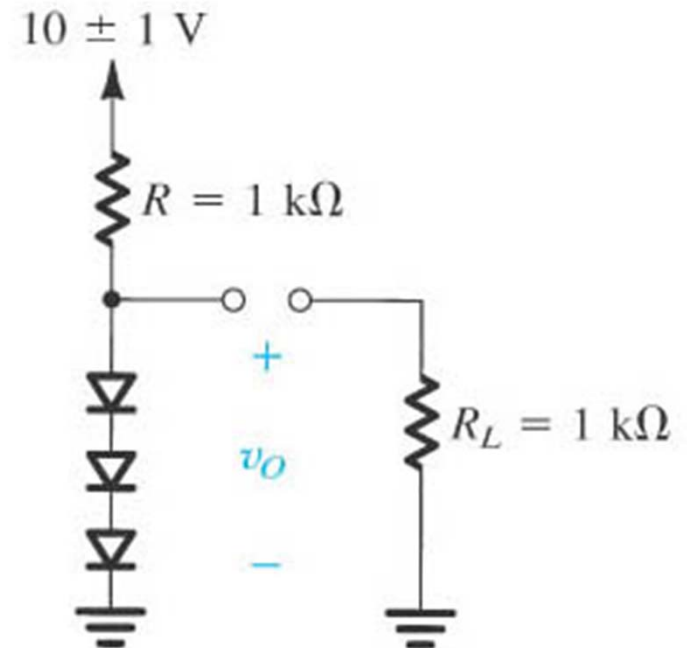
$$\Delta v_o = 2 \frac{r}{r + R} = 2 \frac{0.0189}{0.0189 + 1} = 37.1 \text{ mV} \rightarrow \pm 18.5 \text{ mV} \rightarrow \pm 0.9\%$$




Voltage Regulator – Example (con't)






When $1\text{k}\Omega$ load is connected, it draws a current of 2.1 mA resulting in a decrease in voltage across the 3 diodes given by

$$\Delta v_o = -2.1 \times r$$
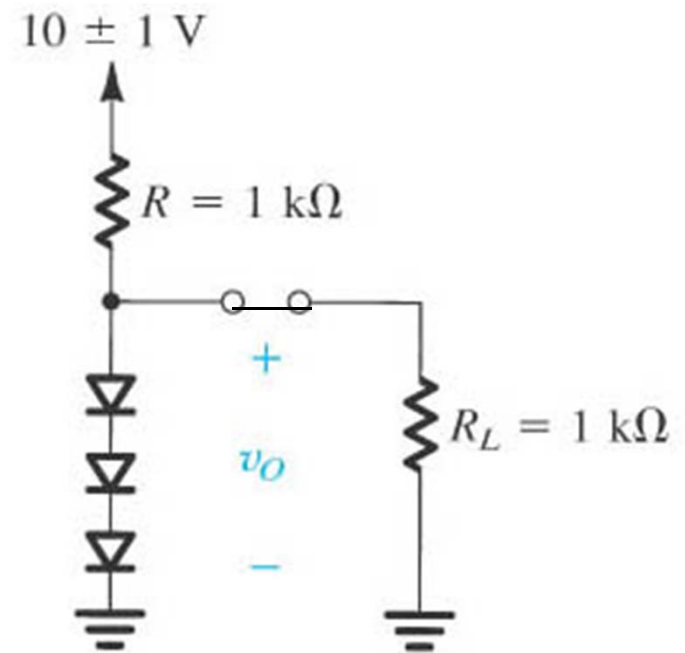
$$\Delta v_o = -2.1 \times 18.9 = -39.7\text{ mV}$$




Diode as Rectifier

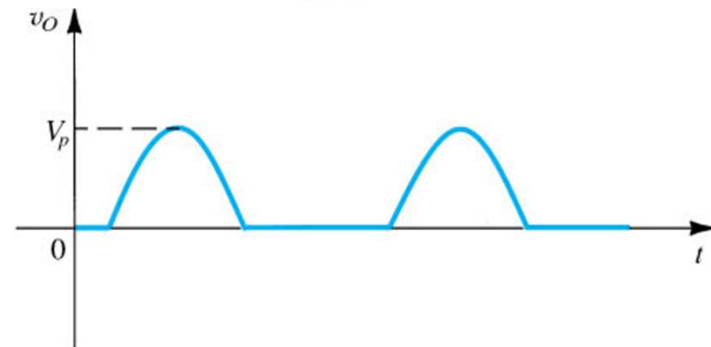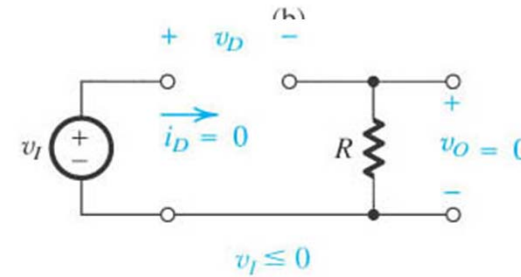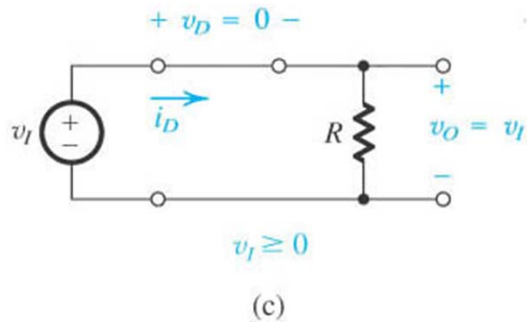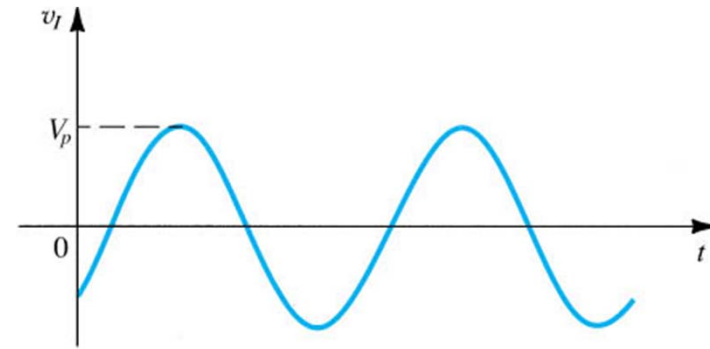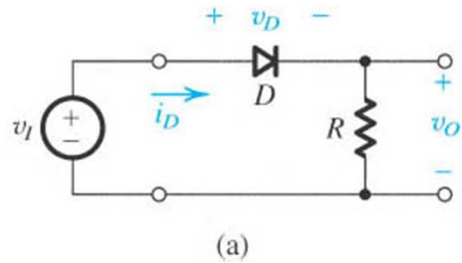

(e)

While applied source alternates in polarity and has zero average value, output voltage is unidirectional and has a finite average value or a *dc component*

Diode as Rectifier

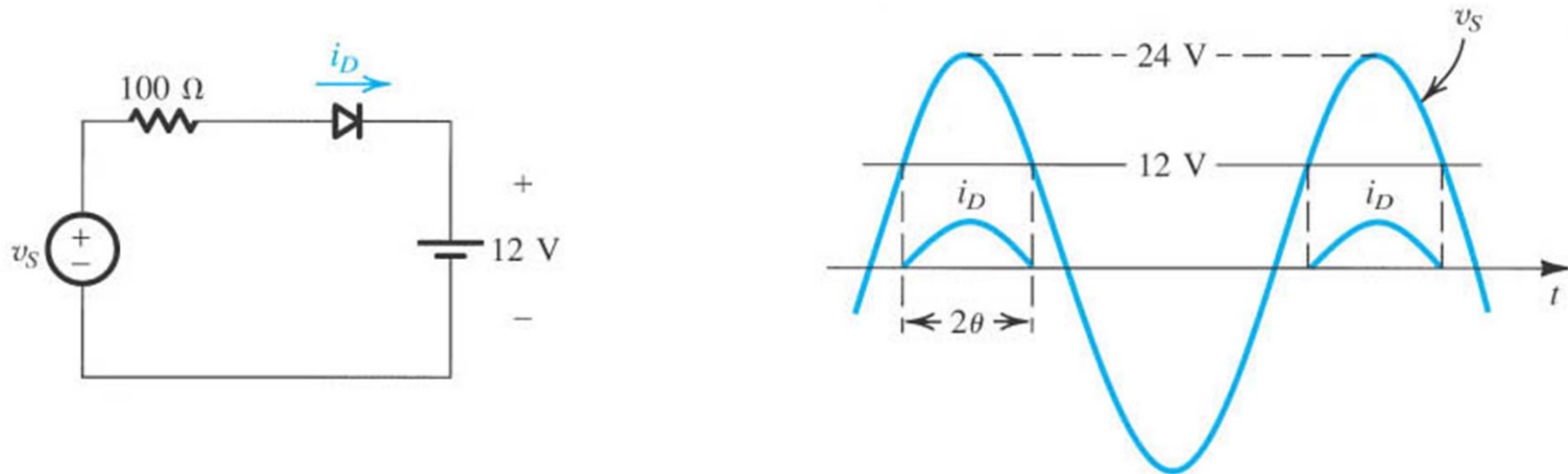

v_s is a sinusoid with 24-V peak amplitude. The diode conducts when v_s exceeds 12 V. The conduction angle is 2θ where θ is given by


$$24 \cos \theta = 12 \Rightarrow \theta = 60^\circ$$

The conduction angle is 120° , or one-third of a cycle. The peak value of the diode current is given by


$$I_d = \frac{24 - 12}{100} = 0.12\text{ A}$$

The maximum reverse voltage across the diode occurs when v_s is at its negative peak: $24 + 12 = 36\text{ V}$



Half-Wave Rectifier

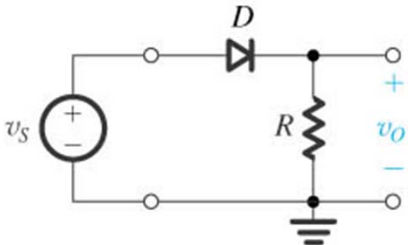

(a)

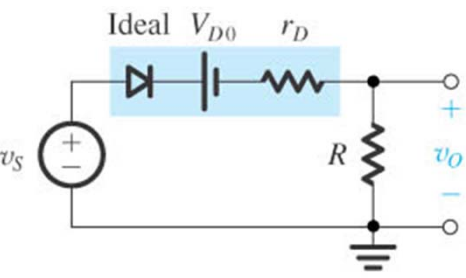


(b)

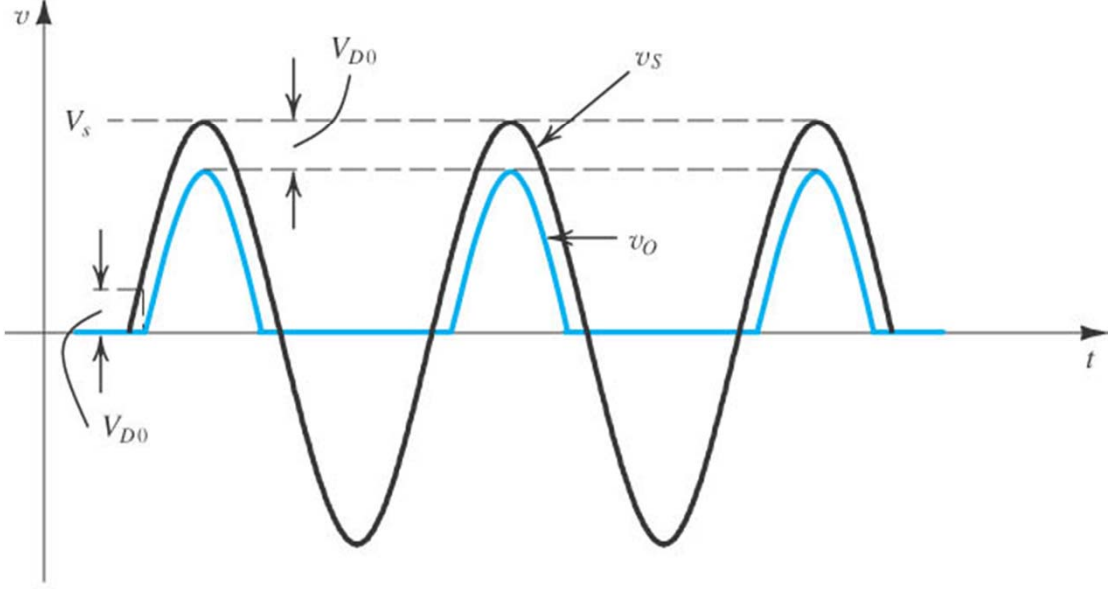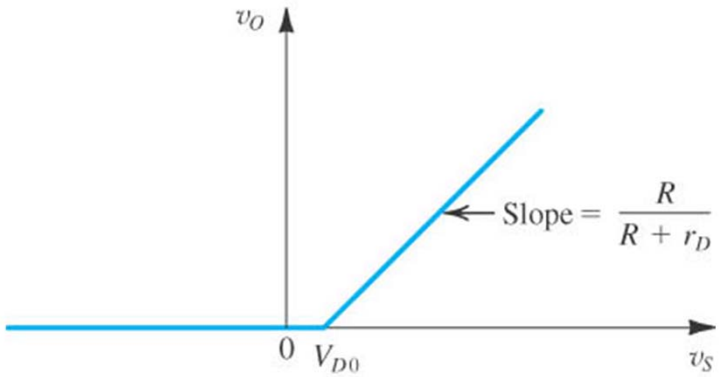


(d)


Full-Wave Rectifier

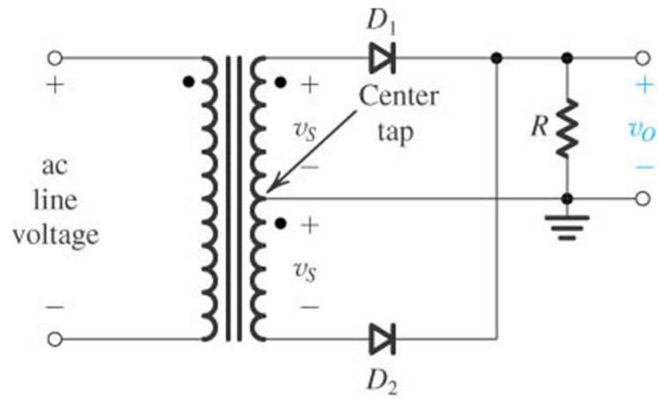

(a)


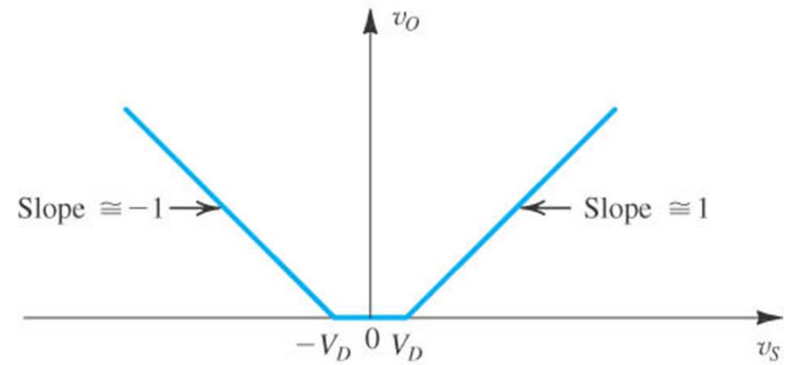


(b)

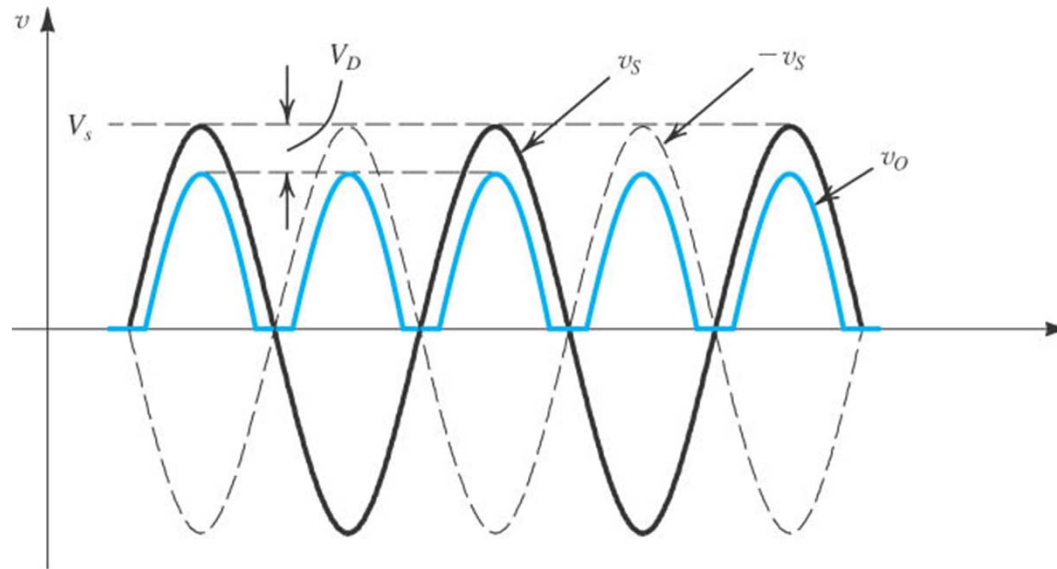


(c)

Bridge Rectifier

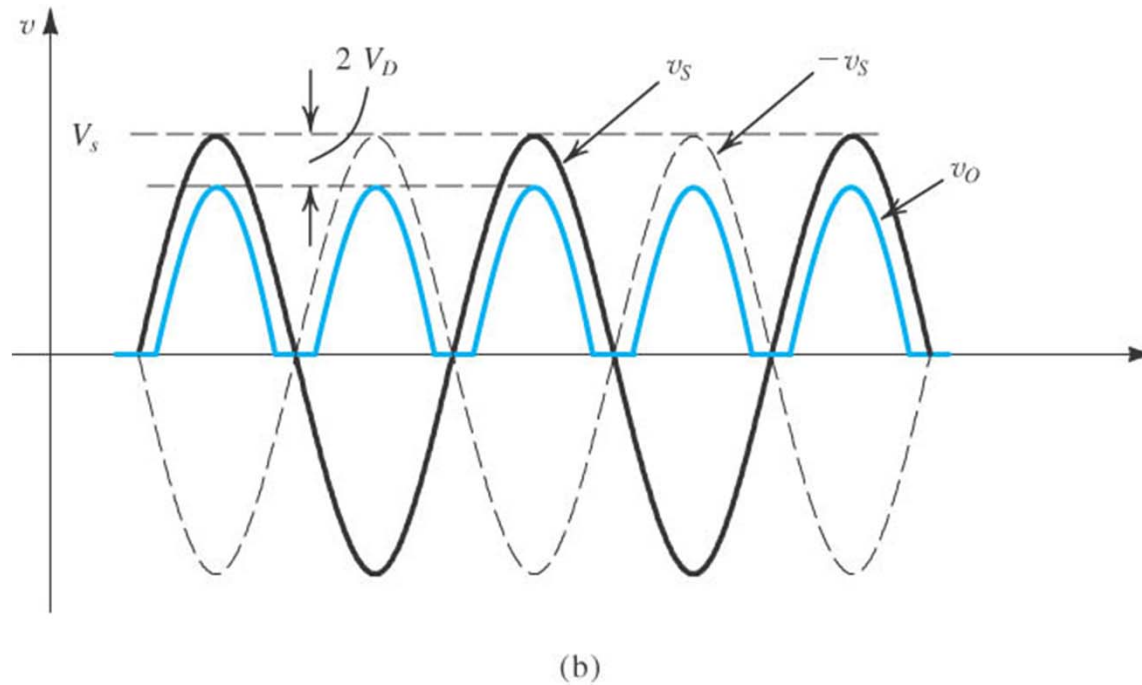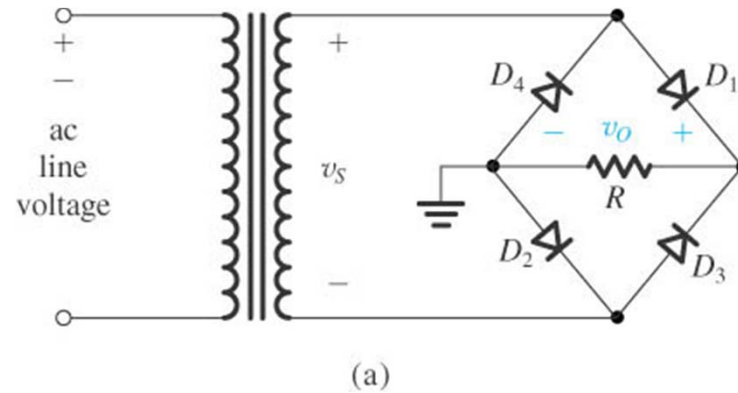

Bridge Rectifier

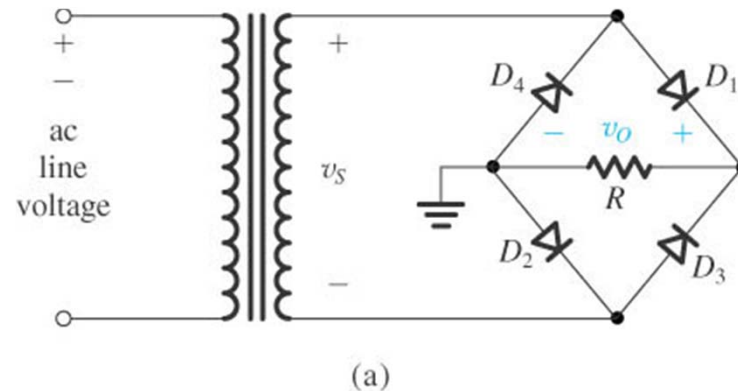

- **Properties**


- Uses four diodes.
- v_o is lower than v_s by two diode drops.
- Current flows through R in the same direction during both half cycles.

The peak inverse voltage (PIV) of each diode:


$$PIV = v_s - 2v_D + v_D = v_s - v_D$$

Peak Rectifier

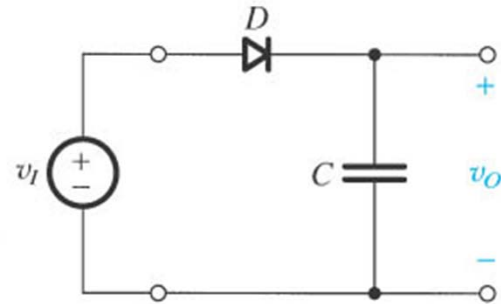Filter capacitor is used to reduce the variations in the rectifier output




(a)

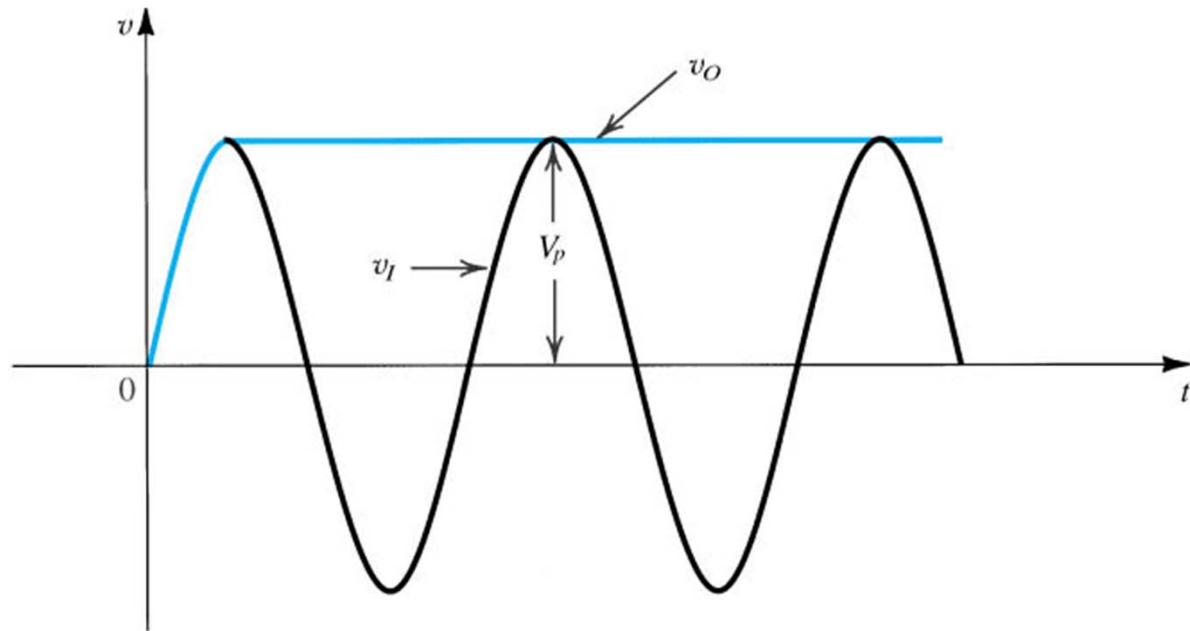

(b)


Rectifier with Filter Capacitor

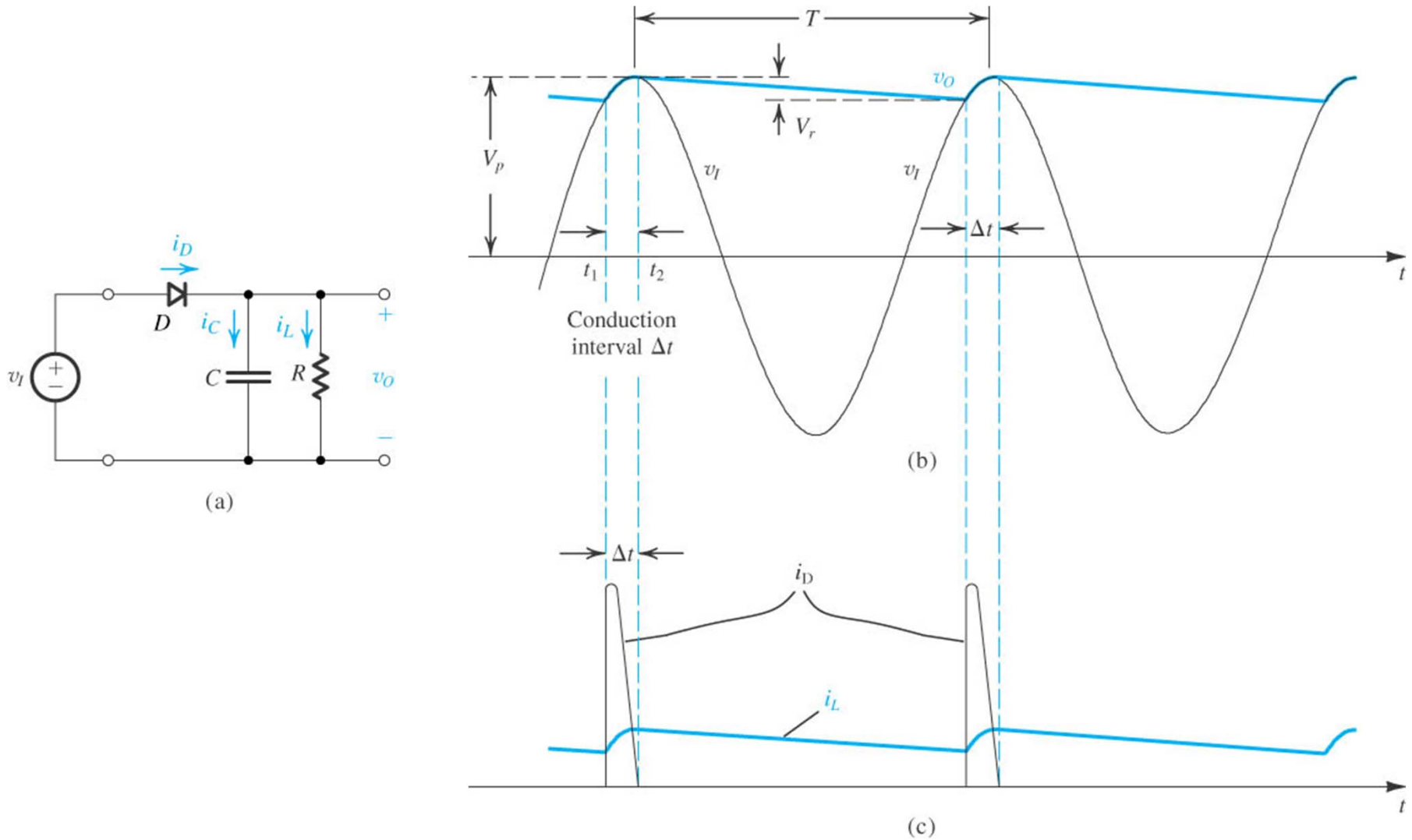

Rectifier with Filter Capacitor

- **Operation**

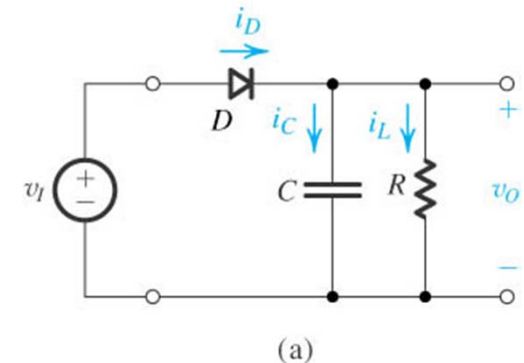- Diode conducts for brief interval Δt
- Conduction stops shortly after peak
- Capacitor discharges through R
- $CR \gg T$
- V_r is peak-to-peak ripple



$$i_L = v_o / R \quad I_L = V_p / R$$

$$i_D = i_C + i_L = C \frac{dv_I}{dt} + i_L$$





$$i_{D_{av}} = I_L \left(1 + \pi \sqrt{2V_p / V_r} \right)$$

$$v_o = V_p e^{-t/CR}$$



$$V_r \approx V_p \frac{T}{CR} = \frac{V_p}{fCR} = \frac{I_L}{fC}$$

$$i_{D_{max}} = I_L \left(1 + 2\pi \sqrt{2V_p / V_r} \right)$$

Diode Circuits - Rectification

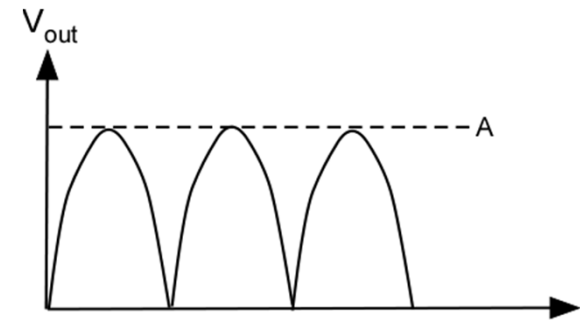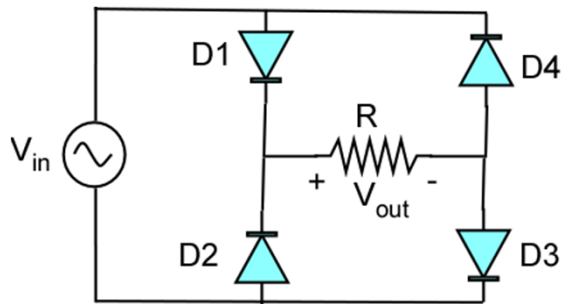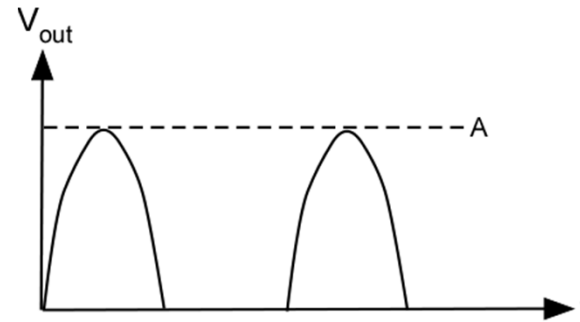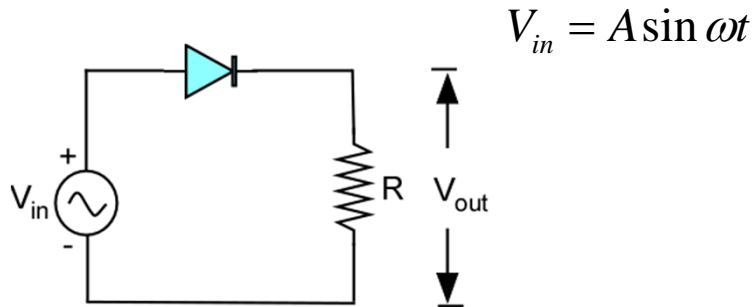


Rectification with ripple reduction.

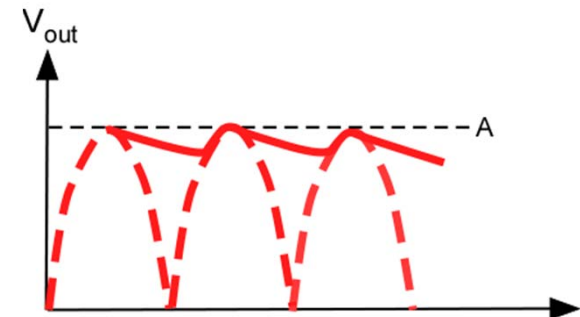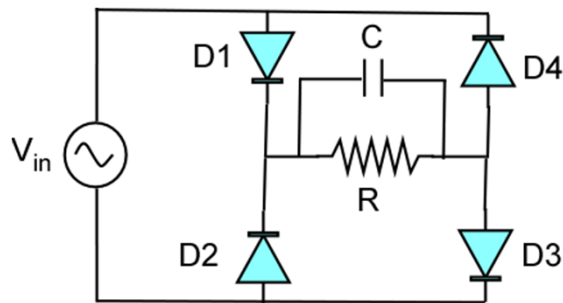

C must be large enough so that RC time constant is much larger than period

Diode Circuits

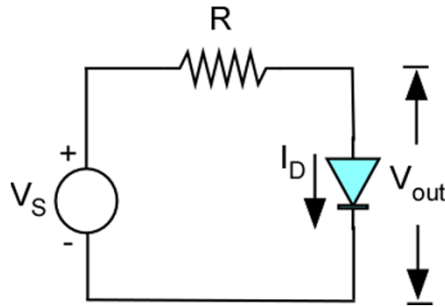


$$V_{out} = V_D$$

$$I_D = I_S \left(e^{V_D/V_T} - 1 \right)$$

$$V_S = RI_D + V_D = RI_D(V_D) + V_D$$

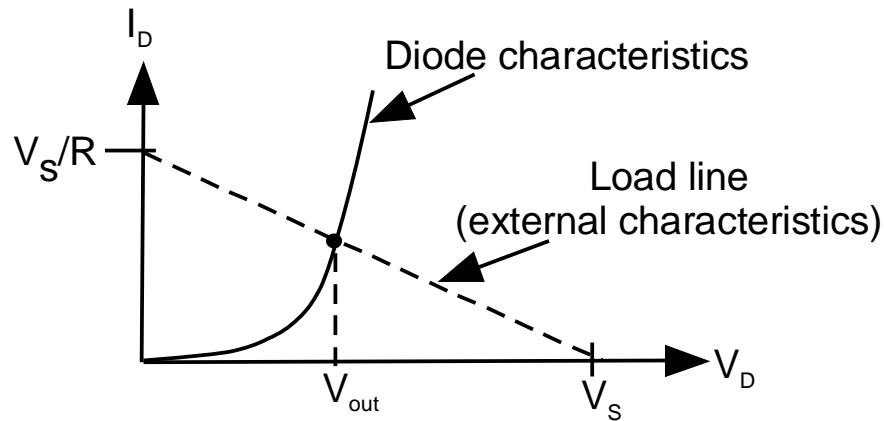Nonlinear transcendental system → Use graphical method



Solution is found at intersection of load line characteristics and diode characteristics

Diode Circuits – Iterative Methods

Newton-Raphson Method

Wish to solve $f(x)=0$ for x

$$\text{Use: } x_{k+1} = x_k - [f'(x_k)]^{-1} f(x_k)$$

$$x^{(k+1)} = x^{(k)} - [f'(x^{(k)})]^{-1} f(x^{(k)})$$

$$f(V_D) = \frac{V_D - V_S}{R} + I_S (e^{V_D/V_T} - 1) = 0$$
$$f'(V_D) = \frac{1}{R} + \frac{I_S}{V_T} e^{V_D/V_T}$$

$$V_D^{(k+1)} = V_D^{(k)} - \frac{\frac{V_D^{(k)} - V_S}{R} + I_S (e^{V_D^{(k)}/V_T} - 1)}{\frac{1}{R} + \frac{I_S}{V_T} e^{V_D^{(k)}/V_T}}$$

Where $V_D^{(k)}$ is the value of V_D at the k th iteration

Procedure is repeated until convergence to final (true) value of V_D which is the solution. Rate of convergence is quadratic.

