



ECE 398GG – ELECTRIC VEHICLES

10a. AC Analysis

Prof. Andrew Stillwell


Department of Electrical and Computer Engineering

University of Illinois at Urbana-Champaign

Today:

- EV Charging System Overview
- AC Circuits

High Level system:

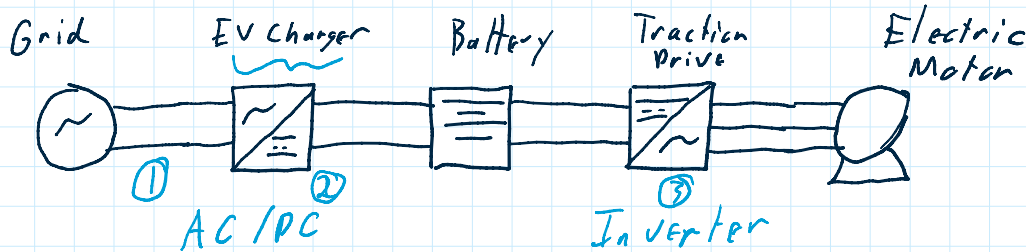

- ① AC Power flow
- ② AC/DC Power Conversion
↳ DC/DC Power conversion
- ③ we learn about this for free
↳ similar to ②

AC circuit analysis


Consider DC ↓



$$V = I (R_1 + R_2)$$

$$P = V \cdot I$$

↳ Algebraic

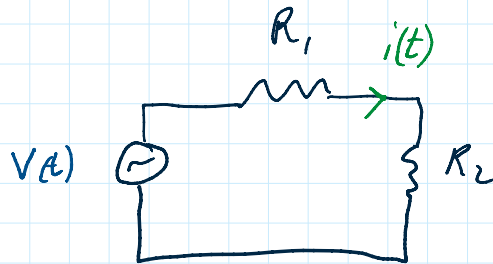


$$V(t) = i(t) (R_1 + R_2)$$

$$P(t) = V(t) \cdot i(t)$$

example: $V(t) = V_p \cdot \sin(\omega t)$


$$\omega = 2\pi \cdot f$$

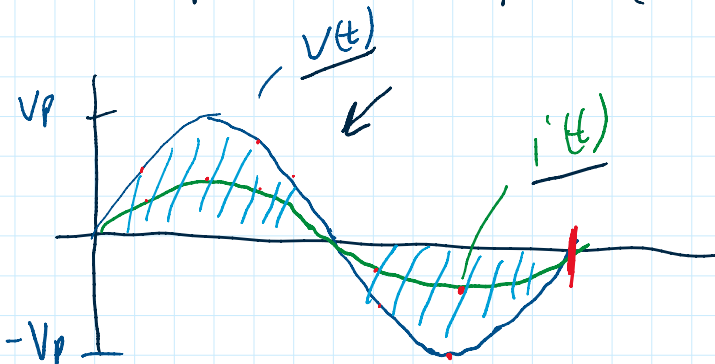

$$i(t) = V(t) / (R_1 + R_2)$$

$$i(t) = I_p \cdot \sin(\omega t)$$

$$I_p = V_p / (R_1 + R_2)$$

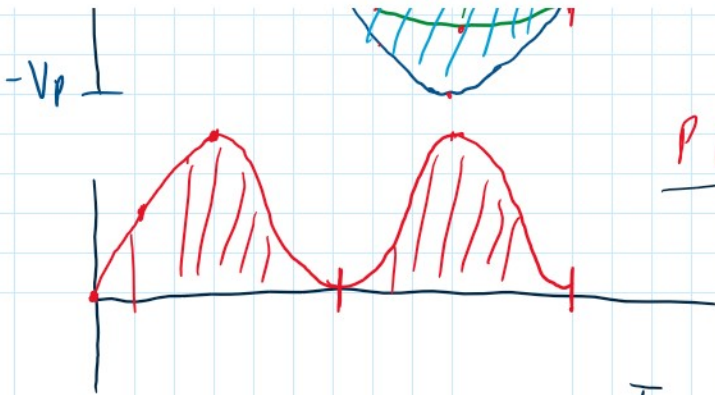


$$P(t) = v(t) \cdot i(t)$$

Typically want Average Power

$$P = \langle P(t) \rangle = \frac{1}{T} \int_0^T P(t) dt \quad T = \frac{1}{f}$$

How do we find P , given $v(t)$, $i(t)$

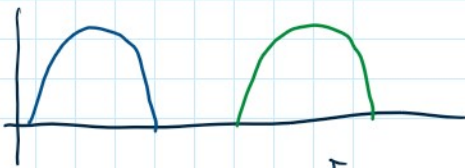

$$\langle P(t) \rangle = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{T} \int_0^T v(t) \cdot i(t) dt$$

$$v(t) = i(t) \cdot R$$

$$P = \frac{1}{T} \int_0^T i(t)^2 \cdot R dt = \frac{1}{T} \int_0^T i(t)^2 dt \cdot R$$

$$P = I_{RMS}^2 \cdot R$$

Root Mean Squared

$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$

$$P = I_{RMS}^2 \cdot R = \frac{V_{RMS}^2}{R}$$


for $v(t) = V_p \cdot \cos(\omega t + \theta_v)$ or $i(t) = I_p \cdot \cos(\omega t + \theta_i)$

$$V_{RMS} = \frac{V_p}{\sqrt{2}} = V$$


$$V_p = \sqrt{2} \cdot V$$

$$I_{RMS} = \frac{I_p}{\sqrt{2}} = I$$

$$I_p = \sqrt{2} \cdot I$$

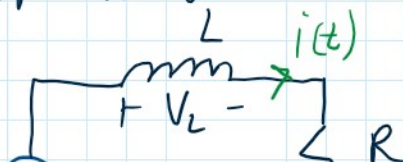
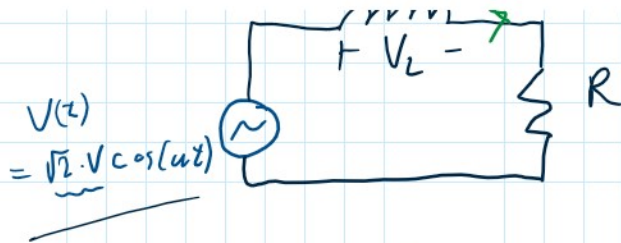
$$v(t) = L \frac{di(t)}{dt} + R \cdot i(t)$$



$$V(t) = L \frac{di(t)}{dt} + R \cdot i(t)$$

↳ First order Diff. Eqn.

We can use Phasors to solve this circuit algebraically



$$\bar{V} = \bar{I} (\bar{Z}_L + \bar{Z}_R)$$

P = ?

Euler's Formula

$$v(t) = V \cdot \sqrt{2} \cdot \cos(\omega t + \theta_v) \Leftrightarrow \bar{V} = V \cdot e^{j\theta_v} = V \angle \theta_v$$


$$i(t) = I \cdot \sqrt{2} \cdot \cos(\omega t + \theta_i) \Leftrightarrow \bar{I} = I \cdot e^{j\theta_i} = I \angle \theta_i$$

$$L \quad \Leftrightarrow \bar{Z}_L = j\omega L = \omega L \angle 90^\circ$$

$$C \quad \Leftrightarrow \bar{Z}_C = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

$$R \quad \Leftrightarrow \bar{Z}_R = R = R \angle 0^\circ$$

Example

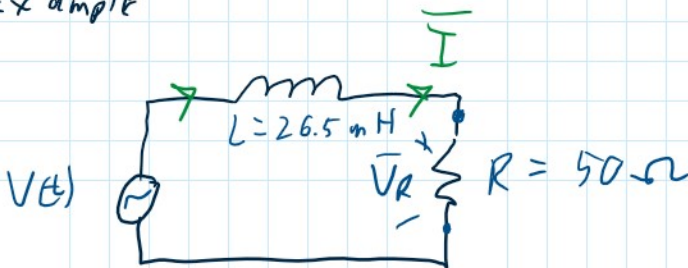

$$V(t) = 100\sqrt{2} \cos(\omega t) \text{ V}$$

$$\omega = 2\pi \cdot f, \quad f = 60 \text{ Hz}$$

$$\omega = 377 \text{ rad/s}$$

$$\bar{V} = 100 \angle 0^\circ \text{ V}$$

$$= 10 \angle 90^\circ$$

$$\bar{Z}_L = j\omega L = j377 \cdot 26.5 \times 10^{-3} = j10$$

$$\bar{Z}_R = 50$$

I-bar?

$$\bar{I} = \frac{\bar{V}}{\bar{Z}_L + \bar{Z}_R} = \frac{100 \angle 0^\circ}{j10 + 50} = \frac{100 \angle 0^\circ}{51 \angle 11.3^\circ}$$

→ -

$$Z_L + Z_R$$

$$10 + 50$$

$$51 \angle 11.5^\circ$$

$$\vec{I} = 1.96 \angle -11.3^\circ \text{ A}$$

$$\vec{V}_R = \vec{I} R = 98 \angle -11.3^\circ \text{ V}$$

$$P_R = \frac{V_{RMS}^2}{R} \quad \text{or} \quad I_{RMS}^2 \cdot R$$


$$\rightarrow \frac{98^2}{50} = 192 \text{ W} \quad 1.96^2 \cdot 50 = 192 \text{ W} \checkmark$$

Note: Purely reactive elements do not dissipate power - just store energy

To supply power (P) to RL load, we must supply 1.96 Arms of current

$$100 \cdot 1.96 = 196 \text{ VA} > 192 \text{ W} - \text{sent to resistive load}$$

Instantaneous Power

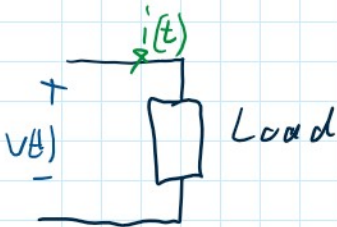

$$P(t) = V(t) \cdot i(t) \leftarrow$$

$$V(t) = V \cdot \sqrt{2} \cdot \cos(\omega t + \theta_v) \leftarrow$$

$$i(t) = I \cdot \sqrt{2} \cdot \cos(\omega t + \theta_i) \leftarrow$$


$$P(t) = \underline{2} \cdot V \cdot I \cos(\omega t + \theta_v) \cdot \cos(\omega t + \theta_i)$$


$$\text{Trig identity: } \cos \theta_1 \cdot \cos \theta_2 = \frac{1}{2} [\cos(\theta_1 - \theta_2) + \cos(\theta_1 + \theta_2)]$$

$$P(t) = V \cdot I \left[\underbrace{\cos(\theta_v - \theta_i)}_{\text{constant}} + \underbrace{\cos(2\omega t + \theta_v + \theta_i)} \right]$$

$P(t)$

constant

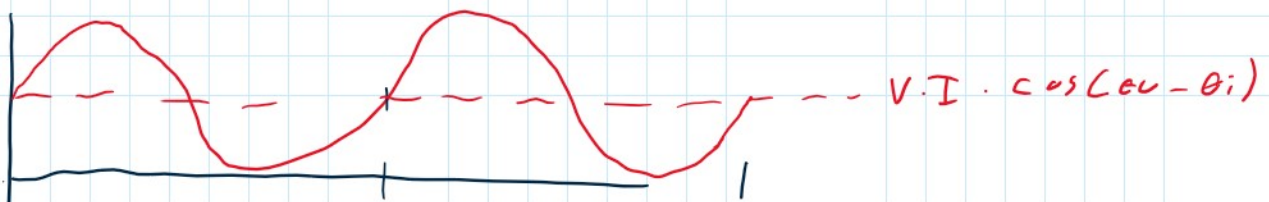

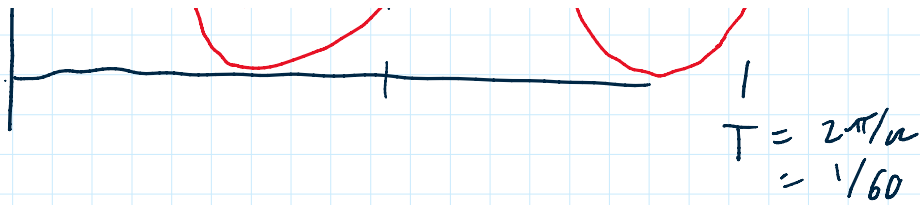

$$P = \frac{1}{T} \int_0^T P(t) dt$$

$$= \frac{1}{T} \int_0^T V \cdot I \left[\underbrace{\cos(\theta_v - \theta_i)}_{\text{const}} + \cos(2\omega t + \theta_v + \theta_i) \right] dt$$

$$\downarrow$$

$$P = V \cdot I \cdot \cos(\theta_v - \theta_i) \leftarrow$$

$S \triangleq V \cdot I = \text{Apparent Power}$

$\cos(\theta_v - \theta_i) = \text{Power factor} = \text{PF}$