
ECE 398GG – ELECTRIC VEHICLES

10b. Complex Power Flow Concepts

Prof. Andrew Stillwell

Department of Electrical and Computer Engineering

University of Illinois at Urbana-Champaign

ECE 398GG © 2022-2023 George Gross, University of Illinois at Urbana-Champaign, all rights reserved.

EV Charging Pt 2

Thursday, March 10, 2022 9:11 AM

Today:

- Complex Power
- 3 Phase Power
- Simple Power Flow

Last time: (Review)

$$V = V_{RMS}$$

→ Phasors

For AC systems ($v(t) = \sqrt{2} \cdot V \cdot \cos(\omega t + \theta_v)$)


Can solve circuits algebraically with phasors

$$\rightarrow v(t) = \sqrt{2} \cdot V \cdot \cos(\omega t + \theta_v) \Leftrightarrow \bar{V} = V \angle \theta_v \leftarrow$$
$$\bar{I} = I \angle \theta_i$$

P , average power for a resistor

$$P = \frac{V^2}{R} = I^2 \cdot R$$

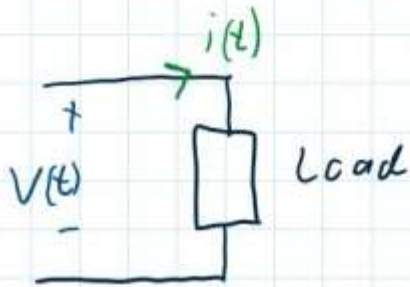Once we introduce reactive elements (L, C)



$$P = V \cdot I \cdot \cos(\theta_v - \theta_i)$$

$$VI \hat{=} S = \text{Apparent Power [VA]}$$

$$\cos(\theta_v - \theta_i) = \text{Power factor}$$

Complex Power: \bar{S}

$$\bar{S} \hat{=} P + jQ$$

Q = Reactive Power \Rightarrow "Power" supplied / Absorbed by reactive elements [VAR]

$$\hookrightarrow Q_C = \frac{V_C^2}{|\bar{Z}_C|}$$


$$Q_L = I_L^2 |\bar{Z}_L|$$

$$\rightarrow \omega C = \frac{V_C}{|Z_C|}$$

$$\omega L = I_C |Z_L|$$

\rightarrow Q is still very important (ECE 476)

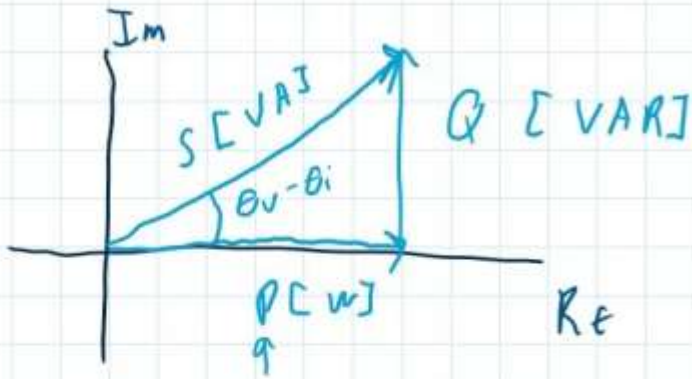Can represent complex power with Power triangle



$$\bar{S} = P + jQ \text{ - complex}$$

$$\rightarrow \underline{S} = \sqrt{P^2 + Q^2} \text{ - Apparent}$$

$$\cos(\theta_v - \theta_i) = \frac{P}{S}$$


$$\underline{P} = \underline{S} \cdot \cos(\theta_v - \theta_i) \checkmark$$

↑
V · I

$$\sin(\theta_v - \theta_i) = \frac{Q}{S}$$

$$\underline{Q} = \underline{S} \cdot \sin(\theta_v - \theta_i)$$

Back to our example:

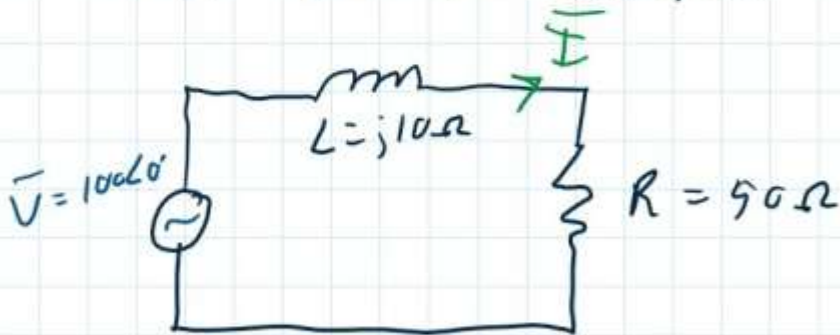

$$\underline{I} = 1.96 \angle -11.3^\circ \text{ A} \quad \underline{P} = 192 \text{ W} \quad V \cdot I = 196 \text{ VA} = \underline{S}$$

$$Q_2? \quad Q_L = I^2 \cdot \omega L = 1.96^2 \cdot 10 = 38.4 \text{ VAR}$$

$$\text{or } S^2 = P^2 + Q^2 \Rightarrow Q = \sqrt{S^2 - P^2} = 38.4 \text{ VAR}$$

$$\text{or } Q = S \cdot \sin(\theta_v - \theta_i) = 196 \sin(0 + 11.3^\circ) = 38.4 \text{ VAR}$$

$$\rightarrow \underline{\bar{S}} = P + jQ = 192 + j38.4 = 196 \angle 11.3^\circ$$


$$\rightarrow \bar{S} = P + jQ = 192 + j38.4 = 196 \angle 11.3^\circ$$

$$\bar{S} = \bar{V} \cdot \bar{I}^* = 100 \angle 0^\circ \times 1.96 \angle +11.3^\circ = 196 \angle +11.3^\circ$$


Measurements

Thursday, March 10, 2022 9:12 AM

Inductor Load

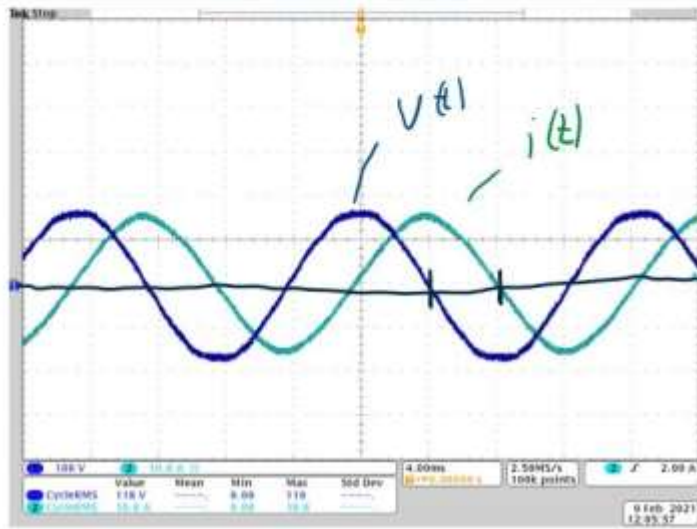

Capacitor Load

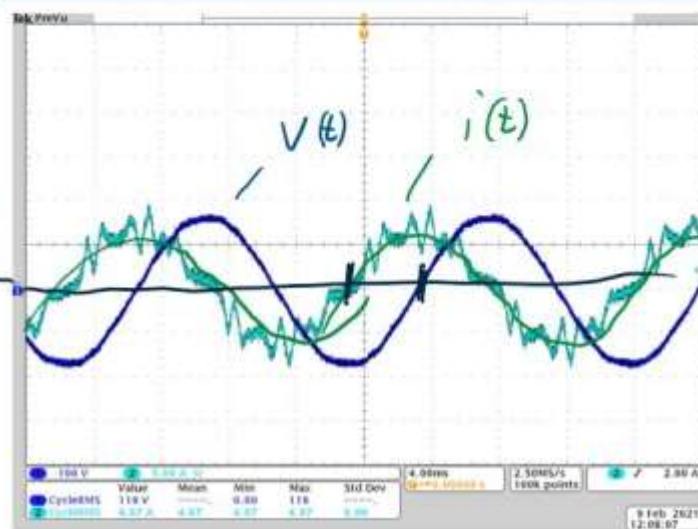

Load Based Notation


$Q > 0 \Rightarrow$ Load consumes VARS
 $Q < 0 \Rightarrow$ Load supplies VARS

$$\bar{Z}_L = j\omega L = \omega L \angle 90^\circ$$


$$\bar{Z}_C = 1/j\omega C = 1/\omega C \angle -90^\circ$$

Loads	$\phi = \theta_v - \theta_i$	PF	Power triangle	Load Q
Inductive	> 0	< 1 "Lagging"		> 0
capacitive	< 0	< 1 "Leading"		< 0
Resistive	$= 0$	1		0

Conservation of complex Power

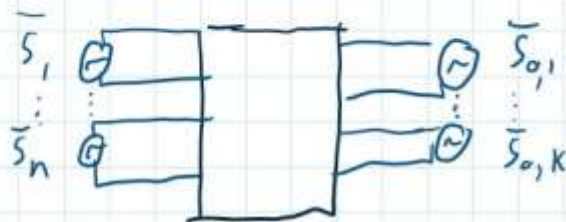


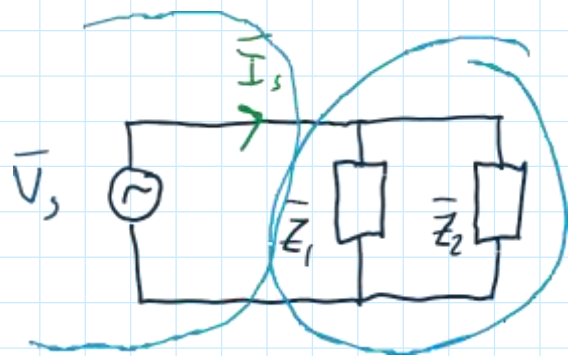Complex power into network = Complex power out of network




$$\bar{S}_s = \bar{S}_1 + \bar{S}_2 = \bar{V}_s \cdot \bar{I}_s^*$$

3-Phase Power


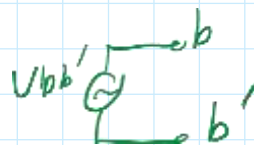


$$\begin{aligned} \bar{V}_{aa'} &= V \angle \theta_v \\ \bar{V}_{bb'} &= V \angle \theta_v - 120^\circ \\ \bar{V}_{cc'} &= V \angle \theta_v + 120^\circ \end{aligned}$$

Positive Sequence

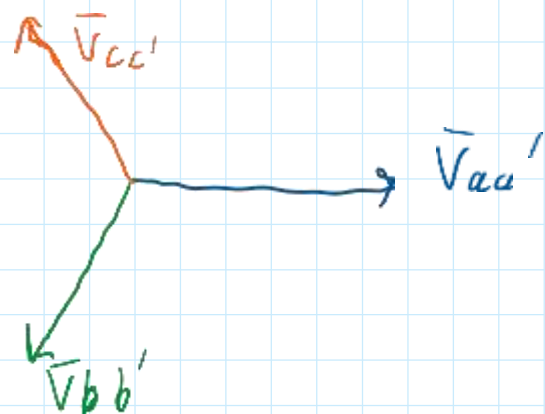


Three Phase Connections

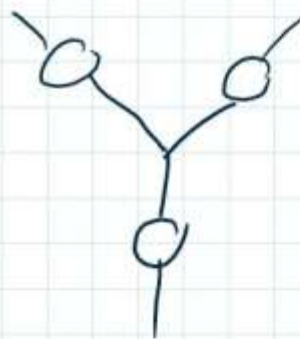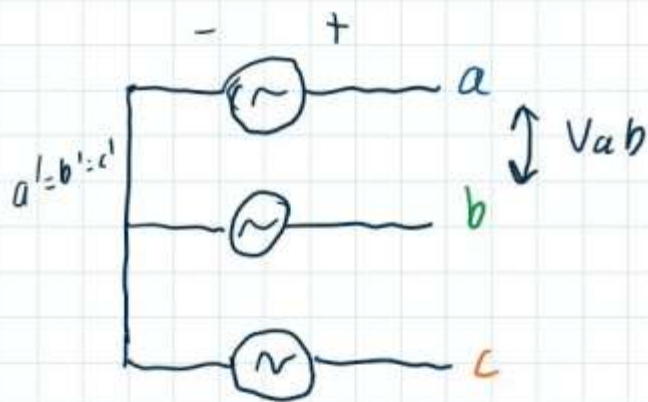

WYE
Connection
(Y)

$$V_{ab} = \sqrt{3} \cdot V_{aa'}$$

$$V_{Line} = \sqrt{3} \cdot V_{Phase}$$

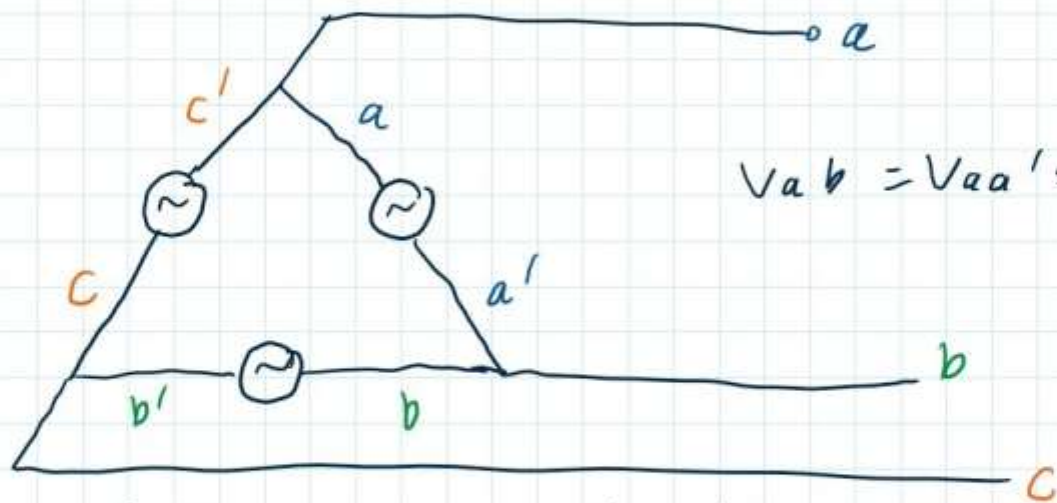



$$V_{ab} = V_{aa'} \Rightarrow V_L = V_{Phase}$$

Delta connection (Δ)

Why three phase?

↳ if balanced, no neutral line current

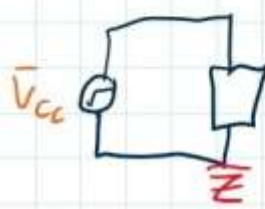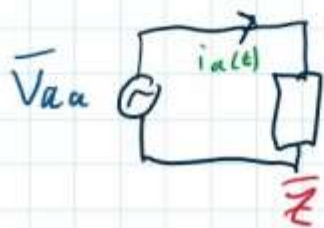Just as important for Power conversion: $P(t)$



$$\begin{aligned} V_{aa'}(t) &= \sqrt{2} \cdot V \cdot \cos(\omega t) \\ V_{bb'}(t) &= \sqrt{2} \cdot V \cdot \cos(\omega t - 120^\circ) \\ V_{cc'}(t) &= \sqrt{2} \cdot V \cdot \cos(\omega t + 120^\circ) \end{aligned}$$

$$\begin{aligned} i_a(t) &= \sqrt{2} \cdot I \cdot \cos(\omega t - \phi) \\ i_b(t) &= \sqrt{2} \cdot I \cdot \cos(\omega t - \phi - 120^\circ) \\ i_c(t) &= \sqrt{2} \cdot I \cdot \cos(\omega t - \phi + 120^\circ) \end{aligned}$$

$$V_{bb'}(t) = \sqrt{2} \cdot V \cdot \cos(\omega t - 120^\circ) \quad i_b(t) = \sqrt{2} \cdot I \cdot \cos(\omega t - \phi - 120^\circ)$$

$$V_{cc'}(t) = \sqrt{2} \cdot V \cdot \cos(\omega t + 120^\circ) \quad i_c(t) = \sqrt{2} \cdot I \cdot \cos(\omega t - \phi + 120^\circ)$$

$$P_a(t) = V \cdot I \cdot [\cos(\phi) + \cos(2\omega t - \phi)]$$

$$P_b(t) = V \cdot I [\cos(\phi) + \cos(2\omega t - \phi - 240^\circ)]$$

$$P_c(t) = V \cdot I [\cos(\phi) + \cos(2\omega t - \phi + 240^\circ)]$$

$$P(t) = P_a(t) + P_b(t) + P_c(t)$$

$$= 3V \cdot I \cos \phi + \underbrace{V \cdot I [\cos(2\omega t - \phi) + \cos(2\omega t - \phi - 240^\circ) + \cos(2\omega t - \phi + 240^\circ)]}_{=0}$$


*

$$P(t) = 3 \cdot V \cdot I \cdot \cos \phi = P$$

Instantaneous power is actually constant!!!

can also show: $\bar{S} = 3 \cdot V \cdot I \cos(\phi) + 3 \cdot V \cdot I \sin(\phi)$

AC Power Flow (Simple) [476]

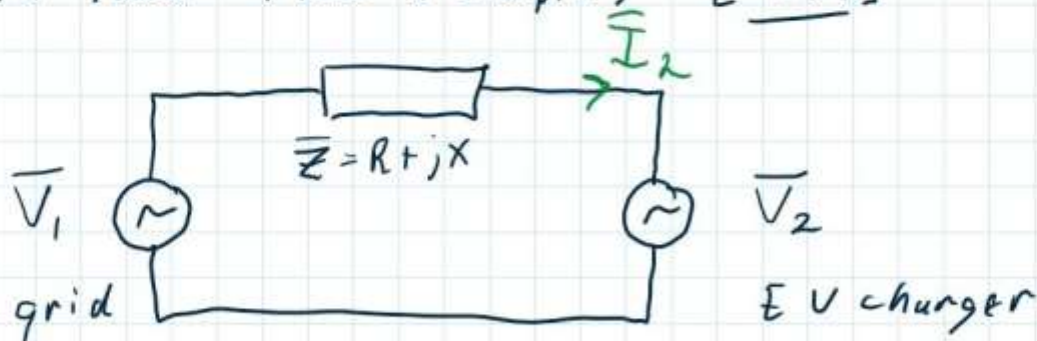

→ assume line is lossless

$$\bar{Z} = jX = Z e^{j90^\circ} = Z \angle 90^\circ \quad (Z = X = \omega L)$$

$$\bar{V}_1 = V_1 \angle \theta_1, \quad \bar{V}_2 = V_2 \angle \theta_2$$

$$\bar{S}_2 = \bar{V}_2 \cdot \bar{I}_2^*$$

$$\bar{I}_2 = \frac{\bar{V}_2 - \bar{V}_1}{\bar{Z}}$$

$$S_2 = V_2 \cdot I_2^*$$

$$I_2 = \frac{V_2 - V_1}{Z}$$


$$= \bar{V}_2 \cdot \frac{\bar{V}_2^* - \bar{V}_1^*}{Z^*} = \frac{V_2 \angle \theta_2 \cdot (V_2 \angle -\theta_2 - V_1 \angle -\theta_1)}{Z \angle -90^\circ}$$

$$\bar{S}_2 = \frac{V_2^2}{Z} \angle 90^\circ - \frac{V_1 \cdot V_2}{Z} \angle \theta_2 - \theta_1 + 90^\circ$$

From Euler's $e^{i\theta} = \underbrace{\cos \theta}_p + j \underbrace{\sin \theta}_q$

$$P_2 = \frac{V_2^2}{Z} \cos(90^\circ) - \frac{V_1 \cdot V_2}{Z} \cos(\theta_2 - \theta_1 + 90^\circ)$$
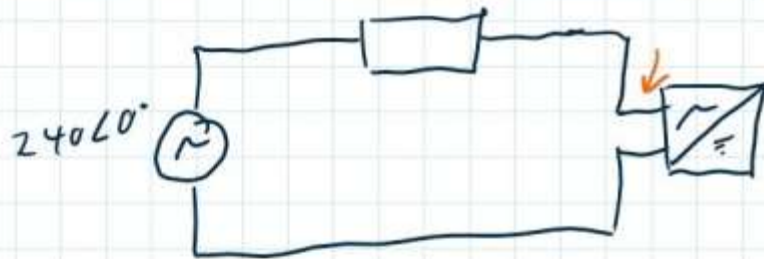
$$P_2 = \frac{V_1 \cdot V_2}{Z} \sin(\theta_2 - \theta_1)$$



EV charger