ECE 398GG

Prof. George Gross Room 339 Everitt Lab Spring 2023

Homework 5 Solution

1. Convert the following instantaneous currents into phasors, using $cos(\omega t)$ as the reference. State your answers in polar form.

(i)
$$i(t) = 400\sqrt{2}\cos(\omega t - 30^\circ)$$

(ii) $i(t) = 5 \sin(\omega t + 15^{\circ})$

(iii)
$$i(t) = 4\cos(\omega t - 30^\circ) + 5\sqrt{2}\sin(\omega t + 15^\circ)$$

Solution: We make use of the relationship that $sin(\mu) = cos(90^{\circ} - \mu)$

(i)

$$\begin{bmatrix}
400\sqrt{2}/\sqrt{2} \\
2/\sqrt{2} \\
2/\sqrt{2$$

2. **Detemine** the r.*m.s.* value of voltage for the sawtooth waveform below.



Solution: We define f(x) = 2x and compute the rms value for an arbitrary period

$$\sqrt{\int_0^1 \left[\frac{1}{1} * (2x)^2\right] dx} = \frac{2}{\sqrt{3}}$$

3. For the following 120-*V*, 60-*Hz* circuit, perform the following:



- (i) **Determine** the reactance and the impedance of the inductor?
- (ii) **Express** the impedance of the combination of *R* and *L* in both polar coordinates and rectangular Z = R + jX form.
- (iii) **Determine** the current expressed as a phasor and as a function of time.
- (iv) **Determine** the power factor of the circuit.
- (v) **Calculate** the output voltage expressed as a phasor and as a function of time.

Solution:

(i)

$$X_L = \omega L = 2\pi \cdot 60 \cdot 0.1 = 37.7\Omega$$
$$Z_L = j\omega L = j37.7 = 37.7 \angle 90^\circ$$

(ii)

$$Z_{Tot} = R + j\omega L = 100 + j37.7$$
$$= \sqrt{100^2 + 37.7^2} \angle \tan^{-1} \left(\frac{37.7}{100}\right) = 106.9 \angle 20.66^{\circ}$$

(iii) the angle -20.66 is written incorrectly in the lines after the first equation $I = \frac{V}{Z} = \frac{120\angle 0^{\circ}}{106.9\angle 20.66^{\circ}} = 1.12\angle -20.66^{\circ}$ $i = 1.12\sqrt{2}\cos(\omega t - 20.22^{\circ}) = 1.12\sqrt{2}\cos(377t - 20.22^{\circ})$

- (iv) p.f. = cos(-20.66) = 0.94
- (v) The two evaluations

$$V_{out} = Z_L I = j37.7 \times 1.12 \angle -20.66 = 42.2 \angle 69.3$$

OR...using the voltage divider approach:
$$V_{out} = V_{in} \cdot \frac{Z_L}{Z_R + Z_L} = 120 \angle 0^o \cdot \frac{37.7 \angle 90^o}{106.9 \angle 20.66^o} = 42.3 \angle 69.3^o$$

$$v_{out} = 42.3\sqrt{2}\cos(\omega t + 69.3^{\circ})$$

4. For the circuit shown below, perform the following:



- (i) **Compute** the voltage across the load terminals
- (ii) Determine the real power delivered to the load in terms of the voltage and current phasors at the load.
- (iii) **Calculate** the real power delivered to the load via the power flow equation derived in class, under the assumption of a lossless transmission line.
- (iv) **Comment** on the differences, if any, between the results in (ii) and (iii).

Solution:

- (i) $V_{load} = 120 \ D 0 60 \ D 0 \ x \ (0.1 + j0.5) = 117 \ D 14.7^{\circ}$
- (ii) $P = V \times I \times \cos(\theta_V \theta_I) = 117 \times 60 \times \cos(-14.7^\circ 0) = 6,790 W$
- (iii) $P = [(V_1 \ge V_2)/x]sin(\theta_1 \theta_2) = 7,150 W$
- (iv) Given that the power flow relation assumes a lossless line and this is not the case since there is a 0.1 *ohm* resistance, the answers are relatively close and so the order of magnitude of the difference is acceptable in this case.