


Exam #1 SOLUTION

SPRING 1990

#1 $P_{\text{wm}} = |\bar{V}_{AB}| |\bar{I}_L| \cos(\angle \bar{V}_{AB} - \angle \bar{I}_L)$ For ABC seq., if $\angle \bar{V}_{AB} = 30^\circ$, then
 $\angle \bar{I}_L = 120^\circ - \phi$ ($\phi = \text{power factor angle}$)

Since $\bar{S}_{3\phi} = \sqrt{3} V_{LL} \bar{I}_L \angle \phi = 1500 + j1500$, $V_{LL} \bar{I}_L = \frac{1}{\sqrt{3}} 1500 \angle \phi$ and $\phi = 45^\circ$

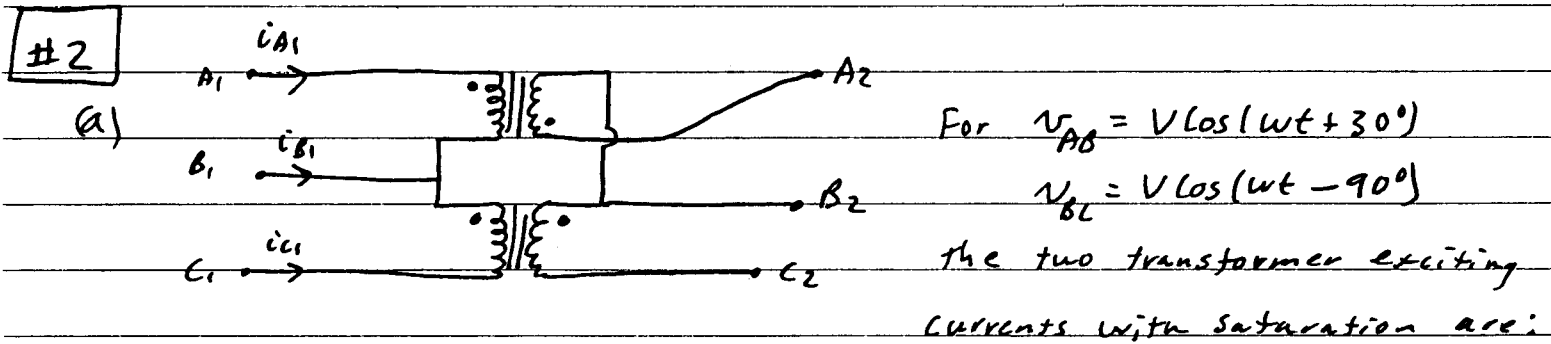$P_{\text{wm}} = V_{LL} I_L \cos(30^\circ - (120^\circ - \phi)) = \frac{1}{\sqrt{3}} 1500 \sqrt{2} \cos(30^\circ - 75^\circ) = \underline{866 \text{ W}}$



(b) $i_{A1} = I_1 \cos(\omega t + \theta) + I_2 \cos(3\omega t + \gamma)$

$i_{C1} = -I_1 \cos(\omega t - 120^\circ + \theta) - I_2 \cos(3\omega t + 360^\circ + \gamma)$

and $i_{B1} = -(i_{A1} + i_{C1}) = - (I_1 \cos(\omega t + \theta) - I_1 \cos(\omega t - 120^\circ + \theta)) = \underline{\sqrt{3} I_1 \cos(\omega t - 150^\circ + \theta)}$

#3 $|\bar{S}_{3\phi}| = \sqrt{3} \times 208 \times 8 = 2880 \text{ VA}$

At no load, $|\bar{S}_{3\phi}| \approx Q_{m3\phi}$ ($P \approx 0$ AT NO LOAD)

To reduce line current to essentially zero, the reactive power must be supplied by the capacitors. The reactive power of the capacitors is $Q_{3\phi} = 3 \times 208^2 / (1/377C)$

So: $C = \frac{2880}{208^2 \times 3 \times 377} = \underline{59 \mu\text{F}}$

#4

From the data, first assume that "full load" means,

$$P_{T0} = (2 \text{ h.p.}) (246 \text{ W/h.p.}) = 1492 \text{ W. From } 60 \text{ Hz, } 6 \text{ pole, } \text{RPM}_{\text{sync}} = 1200.$$

The "full load" slip is $s = \frac{1200 - 1120}{1200} = 0.067$

From the equivalent circuit with $r_s, x_{es}, x'_{er}, g_{cos}, P_{mf}$ all zero,

$$1492 = P_{T0} = (1-s) P_{T0} = (1-0.067) 3 \times |\bar{I}_r'|^2 (R_r' / 0.067), \quad |\bar{I}_r'| = \frac{120}{R_r' / 0.067}$$

So: $1492 = .933 \times 3 \times \frac{120^2}{R_r'} \cdot 0.067, \quad R_r' = 1.81 \Omega, \quad |\bar{I}_r'| = 4.44 \text{ A}$ and

$$T_{T0} = \frac{1492}{\frac{2\pi \cdot 1120}{60}} = 12.7 \text{ Nm. For operation at } 80\% \text{ voltage}$$

and 80% frequency, $|\bar{V}_{as}| = 0.8 \times 120 = 96 \text{ V}, \quad \text{RPM}_{\text{sync}} = 0.8 \times 1200 = 960 \text{ RPM}$

The term "full load" can be interpreted two ways, as follows:

a) Rated h.p., $P_{T0} = 1492 = (1-s) \times 3 \times \frac{96^2 (s)}{1.81}$ or $s^2 - s + 0.0777 = 0$

$s = 0.5 \pm 0.39$, choose $s = 0.1097, \quad \text{RPM}_{\text{shunt}} = (1-0.1097) 960 = 855 \text{ RPM}$

This gives $|\bar{I}_r'| = 5.8 \text{ amps}$ and $T_{T0} = 16.7 \text{ Nm}$

b) Rated rotor current, $|\bar{I}_r'| = 4.44 = 96 \frac{s}{1.81}$ or $s = 0.0837$

$\text{RPM}_{\text{shunt}} = (1-0.0837) 960 = 880 \text{ RPM}$

This gives $P_{T0} = (1-0.0837) \times 3 \times 4.44^2 \frac{1.81}{0.0837} = 1172 \text{ W (1.6 h.p.)}$

$T_{T0} = \frac{1172}{\frac{2\pi \cdot 880}{60}} = 12.7 \text{ Nm. This second interpretation is}$

also the same as assuming $T_{T0} = 12.7 \text{ Nm}$
shunt full load