

Exam #1

March 21, 1994

Closed book, closed notes, open mind, 55 min.

Problem #1  
25 points

A balanced,  $3\phi$ , 3 wire, impedance load is served by a balanced,  $3\phi$ , 3 wire ABC sequence source. A voltmeter between two lines reads 230V. An ammeter in one line reads 15 A. A wattmeter connected to read the power "into" the A-B lines reads 400 W. Find the total  $3\phi$  real and reactive power absorbed by the load.

Problem #2  
25 points

A single phase transformer has the following nameplate data: 12,470 V / 240 V, 100 kVA, 60 Hz, 5% Impedance.

If rated voltage is applied to the high voltage side, what is the low voltage side current when the low voltage side is shorted?

(OVER)

## Problem #3

25 points

A no-load test on a 3 $\phi$ , 60 Hz induction motor gives:

$$|\bar{I}| = 4 \text{ A}, \quad |\bar{V}_{LL}| = 230 \text{ V},$$

$$P_{1\phi} = 50 \text{ W}, \quad \text{Rpm} = 1799$$

a) How many poles is this machine?  
(2, 4, 6, 8 ...)

b) How big should each capacitor be to correct the power factor to unity?  
(3  $\Delta$  connected capacitors across the motor)

## Problem #4

25 points

A 208 V, 6 pole, 3 $\phi$ , 4 wire,  $\Delta$  connected, 60 Hz induction motor has,

$$r_1 = 0, \quad r_2 = \infty, \quad x_\phi = 30 \Omega,$$

$$x_1 = x_2 = 0, \quad r_2' = 1 \Omega. \quad \text{It is supplying } T_{\text{To}} = 15 \text{ NM}$$

shaft

a) what is the frequency of the rotor current?

b) what is the line current?

c) what is the output horsepower?

$$(1 \text{ HP} = 746 \text{ W})$$