

Exam II Solution Spring 1991

#1 open circuit test: $k_f w_s = \frac{120}{2} = 60$

Short circuit test: $k_f w_s \times 1 = 5 \times X_s \quad X_s = 12 \Omega$

(a) $60 I_f \angle \delta = j12(5 \angle 0) + 120 \angle 0 = 120 + j60$

$I_f = 2.24 A$

(b) $\frac{1}{\sqrt{2}} \frac{N_f}{N_s} L_{ms} w_s = 60, \quad w_s (\sqrt{L_s^2 + \frac{3}{2} L_{ms}^2}) = 12$

$w_s L_{ms} = 8 \Omega$

so

$\frac{N_f}{N_s} = 10.6$

#2

$w_t \frac{dw_t}{dt} = w_t (5 - k_2 \sin \delta)$

$\int_0^{\hat{t}} w_t \frac{dw_t}{dt} dt = \int_0^{\hat{t}} (5 - k_2 \sin \delta) \frac{d\delta}{dt} dt$

$\int_0^{w_t(\hat{t})} w_t dw_t = \int_{\delta(0)}^{\hat{\delta}} (5 - k_2 \sin \delta) d\delta$


$\frac{1}{2} w_t^2(\hat{t}) = \int_{\delta(0)}^{\hat{\delta}} (5 - k_2 \sin \delta) d\delta$

A $\hat{\delta}$ must exist so that $w_t(\hat{t}) = 0$

or, $\int_{\delta(0)}^{\hat{\delta}} (5 - k_2 \sin \delta) d\delta = 0$

For the problem given:

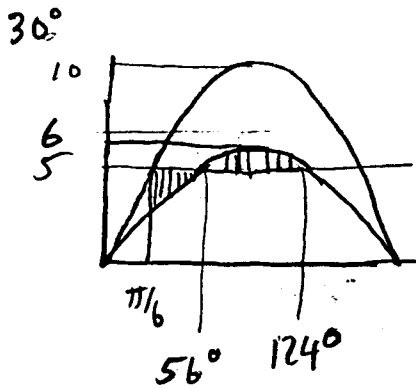Can $\int_{30^\circ}^{56^\circ} (5 - 6 \sin \delta) d\delta = 0$ for $t > 0$



$$A = \int_{30^\circ}^{56^\circ} (5 - 6 \sin \delta) d\delta$$

$$= 5 \left(\frac{56\pi}{180} - \frac{\pi}{6} \right) + 6 \cos(56^\circ) - 6 \cos 30^\circ = 0.43$$

$$B = \int_{56^\circ}^{124^\circ} (6 \sin \delta - 5) d\delta = -6 \cos(124^\circ) + 6 \cos(56^\circ) - 5 \left(\pi - \frac{56\pi}{180} - \frac{56\pi}{180} \right) = 0.78$$

Yes it can be done.

#3 $2000 = \frac{3 \times 120 \times 0.23 \times 2\pi 60 \times I_f}{10} \sin \delta = 3121 I_f \sin \delta$

$$\frac{Q}{3\phi} = 3121 \cos \delta - \frac{3 \times 120^2}{10} = 3121 I_f \cos \delta - 4320$$

$$|\bar{I}_{as}| = \frac{|\bar{S}_{3\phi}|}{3 \times |\bar{V}_{as}|} = \frac{\sqrt{2000^2 + Q^2}}{360}$$

1. minimum field current is at $\delta = 90^\circ$

$$2000 = 3121 I_{f_{\min}} \quad I_{f_{\min}} = 0.64 \text{ A}$$

$$Q = 0 - 4320 \quad |S| = \sqrt{2000^2 + 4320^2} = 4760$$

$$|I_{as}| = \frac{4760}{3 \times 120} = 13.2$$

2. minimum armature current is at $Q = 0$

$$\left. \begin{aligned} 2000 &= 3121 I_f \sin \delta \\ 0 &= 3121 I_f \cos \delta - 4320 \end{aligned} \right\} 3121^2 I_f^2 = 2000^2 + 4320^2$$

$$I_f = 1.53 \text{ A}$$

$$|S| = 2000 \quad |I_{as}| = \frac{2000}{3 \times 120} = 5.56 \text{ A}$$

3. Maximum armature current is $|I_{as}| = 20 \text{ A}$

$$\text{So } |S| = 3 \times 120 \times 20 = 7200 \quad \text{So } Q = \sqrt{7200^2 - 2000^2} = 6916$$

$$\left. \begin{aligned} 2000 &= 3121 I_f \sin \delta \\ 6916 &= 3121 I_f \cos \delta - 4320 \end{aligned} \right\} 3121^2 I_f^2 = 2000^2 + 11236^2$$

$$I_f = 3.66 \text{ A}$$

