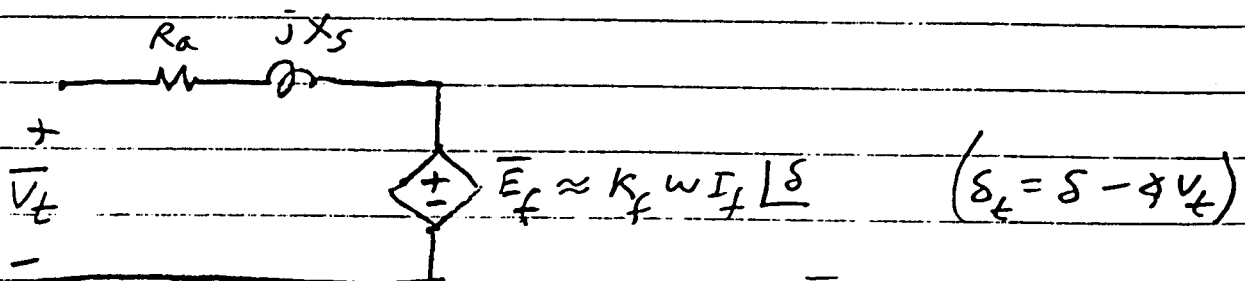


Exam II

SPRING 1994


50 minutes, closed book, closed notes, open mind

Given Information:



$$P_{in} = \frac{3 |\bar{V}_t| |\bar{E}_f|}{X_s} \sin(-\delta_t)$$

$$Q_{in} = \frac{3 |\bar{V}_t|^2}{X_s} - \frac{3 |\bar{V}_t| |\bar{E}_f|}{X_s} \cos(-\delta_t)$$

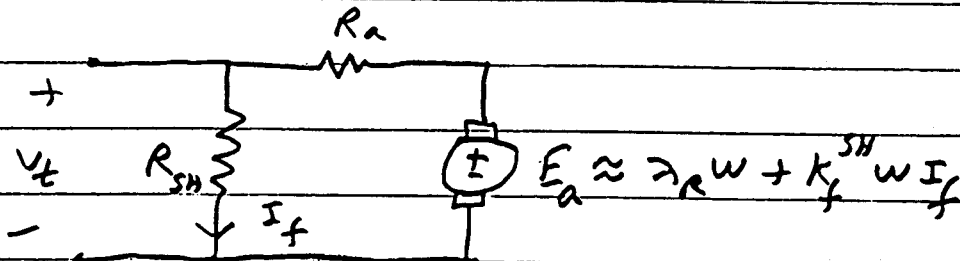

$$T = \frac{P}{\omega}$$

Problem #1
25 points

Given the following test data for a 3 ϕ synchronous machine:

open circuit: $I_f = 5 \text{ A}$ $V_{ll} = 480 \text{ V (l-l)}$

Short circuit: $I_f = 1 \text{ A}$ $I_L = 40 \text{ A}$

(a) What value of I_f do you need to produce rated voltage at rated current if the machine is a generator serving a load with 0.8 power factor lagging?

(b) If you use this value of I_f , will the actual V_f be lower or higher? Explain

Problem #2
25 points

An unloaded synchronous machine (3 ϕ) is connected to an infinite bus at 120 V (l-l). It has a synchronous reactance of 5Ω , when I_f is equal to 2 A, the line current is zero.

(a) What will the line current be if I_f is changed to 3 A?

(b) What is the maximum load this machine can supply when $I_f = 3 \text{ A}$?

Problem #3

25 points

An unloaded self-excited dc generator with $R_A = 0.5 \Omega$ is tested at 1200 RPM. The test results are:

$$I_f = 0 \text{ A} \quad V_t = 10 \text{ V}$$

$$I_f = 1 \text{ A} \quad V_t = 120 \text{ V}$$

(a) What value of total field resistance is needed to keep the terminal voltage at 120V if the speed drops to 1180 RPM when a 30Ω load resistor is applied to the terminals?

(b) If this value of resistance is used, will the actual voltage be higher or lower than 120V? Explain

Problem #4

25 points

A 120V shunt dc motor with $R_A = 0.5 \Omega$ runs at 1400 RPM

at no load with a total field resistance of 120Ω .

(a) What field resistance is needed to change the no-load speed to 1600 RPM?

(b) What will the terminal current and speed be if it is loaded with 10 Nm shaft torque? (original R_f)

(Neglect residual voltage, saturation and armature reaction)