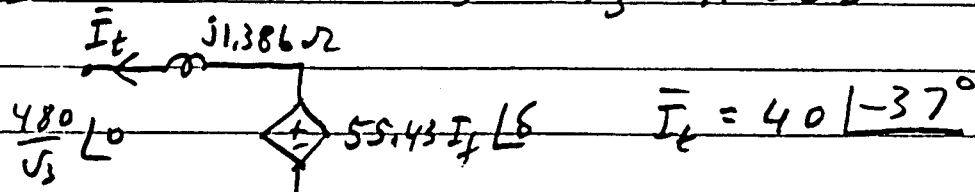


## Exam II Solution

Spring 1994

#1  $OC \quad \frac{480}{\sqrt{3}} = k_f w \times 5 \quad k_f w = 55.43 \Omega$  (neglect  $R_a$ )

$SC \quad 55.43 \times 1 = 40 \times X_s \quad X_s = 1.386 \Omega$




$$55.43 I_f \angle 6 = 40 \angle -37^\circ \times 1.386 \angle 90^\circ + \frac{480}{\sqrt{3}} \angle 0$$

$$= 55.44 \angle 53^\circ + 277 \angle 0$$

(a)  $= 33.36 + j44.3 + 277 = 313.5 \angle 8^\circ$

$I_f = 5.66 A$

(b) Lower because of saturation ( $|E_f|$  is less) and  $t$

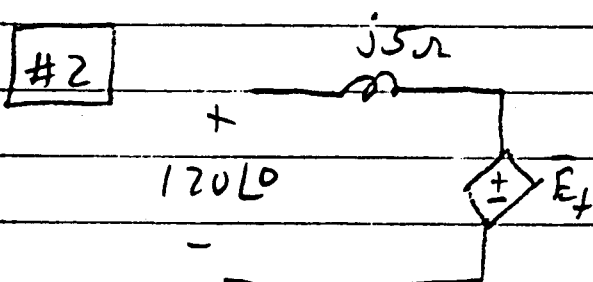

(a)  $k_f w \times 2 = 120$


$k_f w = 60 \Omega$

$$60 \times 3 \angle 6 = j5 \bar{I} + 120 \angle 0$$

No load so  $s = 0 \quad |\bar{I}| = \left| \frac{180 \angle 0 - 120 \angle 0}{j5} \right|$

$|\bar{I}| = 12 A$

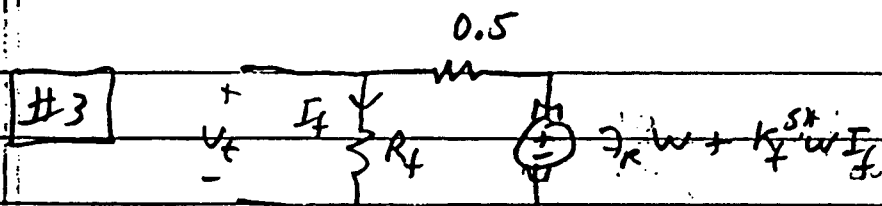(b)  $P_{max} = \frac{3 \times 120 \times 60 \times 3}{5} = \underline{\underline{12,960 W}}$



$$I_f = 0, \quad V_f = I_f R_f \quad 0.5 = \frac{10}{1200 \frac{2\pi}{60}} = 0.0796$$

$$I_f = 1, \quad V_f = 120V \quad 10 + K_f^{SH} 1200 \frac{2\pi}{60} \times 1 = 0.5 \times 1 + 120$$


$$K_f^{SH} = 0.879$$

$$(a) \quad 10 \frac{1180}{1200} + 0.879 \times 1180 \frac{2\pi}{60} \frac{120}{R} = 0.5 \left( \frac{120}{30} + \frac{120}{R} \right) + 120$$

$$9.833 + \frac{13034}{R} = 2 + \frac{60}{R} + 120$$

$$9.833R + 13034 = 2R + 60 + 120R \quad R = 115.7\Omega$$

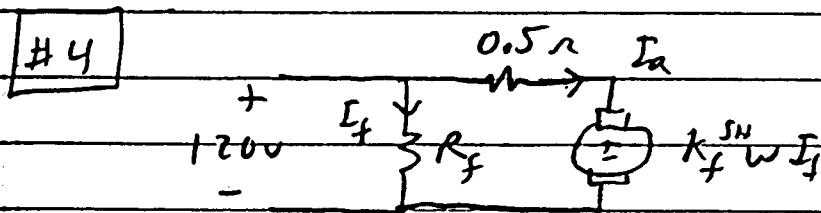(b) Lower because of saturation. The actual internal voltage will be less than the above.



$$(a) \quad \text{For } I_f = 1 \quad \omega = 1400 \frac{2\pi}{60} \quad I_a = 0 \quad K_f^{SH} \times 1400 \frac{2\pi}{60} \times 1 = 120$$

$$K_f^{SH} = \frac{120}{1400 \frac{2\pi}{60}} = 0.819$$

For RPM = 1600, use

$$120 = 0.819 \times 1600 \frac{2\pi}{60} I_f$$

$$I_f = 0.874 \quad R_f = 137\Omega$$

$$(b) \quad 120 = 0.5 I_a + 0.819 \omega I_f$$

$$\frac{0.819 \omega I_f \times I_a}{\omega} = 10$$

$$I_a = 12.2A$$

$$I_f = 13.1A$$

$$\omega = 139.1 \text{ rad/s} \quad (1328 \text{ RPM})$$