

ECE 333

Second Exam – Spring 1999 – Closed book, closed notes, 55 minutes

Problem #1 (25 points)

Given the following test data for a 3-phase, synchronous machine:

Open circuit: $I_f = 3\text{ A}$ $V_t = 120\text{ V}$ (line-to-neutral) (Rated)

Short circuit: $I_f = 1\text{ A}$ $I_a = 7\text{ A}$ (Rated)

- (a) What value of I_f is required to produce rated voltage when the machine is operating as a generator delivering rated current to an induction motor load at 0.9 power factor lag? (neglect R_a and saturation)
 - (b) If you use this value of I_f , will the actual V_t be lower or higher? Explain
 - (c) Is the machine underexcited or overexcited? Explain
 - (d) What will happen if I_f is accidentally reduced to zero while supplying the load of (a)?
-

Problem #2 (25 points)

A synchronous motor dynamic model is:

$$d\delta/dt = \omega - \omega_s$$

$$d\omega/dt = K_1 - 10 \sin\delta$$

- (a) Can the motor be suddenly loaded so that K_1 changes from 0 to negative 8? Explain why or why not with figures and words.
- (b) Can the motor be suddenly loaded so that K_1 changes from negative 7 to negative 8? Explain why or why not with figures and words.

(OVER)

Problem #3 (25 points)

Tests on a self-excited shunt d.c. generator with $R_a = 4$ Ohms are:

Open circuit: RPM = 1200, $I_f = 2$ A, $V_t = 240$ V.

Short circuit: RPM = 1200, $I_t = 3$ A. (we never did this test)

- (a) What is the open circuit voltage if the speed is changed to 1100 RPM?
- (b) How much resistance should be removed from the shunt field circuit to maintain the open circuit voltage at 240 V at 1100 RPM?
-

Problem #4 (25 points)

A shunt d.c. motor with $R_a = 1$ Ohm and $V_t = 240$ V has the following piecewise linear model of the internal voltage at 1200 RPM:

$$E_a = 10 + 115 I_f \quad \text{for } 0 \leq I_f \leq 2 \text{ A}$$

$$E_a = 240 + 80 (I_f - 2) \quad \text{for } I_f \geq 2 \text{ A}$$

- (a) Find the shunt field resistance needed to make the speed be 1000 RPM when it is unloaded.
- (b) Find the RPM if $I_t = 10$ A (using the resistance from (a))
-

Spring bonus (5 points)

A shunt d.c. motor is started and runs with constant voltage at 1250 RPM. As it sits there running, the speed slowly increases slightly. Why?